

Quiz #1 EE 221 Spring 2020

Name: _____

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. What are V_s and V_x in the following circuit? (4 points)

