

Quiz #2 EE 221 Spring 2020

Name: \_\_\_\_\_

Closed book and notes.

**Show your work for credit and place a box around each of your answers.**

1. In the following circuit find the currents in the directions indicated and  $V_2$  using mesh analysis. (4 points)

