

Closed book and notes.

Show your work for credit and place a box around each of your answers.

- In the following circuit find the currents in the directions indicated and V_2 using any hand calculation method you would like. (4 points)

