

Quiz #4 EE 221 Spring 2020

Name: \_\_\_\_\_

Closed book and notes.

**Show your work for credit.**

1. Find the Thevenin and Norton equivalents of the following circuit at the red terminals indicated. (4 points)

