

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. In the following circuit calculate the output voltage  $V_{out}$ . (4 points)

