

Quiz #7 EE 221 Spring 2020

Name: _____

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Find the AC current (an equation in the time-domain) that flows in the following circuit and sketch, along with V_S , to show the magnitudes and phase shift. (4 points)

