
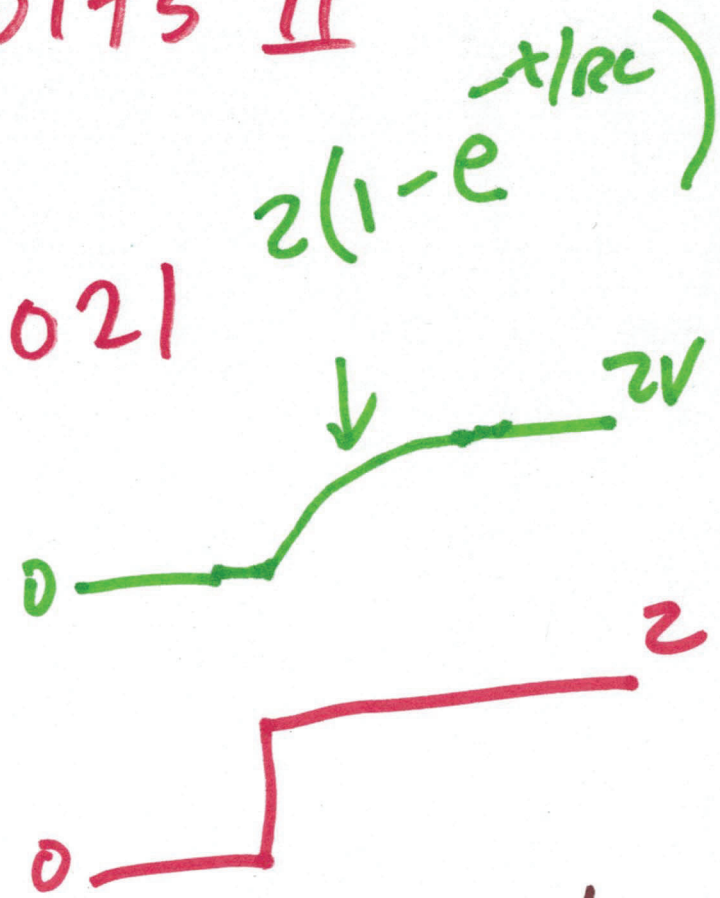


EE 221 Circuits II

Lecture 14


MARCH 22, 2021

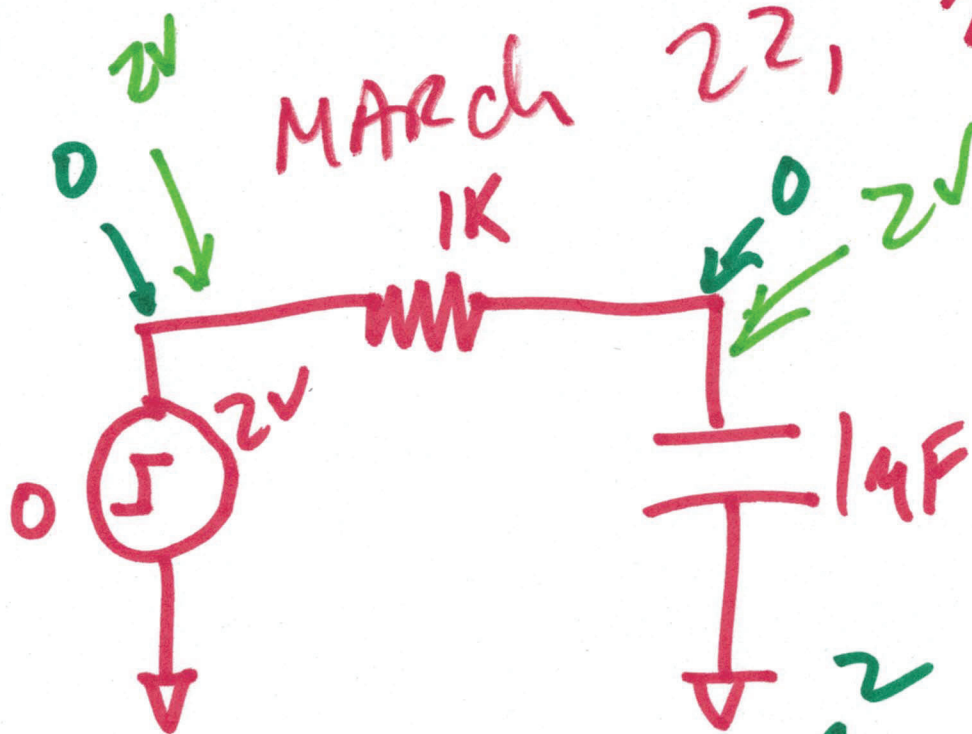

$$v_c(t) = v_f + (v_i + v_f) e^{-t/\tau}$$

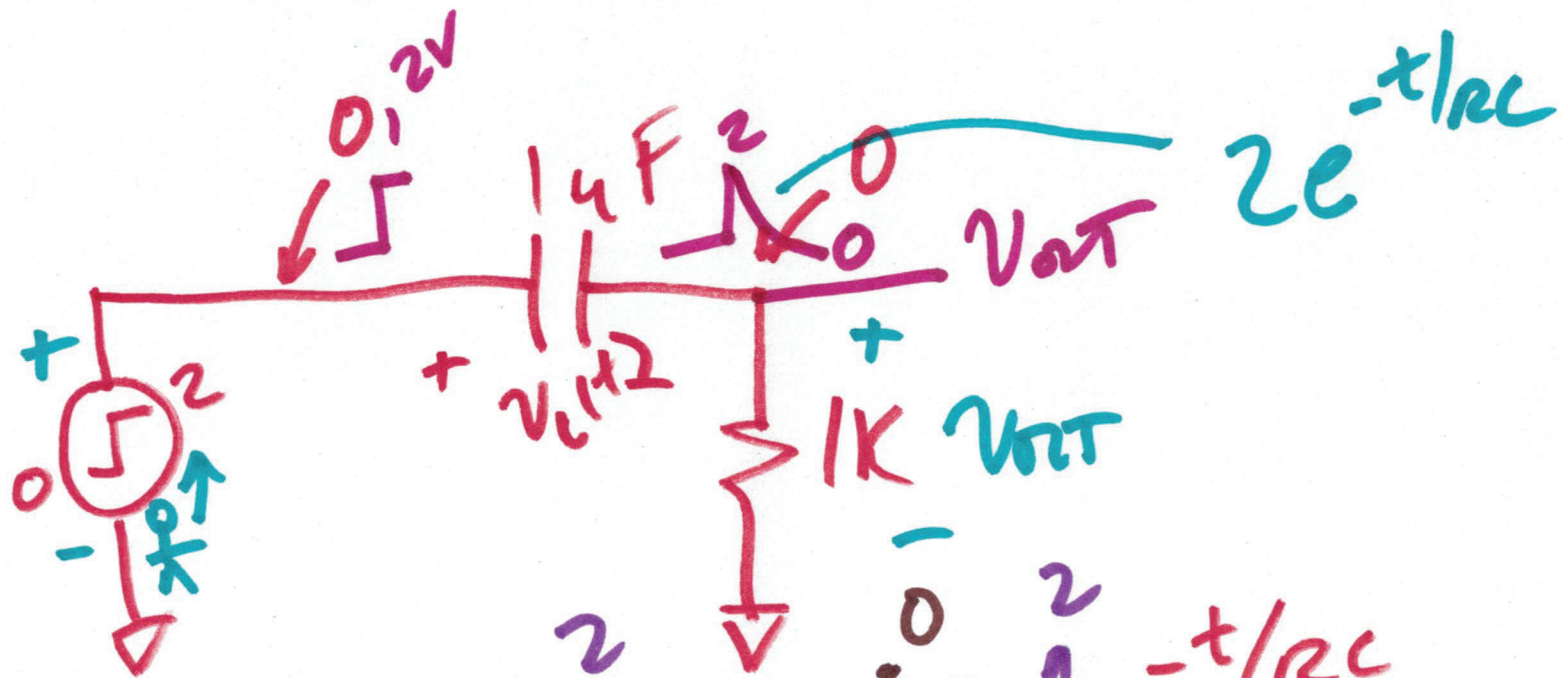v_f (final voltage) is 2V.
 v_i (initial voltage) is 0V.
 τ (time constant) is RC .





$$v_c(t) = v_f + (v_i + v_f) e^{-t/RC}$$


$$v_c(t) = 2(1 - e^{-t/RC})$$

$$2 - v_c(t) - v_{out} = 0 \quad -t/RC$$

$$v_{out} = 2 - 2e^{-t/RC}$$

$$= 2e^{-t/RC}$$

2)

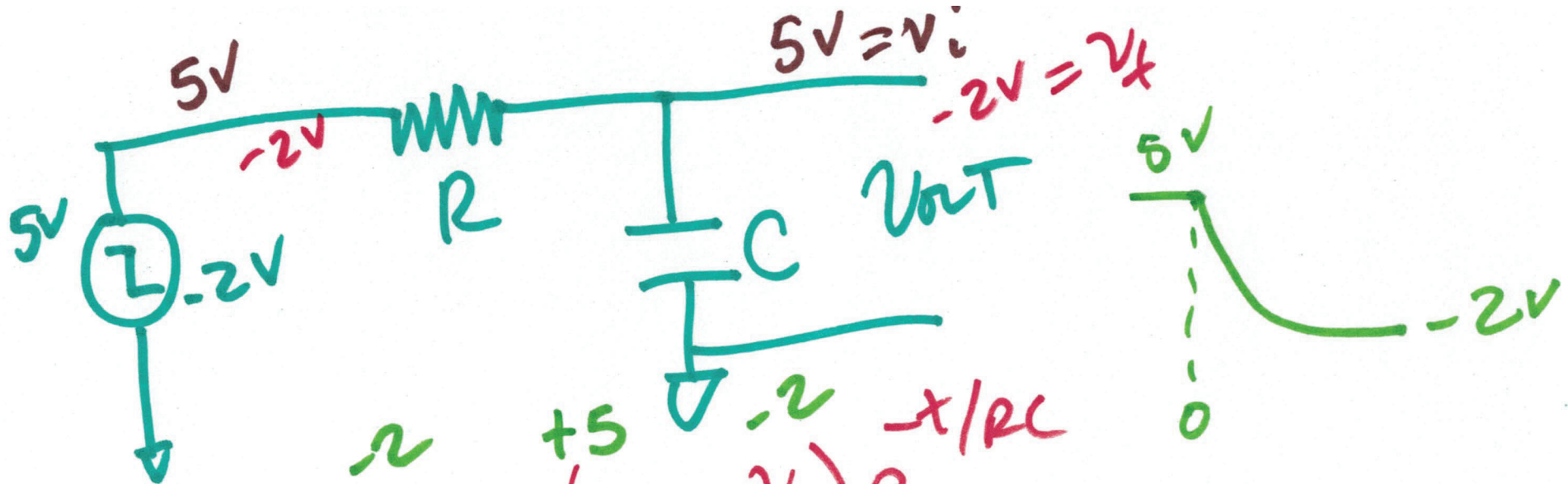

$$V_{out} = V_f - (V_i + V_f)e^{-t/RC}$$


$$V_{out} = -2 + 5e^{-t/RC}$$

$$V_{out} = -2 - 3e^{-t/RC}$$

$$V_{out} = V_f + (V_i - V_f)e^{-t/RC}$$

$$-2 + (5 + 2)e^{-t/RC}$$

3)

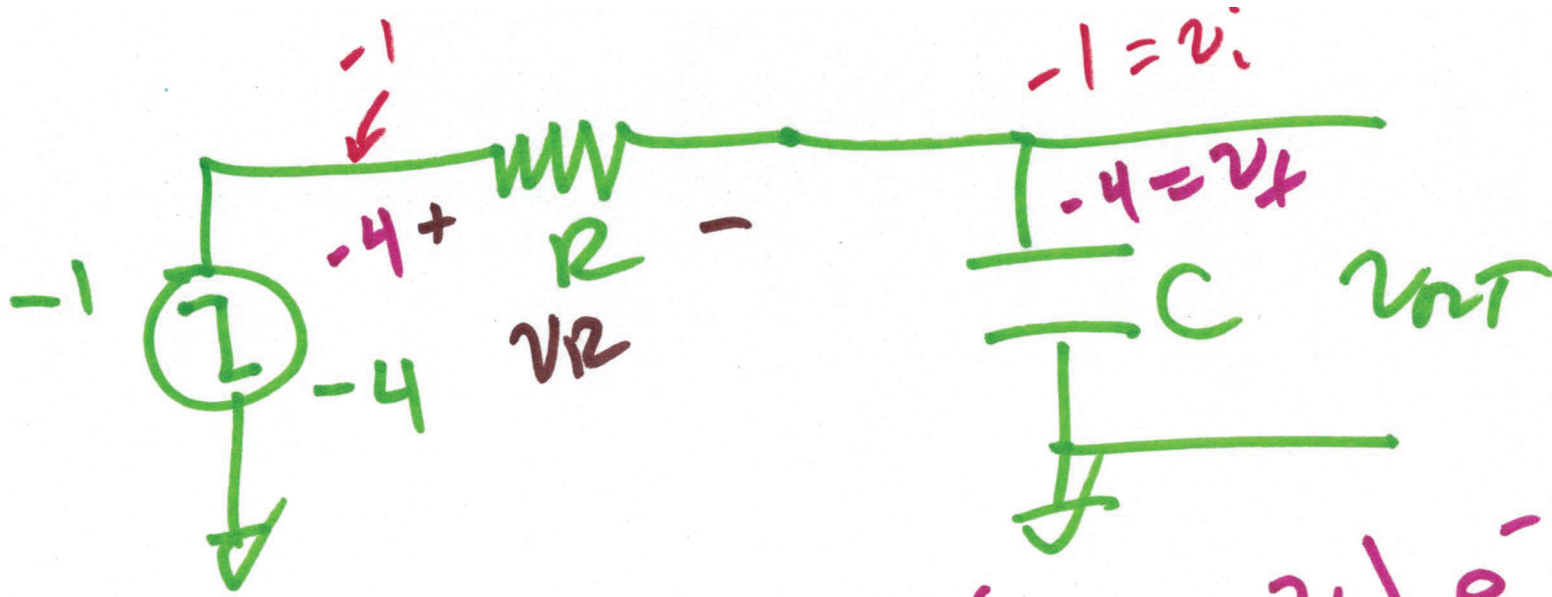

$$v_{OUT} = v_f + (v_i - v_f) e^{-t/RC}$$



$$= -4 + (-1 + 4) e^{-t/RC}$$

$$v_{OUT} = -4 + 3 e^{-t/RC}$$


$$v_R = -4 - v_{OUT}$$

$$= -3 e^{-t/RC}$$

4)

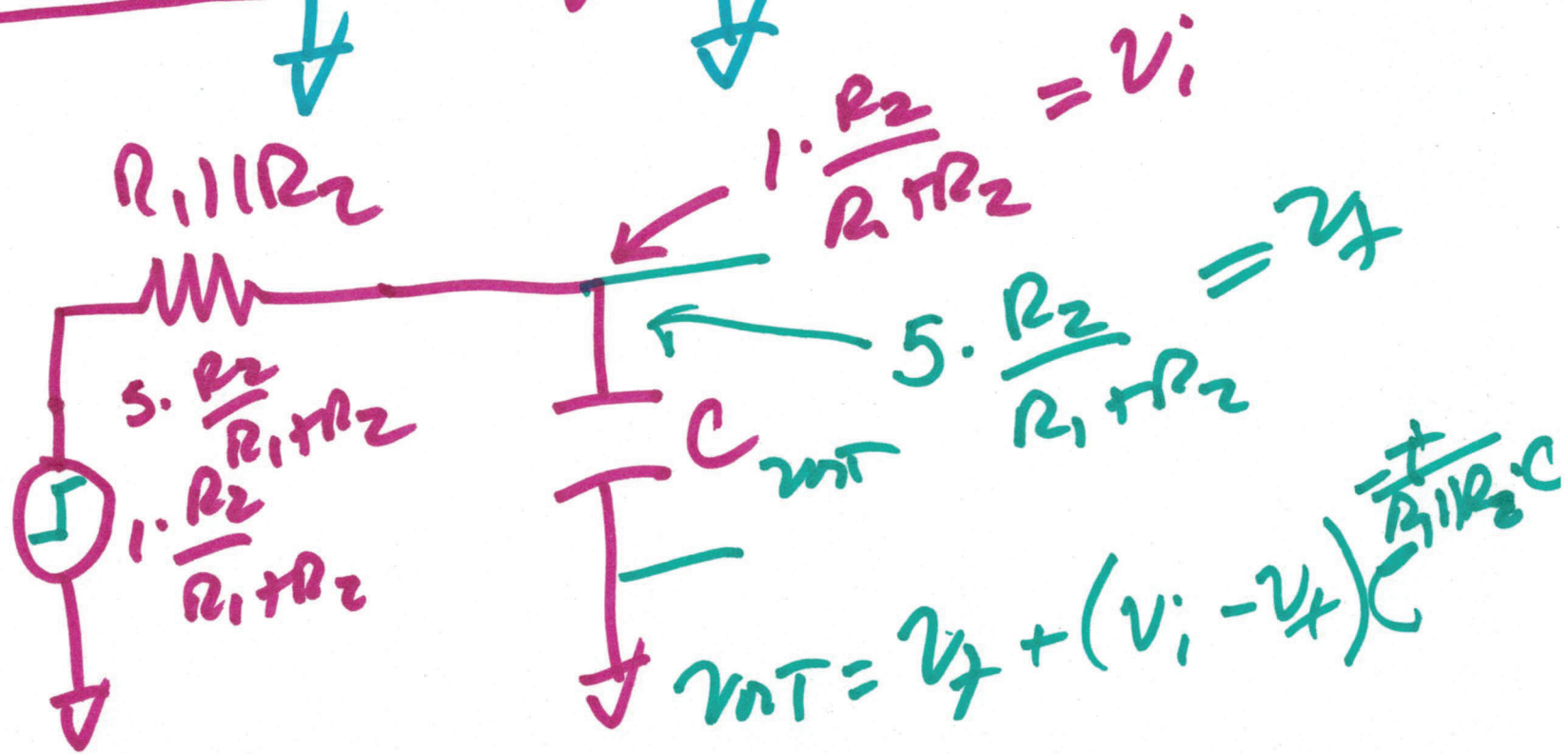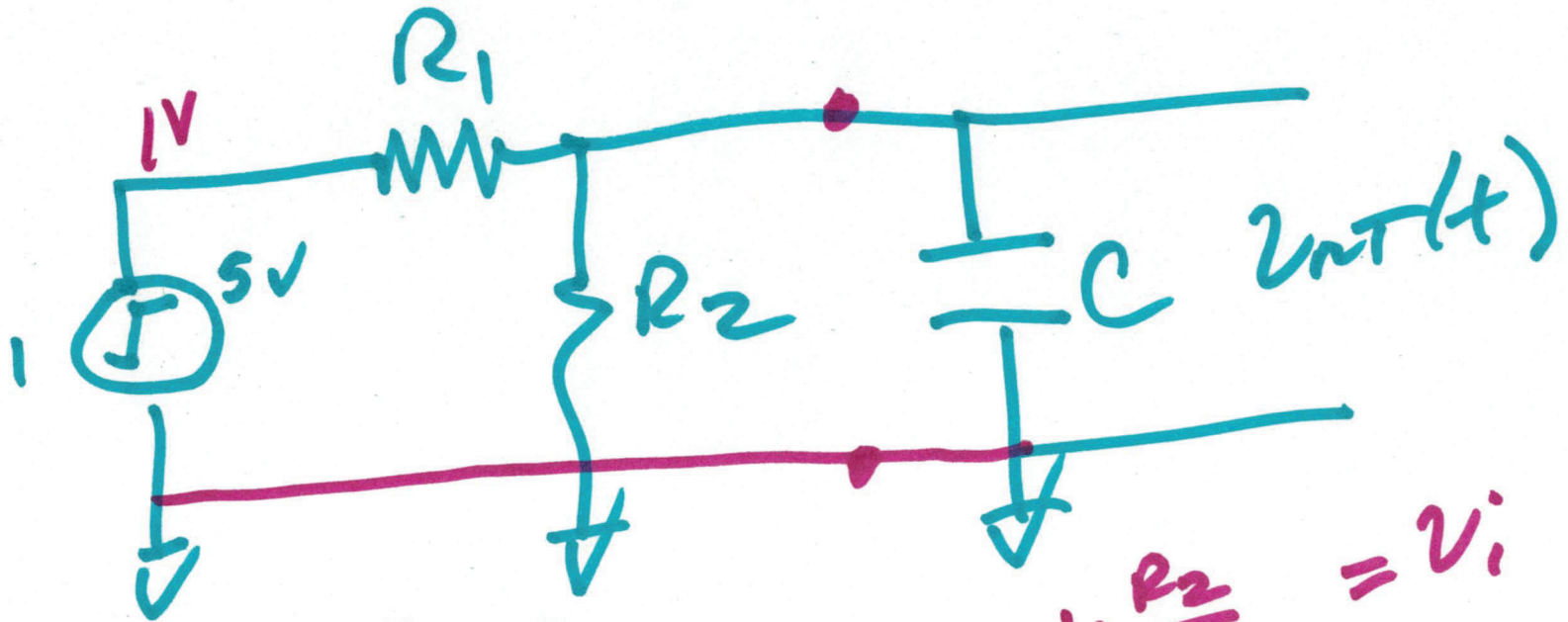


5)

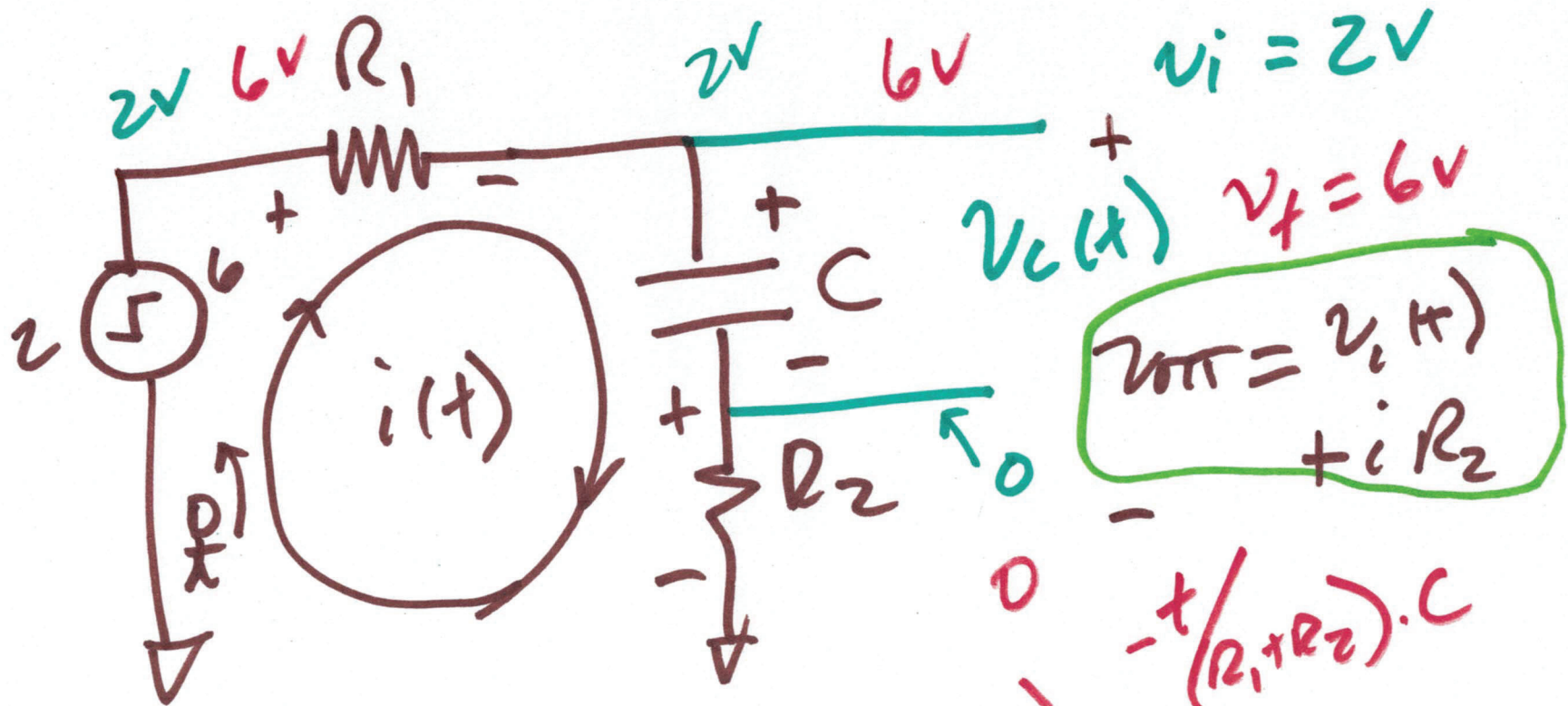

$$v_c(t) = 6 + (2 - 6)e^{-\frac{t}{(R_1 + R_2) \cdot C}}$$

$$6 - iR_1 - v_c(t) - iR_2 = 0$$

$$i = \frac{6 - v_c(t)}{R_1 + R_2}$$

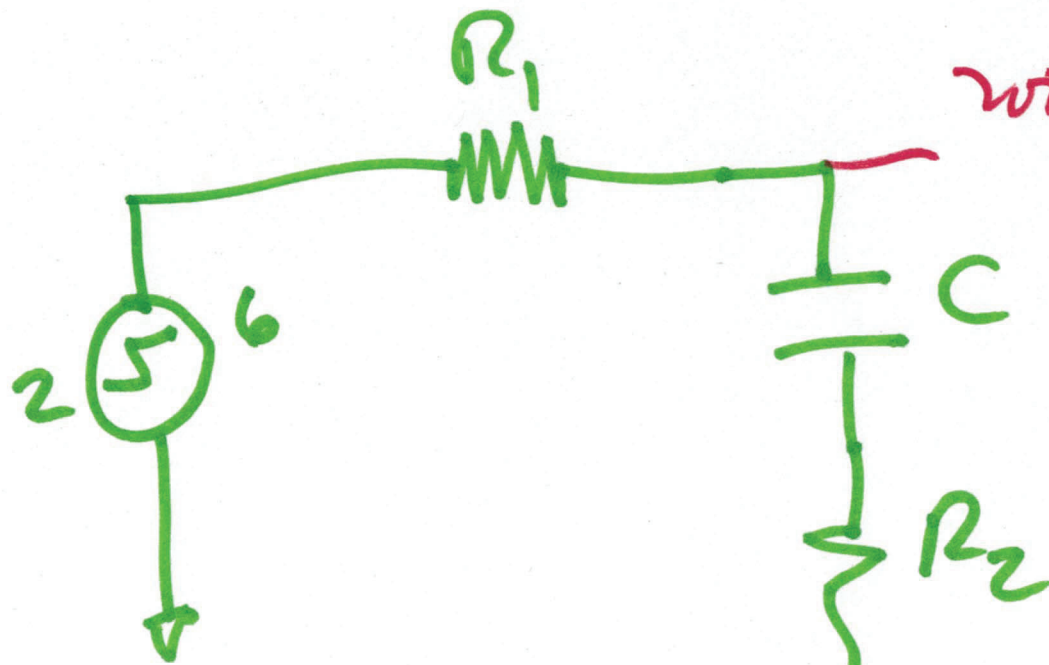


with $v_c(t) = 6 - 4e^{-t/(R_1 R_2)C}$

$$i = C \frac{dv_c(t)}{dt}$$

$$i = \phi \left(\frac{0 - 4e^{-t/(R_1 R_2)C}}{-(R_1 + R_2)C} \right)$$
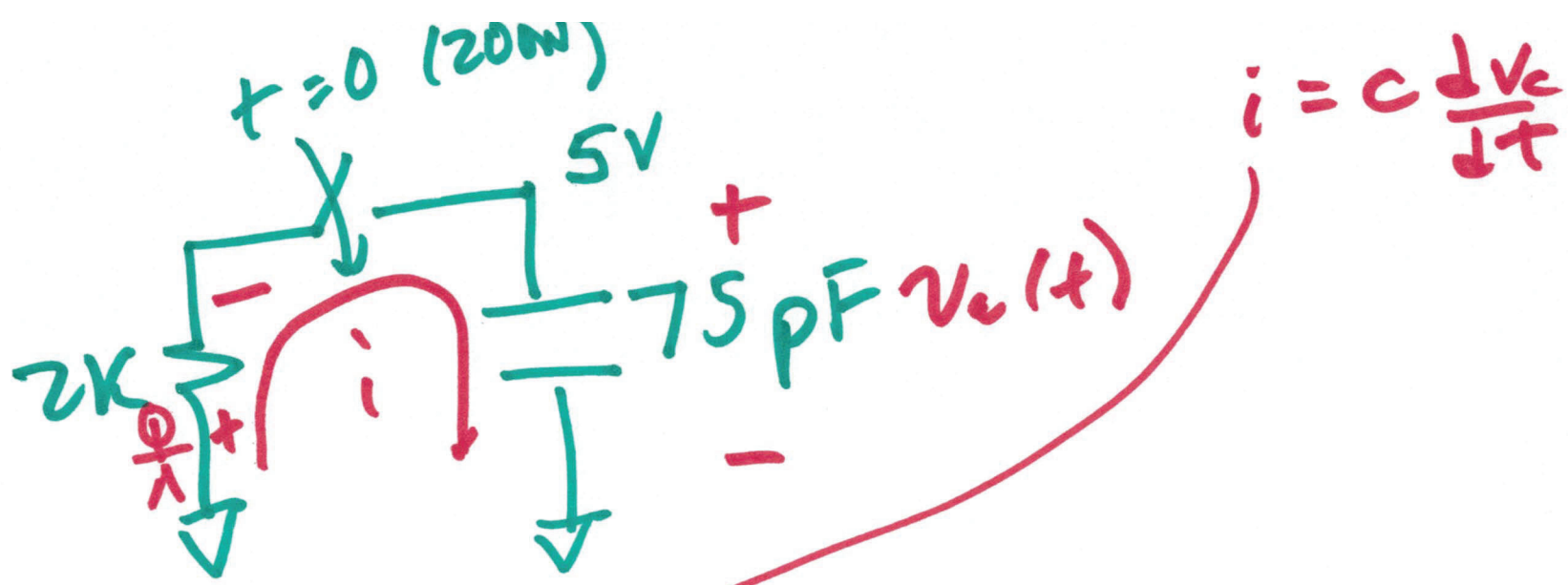
$$i = \frac{+4e^{-t/(R_1 + R_2)C}}{R_1 + R_2}$$



$$-2k \cdot i - v_c(t) = 0$$

$$-2k \cdot 75 \text{ pF} \cdot \frac{dv_c}{dt} - v_c = 0$$

$$v_c = -RC \cdot \frac{dv_c}{dt}$$

$$\frac{dt}{-RC} = \frac{dv_c}{v_c}$$

8)


$$\int_0^t \frac{dt}{RC} = \int_{v_i}^{v_f} \frac{dv_c}{v_c}$$
$$-\frac{t}{RC} = \ln v_c \Big|_{v_i}^{v_f}$$

$$= \ln v_f - \ln v_i$$

$$-\frac{t}{RC} = \ln \frac{v_f}{v_i}$$

$$v_i \cdot e^{-t/RC} = v_f$$

a)

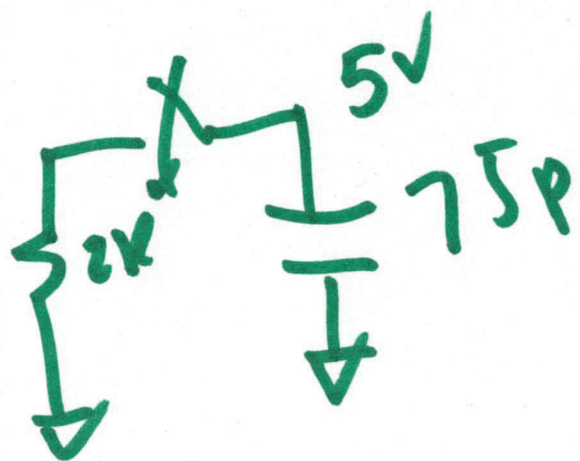

$$P = 10^{-9} \text{ W}$$

$$k = 10^{+3}$$

$$n = 10^{-9}$$

$$v_c = 5e^{-t/150n}$$

