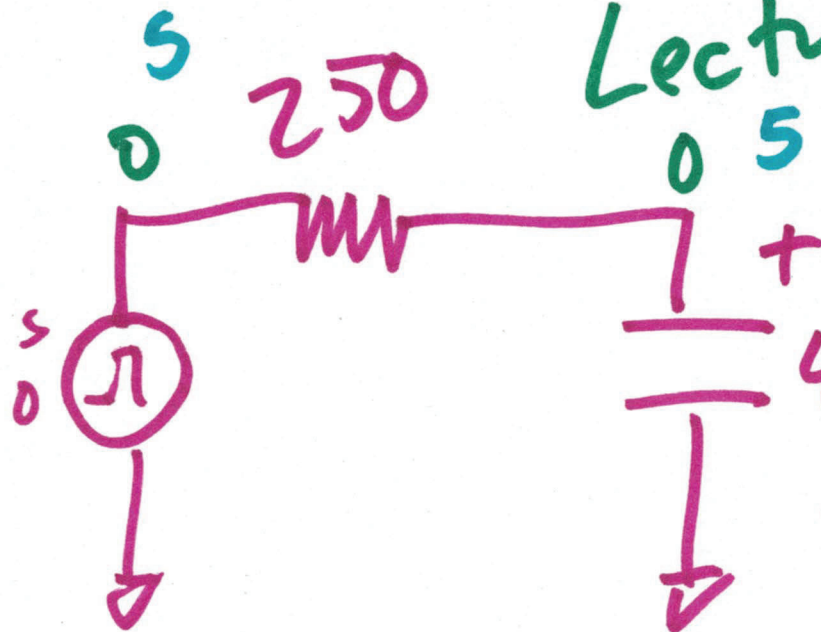


EE 221 circuits II

March 29, 2021

Lecture 16

$RC = 100\text{ns}$



$$v_i = 0$$

$$v_f = 5$$

$$v_c(t) = v_f + (v_i - v_f)e^{-t/\tau}$$
$$= 5(1 - e^{-t/100\text{ns}})$$


$$t \leq 100 \text{ ns} \quad v_c(t) = 0$$

$$t \geq 100 \text{ ns} \quad v_c(t) = 5 \left(1 - e^{-\frac{(t-100 \text{ ns})}{100 \text{ ns}}} \right)$$

$$t \leq 1 \mu\text{s}$$




$$100 \text{ ns} \leq t \leq 1.1 \mu\text{s}$$
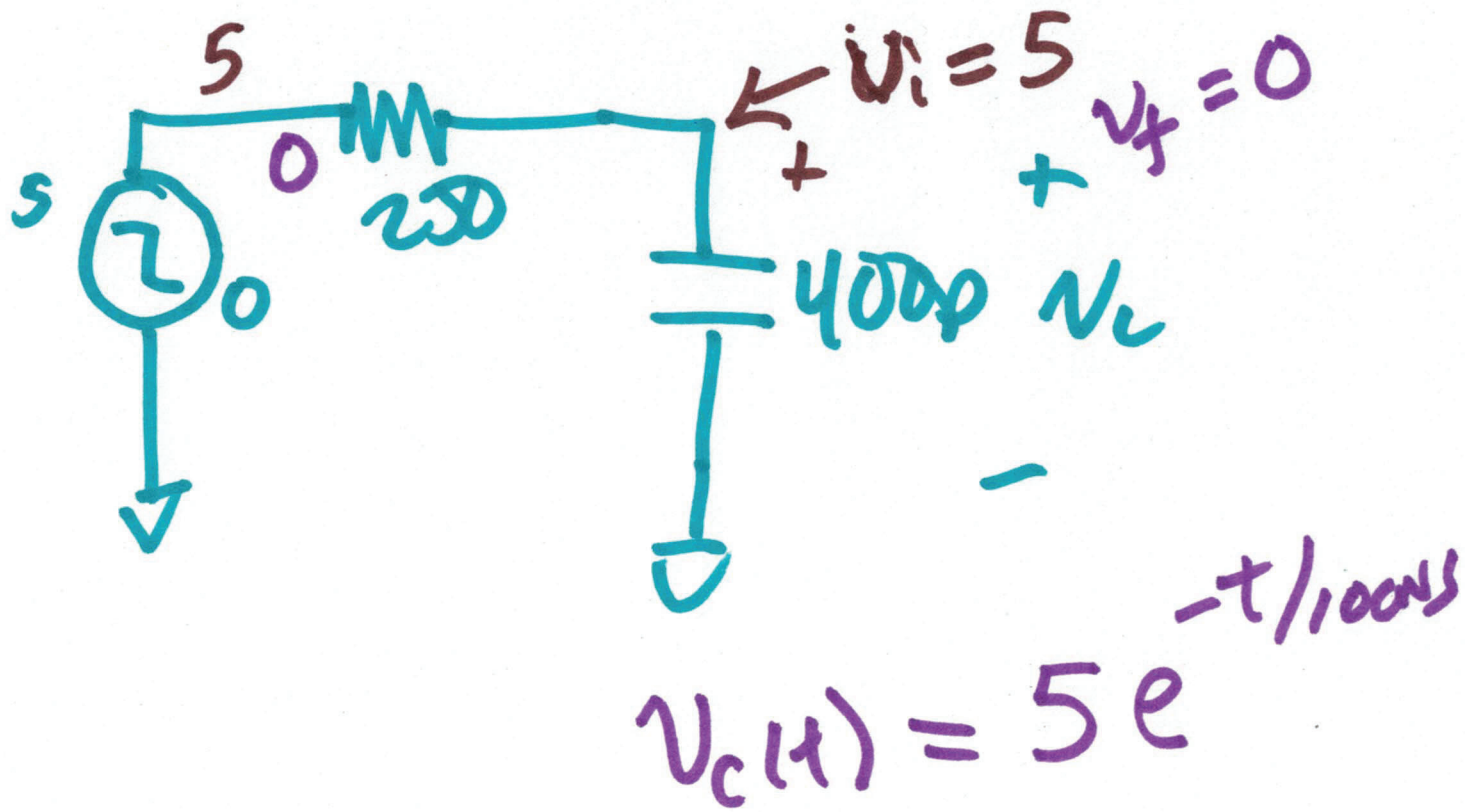
$$t \geq 1.1 \mu\text{s} \quad v_c(t) = 5 e^{-\frac{(t-1.1 \mu\text{s})}{100 \text{ ns}}}$$



5)

$$v_c(t) = 5(1 - e^{-t/100ns})$$

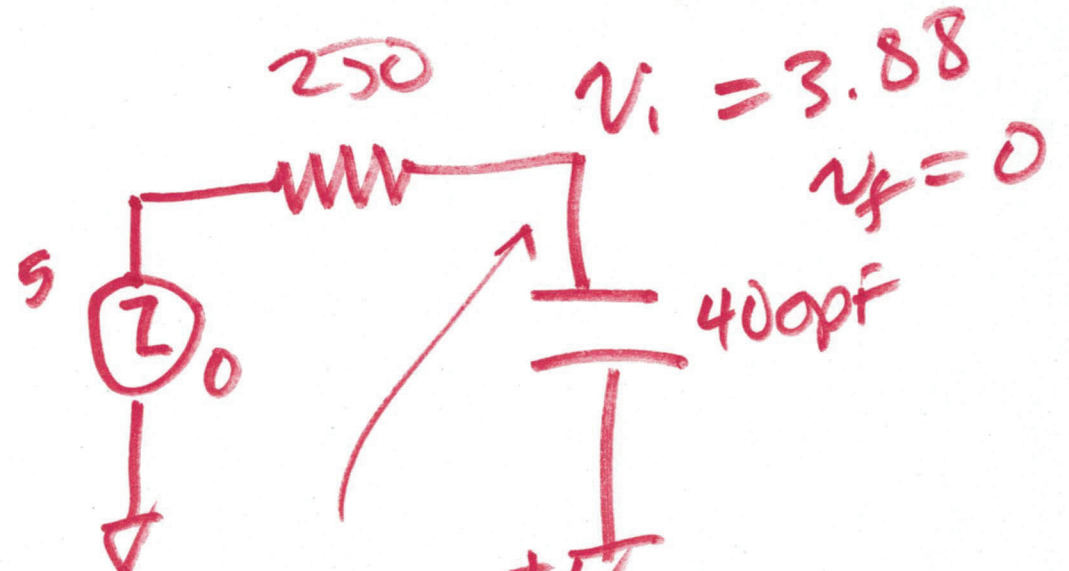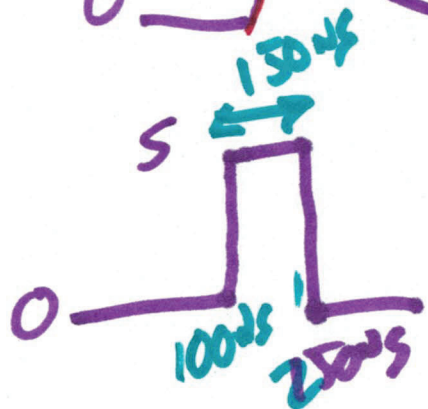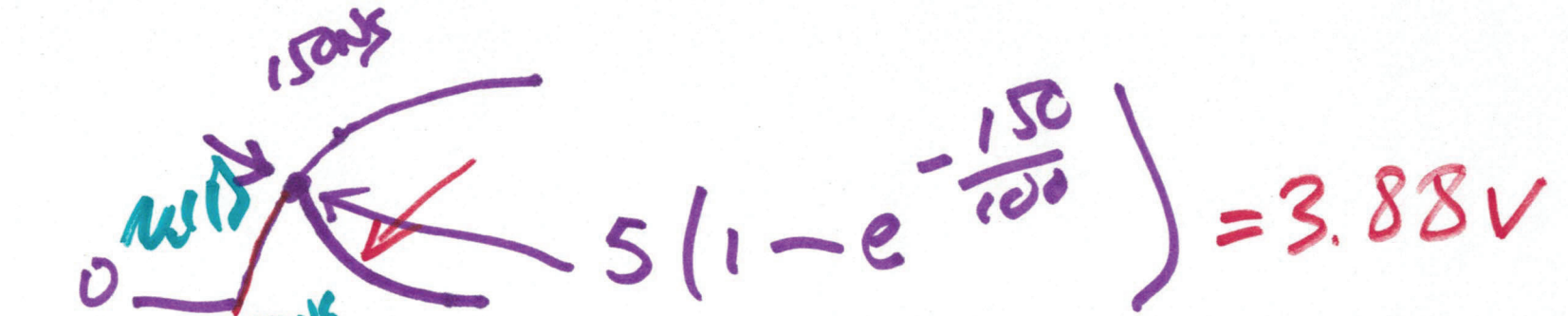

$$v_c(t) = 3.88 e^{-t/100ns}$$



a)

$$v_c(t) = 0 \quad t > 0 \quad 0 \leq t \leq 100\text{ns}$$

$$t \leq 100\text{ns}$$

$$v_c(t) = 5 \left(1 - e^{-\frac{(t-100\text{ns})}{100\text{ns}}} \right) \quad 100\text{ns} \leq t \leq 250\text{ns}$$
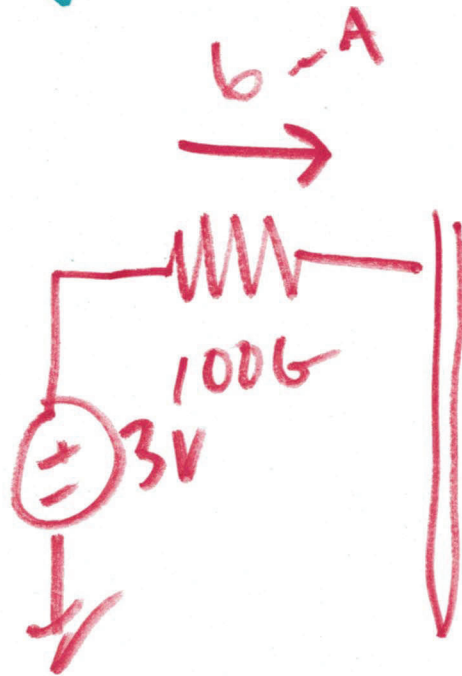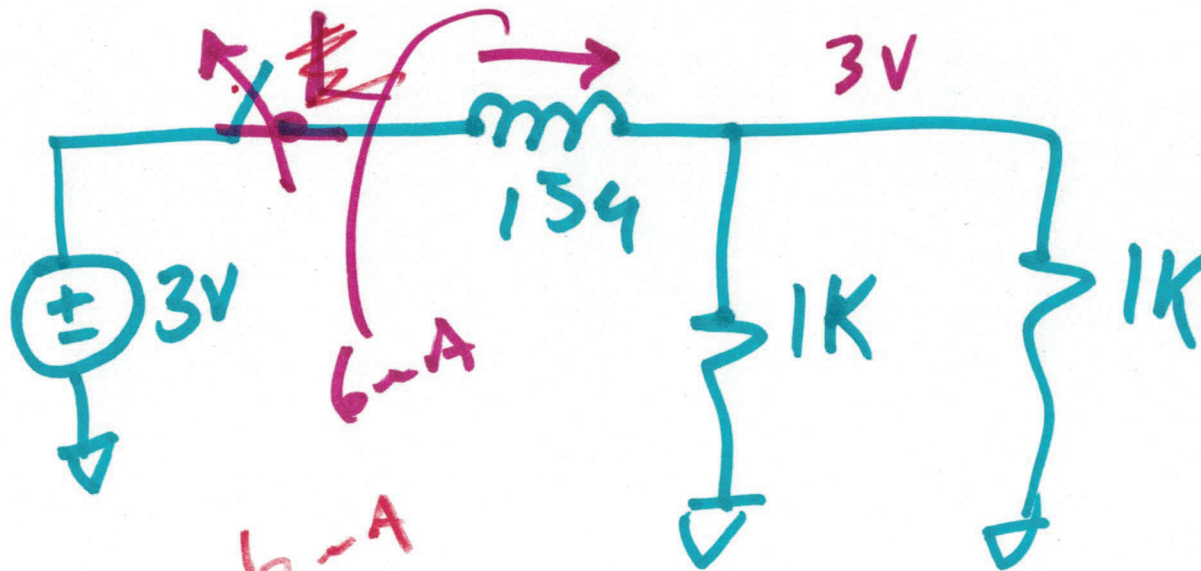
$$v_c(t) = 3.88 e^{-\frac{(t-250\text{ns})}{100\text{ns}}} \quad t > 250\text{ns}$$





Unit step function

$u(t)$

$$u(t) = 1 \quad t \geq 0$$

$$u(t) = 0 \quad t < 0$$

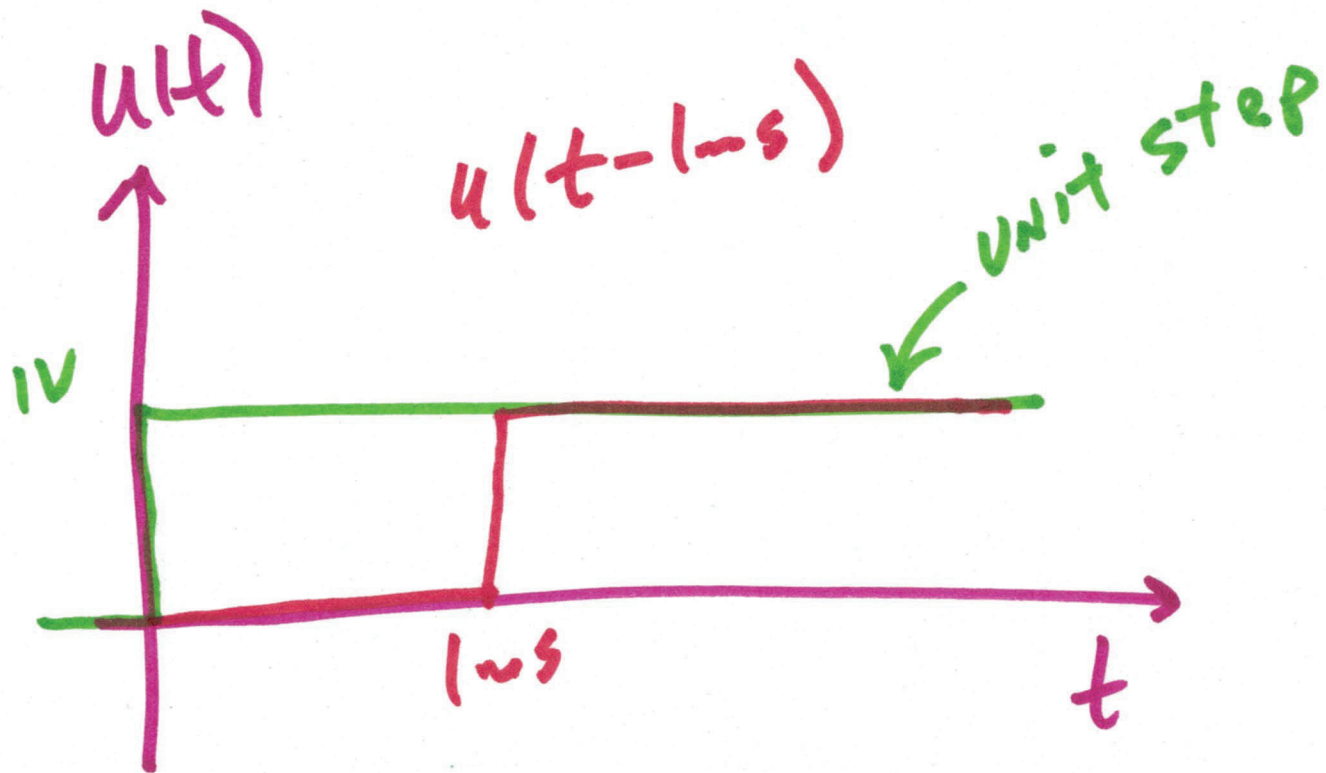

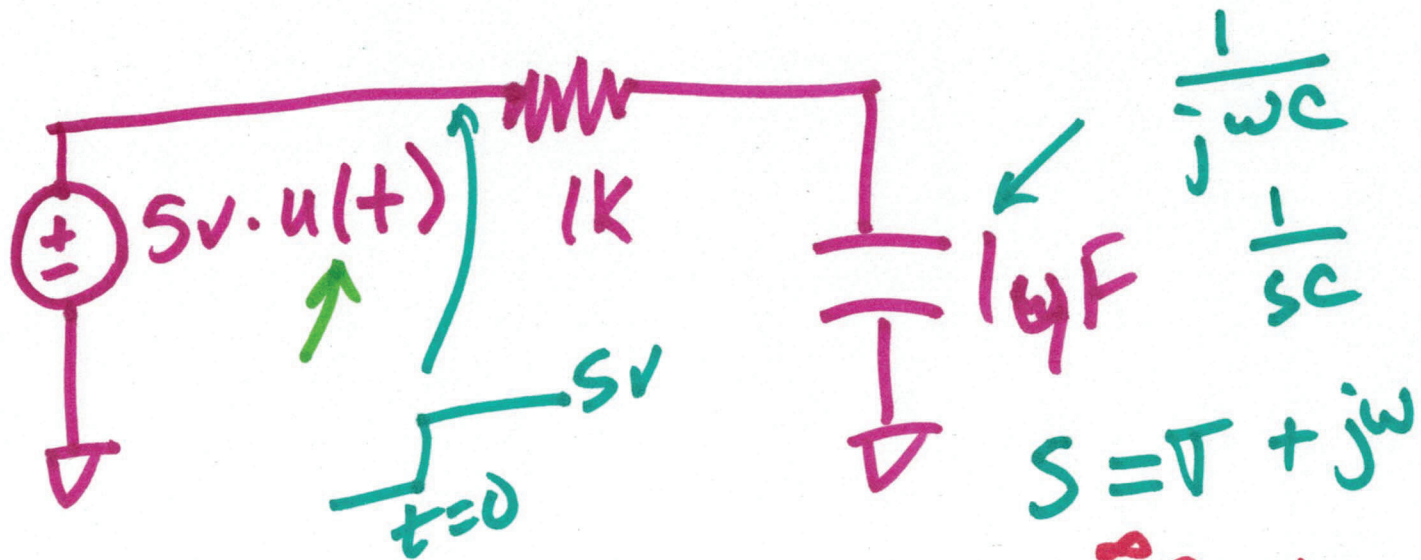

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} f(t) e^{-st} \cdot dt$$

$$\int_0^{\infty} e^{-st} \cdot \frac{dz}{-s} = -\frac{1}{s} \cdot \int_0^{\infty} e^{-z} dz$$

$$\mathcal{L}\{u(t)\} = \int_0^{\infty} u(t) e^{-st} \cdot dt = \int_0^{\infty} e^{-st} \cdot dt$$

$$\text{let } z = -st$$

$$\frac{dz}{dt} = -s \rightarrow dt = \frac{dz}{-s}$$

$$\mathcal{L}\{u(t)\} = \int_0^{\infty} u(t) \cdot e^{-st} dt$$


$$= -\frac{1}{s} \cdot \int_0^{\infty} e^z dz$$

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

$$= -\frac{1}{s} e^z \Big|_0^{\infty}$$

$$= (0 - e^0) \cdot -\frac{1}{s}$$

$$= \frac{1}{s}$$

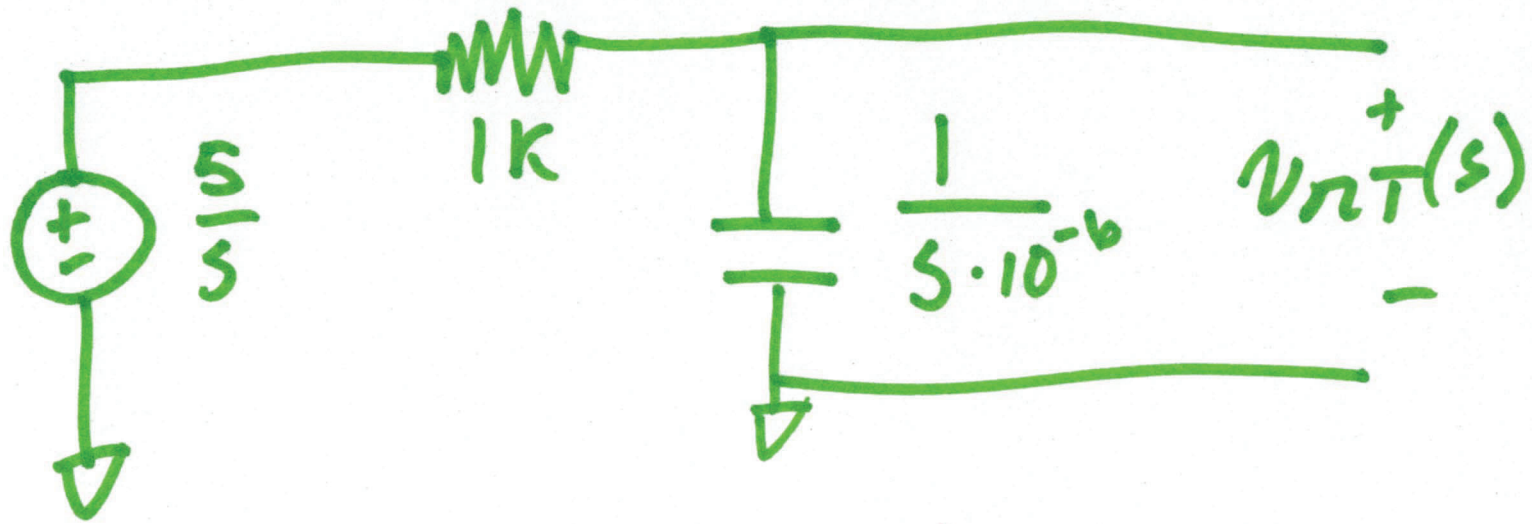

$$v_{OUT}(s) = \frac{5}{s} \cdot \frac{\frac{1}{s \cdot 10^{-6}}}{10^3 + \frac{1}{s \cdot 10^{-6}}}$$

$$= \frac{5}{s(1 + s \cdot 10^{-3})}$$

$$V_{out}(s) = \frac{\cancel{s} \cdot 5 \cdot 10^3}{\cancel{s} (10^3 + s \cdot \cancel{10^3})} = \frac{A \cdot \cancel{s}}{\cancel{s}} + \frac{B \cdot s}{s + 10^3}$$

$s = 0$

$$\frac{5 \cdot 10^3}{10^3} = A + 0$$

$$A = 5V$$

$$\frac{5 \cdot 10^3}{s} = \frac{A}{s} (s + 10^3) + B$$

$s = -10^3$


$$\boxed{-5 = B}$$

11)


$$\mathcal{L}^{-1}\{V_{out}(s)\} = \mathcal{L}^{-1}\left\{\frac{5}{s} + \frac{-5}{s+10^3}\right\}$$

$$v_{out} = 5u(t) + -5e^{-10^3 \cdot t} \cdot u(t)$$
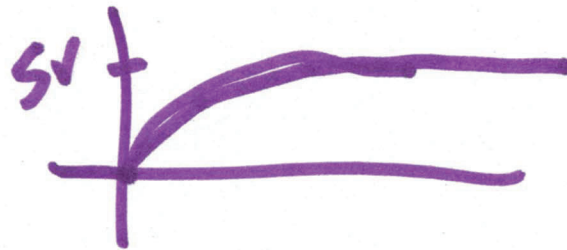
$$v_{out}(t) = 5(1 - e^{-t/10^{-3}}) \cdot u(t)$$



12)

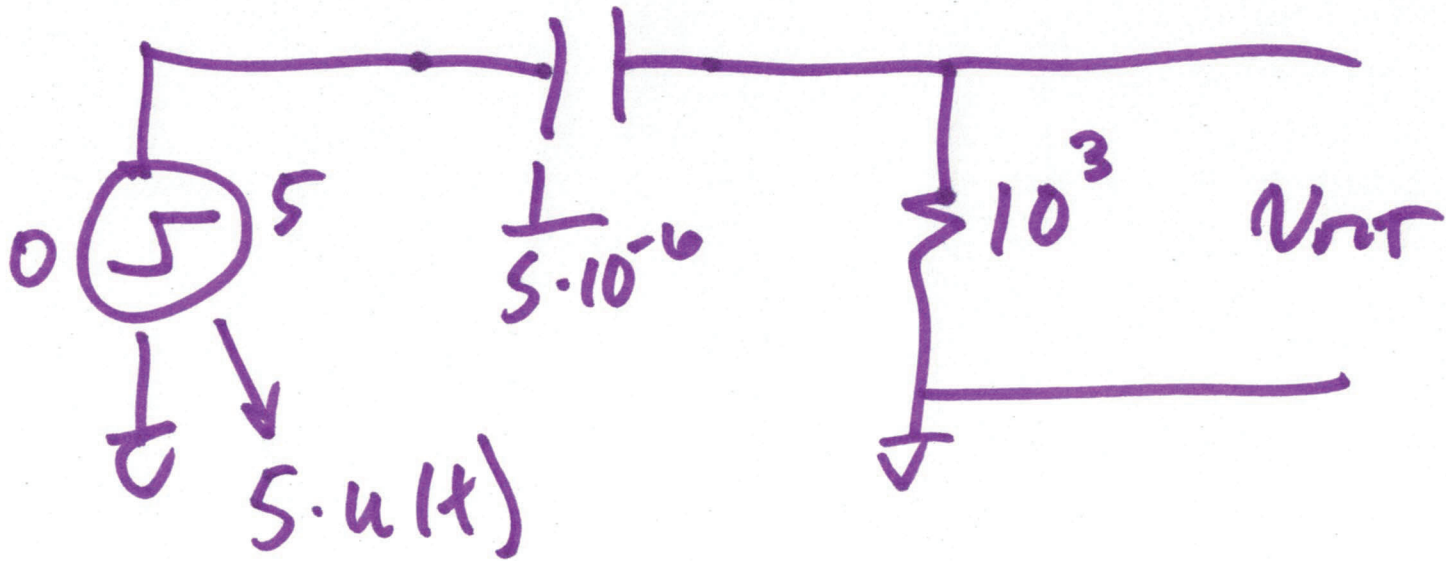

$$\begin{aligned}
 V_{NVT}(s) &= \frac{5}{s} \cdot \frac{10^3}{10^3 + \frac{1}{5 \cdot 10^{-6}}} \\
 &= \frac{5 \cdot 5 \cdot 10^{-3}}{s(s \cdot 10^{-3} + 1)}
 \end{aligned}$$

9)

$$V_{out}(s) = \frac{5 \cdot s}{s(s + 10^3)}$$

$$v_{out}(t) = 5 \cdot e^{-10^3 \cdot t} u(t)$$

$$v_{out}(t) = 5 e^{-t/10^{-3}} \cdot u(t)$$

