

Lecture 17

March 31, 2021

EE 221

Circuits II

$$\mathcal{F}\{f(t)\} = \int_0^{\infty} f(t)e^{-st} \cdot dt$$

$$u_t(t) = 1 \quad t > 0$$

$$\mathcal{F}\{u_t(t)\} = \int_0^{\infty} e^{-st} \cdot dt$$

$$\text{let } u = -st \rightarrow t = \frac{u}{-s}$$

$$du = -s \cdot dt$$

$$-s dt = \frac{du}{-s}$$

$$\mathcal{L}\{u(t)\} = \int_0^{-\infty} e^u \cdot \frac{du}{-s}$$

$$\lim_{u \rightarrow -\infty} e^u = 0$$
$$e \cdot e^s$$

$$= -\frac{1}{s} \int_0^{-\infty} e^u \cdot du$$

$$= -\frac{1}{s} e^u \Big|_0^{-\infty \cdot s} = -\frac{1}{s} (e^{-\infty \cdot s} - 1)$$

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

$$\mathcal{L}\{e^{-at}\} = \int_{-\infty}^{\infty} e^{-at} \cdot e^{-st} \cdot dt$$

$$= \int_0^{\infty} e^{-(a+s)t} \cdot dt$$


let $u = -(a+s)t$

$du = -(a+s)dt$


$$= \int_0^{\infty} e^u \cdot \frac{du}{-(a+s)} = \frac{-1}{a+s} e^u \Big|_0^{\infty}$$

$$= \frac{1}{a+s}$$

5)

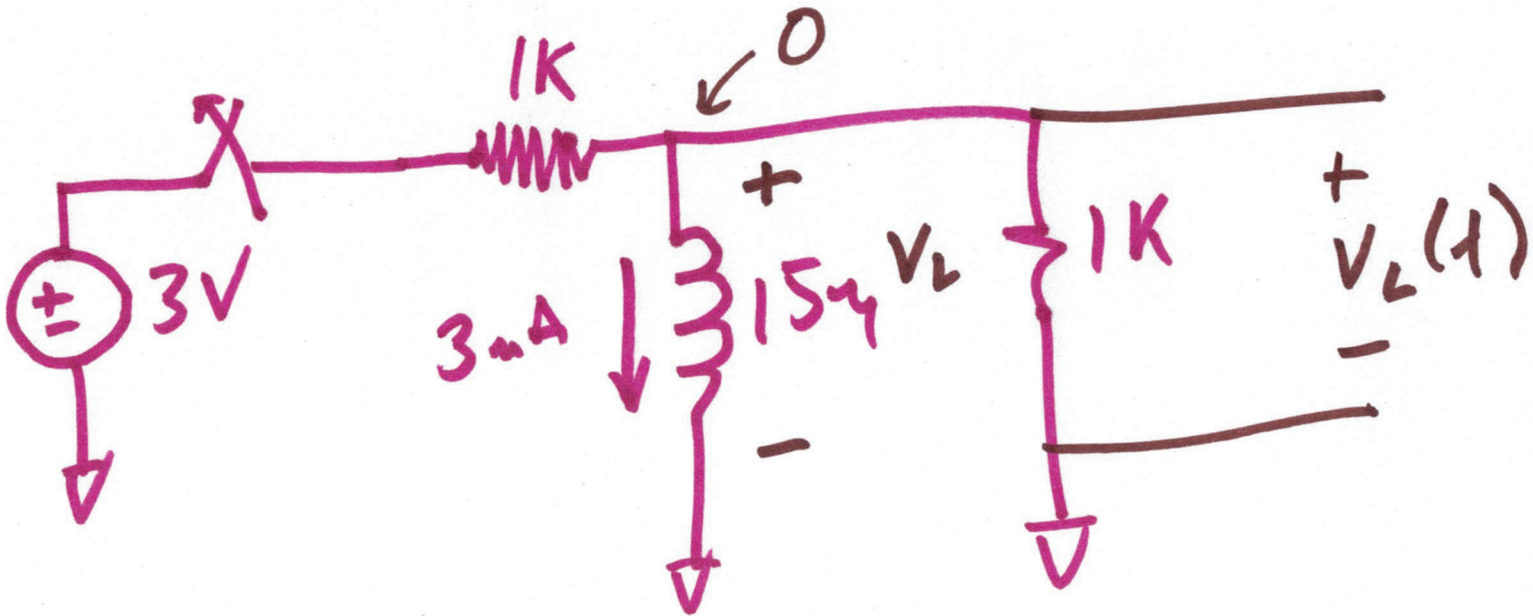

$$s \cdot L - i_L(0^-) \cdot L$$

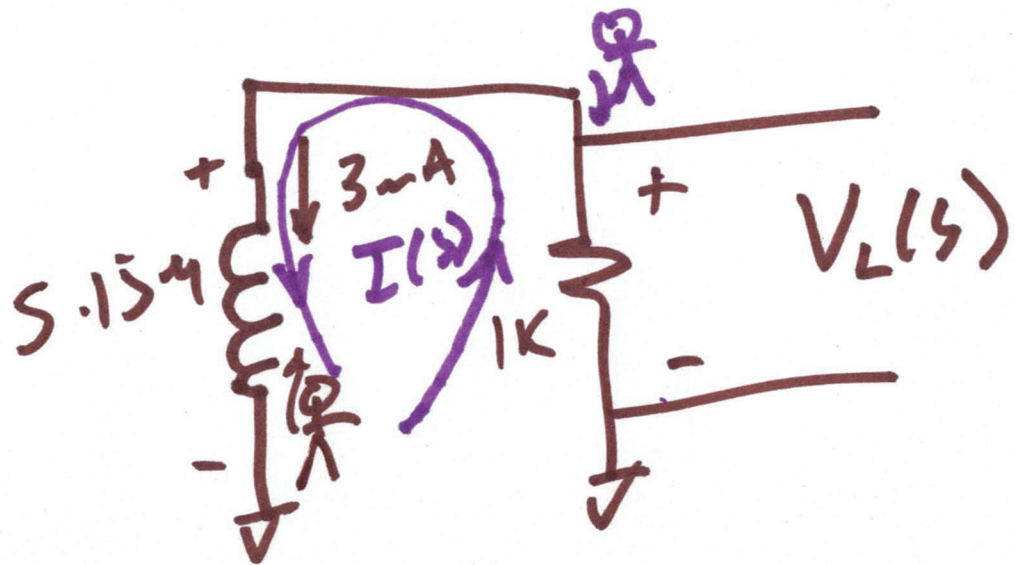

$$+s \cdot 154 \cdot I(s) - 154 \cdot 3 \mu A - 1K(-I(s)) = 0$$

$$I(s) \cdot (s \cdot 154 + 1K) = 154 \cdot 3 \mu A$$

$$+ 1K \cdot (-i_L)$$

$$\mathcal{L}^{-1}\{I(s)\} = \mathcal{L}^{-1}\left\{ \frac{3 \mu A}{s + \frac{1K}{154}} \right\}$$

$$i_L(t) = 3 \mu A \cdot e^{-\frac{1K}{154} \cdot t}$$


$$= 3 \mu A \cdot e^{-\frac{t}{\frac{154}{1K}} \cdot \frac{V}{R}}$$

$$v_L(t) = \frac{-1K \cdot 3 \mu A}{-3V} \cdot e^{-\frac{t}{\frac{154}{1K}}}$$

CMOSedu.com

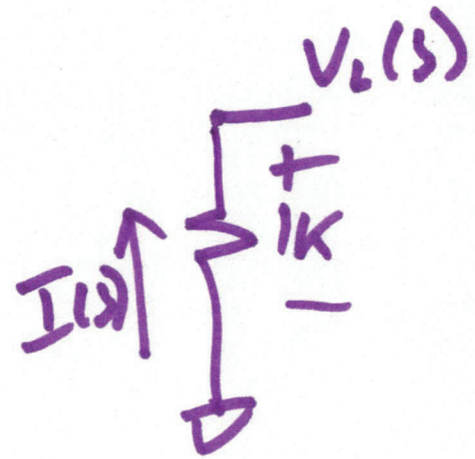5)

$$I(s) = \frac{3 \text{ mA}}{s + \frac{1\text{K}}{15\mu}}$$




$$V_L(s) = 1\text{K} \cdot (-I_L(s))$$

$$V_L(s) = \frac{-3\text{V}}{s + \frac{1\text{K}}{15\mu}}$$

$$V_L(t) = -3 e^{-\frac{1\text{K}}{15\mu} t} = -3 e^{-\frac{t}{15\mu/1\text{K}}}$$

$$v_i(t) = -3e^{-\frac{(t-1\mu)}{15\mu}} \cdot u(t-1\mu)$$

$u(t-t_0)$

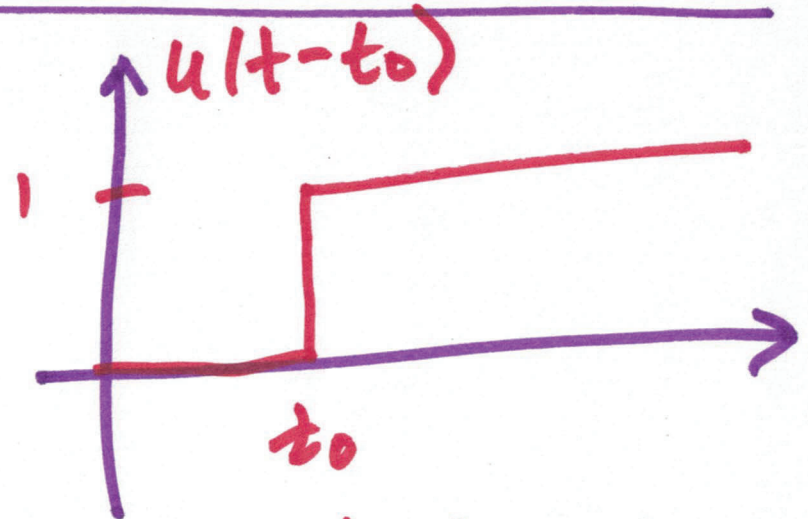

$$\int_0^{\infty} u(t-t_0) \cdot e^{-st} \cdot dt$$

$$\int_{t_0}^{\infty} e^{-st} \cdot dt \rightarrow \int_{-st_0}^{-s\infty} e^u \cdot \frac{du}{-s}$$

$$\text{at } u = -st$$

$$du = -s \cdot dt$$

t_0 is pos.




$$\mathcal{L}\{u(t-t_0)\} = \frac{1}{s} e^{-st_0} \Big|_{-\infty}^{-st_0}$$

$$= \frac{1}{s} (e^{-\infty s} - e^{-st_0})$$

$$= \frac{1}{s} (\cancel{e^{-\infty s}} - e^{-st_0})$$

$$= \frac{e^{-st_0}}{s}$$

8)

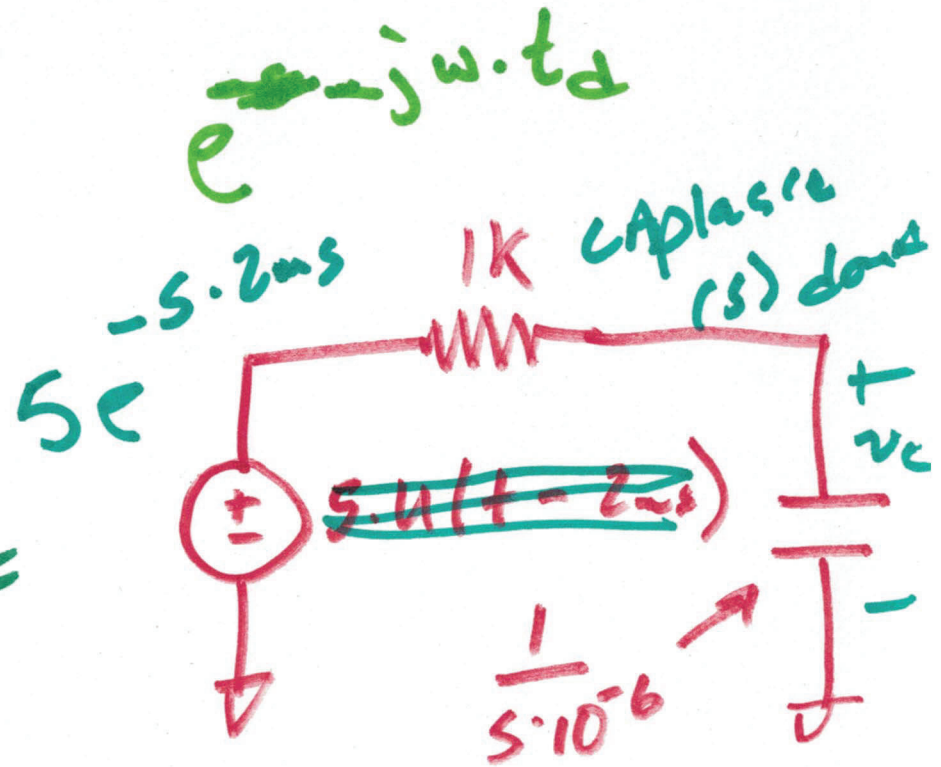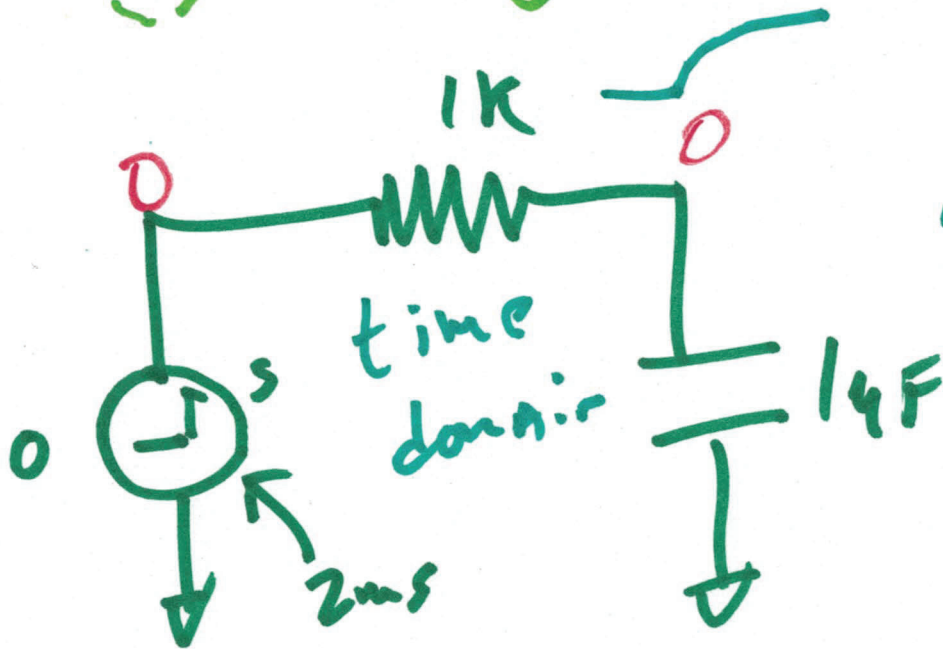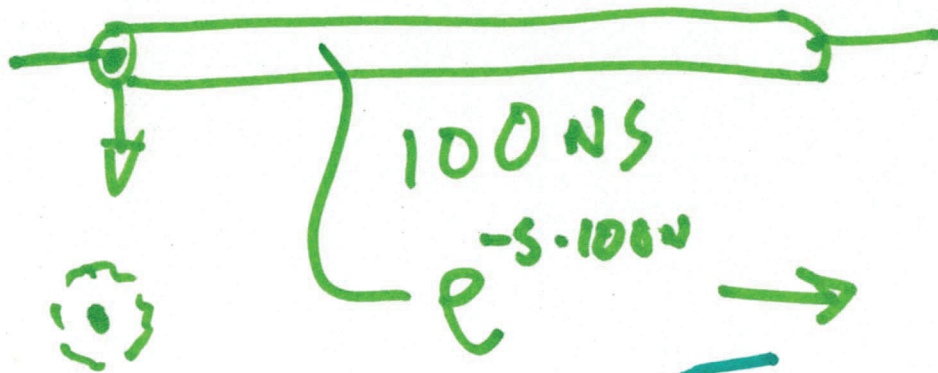

$$v_c = \frac{5e^{-s \cdot 2ms} \cdot \frac{1}{s \cdot 10^{-6}}}{\frac{1}{s \cdot 10^{-6}} + 1K}$$

9)



$$v_c(t) = 5 \cdot \cancel{u(t-2s)} \cdot \frac{1}{1 + 5 \cdot 10^{-3}}$$

$$= 5 \cdot 10^3 \cdot e^{-5 \cdot 2s} \cdot \frac{1}{5 + 10^3}$$

$$v_c(t) = 5 \cdot 10^3 \cdot e^{-10^3(t-2s)} \cdot u(t-2s)$$



10/

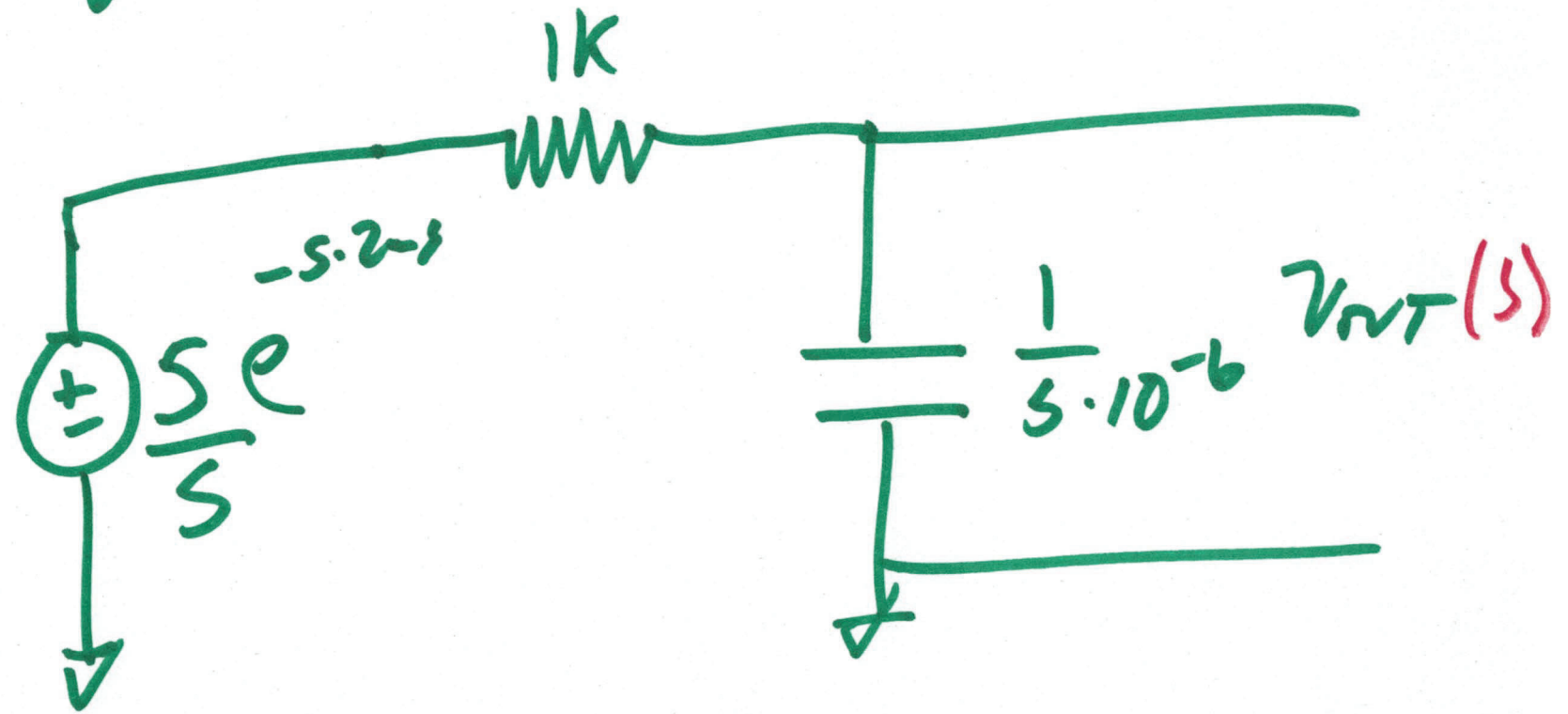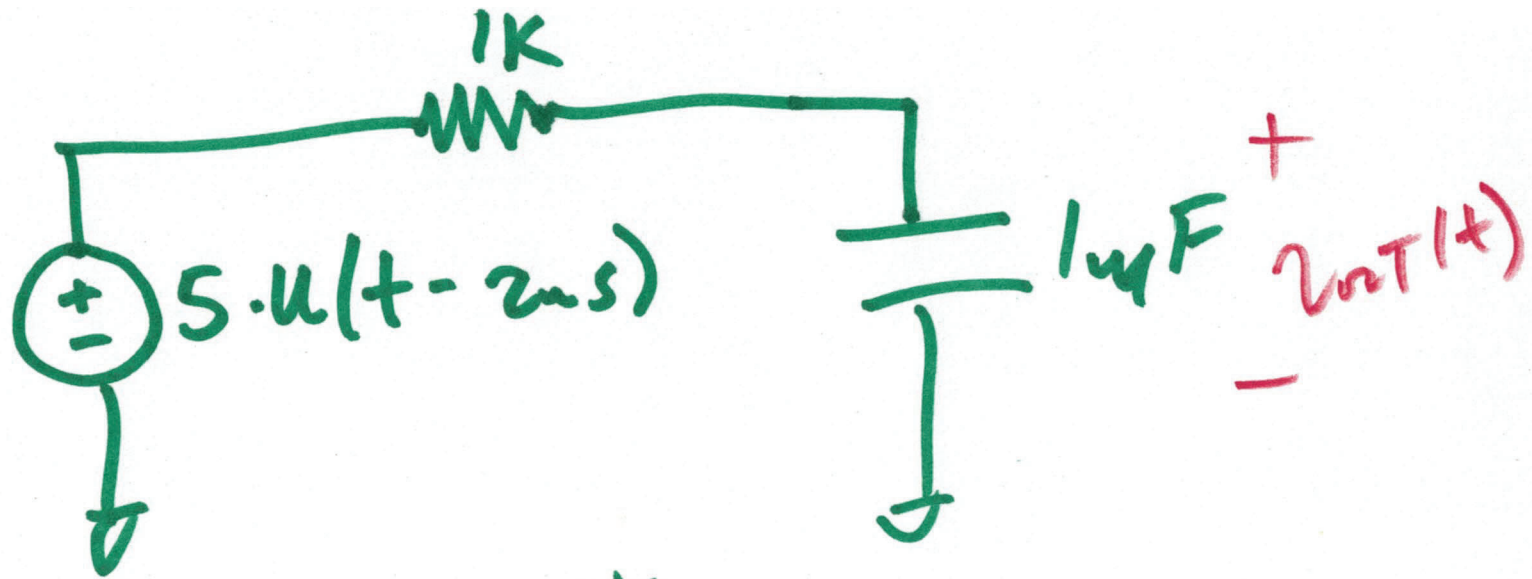

11)

$$\begin{aligned}
 V_o(s) &= \frac{5e^{-s \cdot 2ms}}{s} \cdot \frac{\frac{1}{s \cdot 10^{-6}}}{\frac{1}{s \cdot 10^{-6}} + 10^3} \\
 &= \frac{5e^{-s \cdot 2ms}}{s} \cdot \frac{1}{1 + s \cdot 10^{-3}} \\
 &= \frac{5 \cdot 10^3 \cdot e^{-s \cdot 2ms}}{s} \cdot \frac{1}{s + 10^3}
 \end{aligned}$$

(12)

$$V_0(s) = \frac{5 \cdot 10^3 e^{-s \cdot 2ms}}{s(s+10^3)} = \frac{A \cdot s}{s} + \frac{B \cdot s}{s+10^3}$$

$$s=0$$

$$= \frac{5 \cdot 10^3 e^0}{0+10^3} = \boxed{A=5} e^{-s \cdot 2ms}$$

$$V_0(s) = \frac{5 \cdot 10^3 e^{-s \cdot 2ms}}{s(s+10^3)} = \frac{A(s+10^3)}{s} + \frac{B(s+10^3)}{s+10^3}$$

$$s = -10^3$$

$$= \frac{5 \cdot 10^3 e^{+10^3 \cdot 2ms}}{-10^3} = B = -5e^{10^3 \cdot 2ms}$$

$$\begin{aligned}
 V_o(s) &= \frac{5 e^{-s \cdot 2\text{ms}}}{s} + \frac{-5 e^{s \cdot 2\text{ms}}}{s + 10^3} \\
 &= 5 \cdot u(t - 2\text{ms}) - 5 e^{-10^3 t} \cdot u(t - 2\text{ms}) \\
 &= 5 \left(1 - e^{-t/10^{-3}} \right) \cdot u(t - 2\text{ms})
 \end{aligned}$$

(14)