
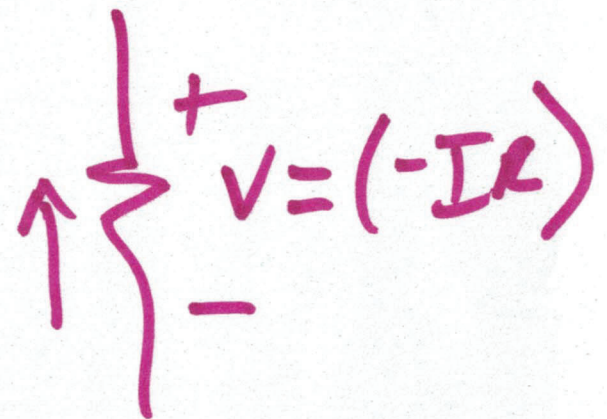



EE 221 Circuits II

Lecture 1


Jan. 20, 2021

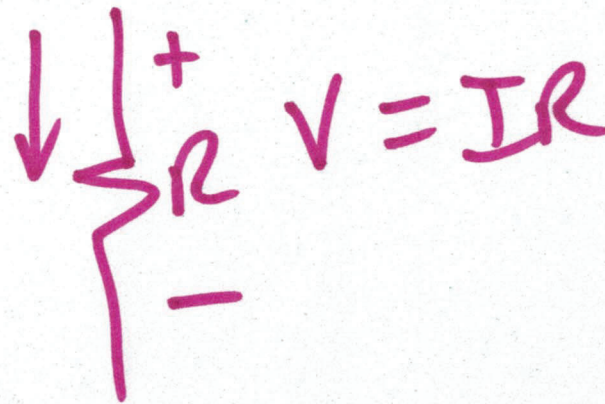Voltage = Current · Resistance
Volts Ampere Ω



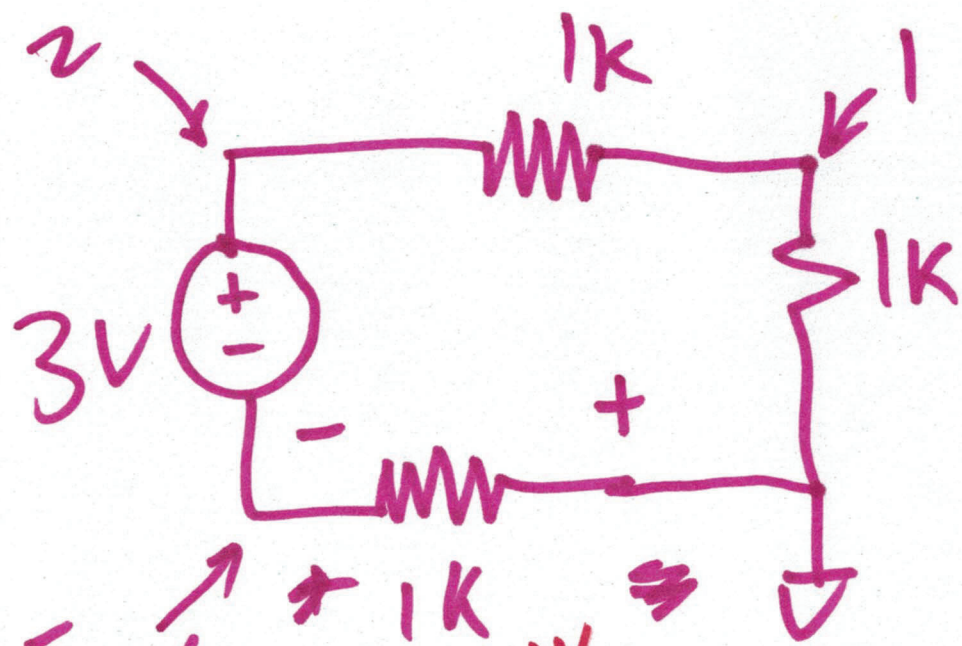

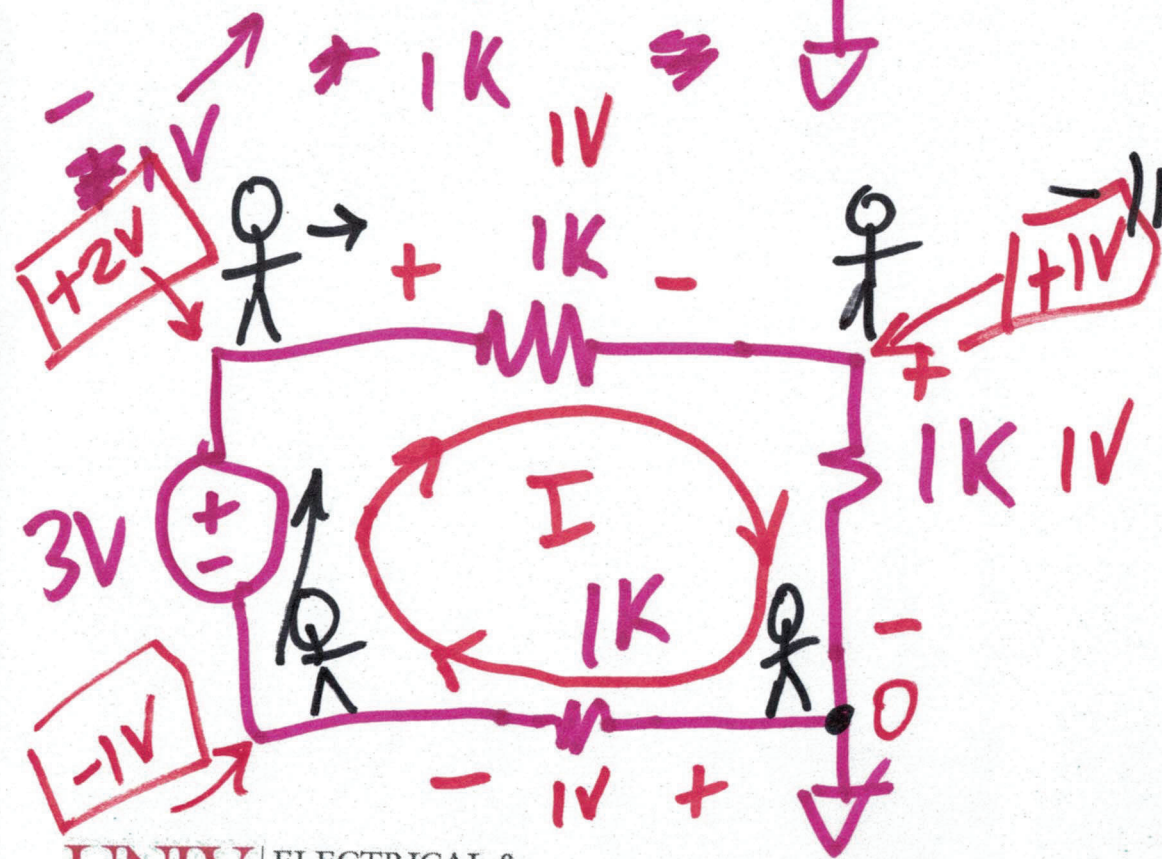
$$I \downarrow \begin{matrix} + \\ R \\ - \end{matrix} V = I \cdot R$$



$$1k \cdot I - 1k \cdot I - 1kI + 3 = 0$$

$$I = \frac{3}{3k} = 1 \mu A$$

2)

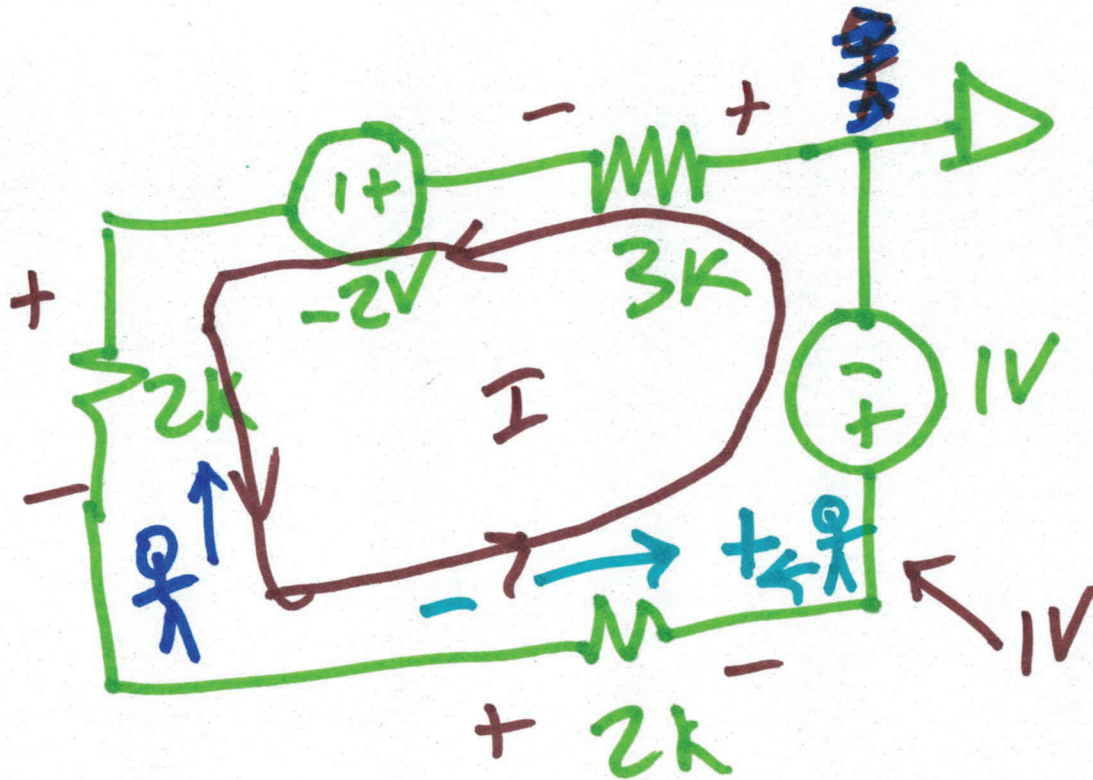

$$I \downarrow \begin{matrix} + \\ V \\ - \end{matrix} = IR$$


$$\begin{matrix} + \\ \uparrow I \\ - \end{matrix} V = -I \cdot R$$


$$I \cdot 2k + (-2V) + 3kI + 4V + 2kI = 0$$

$$= (-2kI) = 0$$

$$I(7k) + (-1) = 0$$

$$I = \frac{1}{7} \text{ mA}$$

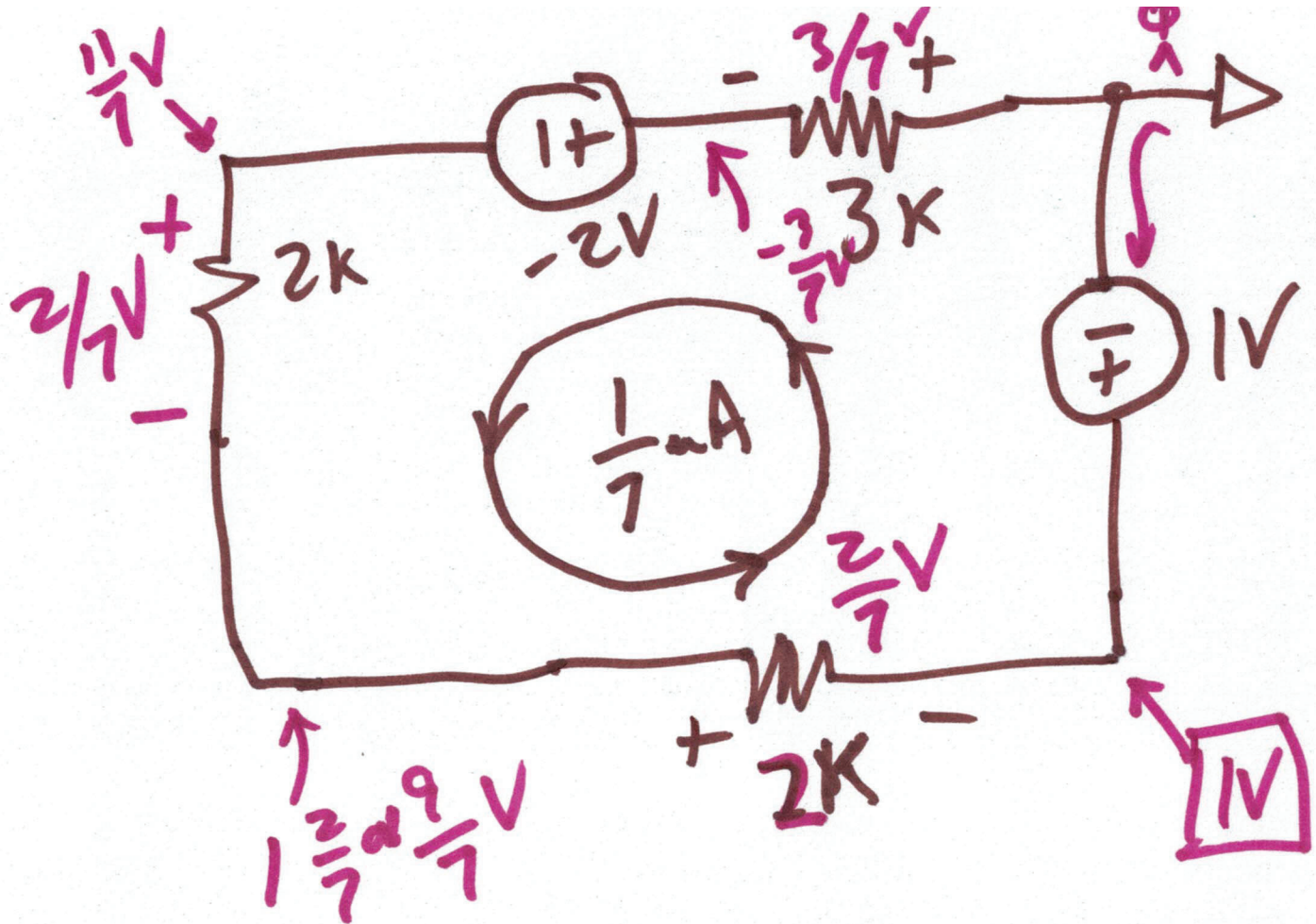

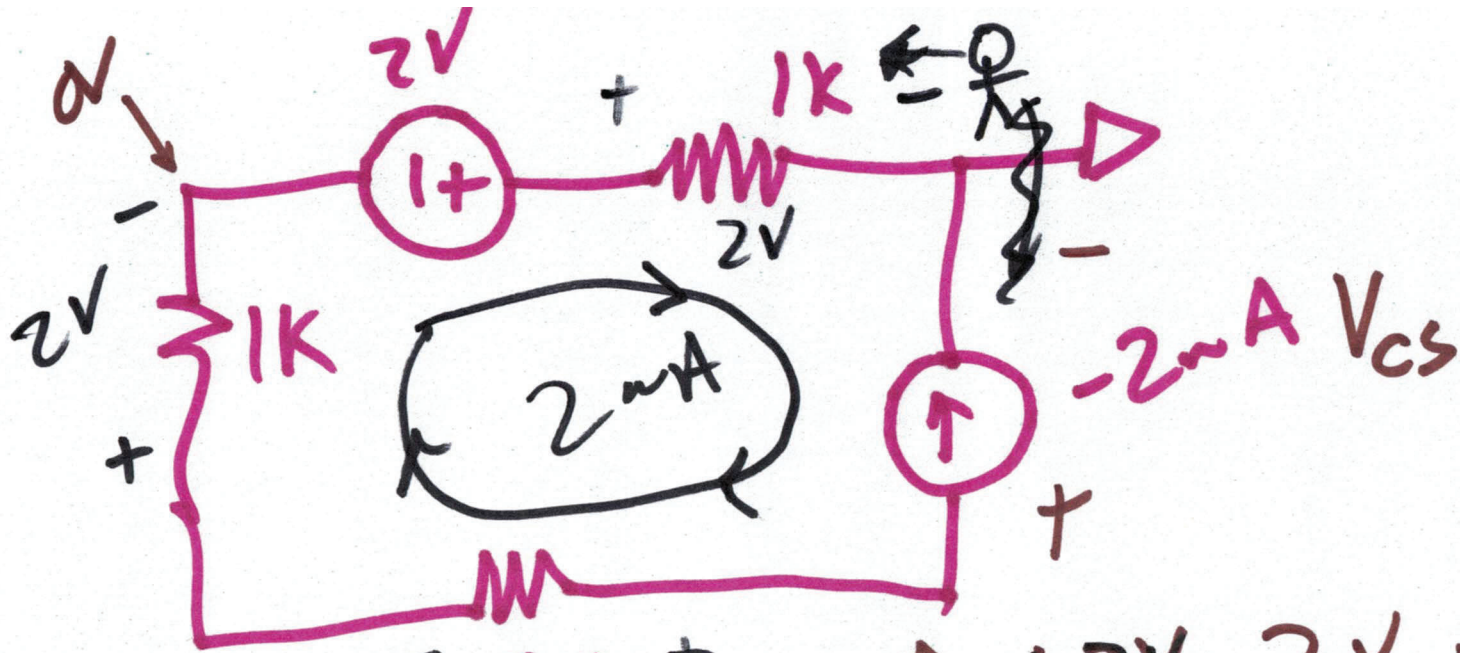


$$+2V - 2V + 2 + 10 - V_{cs} = 0$$

$$\boxed{+12V}$$

$$\boxed{V_{cs} = 12V}$$

5)

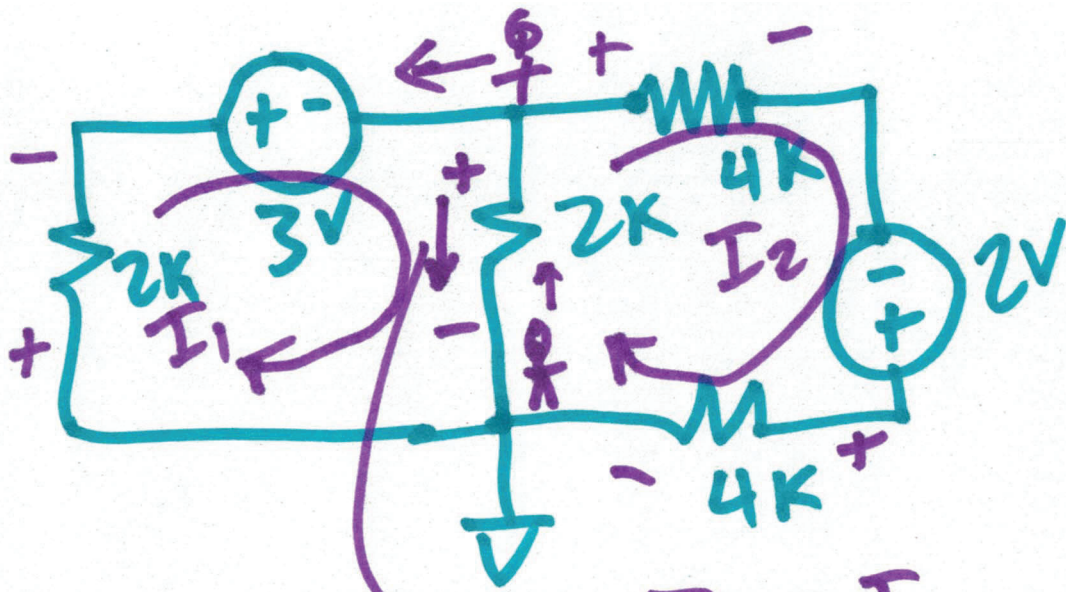

$$I = I_1 - I_2$$

$$+2k(I_1 - I_2) - 4k I_2 + 2 - 4k I_2 = 0$$

$$+2k(I_1 - I_2) + 3V + 2k I_1 = 0$$

$$4k \cdot I_1 + 3V - 2k I_2 = 0$$

$$4k \cdot I_1 = 2k I_2 - 3$$

$$I_1 = \frac{I_2}{2} - \frac{3}{4}$$

6)

$$2kI_1 - 10kI_2 + 2 = 0$$

$$I_1 = \frac{I_2}{2} - \frac{3}{4} \text{ mA}$$

$$1kI_2 - 1.5V - 10kI_2 + 2V = 0$$


$$-9kI_2 = -\frac{1}{2}V$$

$$I_1 = -\frac{13}{18} \text{ mA}$$

$$I_2 = \frac{1}{18} \text{ mA}$$

$$I_1 = \frac{1}{36} \text{ mA} - \frac{3}{4} \text{ mA}$$
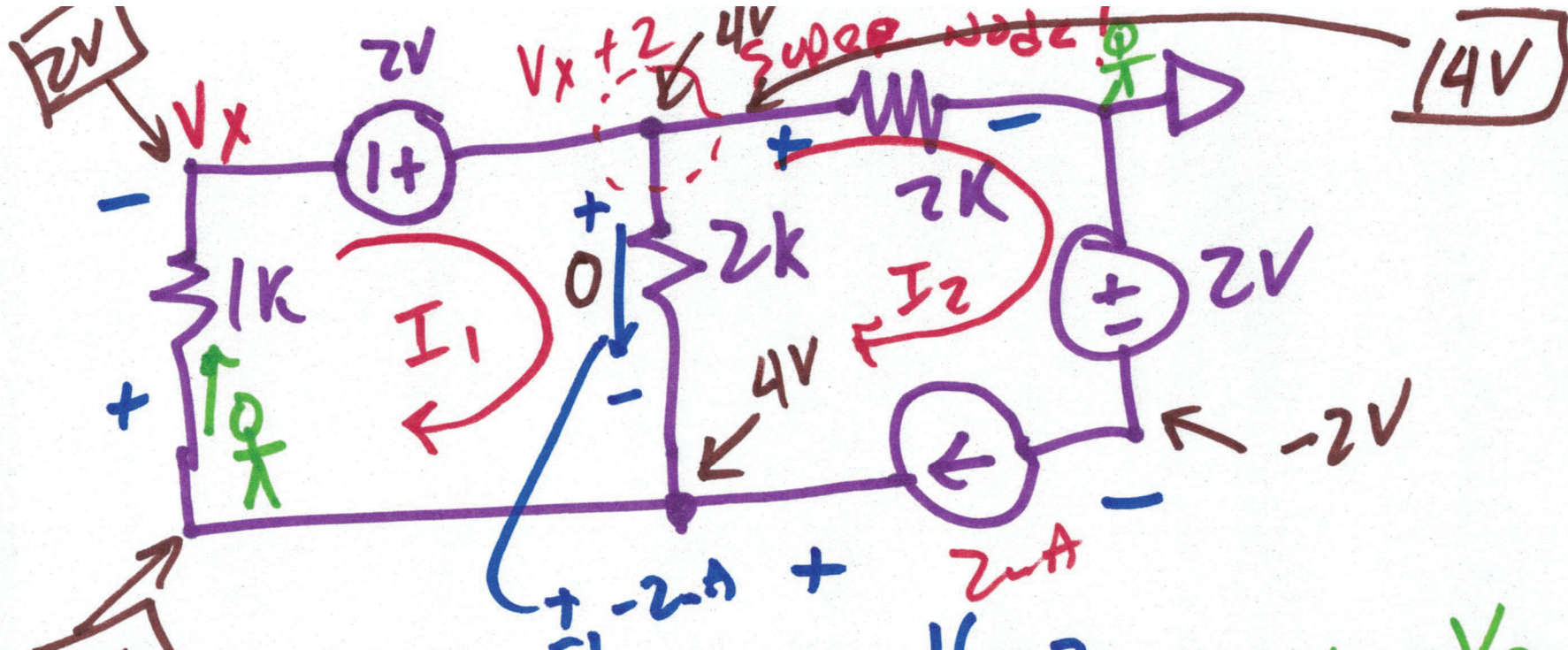
$$I_1 = -\frac{26}{36} \text{ mA} \Rightarrow \frac{1}{36} \text{ mA} - \frac{27}{36} \text{ mA}$$



$$-I_1 \cdot 1k + 2V - 2k \cdot (2mA) - 2V + V_2 = 0$$

$$-I_1 \cdot 1k + 2V - 2k(I_1 - 2mA) = 0$$

$$-3kI_1 + 4V = 0 \rightarrow I_1 = \frac{4}{3k}$$

$$I_1 = \frac{4}{3k} \text{ mA}$$

8)