

EE 221 Circuits II

April 12, 2021

Lecture 20

Problem solving



Tuesday

April 13

2:30 pm

TBE B-174



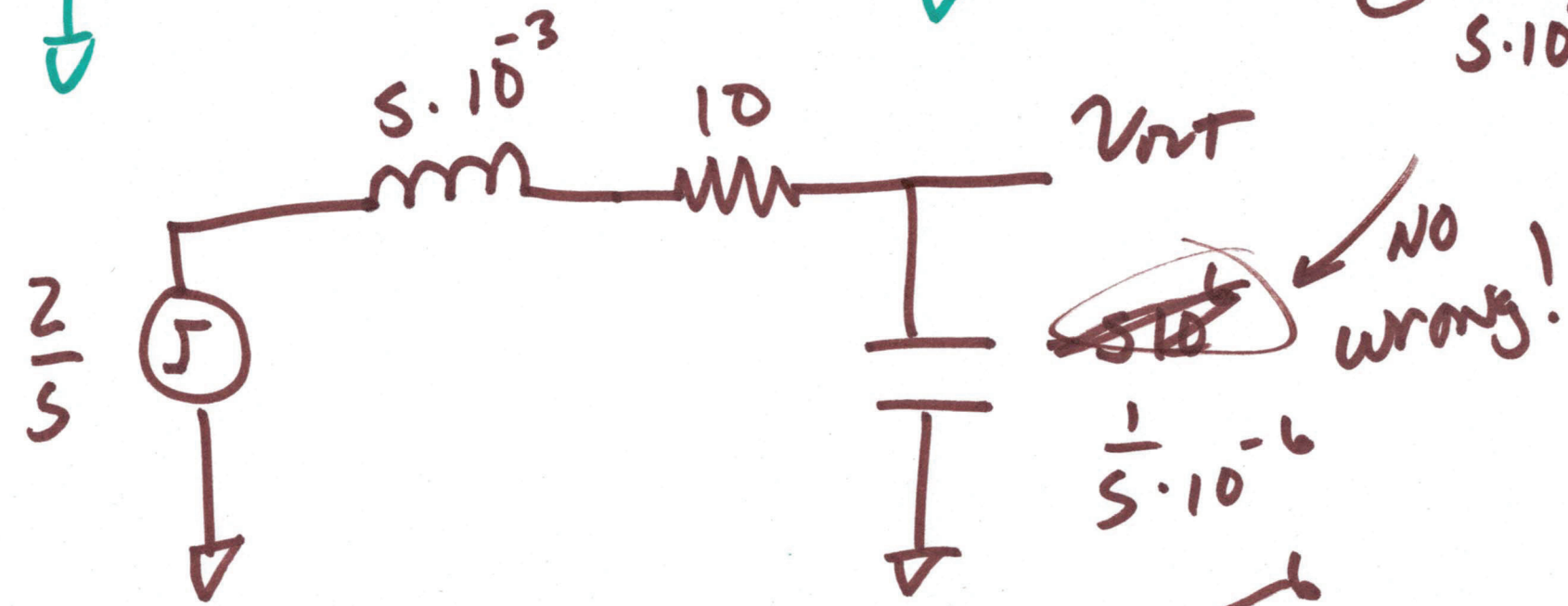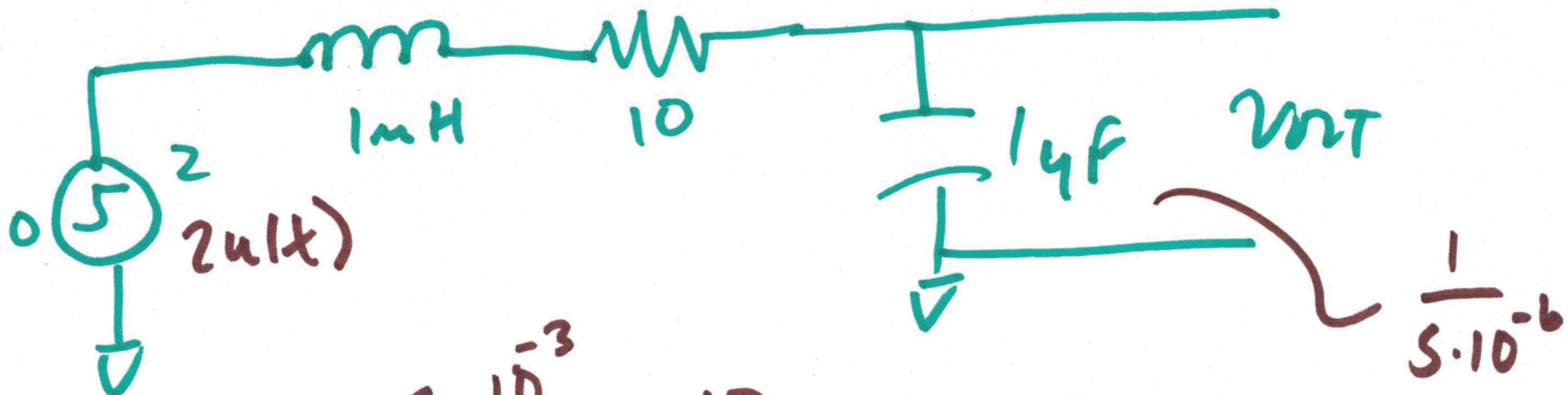

~~$$V_{out} = \frac{2}{s} \cdot \frac{10}{10 + s(10^{-3} - 10^6)}$$~~

2)

$$V_{out}(s) = \frac{2}{s} \cdot \frac{\frac{1}{5 \cdot 10^{-6}}}{\frac{1}{5 \cdot 10^{-6}} + 10 + s \cdot 10^{-3}}$$

$$= \frac{2}{s} \cdot \frac{1}{1 + s \cdot 10^{-5} + s^2 \cdot 10^{-9}}$$

$$s_{1,2} = \frac{-10^{-5} - \sqrt{4 \cdot 10^{-9} \cdot 1 + (10^{-5})^2}}{2 \cdot 10^{-9}}$$

$$\frac{10^9}{s^2 + s \cdot 10^4 + 10^9}$$

3)

$$V_{OUT}(s) = \frac{2}{s}$$

$$s = \frac{-10^4 \pm \sqrt{(10^4)^2 - 4 \cdot 10^9}}{10^9 \cdot 2}$$

$$\rightarrow \frac{1}{2} \left(-10^4 \pm \sqrt{10^8 - 4 \cdot 10^9} \right)$$

$$\frac{1}{2} \left(-10^4 \pm j \begin{matrix} 62.5k \\ \cancel{62.5k} \end{matrix} \right)$$

$$V_{out}(s) = \frac{2}{s} \cdot \frac{10^9}{\left(s + \left(\frac{1}{2}(-10^4 + j62.5k)\right)\right) \left(s + \left(\frac{1}{2}(-10^4 - j62.5k)\right)\right)}$$

$$\frac{A}{s} + \frac{B}{s - \frac{1}{2}(-10^4 + j62.5k)} + \frac{C}{s - \frac{1}{2}(-10^4 - j62.5k)}$$

$$A = \frac{2 \cdot 10^9}{\frac{1}{2}(-10^4 + j62.5k) \left(\frac{1}{2}(-10^4 - j62.5k)\right)}$$

$$= \frac{-1}{4} - 10^8 - \cancel{j10^4 \cdot 62.5k} + \cancel{j10^4 \cdot 62.5k} - (62.5k)^2$$

$$A = \frac{2 \cdot 10^9}{-\frac{1}{4} \cdot 10^8 - (62.5k)^2} = -\frac{1}{2}$$

$$B = \frac{2}{s} \cdot \frac{10^9}{s - \left(\frac{1}{2}(10^4 + j62.5k)\right)}$$

$$B = \frac{2}{s} \cdot \frac{10^9}{\frac{1}{2}(-10^4 + j62.5k) - \frac{1}{2}(10^4 + j62.5k)}$$

$$s = +\frac{1}{2}(-10^4 + j62.5k)$$

$$B = \frac{10^9}{-10^4}$$

$$= \boxed{-10^5 = B}$$

CMOSedu.com

6)

$$B = \frac{2}{\frac{1}{2}(-10^4 + j67.5k)} \cdot \frac{10^9}{-10^4}$$

$$= \frac{-4 \cdot 10^5}{\frac{1}{2} \cdot (-10^4 + j67.5k)}$$

$$C = \frac{-4 \cdot 10^5}{\frac{1}{2}(-10^4 - j67.5k)}$$

$$A = -\frac{1}{2}$$

1)

$$\begin{aligned}
 V_{out}(s) &= -\frac{1}{2} \frac{1}{s} + \frac{-4 \cdot 10^5}{(-10^4 + j62.5k)(s - \frac{1}{2}(-10^4 + j62.5k))} \\
 &+ \frac{-4 \cdot 10^5}{(-10^4 - j62.5k) \cdot s - \frac{1}{2}(10^4 + j62.5k)} \\
 &= -\frac{1}{2} \cdot \frac{1}{s} + \frac{-4 \cdot 10^5}{625 \cdot 10^6 L_{81}} \cdot \frac{1}{s - \frac{1}{2}(-10^4 + j62.5k)} \\
 &+ \frac{-4 \cdot 10^5}{625 \cdot 10^6 L_{81}} \cdot \frac{1}{s - \frac{1}{2}(10^4 + j62.5k)}
 \end{aligned}$$

8)

$$V_{out}(s) = -\frac{1}{2} \cdot \frac{1}{s} + \frac{-6.4 \times 10^{-4} \angle 81}{s - \frac{1}{2}(-10^4 + j67.5k)}$$

$$+ \frac{-6.4 \times 10^{-4} \angle 81}{s - \frac{1}{2}(-10^4 - j67.5k)}$$

$e^{j81} \cdot e^{\frac{1}{2}(-10^4 - j67.5k)t}$
 $+ e^{\frac{1}{2}(-10^4 + j67.5k)t}$

$$v_{out}(t) = -\frac{1}{2} u(t) - 6.4 \times 10^{-4} \left(e^{j81} \cdot e^{\frac{1}{2}(-10^4 - j67.5k)t} + e^{\frac{1}{2}(-10^4 + j67.5k)t} \right)$$

9)