

# EE 221 Circuits II

April 14, 2021

Lecture 21



$$v_{out}(t) = 2 + 2e^{-t/2004} \cdot \cos(31.25\pi t - 189)$$

$$t=0 \quad 2 + 2 \cdot 1 \cdot \frac{\cos(-189)}{\approx -1} \quad \begin{array}{l} 189 \cdot \frac{\pi}{180} \\ \approx 3.3 \end{array}$$

$2 - 2 = 0$

$$t = 2004s$$

$$2 + 2e^{-1} \cdot (-1) = 2 - .735 = 1.26V$$

$\downarrow$   
.37

$$31.25 \text{ k} \cdot t \quad -189$$

↑  
radians

↑  
deg.

$$2\pi \cdot f \cdot \frac{360}{2\pi}$$

$$\frac{31250}{2\pi} = f = 5 \text{ kHz}$$

$$(2\pi \cdot f) \frac{180}{\pi}$$


$$(31,250) \cdot \frac{180}{\pi} = 1.79 \text{e}6$$

$$-1 \approx \cos(1.79 \text{e}6 \cdot 200 \text{ns} - 189)$$

$$2 + 2e^{-1} \cdot \cos(31.25k \cdot 200\mu - 3.3)$$

$$t = 200\mu \quad \approx -1$$

same answer

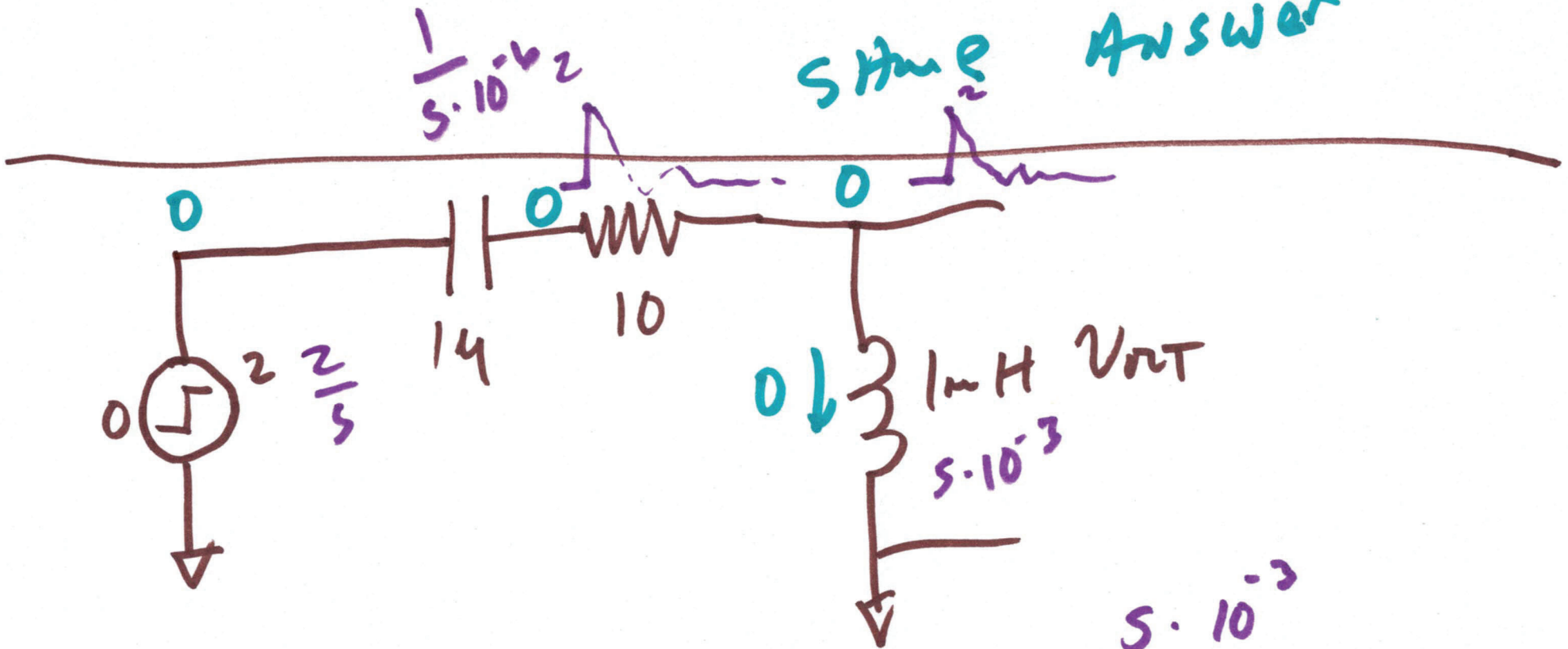

$$V_{out} = \frac{2}{s} \cdot \frac{5 \cdot 10^{-3}}{5 \cdot 10^{-3} + 10 + \frac{1}{5 \cdot 10^{-6}}}$$

37



$$V_{out}(s) = \frac{2 \cdot s^2 \cdot 10^{-9}}{s \cdot (s^2 \cdot 10^{-9} + s \cdot 10^{-5} + 1)}$$

$$= \frac{2 \cdot s^2}{s (s^2 + s \cdot 10^4 + 10^9)} = \frac{2 \cdot s}{s(s-p_1)(s-p_2)}$$

$$p_{1,2} = \frac{-10^4 \pm \sqrt{10^8 - 4 \cdot 10^9}}{2} = -5k \pm j 31.25k$$

$$V_{out}(s) = \frac{2 \cdot s}{(s-p_1)(s-p_2)} = \frac{A}{s-p_1} + \frac{B}{s-p_2}$$

$$v_{out}(t) = A e^{+p_1 t} + B e^{p_2 t} u(t)$$

4)

$$A|_{s=P_1} = \frac{2 \cdot P_1}{P_1 - P_2} = \frac{2 \cdot 31.65K \angle 99^\circ}{j \cdot 62.5K}$$

$$B|_{s=P_2} = \frac{2 \cdot P_2}{P_2 - P_1} = \frac{2 \cdot 31.65K \angle -99^\circ}{-j \cdot 62.5K}$$

$$P_1 = -5K + j31.25K \rightarrow$$


$$P_2 = -5K - j31.25K \rightarrow$$

$$31.65K \angle 99^\circ$$

$$31.65K \angle -99^\circ$$

$$31.65K e^{j99}$$

$$31.65K e^{j(-99)}$$

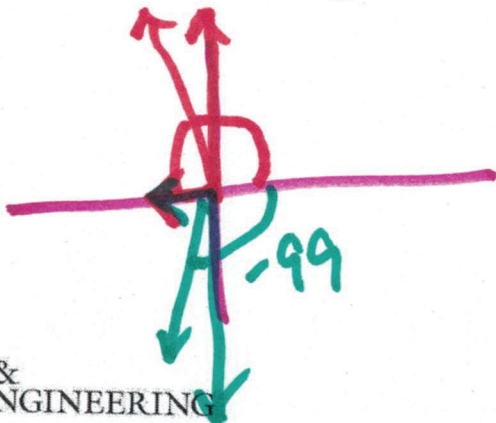

5)

$$A = \frac{63.3k \cdot \angle 99}{62.5k \angle 90} \approx 1 \angle 9 = e^{j9}$$

$$B = \frac{63.3k \angle -99}{62.5k \angle -90} \approx 1 \angle -9 = e^{-j9}$$

$$V_{out}(t) = e^{j9} e^{(-5k + j31.25k)t} + e^{-j9} e^{(-5k - j31.25k)t} \cdot u(t)$$

$$\cos x = \frac{e^{jx} + e^{-jx}}{2}$$

$$= 2 \cdot e^{-5kt} \left( \frac{e^{j(31.25k \cdot t + 9)} + e^{-j(31.25k \cdot t + 9)}}{2} \right) u(t)$$


$$5k = \frac{1}{200\mu}$$

b)





$$V_{out}(t) = 2e^{-t/200n} \cdot \cos(31.25kt + 9) \cdot u(t)$$

$$9 \cdot \frac{\pi}{180} = .157$$

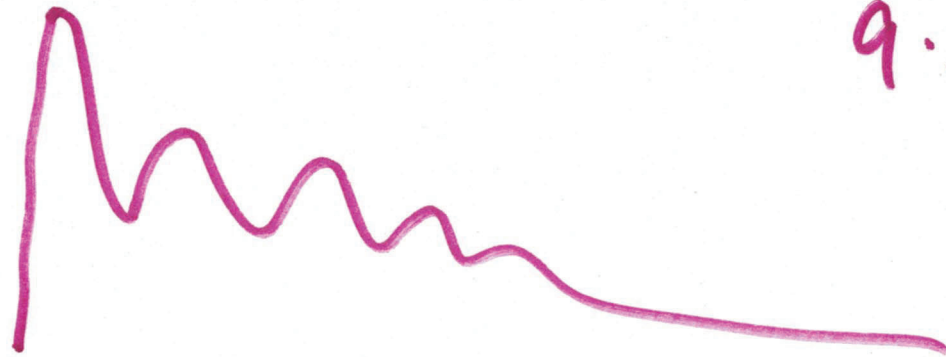

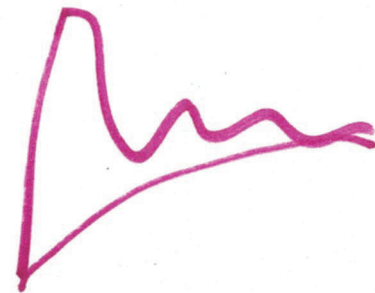
$$2 \cdot 6 \cdot (-1) = \underline{\underline{-1.2V}}$$



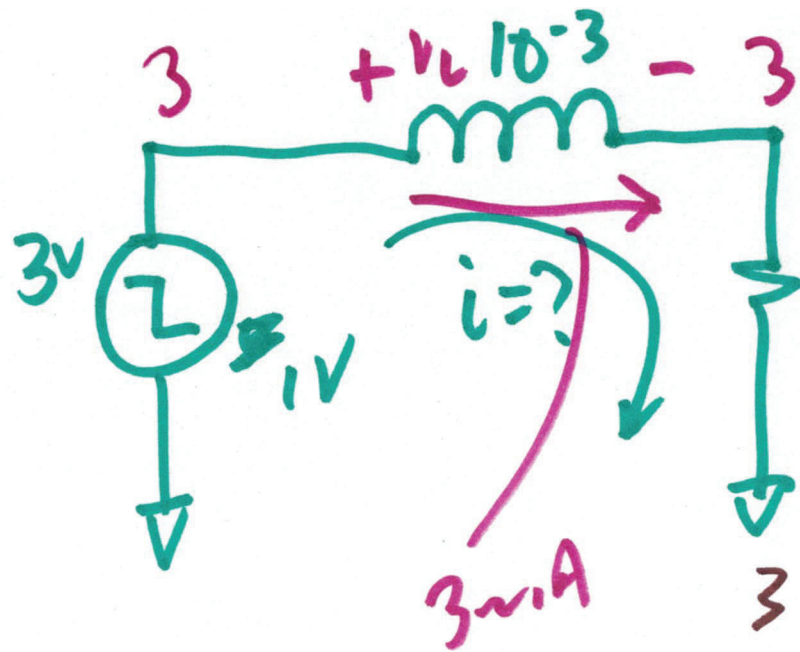


$$V_L = 5 \cdot 10^{-3} - 10^{-3} \cdot 3mA$$


$$3 - 2u(t) \rightarrow$$

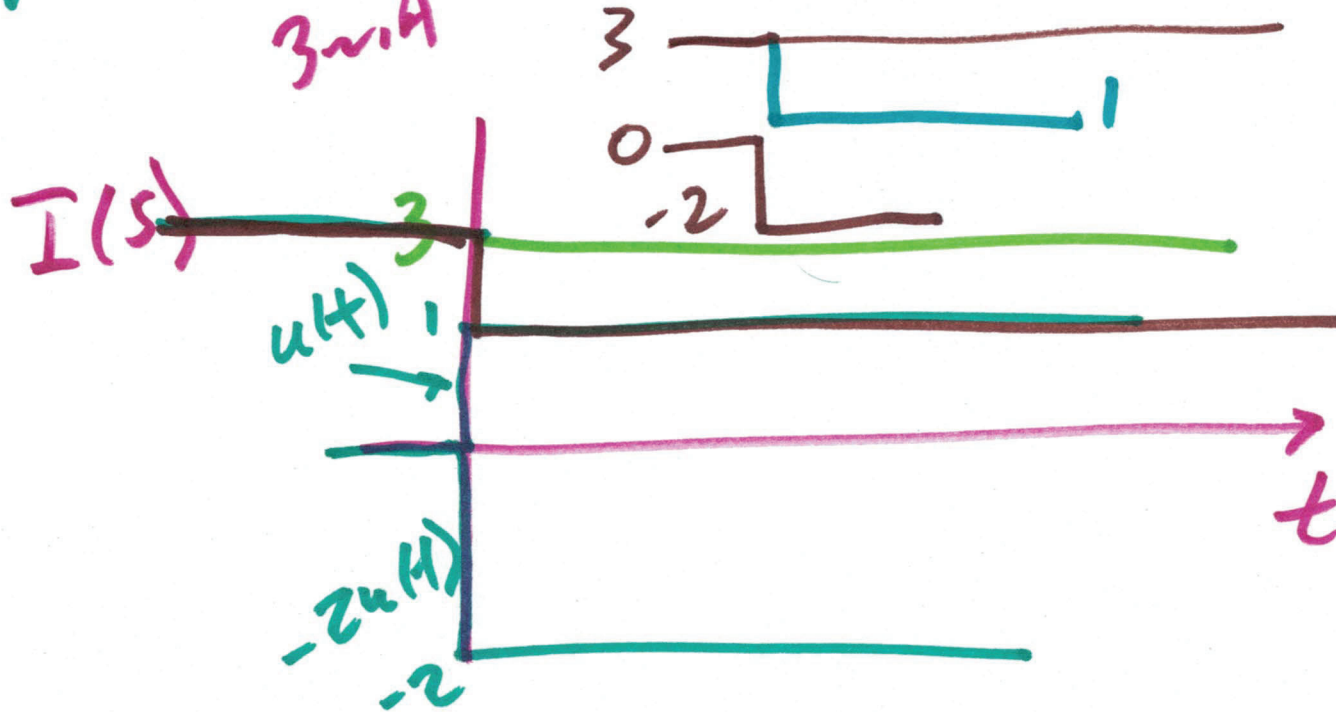



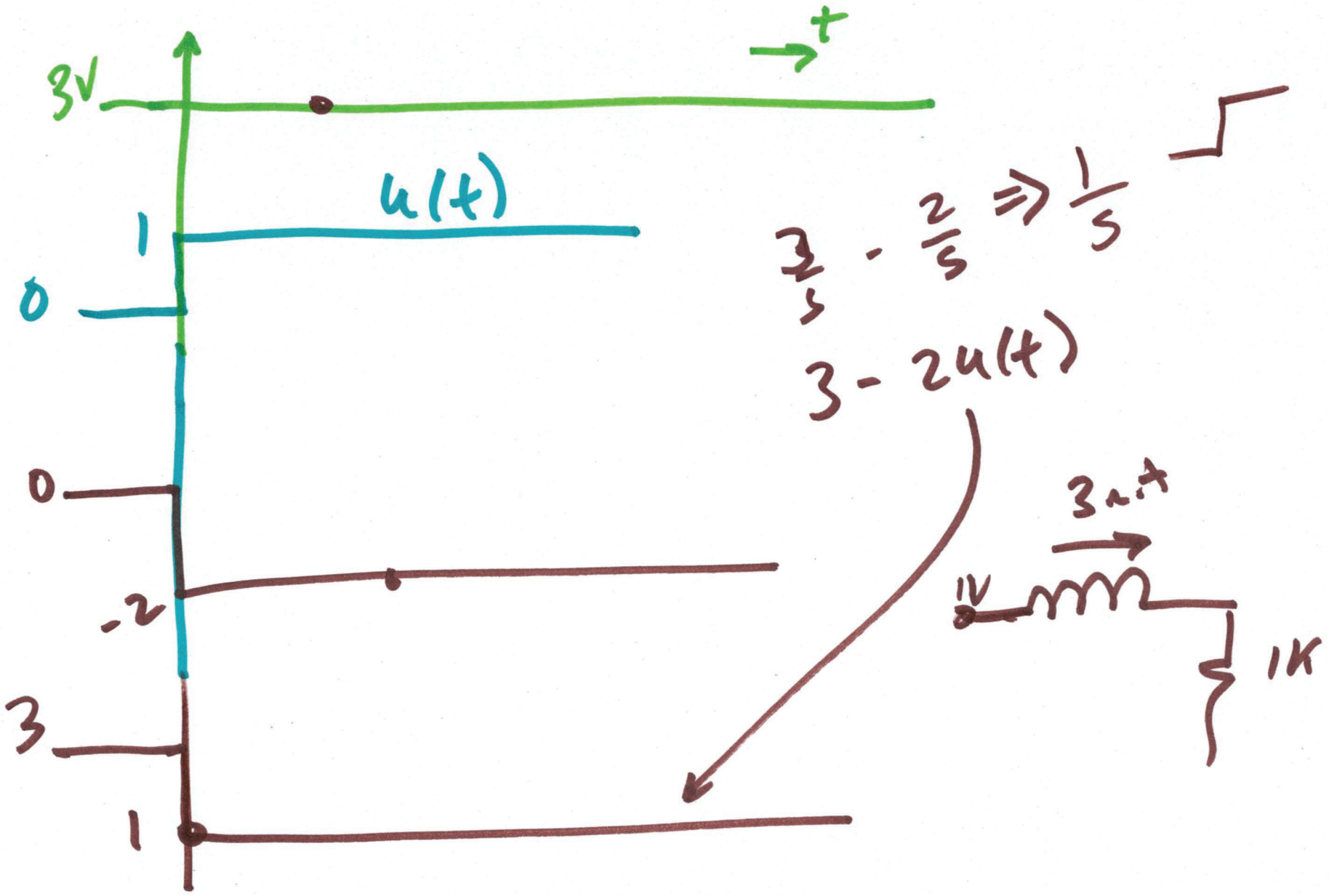
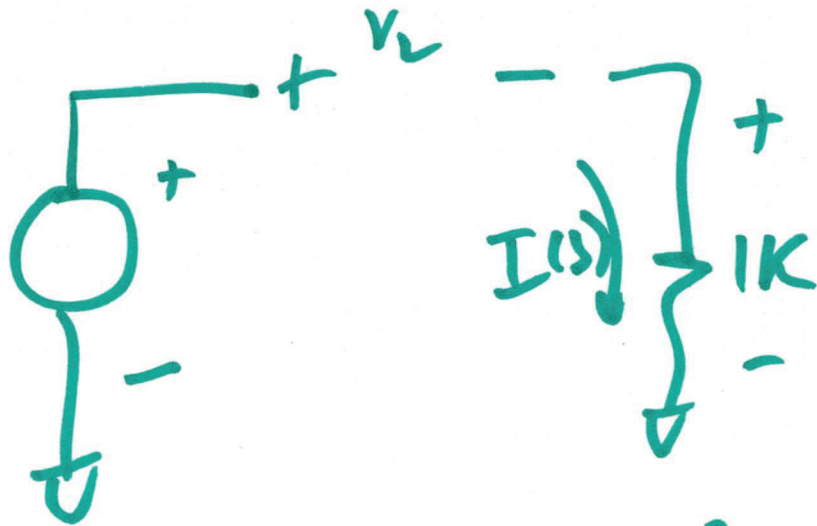
$$I(s) = \frac{\frac{1}{s}}{s \cdot 10^{-3} - 10^{-3} \cdot 3 \mu\text{A} \cdot \cancel{10^{-3}} \cdot 1\text{K}}$$



$$\frac{1}{s} - s \cdot 10^{-3} \cdot \frac{1}{I(s)} + 10^{-3} \cdot 3 \mu\text{A} - I(s) \cdot 1\text{K} = 0$$

$$I(s) = \frac{10^{-3}}{s} - s \cdot 10^{-6} + 10^{-3} \cdot 3 \mu\text{A}$$