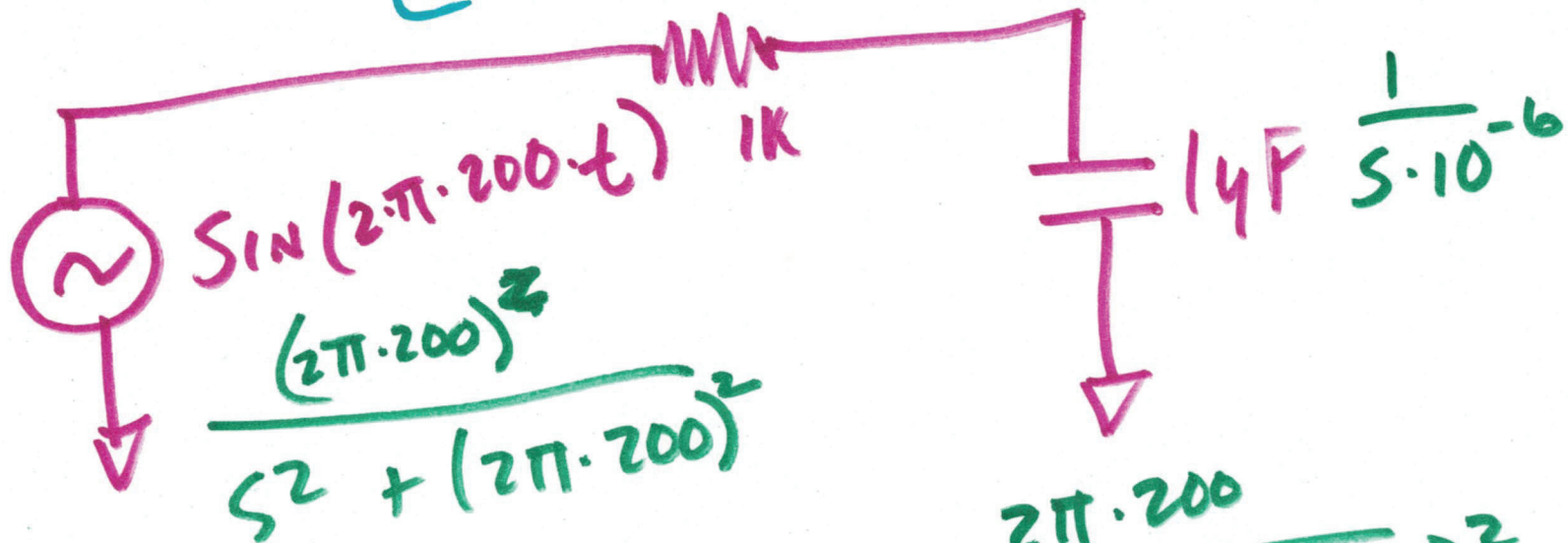


# EE 221 Circuits II

April 19, 2021

## Lecture 22



$$\frac{(2\pi \cdot 200)^2}{s^2 + (2\pi \cdot 200)^2}$$

$$I(s) =$$

$$\frac{2\pi \cdot 200}{s^2 + (2\pi \cdot 200)^2} \cdot \frac{1}{10^3 + \frac{1}{5 \cdot 10^{-6}}}$$

$$\bar{I}(s) = \frac{2\pi \cdot 200 \cdot s \cdot 10^{-6}}{(s^2 + (2\pi \cdot 200)^2) \cdot (10^3 + \frac{1}{s \cdot 10^{-6}}) \cdot s \cdot 10^{-6}}$$

$$\bar{I}(s) = \frac{2\pi \cdot 200 \cdot s \cdot 10^{-6} \cdot 10^3}{(s - p_1)(s - p_2)(s \cdot 10^{-3} + 1) \cdot 10^3}$$

$$= \frac{2\pi \cdot 0.2 \cdot s}{(s - p_1)(s - p_2)(s + 10^3)}$$

$$p_1, p_2 = \frac{\pm \sqrt{-4 \cdot (2\pi \cdot 200)^2}}{2} = \pm j 2\pi \cdot 200$$

2)

$$P_1 = j2\pi \cdot 200 = 2\pi \cdot 200 \angle 90 = 2\pi \cdot 200 e^{j90}$$

$$P_2 = -j2\pi \cdot 200 = 2\pi \cdot 200 \angle -90 = 2\pi \cdot 200 \cdot e^{-j90}$$

$$\frac{2\pi \cdot (0.2) \cdot s}{(s - P_1)(s - P_2)(s + 10^3)} = \frac{A}{s - P_1} + \frac{B}{s - P_2} + \frac{C}{s + 10^3}$$

$$A = \frac{2\pi \cdot 0.2 \cdot P_1}{(P_1 - P_2)(P_1 + 10^3)} = \frac{0.4\pi \cdot 2\pi \cdot 200 e^{j90}}{(j4\pi \cdot 200)(j2\pi \cdot 200 + 10^3)}$$

$$B = \frac{2\pi \cdot 0.2 \cdot P_2}{(P_2 - P_1)(P_2 + 10^3)} = \frac{0.4\pi \cdot 2\pi \cdot 200 e^{-j90}}{(-j4\pi \cdot 200)(-j2\pi \cdot 200 + 10^3)}$$

$$C = \frac{2\pi \cdot (0.2) \cdot (-10^3)}{(-10^3 - P_1)(-10^3 - P_2)}$$

3)



$$j2\pi \cdot 200 + 10^3 = 1605 \angle 51.5^\circ = 1605 e^{j51.5}$$

$$10^3 + j(-2\pi \cdot 200) = 1605 \angle -51.5^\circ = 1605 e^{-j51.5}$$

$$C = \frac{-0.4\pi \cdot 10^3}{(-10^3 - j2\pi \cdot 200)(-10^3 - (-j2\pi \cdot 200))}$$

$$= \frac{400\pi}{(10^3 + j2\pi \cdot 200)(-10^3 + j2\pi \cdot 200)}$$

$1605 e^{j51.5}$ 
 $1605 \angle 128.5$ 
 $\rightarrow \leftarrow \phi$

4)

$$A = \frac{0.9\pi \cdot \cancel{2\pi} \cdot 200 e^{j90}}{\cancel{2} 4\pi \cdot 200 e^{j90} \cdot 1605 e^{j51.5}} = 391.4 A e^{-j51.5}$$

$$B = 391.4 A e^{j51.5}$$

$$C = \frac{400\pi}{1605 e^{j51.5} \cdot 1605 e^{j28.5}} = \frac{400\pi}{(1605)^2} e^{j180}$$

$$C = -487.4 A$$

$$I(s) = \frac{3914 e^{-js1.5}}{s - j2\pi \cdot 200} + \frac{3914 e^{js1.5}}{s + j2\pi \cdot 200} + \frac{-4874}{s + 10^3}$$

$$i(t) = u(t) \cdot \left( 3914 \left( e^{-js1.5} \cdot e^{j2\pi \cdot 200 \cdot t} + e^{js1.5} \cdot e^{-j2\pi \cdot 200 \cdot t} \right) + (-4874) e^{-\frac{t}{10^{-3}}} \right)$$

6)

$$i(t) = u(t) \cdot \left( 391 \mu \cdot \frac{2}{2} \left( e^{j(2\pi \cdot 200t - 51.5)} + e^{-j(2\pi \cdot 200t - 51.5)} \right) + (-487 \mu e^{-t/10^{-3}}) \right)$$

$$i(t) = u(t) \cdot \left( 782 \mu \cos(2\pi \cdot 200t - 51.5^\circ) - 487 \mu e^{-t/10^{-3}} \right)$$


$360 \cdot 200 \cdot 1 \text{ ms} - 51.5$   
 $20.5$

$$486 - 487 \approx 0$$

$$732 - 180$$

$$e^{-0.37}$$



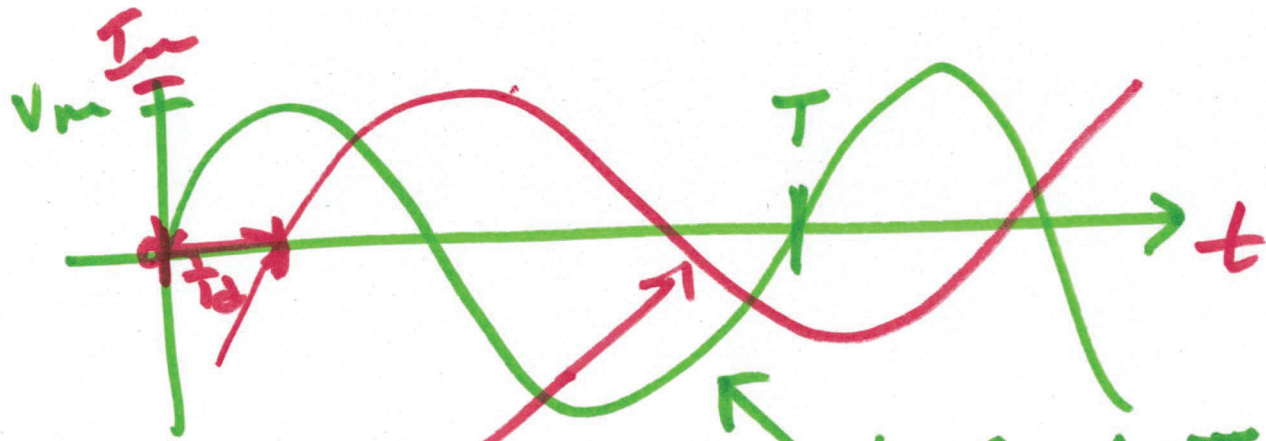

$$V_m \cdot \sin(2\pi \cdot f \cdot t)$$

$$= V_m \cdot \sin\left(2\pi \cdot \frac{1}{T} \cdot t\right)$$

$$I_m \sin\left(2\pi \cdot \frac{1}{T} \cdot t - \theta\right)$$


$$f = \frac{1}{T}$$

$$\theta = \frac{t_d}{T} \cdot 360 = t_d \cdot f \cdot 360$$

$$f = \frac{1}{T}$$

8)



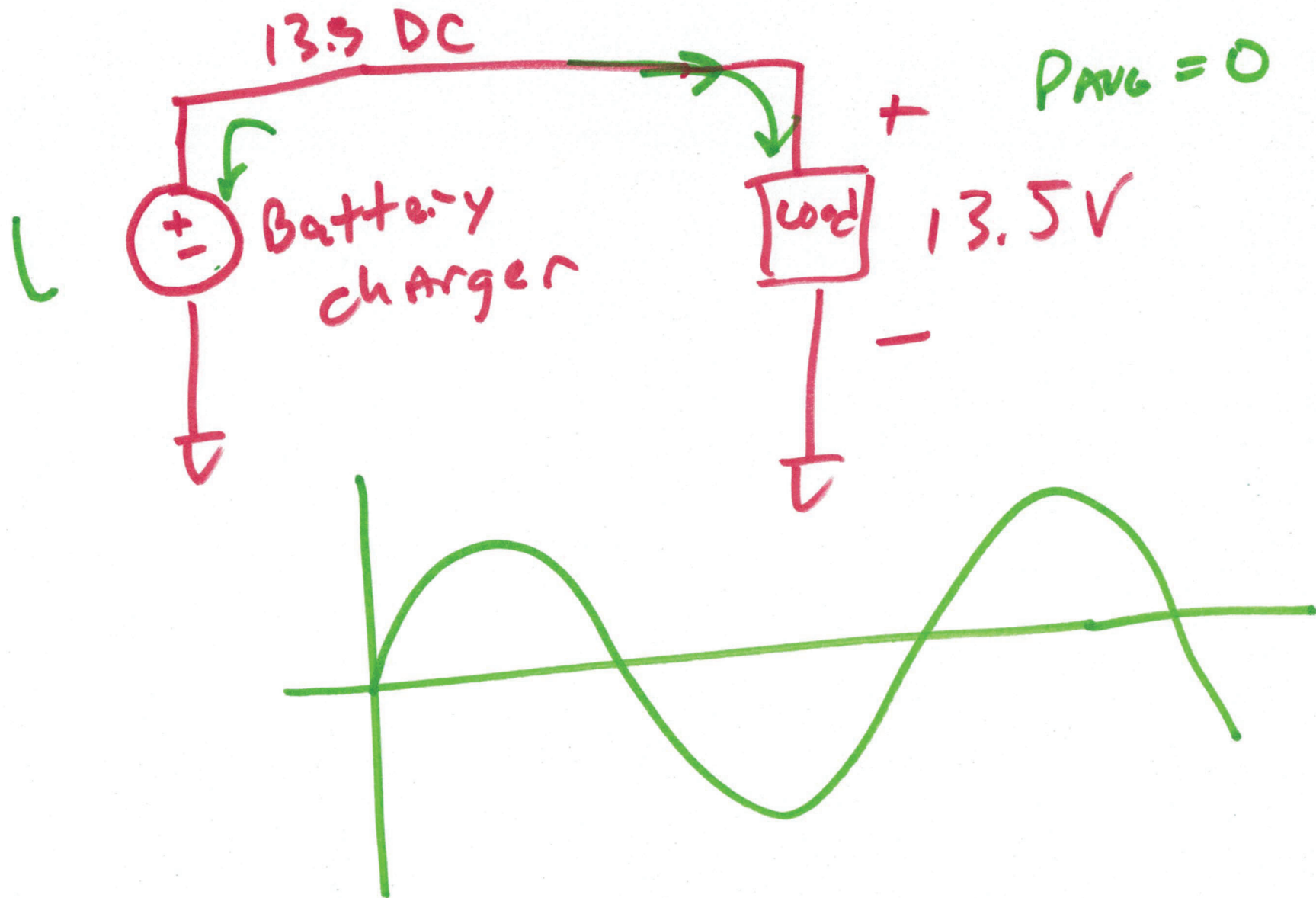

Sinusoids

170V

120V


RMS

$$\frac{V_m}{\sqrt{2}} = V_{RMS}$$

Power

instantaneous  
power

$$= p(t) = i(t) \cdot v(t)$$

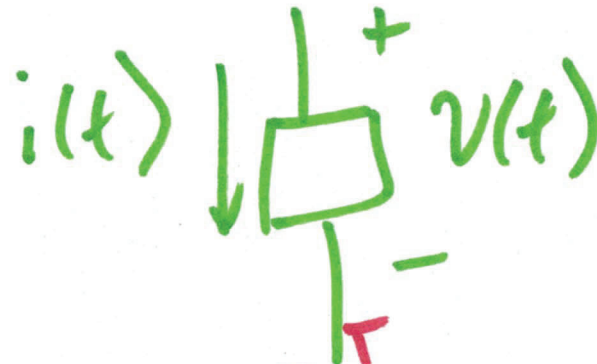

Average power ✓

$$P_{avg} = \frac{1}{T} \int_0^T p(t) \cdot dt$$

10)

$$v(t) = V_m \cdot \cos(2\pi f \cdot t + \phi_v)$$

$$i(t) = I_m \cos(2\pi f \cdot t + \phi_i)$$

$$\cos a \cos b = \frac{1}{2} \cos(a+b) + \frac{1}{2} \cos(a-b)$$

$$P_{avg} = f \int_0^{\frac{1}{f}} V_m I_m \cos(2\pi \cdot f \cdot t + \phi_v) \cdot \cos(2\pi f t + \phi_i) \cdot dt$$

$\frac{1}{T}$

$\frac{1}{T}$

$$\frac{V_m I_m}{2} \left( \cos(\phi_v - \phi_i) + \cos(4\pi \cdot f \cdot t + \phi_v + \phi_i) \right)$$

$p(t)$

11)



$$\frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos(\phi_v - \phi_i)$$

$$V_{rms} \cdot I_{rms} \cdot \underbrace{\cos(\phi_v - \phi_i)}_{\text{power factor}} \text{Angle}$$

