



Lecture 24

EE 221

Circuits II



April 26, 2021

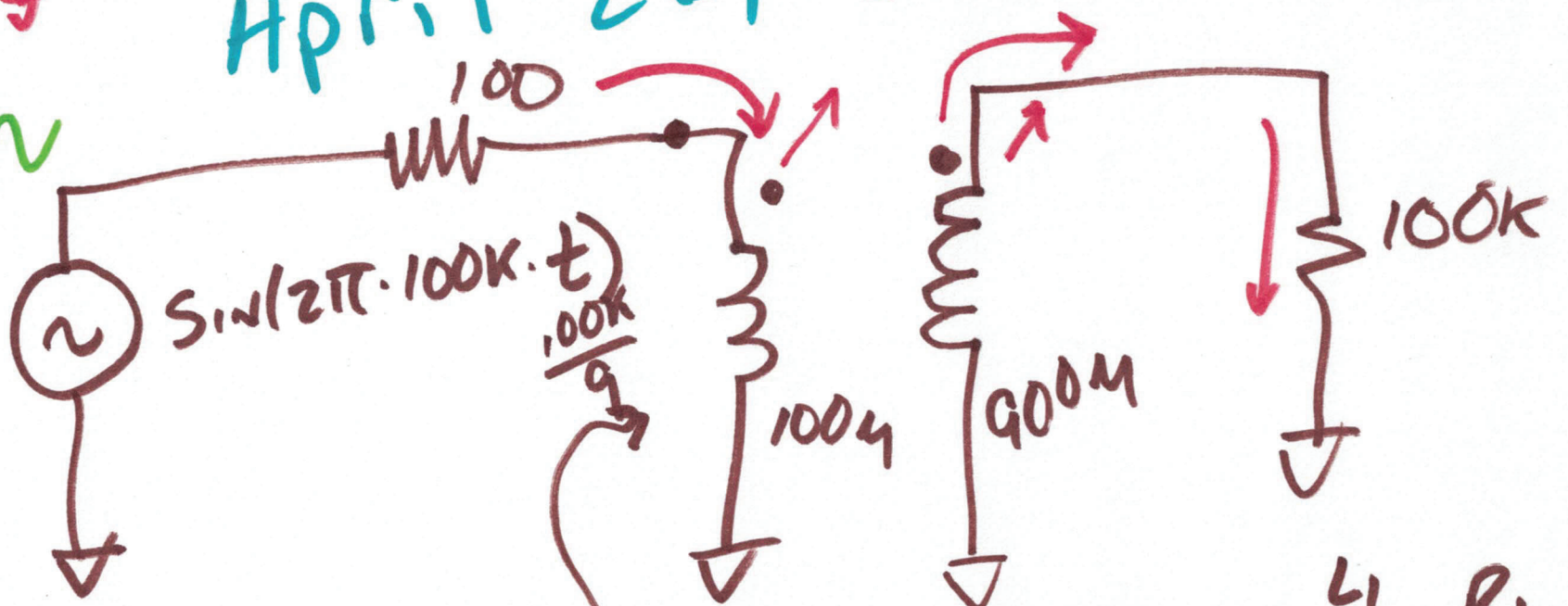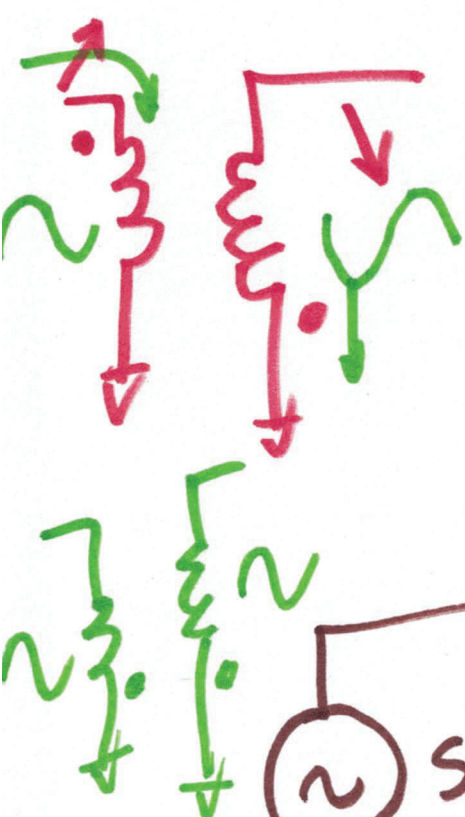



$$R_{in} = \left(\frac{N_1}{N_2}\right)^2 \cdot R_L = \frac{L_1}{L_2} \cdot R_L$$
$$\sqrt{\frac{L_1}{L_2}} = \frac{N_1}{N_2}$$



$\frac{1}{100k} = 10^{-4}$ Magnetizing inductance

inductance

Load $i = 0$

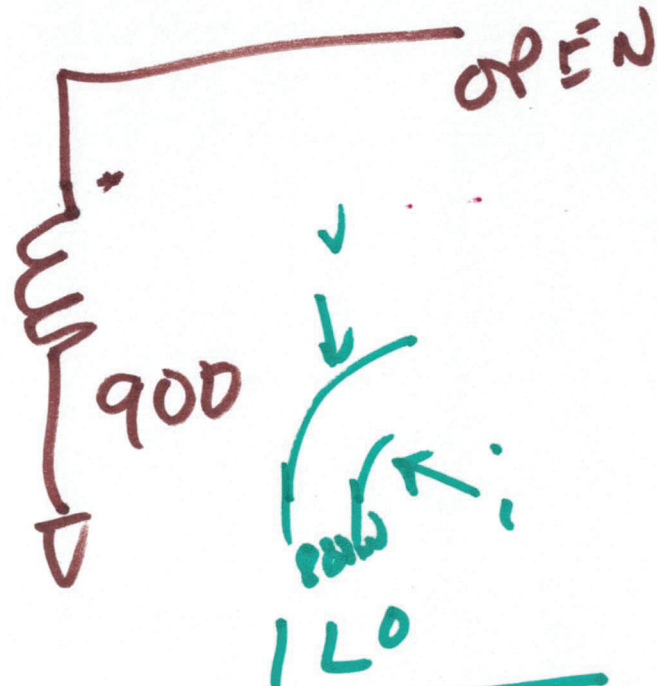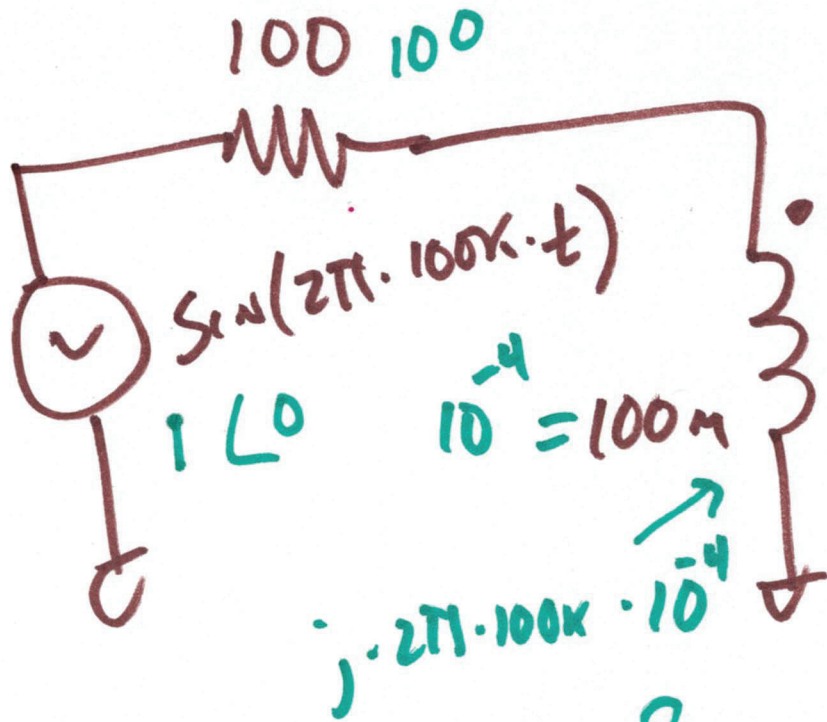

$j 62.8$




$i = \frac{100}{100 + j 62.8}$
 $118 \angle -32.1$

$\frac{t_d}{10\mu} \cdot 360 = 32$

$t_d = 888ns$

$i = 8.47mA \sin(2\pi \cdot 100k \cdot t - 32.1)$

2)

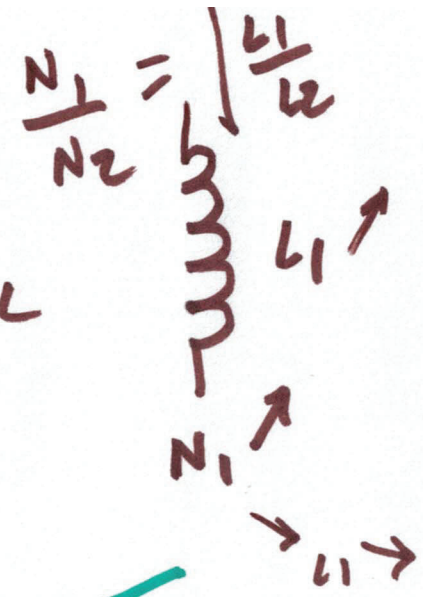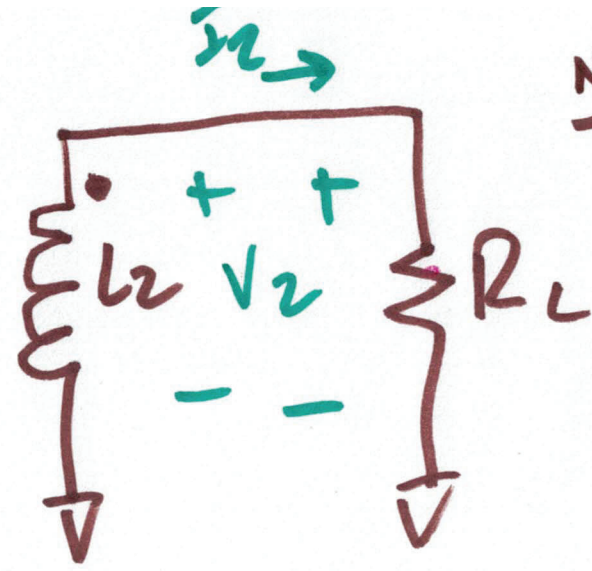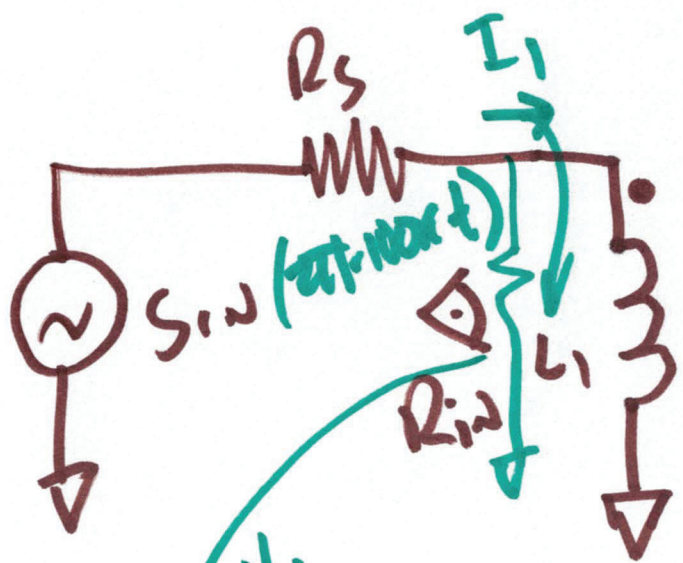


$$R_{in} = \frac{V_1}{I_1}$$

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$

$$R_L = \frac{V_2}{I_2}$$


$$R_{in} = \frac{V_1}{I_1} = \frac{V_2 \cdot \frac{N_1}{N_2}}{I_2 \cdot \frac{N_1}{N_2}} = \frac{V_2 \cdot \frac{N_1}{N_2}}{I_2 \cdot \frac{N_1}{N_2}} = \frac{V_2}{I_2} \cdot \left(\frac{N_1}{N_2}\right)^2$$

3)

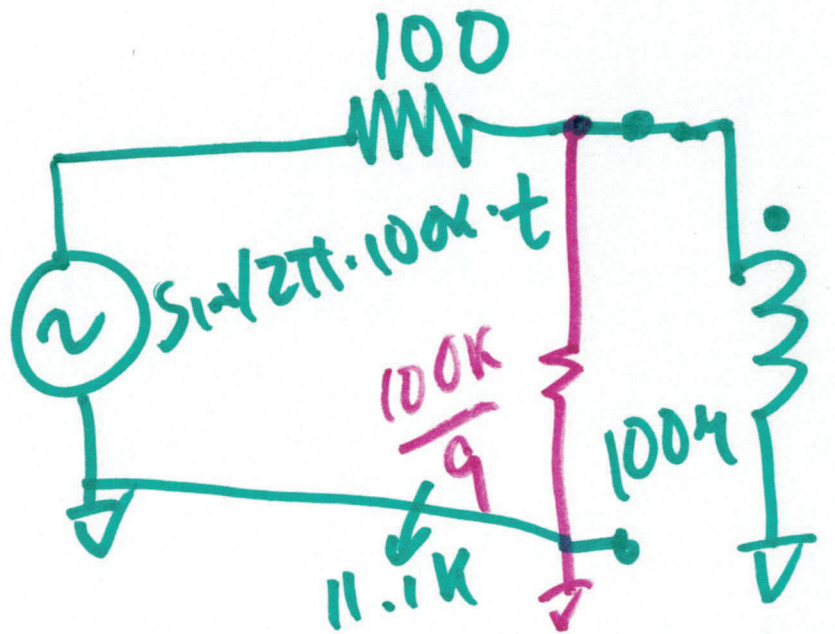


$$\frac{100k}{9}$$

$$100 \parallel 11.1k$$

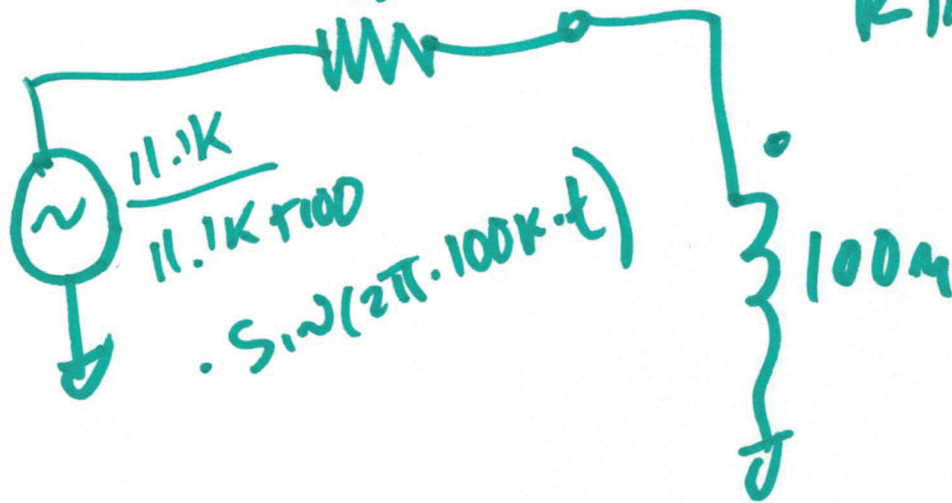


$$\frac{11.1k}{11.1k + 100}$$

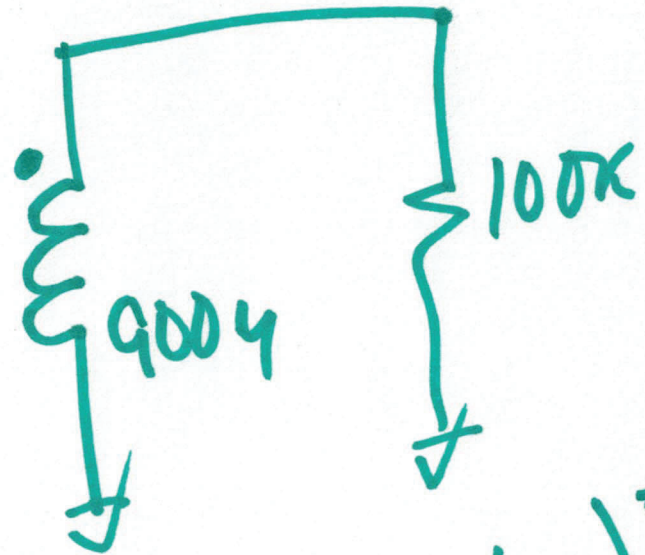

$$R_{IN} = \frac{V_2}{I_2} \cdot \left(\frac{N_1}{N_2} \right)^2$$

$$= \frac{100k}{\left(\sqrt{\frac{L_1}{L_2}} \right)^2} \cdot \frac{1}{9}$$

4)

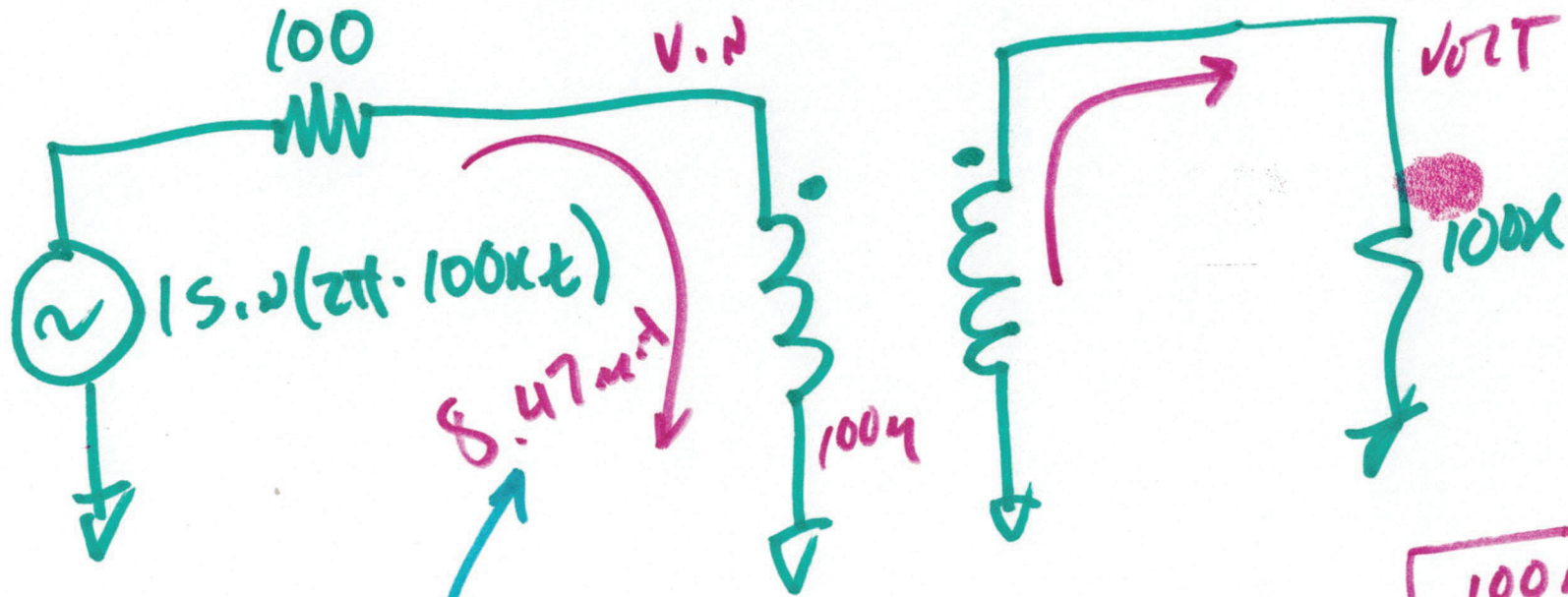


wrong

don't
use
magn. + 2.25 I₂
current

$$I_2 = 8.47 \text{ mA} \cdot \sqrt{\frac{100 \Omega}{900 \Omega}}$$
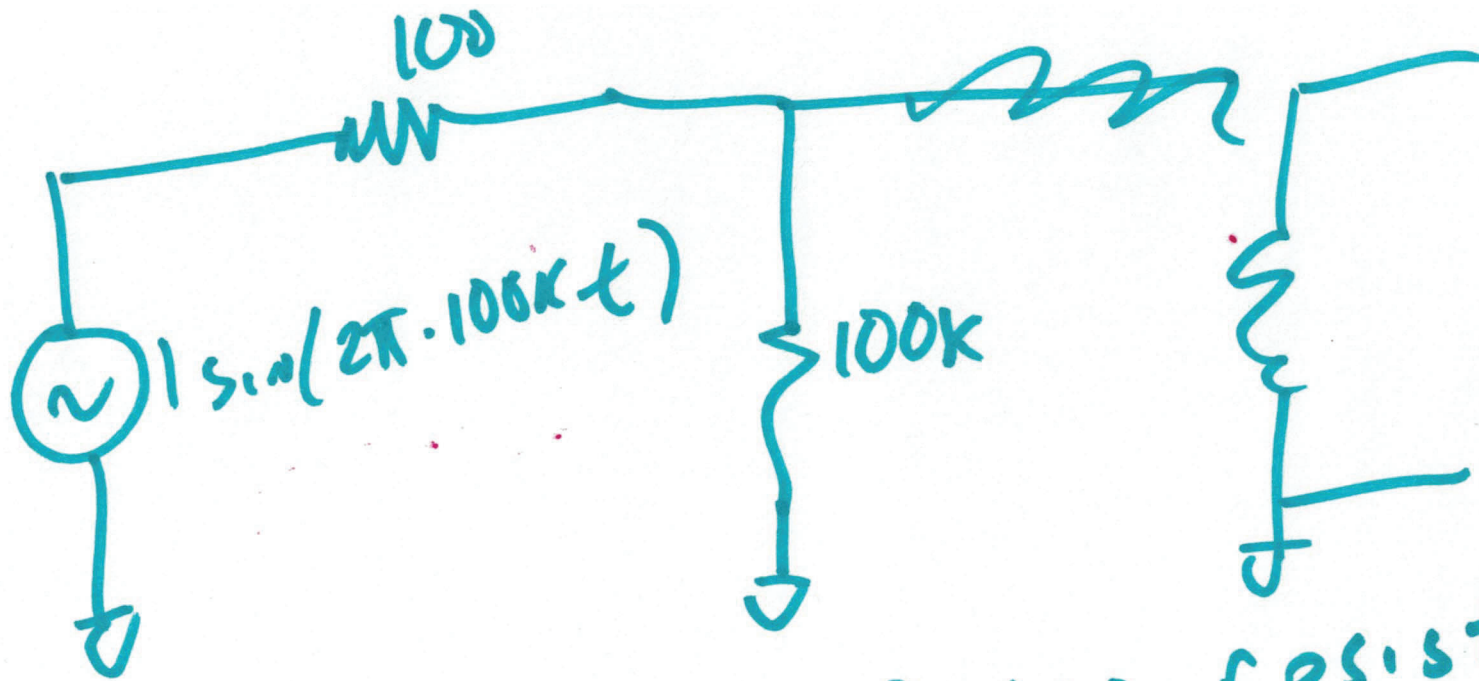
$$V_{out} = I_2 \cdot 100 \text{ k}\Omega = 282 \text{ V}$$






Average Power resistor

$$P_{avg} = \frac{V_{rms}^2}{R} = I_{rms}^2 \cdot R$$
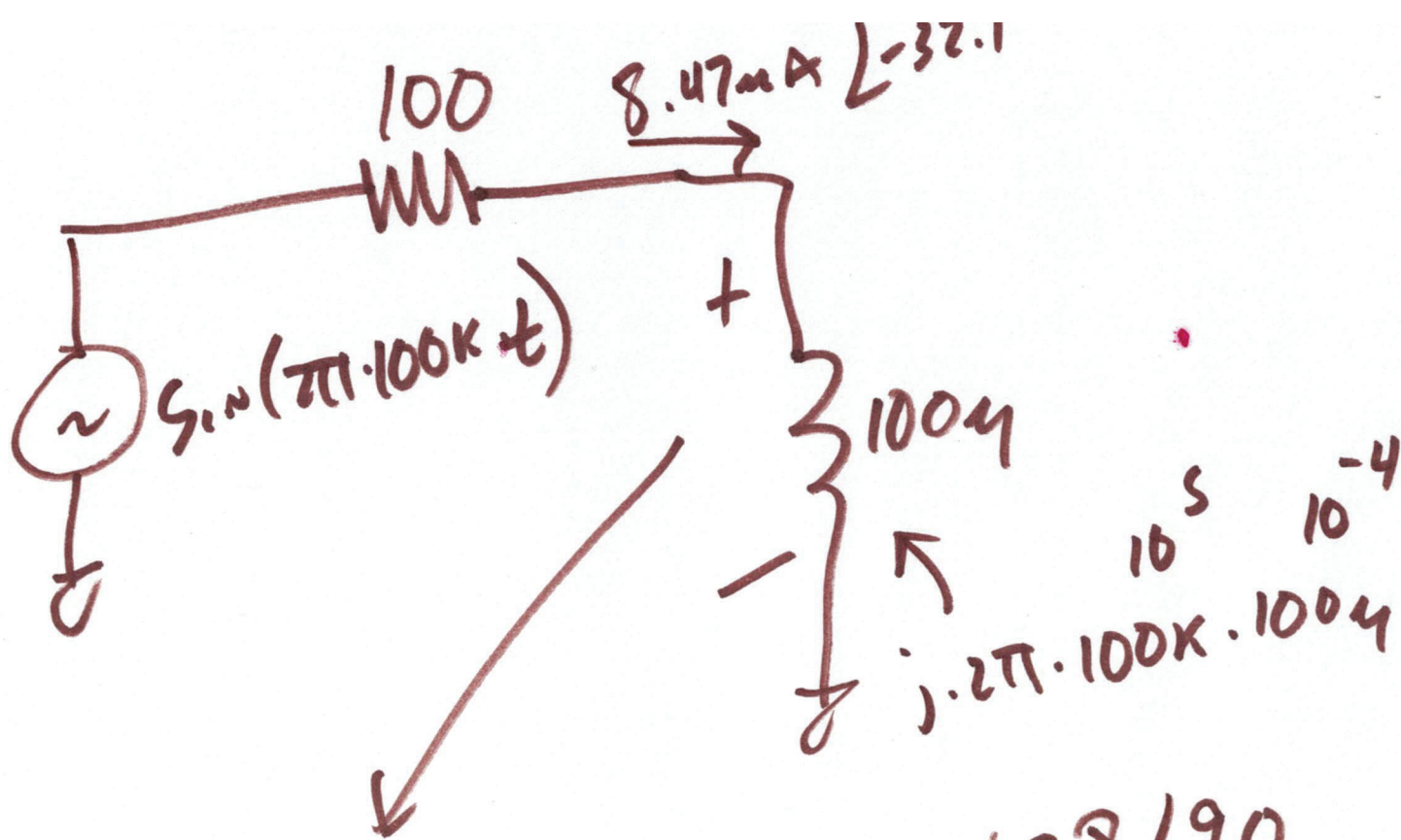
$$= \frac{\left(\frac{1.6}{\sqrt{2}}\right)^2}{100k} = \frac{1.6^2}{200k}$$





$$V_1 = 8.47 \text{ mA } \angle -32.1^\circ \cdot 62.8 \angle 90^\circ$$

$$V_1 = .53 \angle 58^\circ$$

$$V_1 = 530 \text{ nV} \cdot \sin(2\pi \cdot 100k \cdot t + 58^\circ)$$

7)