
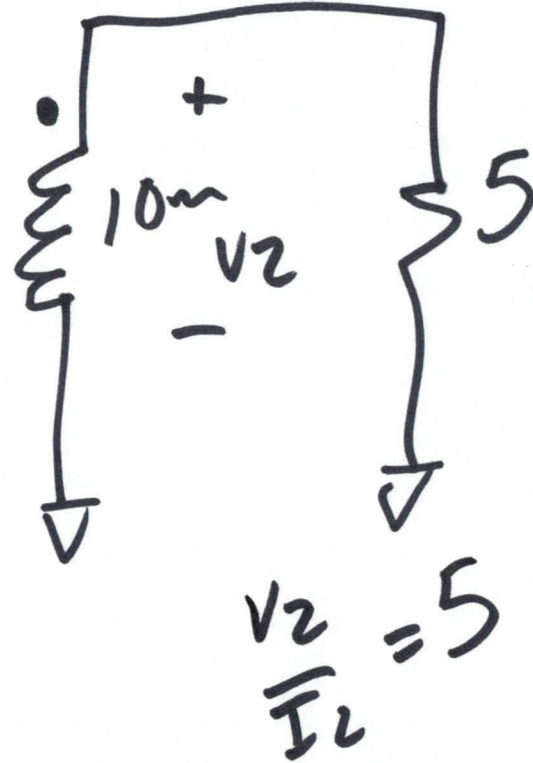



EE 221 Circuits II

Lecture 27

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$

MAY 5 12 20 21

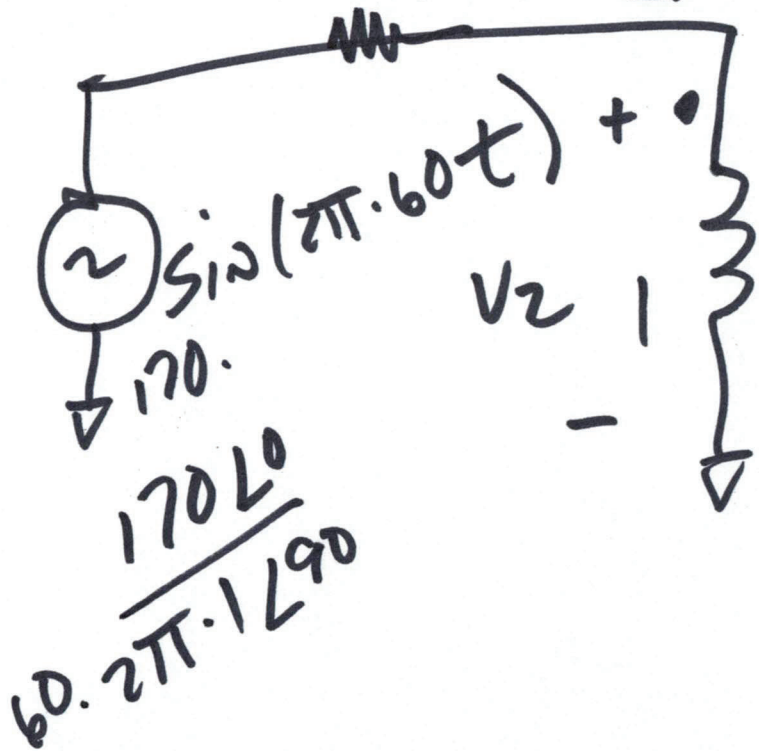

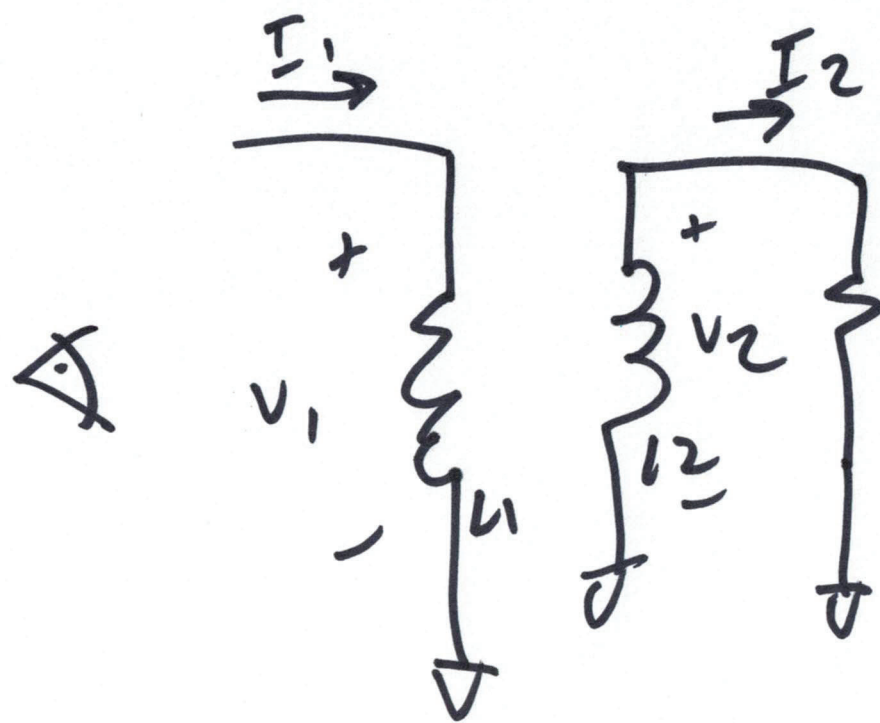

$$R_{in} = \left(\frac{N_1}{N_2}\right)^2 R_L$$

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$R_{in} = \frac{V_1}{I_1} = \frac{N_1/N_2}{N_2/N_1} R_L = \frac{V_1}{V_2} \frac{V_2}{I_2}$$

\uparrow $\frac{V_1}{I_1}$ is R_{in}
 \uparrow $\frac{V_2}{I_2}$ is R_L

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$R_L = \frac{V_2}{I_2}$$



$$V_2 = V_1 \cdot \frac{N_2}{N_1}$$

$$I_2 = I_1 \cdot \frac{N_1}{N_2}$$

$$R_L = \frac{V_1 \cdot \frac{N_2}{N_1}}{I_1 \cdot \frac{N_1}{N_2}} = R_{in} \left(\frac{N_2}{N_1} \right)^2$$

$$R_{in} = R_L \cdot \left(\frac{N_1}{N_2} \right)^2$$


3)

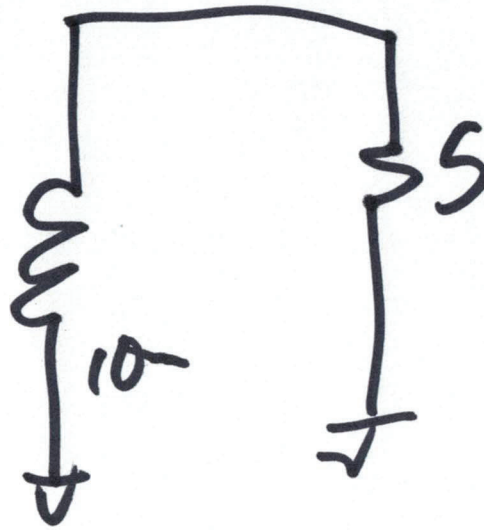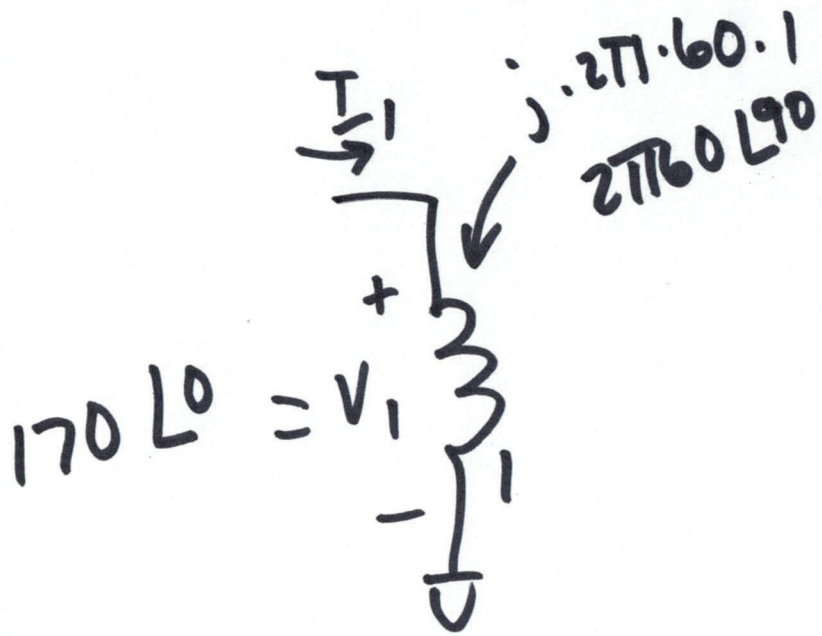

$$\frac{N_1}{N_2} = \sqrt{\frac{1}{.01}}$$

$$\frac{N_1}{N_2} = 10$$

$$R_{in} = 5 \cdot 10^2 = 500$$

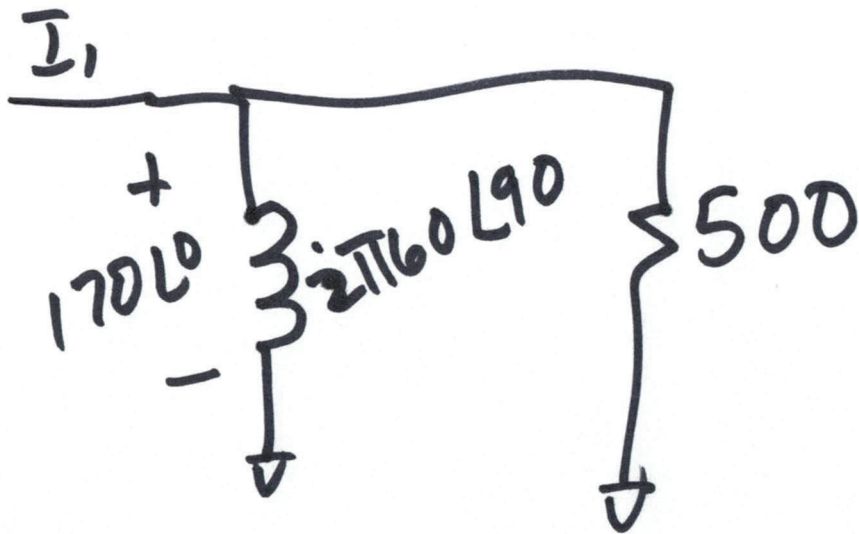

$$I_1 = \frac{170 \text{ L}0}{2\pi \cdot 60 \text{ L}90 \cdot 500}$$

$$500 + j \cdot 2\pi \cdot 60$$

$$626 \text{ L}37^\circ$$


$$I_1 = \frac{170 \angle 0^\circ}{188k \angle 90^\circ} = \frac{626 \angle 37^\circ \cdot 170 \angle 0^\circ}{188k \angle 90^\circ}$$
$$= 0.565 \angle -53^\circ$$

$$i_1(t) = 565 \mu\text{A} \sin(2\pi \cdot 60 \cdot t - 53^\circ)$$


NAME: _____


Closed book and notes. No extra paper, do your work on this exam, use the back if needed.
Show your work for credit and be neat! Place a box around each of your answers. No
 Laplace transform table is allowed or (again) any other extra material (scratch paper).

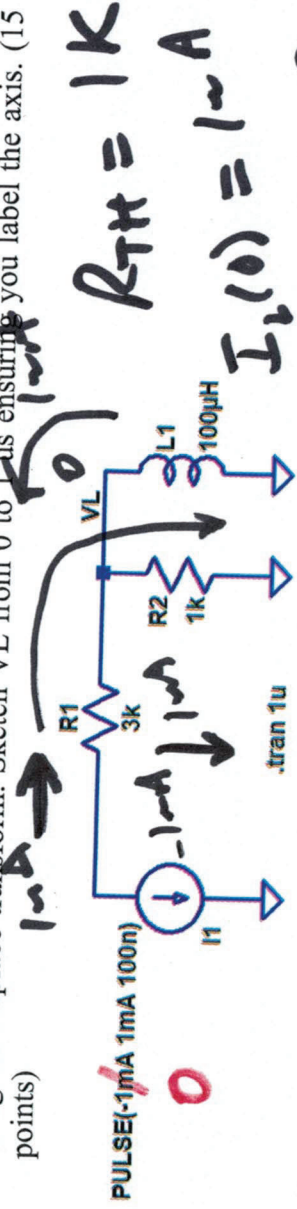1. Find V_L (an equation that includes the input current pulse's delay) in the following circuit using the Laplace transform. Sketch V_L from 0 to 1 μ s ensuring you label the axis. (15 points)




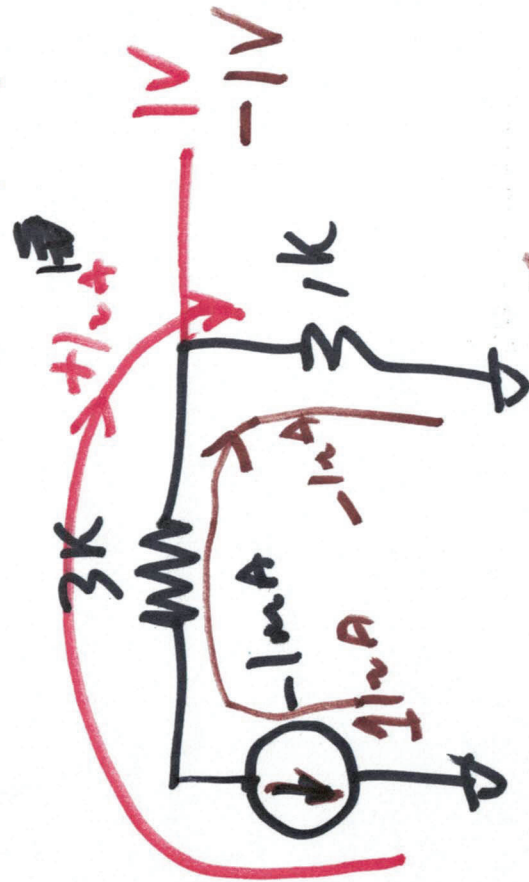$R_{TH} = 1K$
 $I_L(0) = 1mA$
 $V_L(0) = 0$



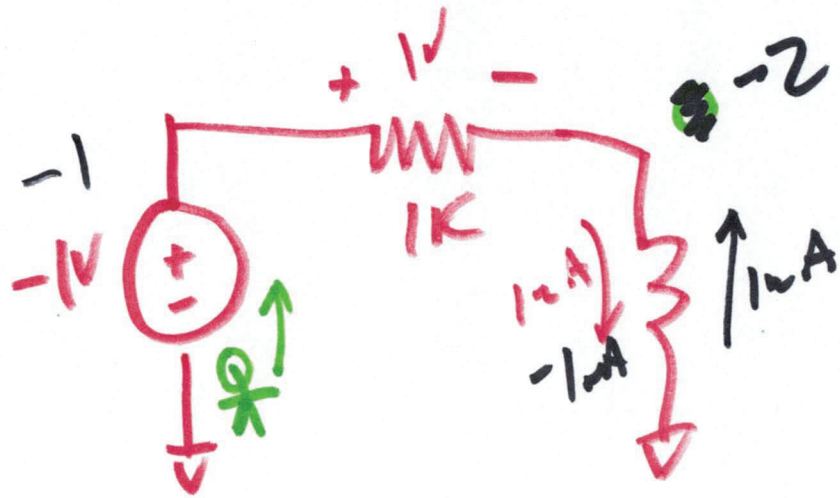

$$+(-1) - 1 = -2$$

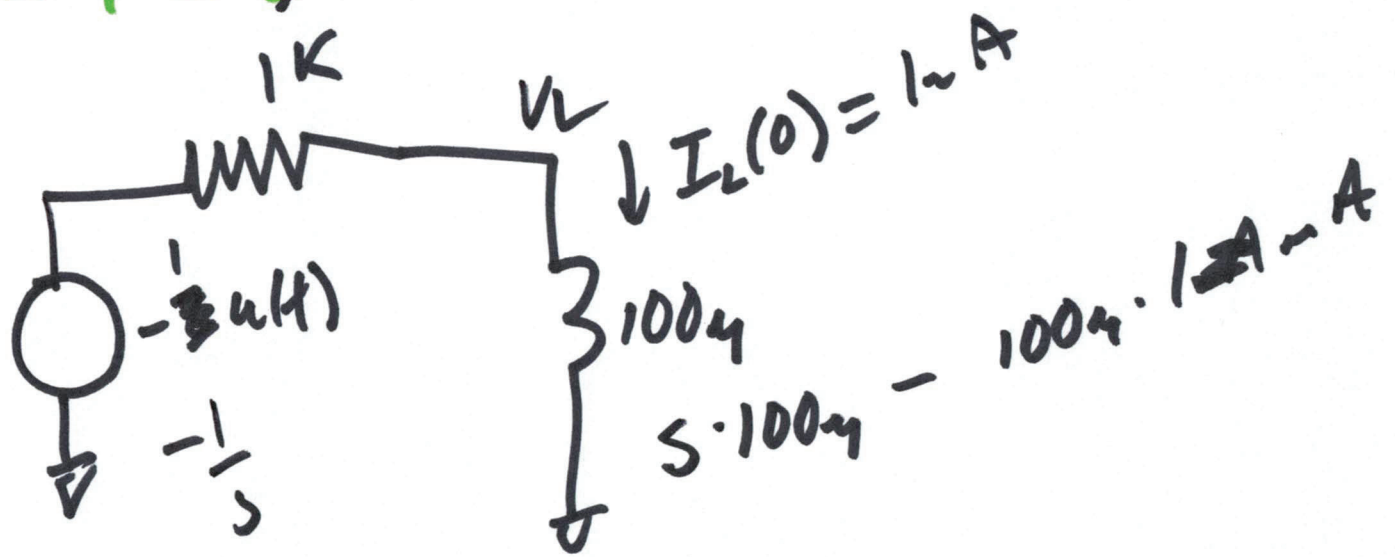


$$I_2(0) = 1\mu A$$

$$5 \cdot 100\mu - 100\mu \cdot 1\mu A = A$$


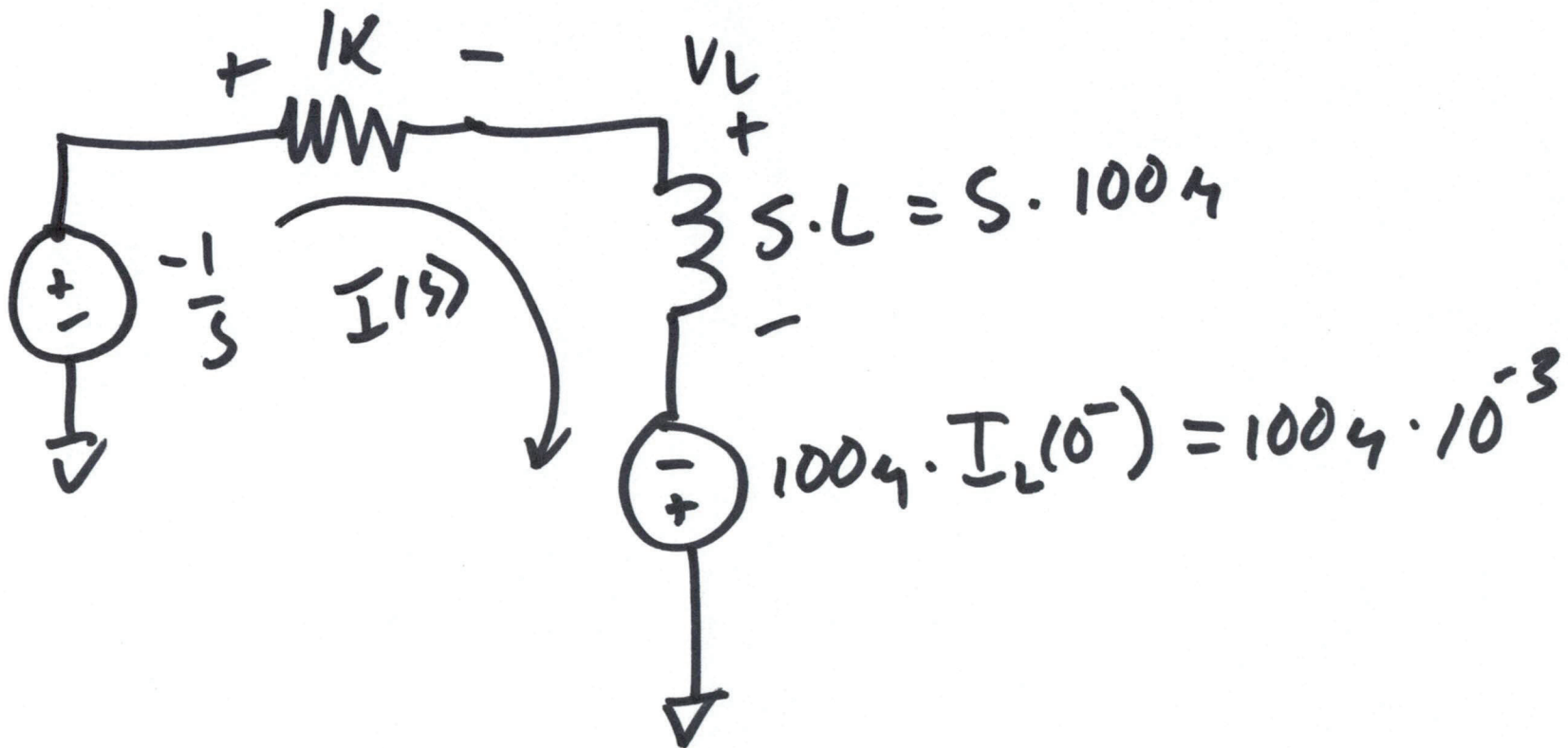
$$V_L = -\frac{1}{s} \cdot \frac{s \cdot 1004}{10^3 + s \cdot 1004} - 1004 \cdot 10^{-3}$$



$$0 = -\frac{1}{s} - I(s) \cdot 1k - I(s) \cdot s \cdot 1004 + 1004 \cdot 10^{-3}$$

8)


$$V_L = I(s) \cdot s \cdot 100\mu - 100\mu \cdot 10^{-3} \\ + \frac{1}{s} \cdot 100\mu \cdot 10^{-3} = -I(s) (1K + s \cdot 100\mu)$$

$$I(s) = \frac{\frac{1}{s} - 100\mu \cdot 10^{-3}}{1K + s \cdot 100\mu}$$

$$I(s) V_L(s) = \frac{\frac{1}{s} - 100\mu \cdot 10^{-3}}{1K + s \cdot 100\mu}$$

a)

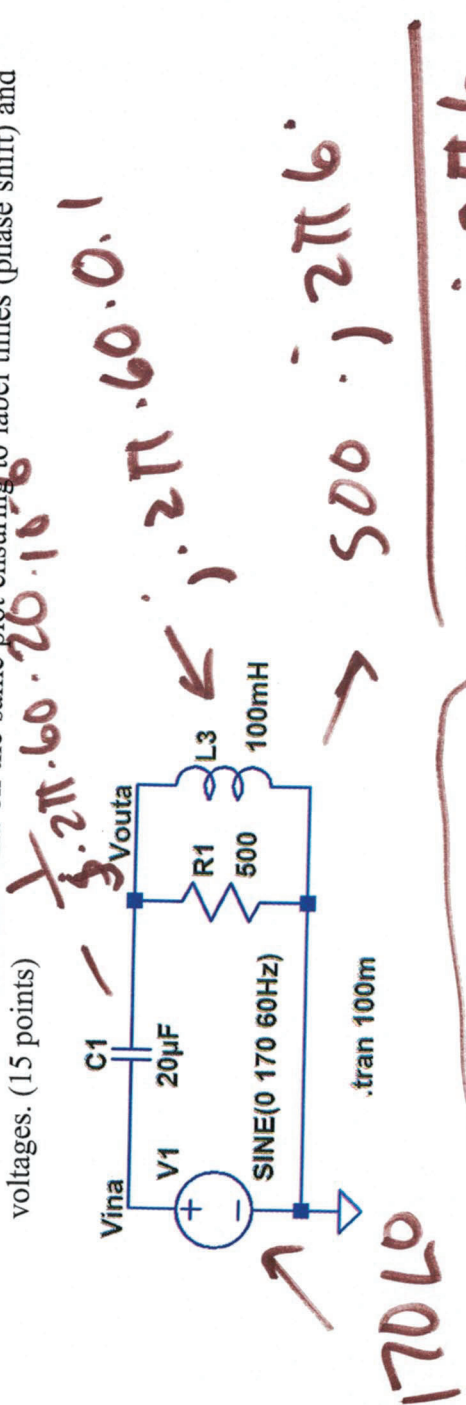2. Assuming the circuit seen below is operating in steady-state, use AC analysis to determine V_{out} . Sketch V_{out} and V_{in} on the same plot ensuring to label times (phase shift) and voltages. (15 points)



$$170 \angle 0^\circ$$

$$V_{RTA} = \frac{170 \angle 0^\circ \cdot 37.68 \angle 85.7^\circ}{500 + j2\pi \cdot 60 \cdot 0.1}$$

$$= \frac{37.68 \angle 85.7^\circ}{500 \angle 4.3^\circ}$$

$$+ \frac{1}{j \cdot 2\pi \cdot 60 \cdot 20 \cdot 10^{-6}}$$

$$= 2.92 + j37.57 - j132 - 94.43j$$


$$= 170 \angle 0^\circ \cdot 37.68 \angle 85.7^\circ$$

$$V_{RTA} =$$

$$94.47 \angle -88^\circ$$

$$= 67.8 \sin(2\pi 60t + 173.7^\circ) \quad 67.8 \angle 173.7^\circ$$

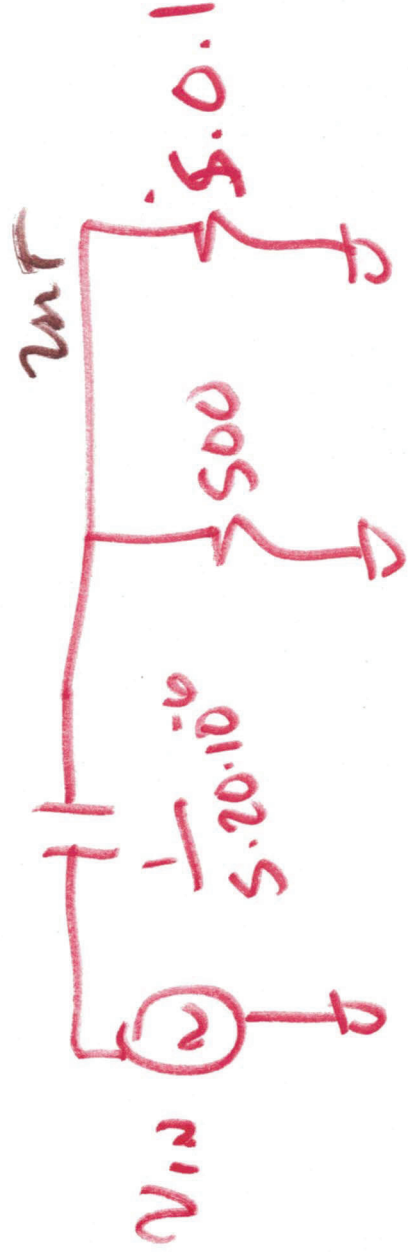3. Determine the transfer function (V_{out}/V_{in}) of the circuit in problem 2 and then determine the (magnitude and phase) frequency responses. Sketch the frequency responses and discuss, using numbers, how your results in problem 2 are correct. (20 points)



$$\frac{s \cdot 500}{s + 5000} = \frac{500 \cdot s \cdot 0.1}{500 + s \cdot 0.1}$$

$$\frac{s \cdot 500}{s + 5000}$$

$$V_{out} = V_{in} \cdot \frac{1}{s \cdot 20 \cdot 10^{-6}} + \frac{s \cdot 500}{s + 5000}$$

$$\frac{V_{out}}{V_{in}} = \frac{s \cdot 500}{s \cdot 500 + \frac{5000 + s}{s \cdot 20 \cdot 10^{-6}}}$$

(11)

$$\frac{v_{out}}{v_{in}} = \frac{s}{s + \frac{10 + s/500}{s \cdot 20 \cdot 10^{-6}}}$$

$$\frac{v_{out}}{v_{in}} = \frac{\cancel{s^2 \cdot 20 \cdot 10^{-6}}}{\cancel{s^2 \cdot 20 \cdot 10^{-6}} + \frac{s}{20 \cdot 10^{-6} \cdot 500} + \frac{10}{20 \cdot 10^{-6}}}$$

$$= \frac{s^2}{s^2 + 100 \cdot s + 500K}$$

P_1, P_2

$$(s - P_1)(s - P_2)$$

(2)

$$P_1, P_2 = \frac{-100 \pm \sqrt{10^4 - 4 \cdot 500k}}{2}$$

$$= -50 \pm j1.41k$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2}{(s + 50 - j1.41k)(s + 50 + j1.41k)}$$