

EE 221 Circuits II


January 25, 2021

人
大
#

Lecture 2




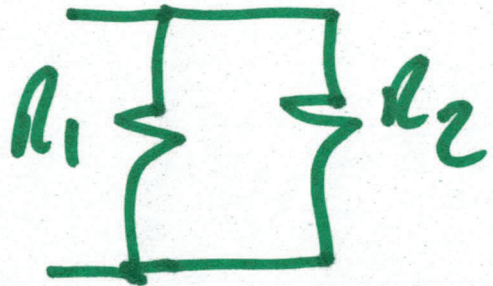
$$\frac{1}{T} = \frac{1}{20} + \frac{1}{30}$$
$$T = \frac{20 \cdot 30}{20 + 30}$$




$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$
$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

11

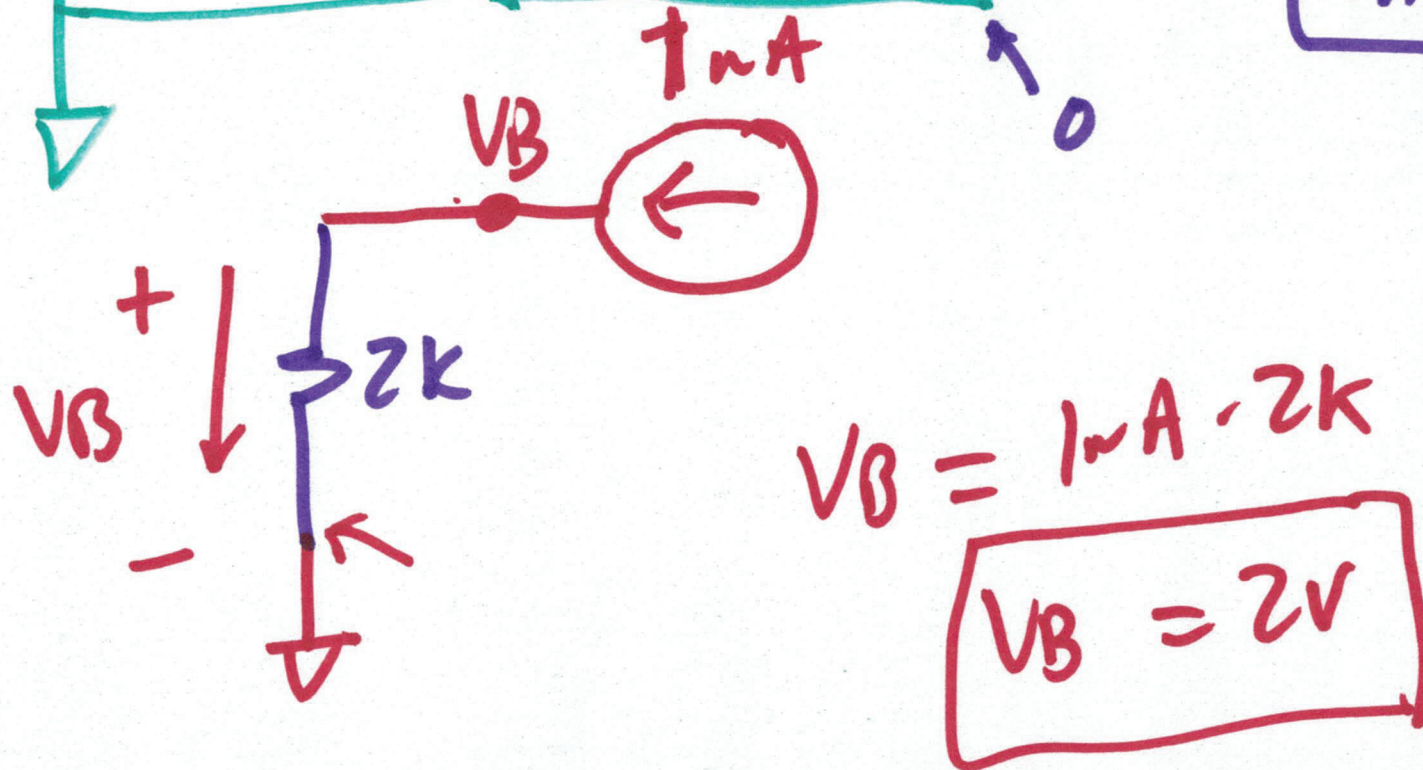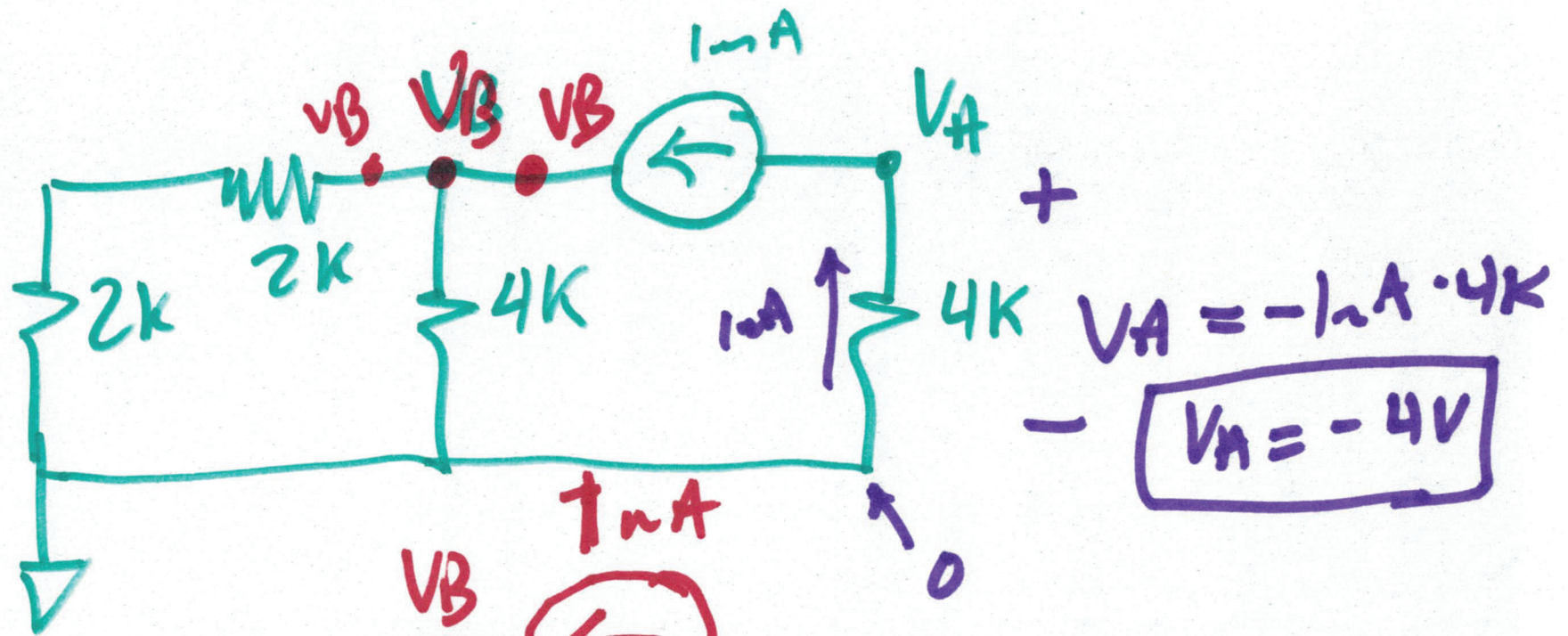

2)

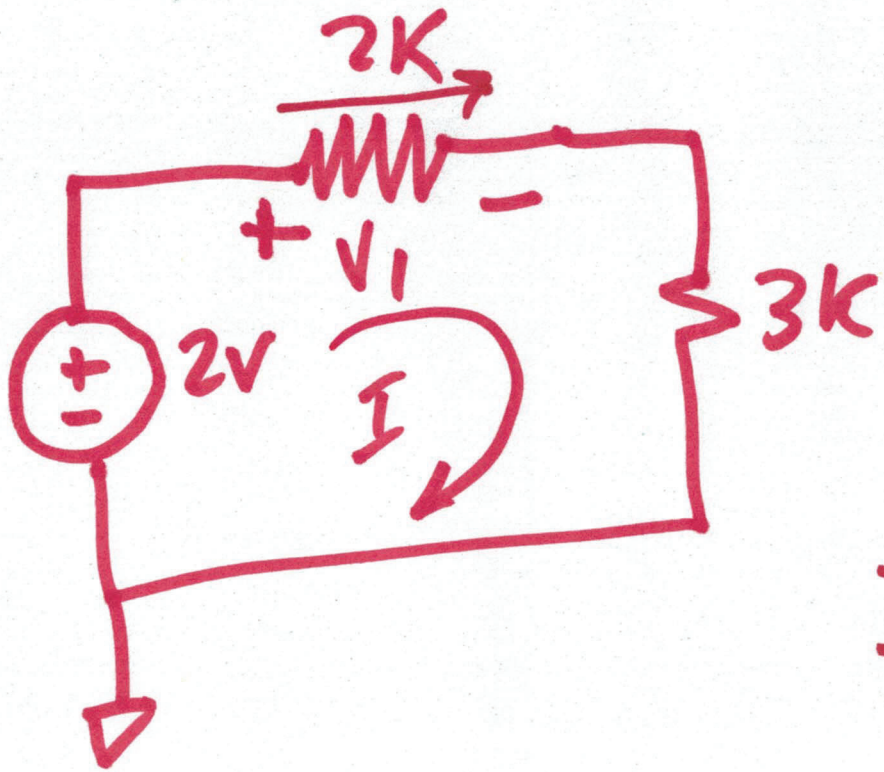


$$V_1 = 2 \cdot \frac{2k}{2k + 3k}$$

$$I = \frac{2}{2k + 3k}$$

$$V_1 = 2k \cdot I = 2 \cdot \frac{2k}{2k + 3k}$$

3)

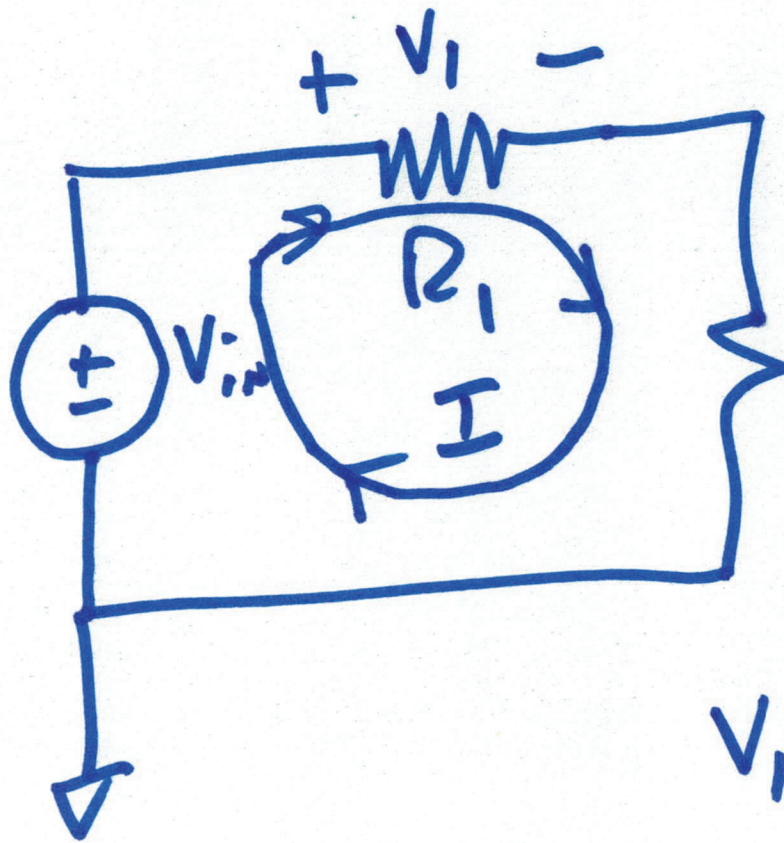


$$+ \quad V_1 = I \cdot R_1$$

$$- \quad V_2 = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

$$V_{in} - R_1 I - R_2 I = 0$$

$$V_2 = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

$$I = \frac{V_{in}}{R_1 + R_2}$$

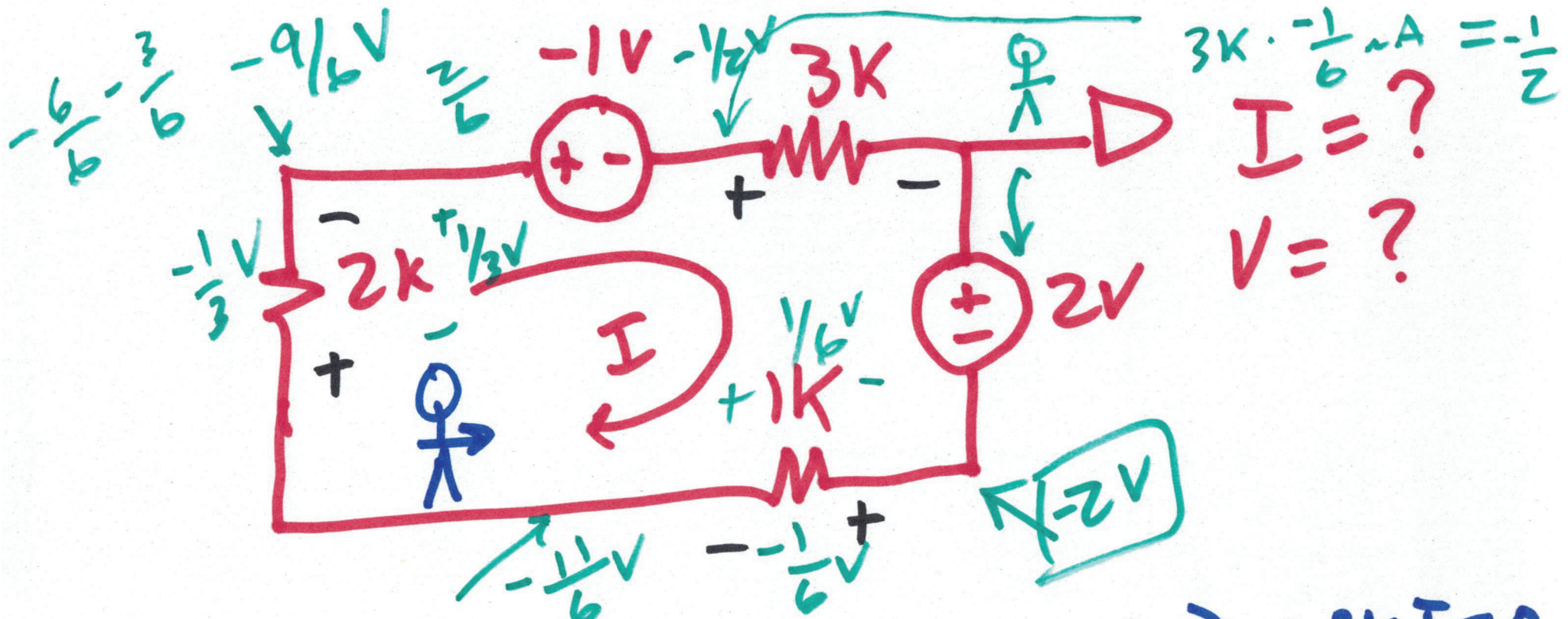


$$I \cdot 1k + 2 + I \cdot 3k + (-1) + 2kI = 0$$

$$I \cdot 6k = -1$$

$$I = -\frac{1}{6} \text{ mA}$$


5)

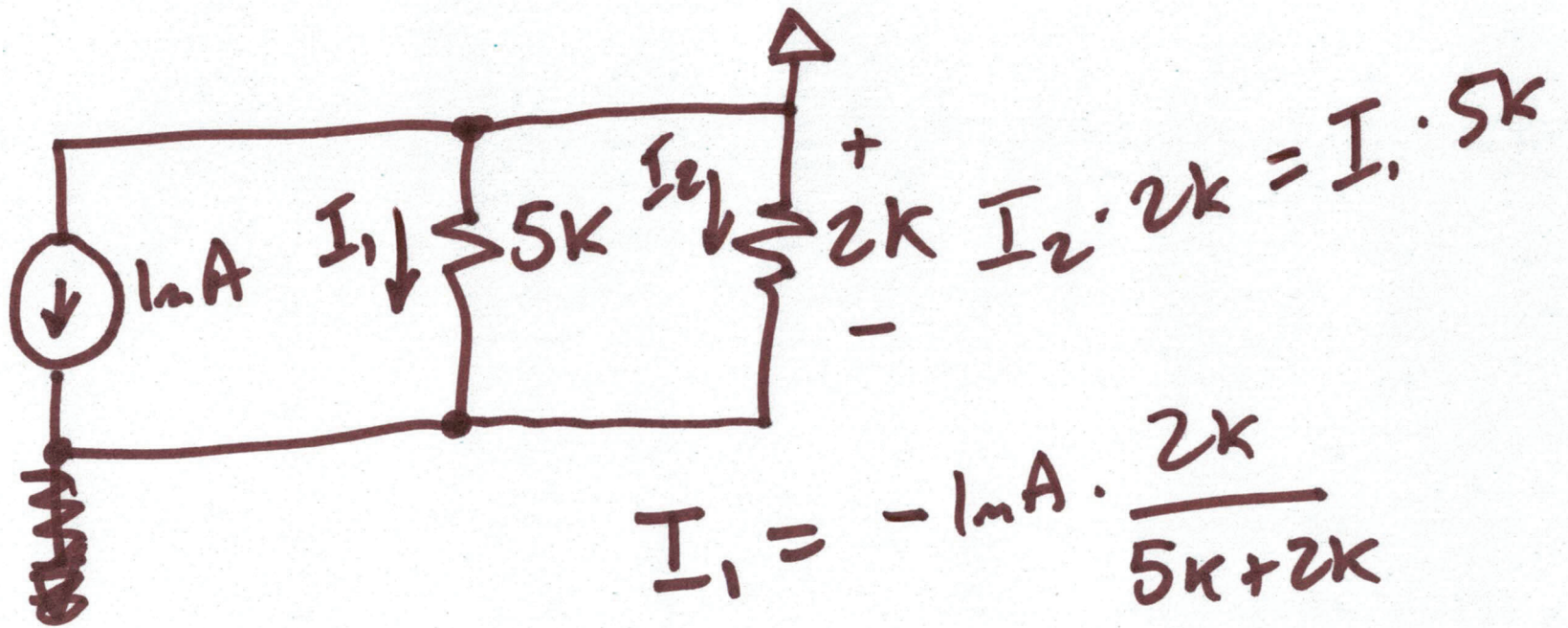

$$I_1 = -1mA \cdot \frac{2k}{5k + 2k}$$

$$I_2 = -1mA \cdot \frac{5k}{5k + 2k}$$

6)

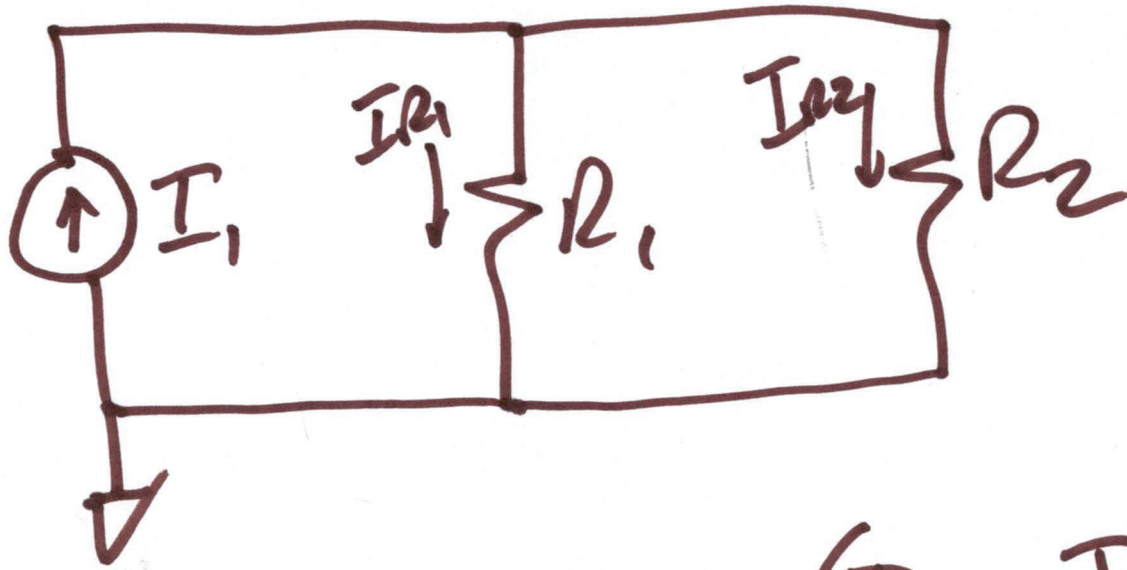


$$I_1 = I_{R1} + I_{R2}$$
$$I_{R1} \cdot R_1 = I_{R2} R_2$$

$$I_{R1} \cdot R_1 = (I_1 - I_{R1}) R_2$$

$$I_{R1} (R_1 + R_2) = I_1 \cdot R_2$$

$$I_{R1} = I_1 \cdot \frac{R_2}{R_1 + R_2}$$


11

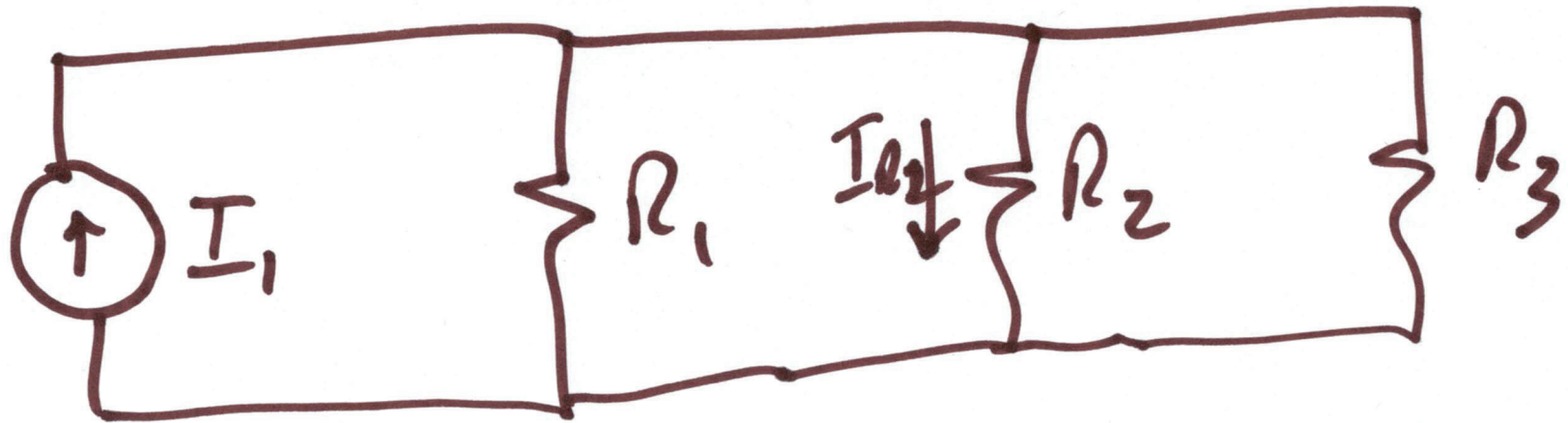

$$I_{R2} = I_1 \cdot \frac{R_1 \parallel R_3}{R_1 \parallel R_3 + R_2}$$

$$= I_1 \cdot \frac{\frac{R_1 \cdot R_3}{R_1 + R_3}}{\frac{R_1 R_2}{R_1 + R_2} + R_2}$$

8)

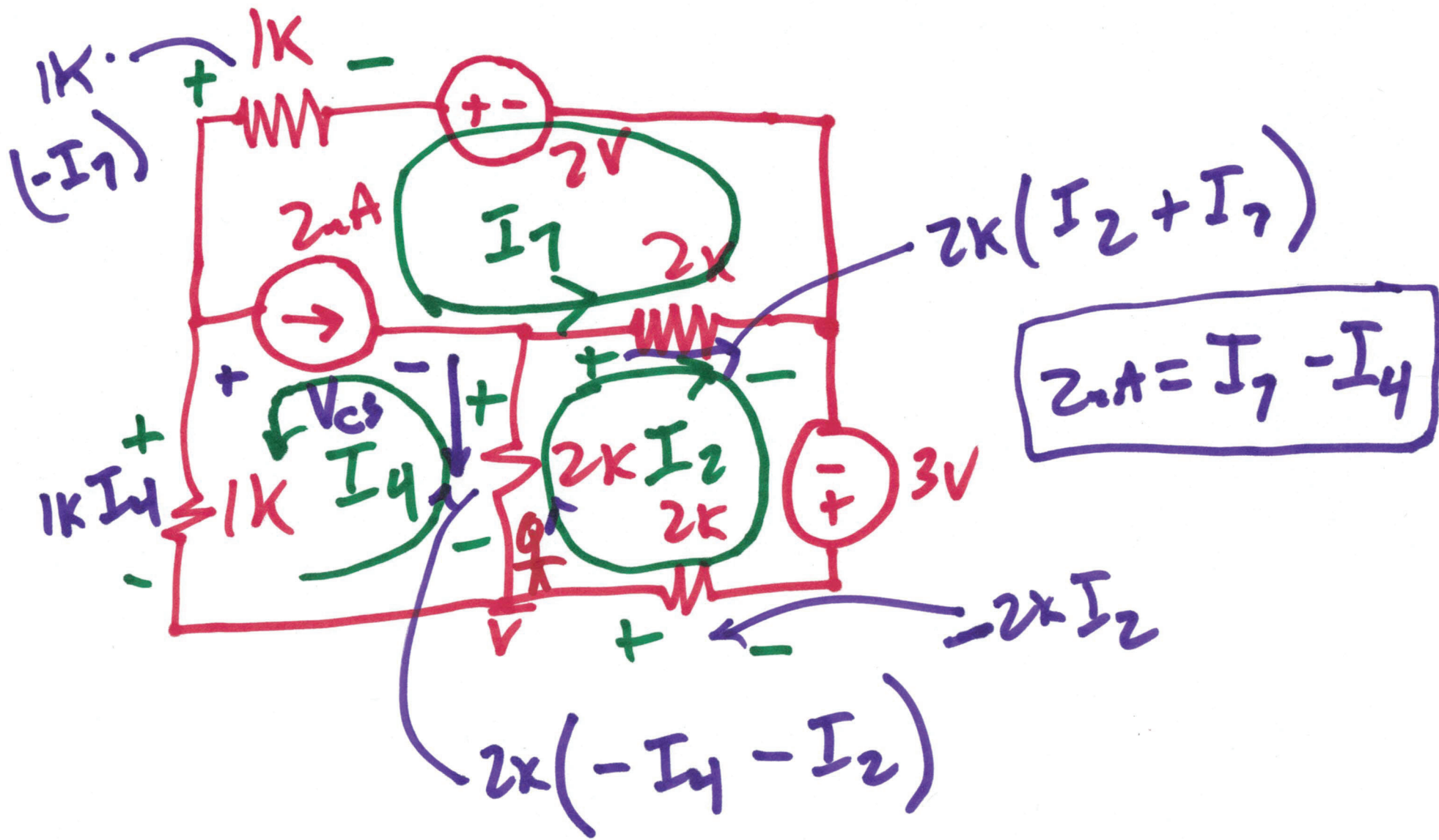

↑

$$0 = -(-2kI_2) - 3 + 2 + (1k(-I_7)) - 1kI_4$$

$$2\mu A = I_7 - I_4$$

$$-2k(I_4 + I_2) - 2k(I_2 + I_7) + 3 - 2kI_2 \stackrel{?}{=}$$

$$0 = I_7(-1k) + I_4(-1k) + I_2 \cdot (2k) - 1$$

$$\ast 0 = I_7 + I_4 - 2I_2 + 1\mu A$$

$$0 = I_7(-2k) + I_4(-2k) + I_2(-6k) + 3 = 0$$

$$\ast 0 = I_7 + I_4 + 3I_2 - 1.5\mu A = 0$$

$$\ast I_7 = 2\mu A + I_4$$

10)

$$2\mu\text{A} + I_4 + I_4 - 2I_2 + 1\mu\text{A} = 0$$

$$2\mu\text{A} + I_4 + I_4 + 3I_2 - 1.5\mu\text{A} = 0$$

$$2I_4 + 3I_2 + \frac{1}{2}\mu\text{A} = 0$$


$$I_2 = -\frac{1}{6}\mu\text{A} - \frac{2}{3}I_4$$

$$2\mu\text{A} + 2I_4 + \frac{1}{3}\mu\text{A} + \frac{4I_4}{3} + 1\mu\text{A} = 0$$



$$\frac{10}{3}I_4 = -\frac{10}{3}\mu\text{A}$$



$$I_4 = -1\mu\text{A}$$

CMOSedu.com

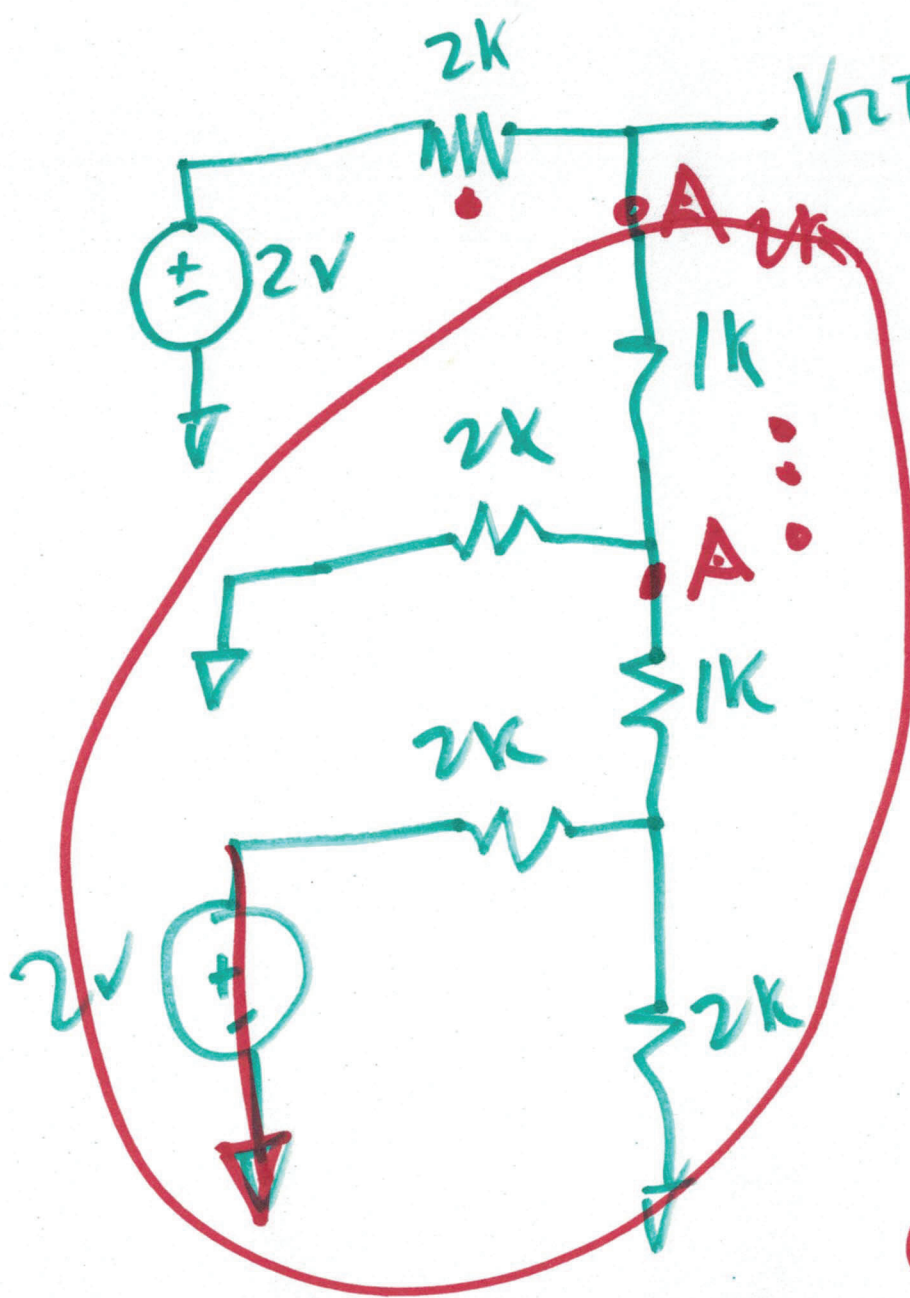
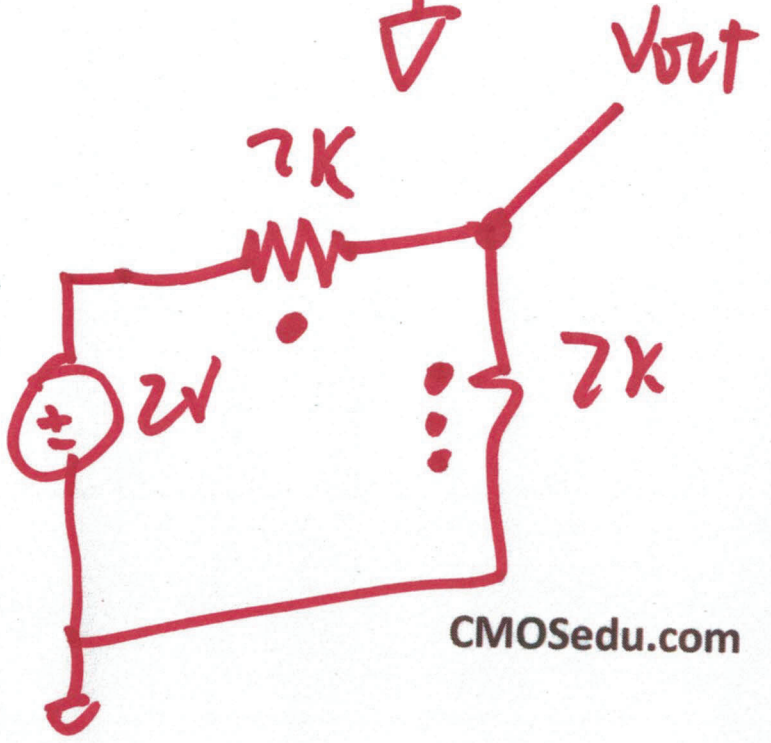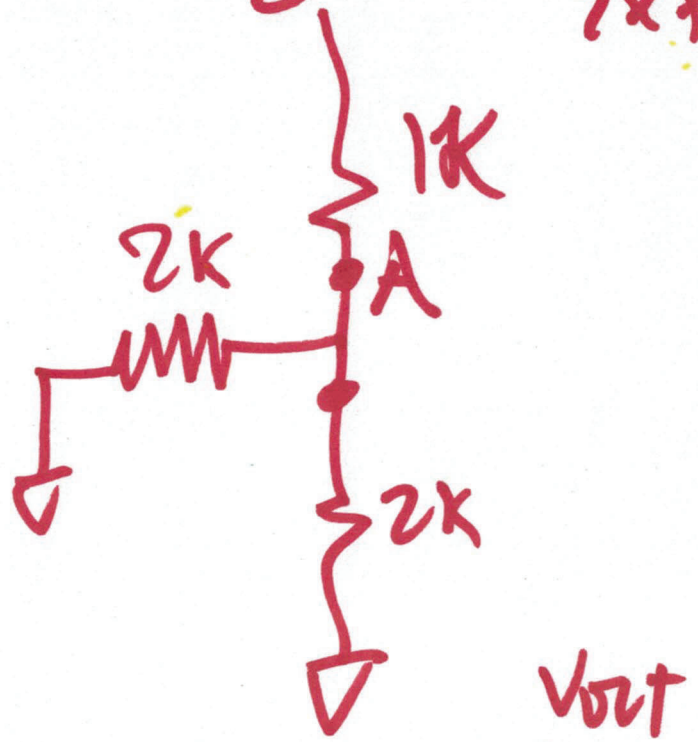
$$V_{RT} = 2 \cdot \frac{1}{2} = 2 \cdot \frac{2K}{2K + 2K}$$





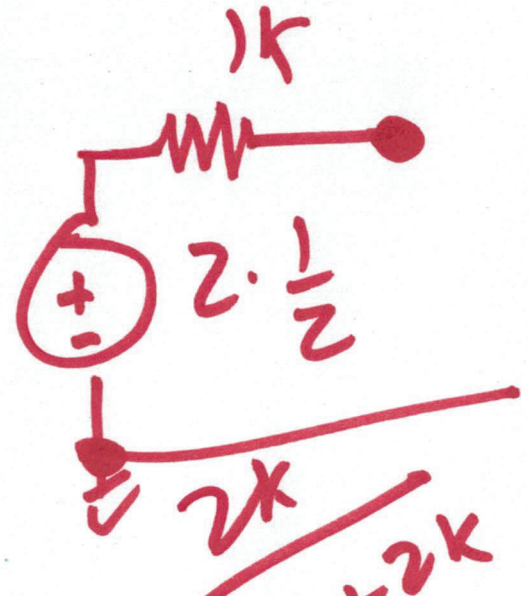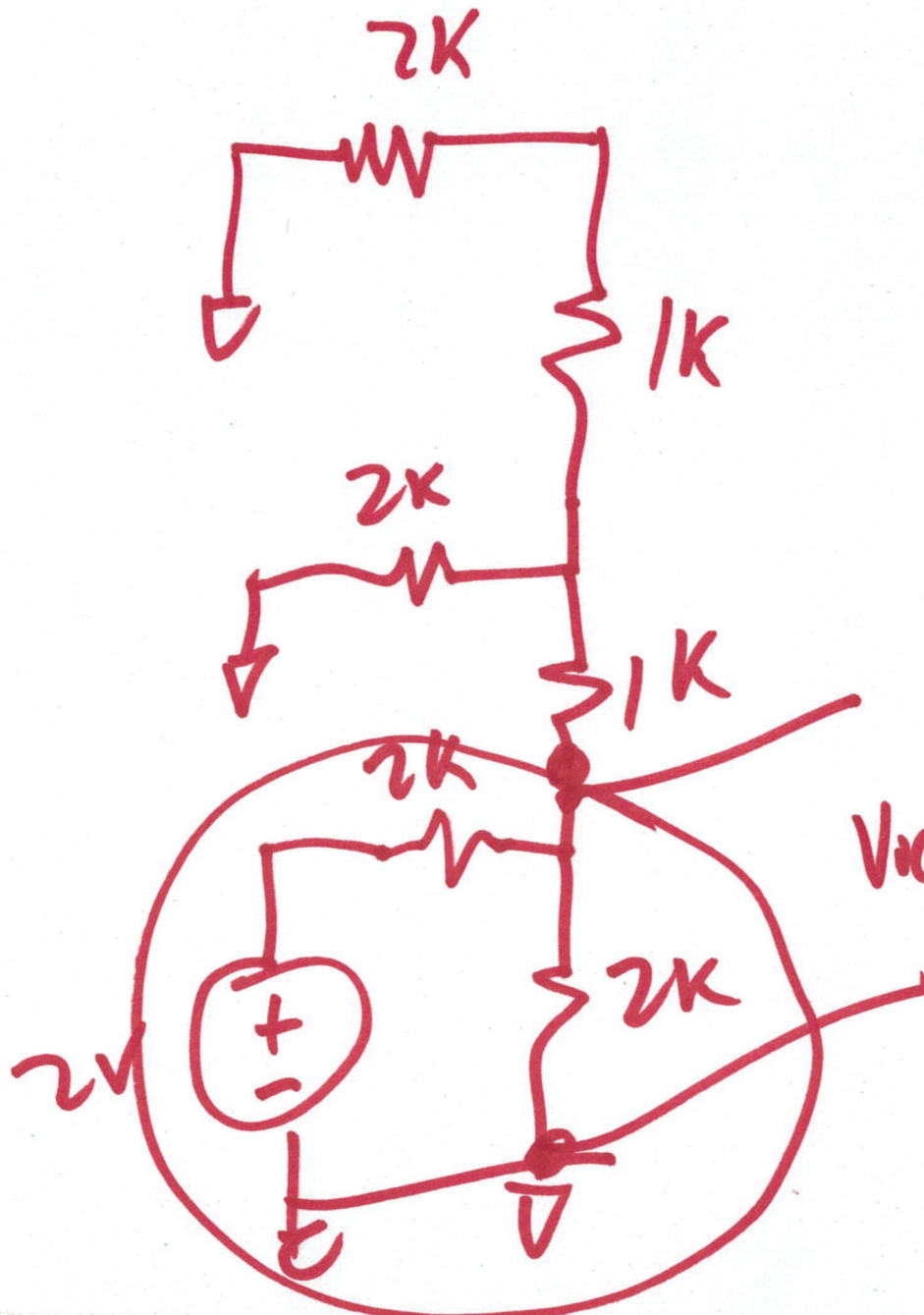

$$V_{OC} = 2 \cdot \frac{2k}{2k + 2k} = 2 \cdot \frac{1}{2}$$

$$R_{TH} = 1k$$

13)

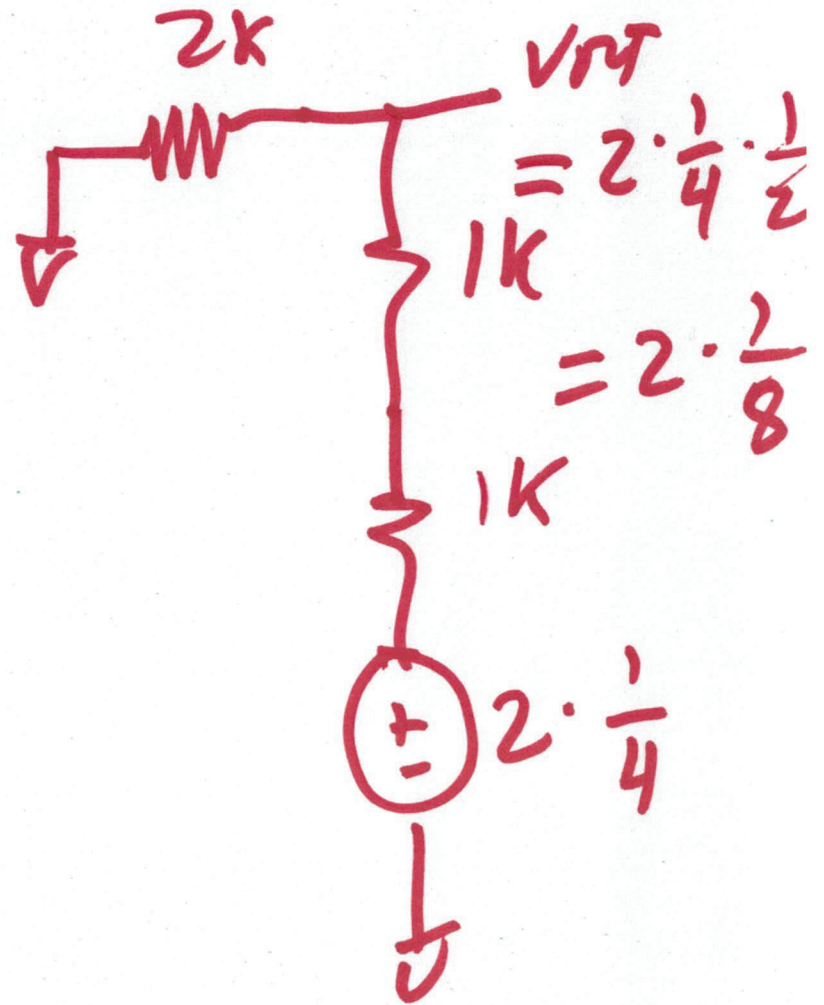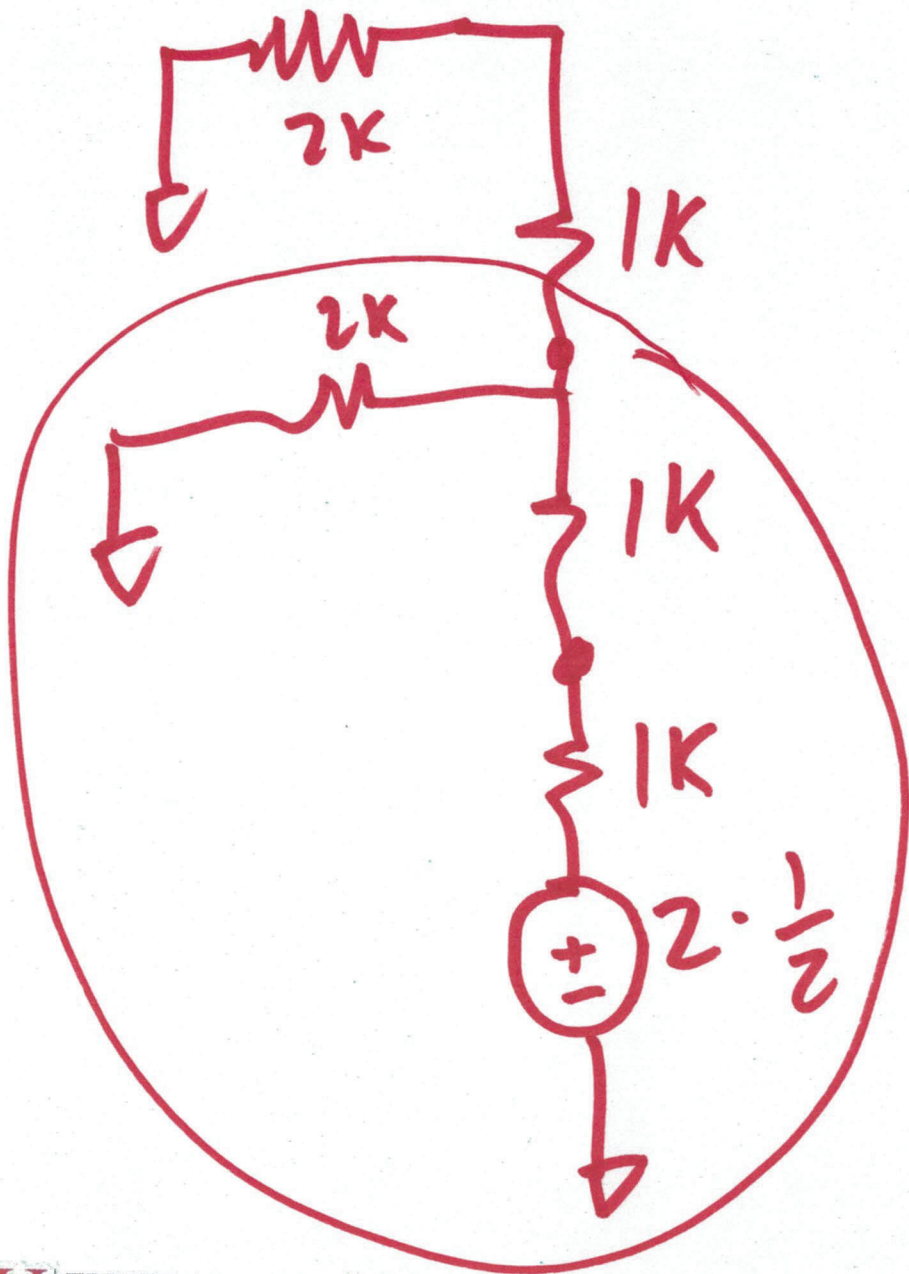

14)