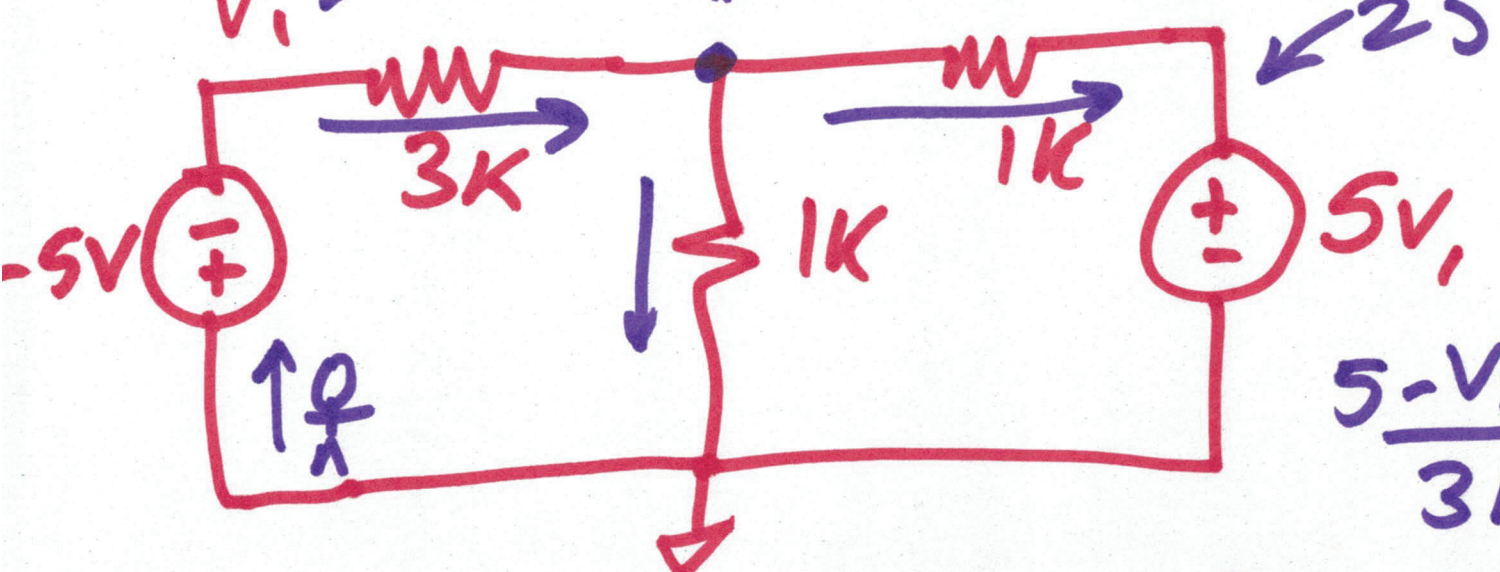


EE 221

Circuits II

February 1, 2021


$v_i = 5$ v_x Lecture 4



$$\frac{5 - v_x}{3k} = \frac{v_x}{1k} + \frac{v_x - 25}{1k}$$

$$5 - v_x = 3v_x + 3v_x - 75$$
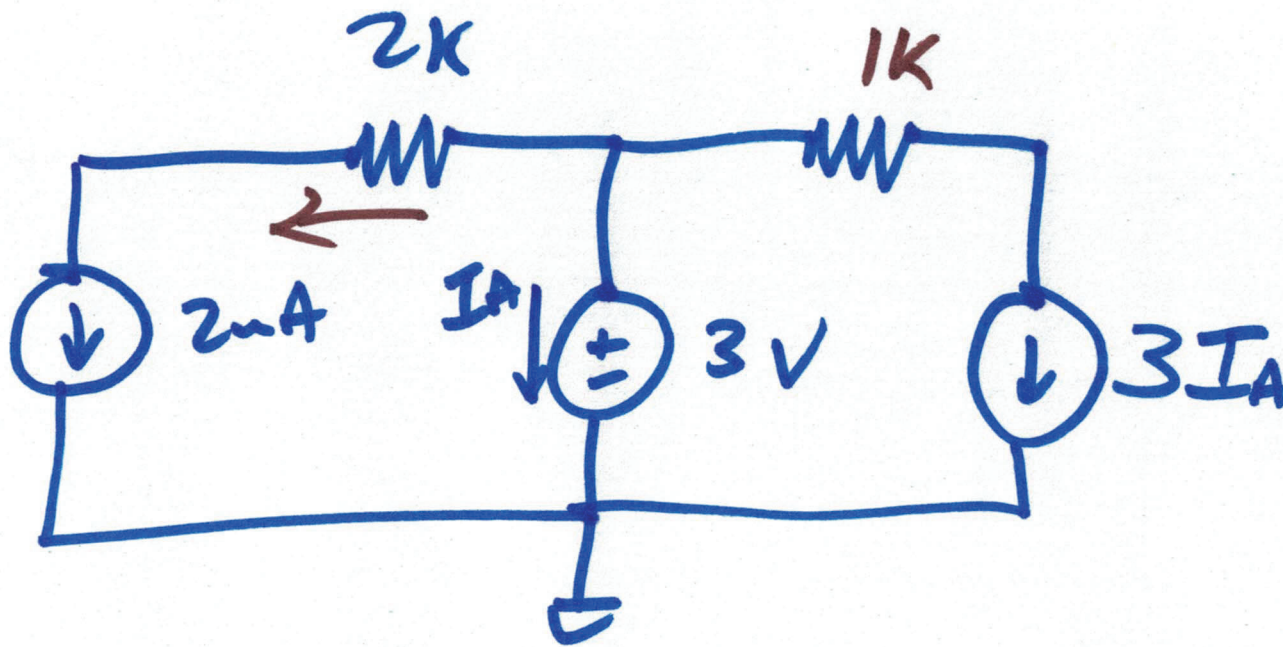
$$80 = 7v_x \quad v_x = \underline{\underline{80}} \text{ V}$$





$$2\mu\text{A} + I_A + 3I_A = 0$$

$$4I_A = -2\mu\text{A}$$

$$I_A = -\frac{1}{2}\mu\text{A} = -500\text{nA}$$

2)

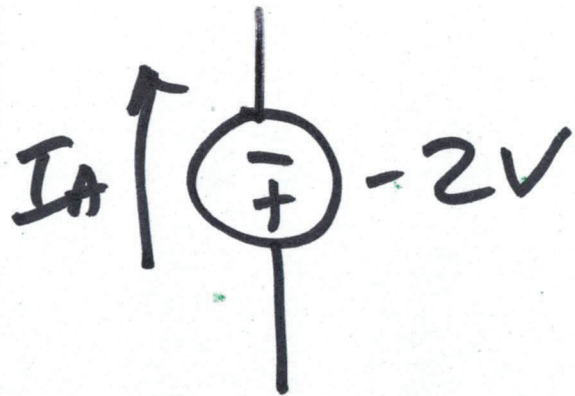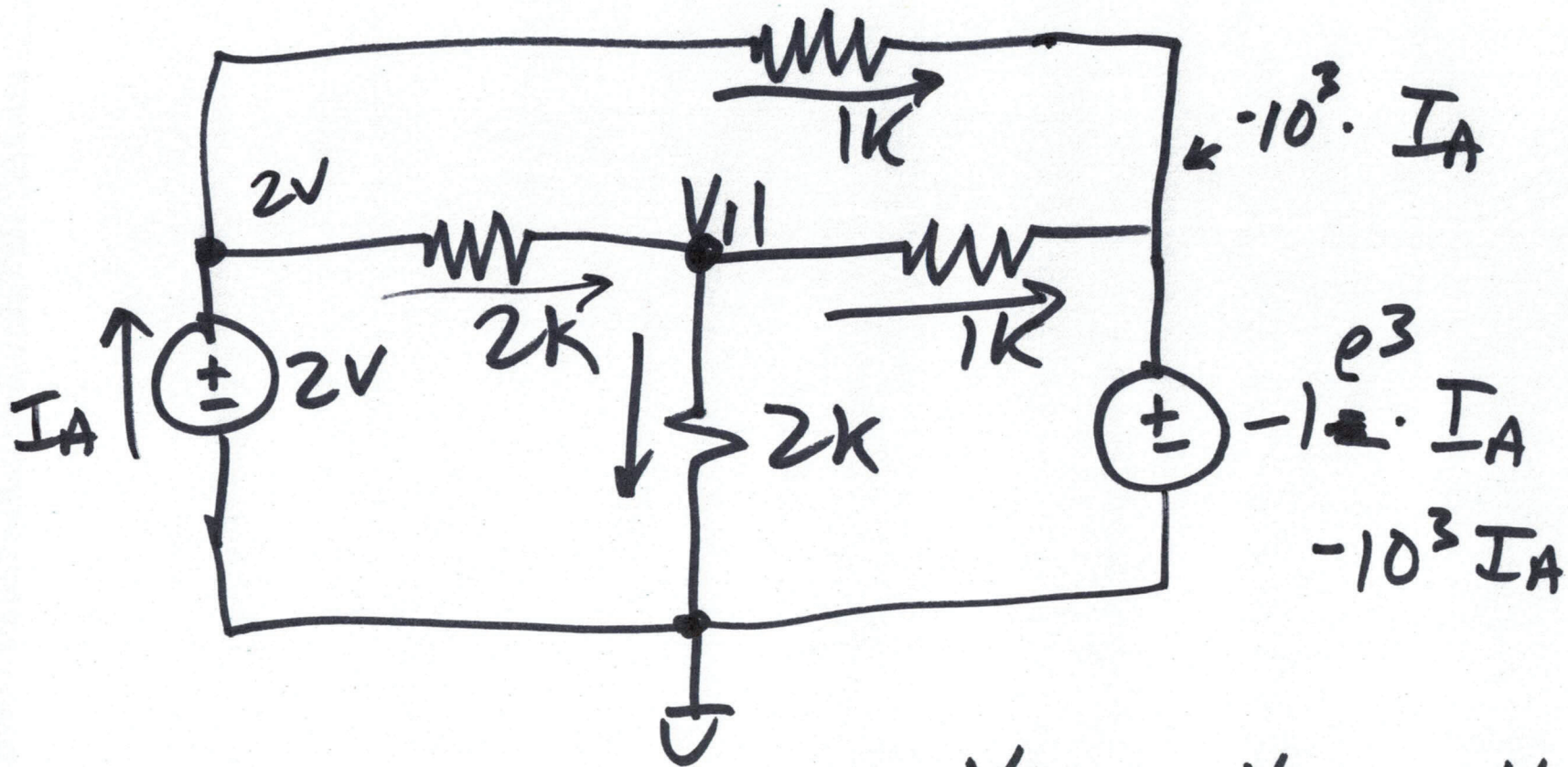

$$\frac{2 - V_{11}}{2k} = \frac{V_{11}}{2k} + \frac{V_{11} - (-10^3 I_A)}{1k}$$

$$I_A = \frac{2 - V_{11}}{2k} + \frac{2 - (-10^3 I_A)}{1k}$$


$$2 - V_{11} = V_{11} + 2V_{11} + 2,000I_A$$

$$2000I_A = 2 - V_{11} + 2V_{11} + 2000I_A$$

$$V_{11} = 6V$$

$$-4 = 6 + 12 + 2,000I_A$$

$$\frac{-22}{2,000} = I_A = -11\mu A$$

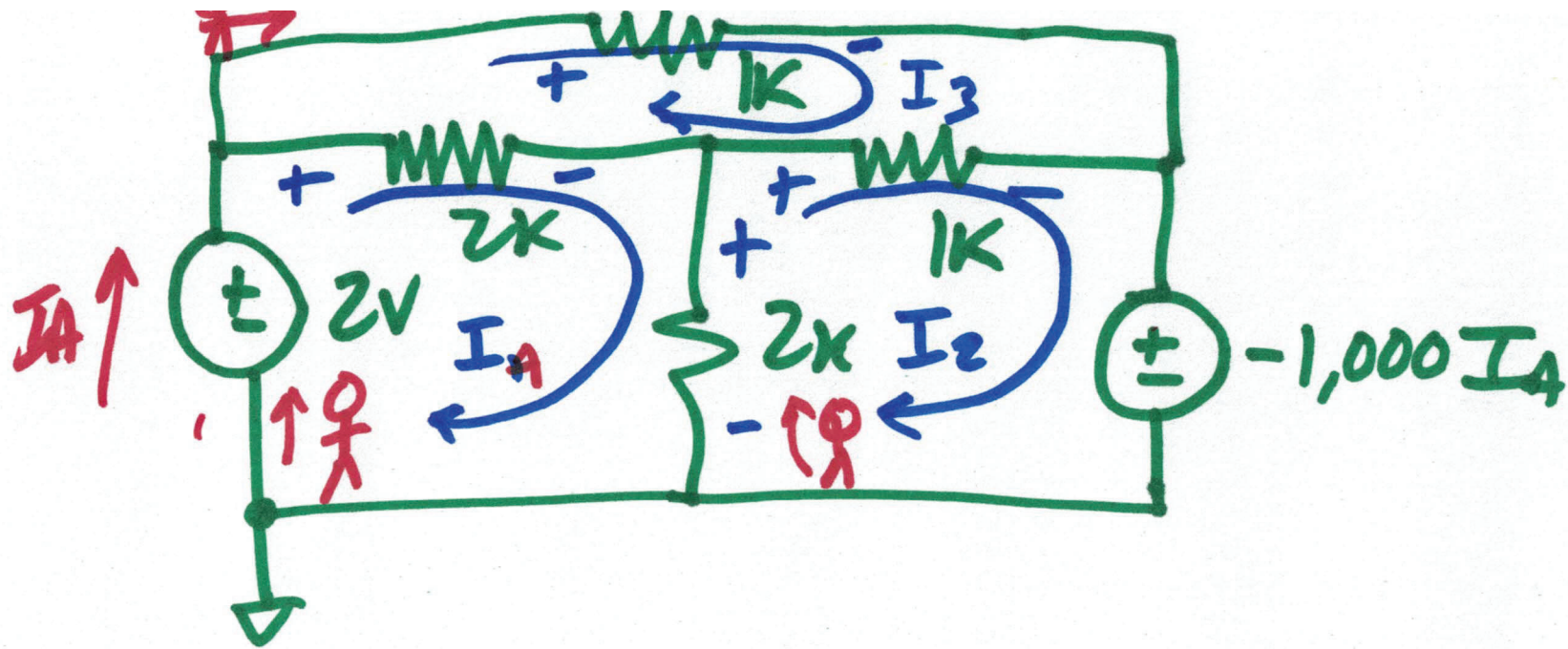


$$2 - 2k(I_A - I_3) - 2k(I_A - I_2) = 0$$

$$0 = +2k(I_A - I_2) - 1k(I_2 - I_3) - (-10^3 I_A)$$

$$-1k(I_3) + 10^3 I_A + 2V = 0$$


6)

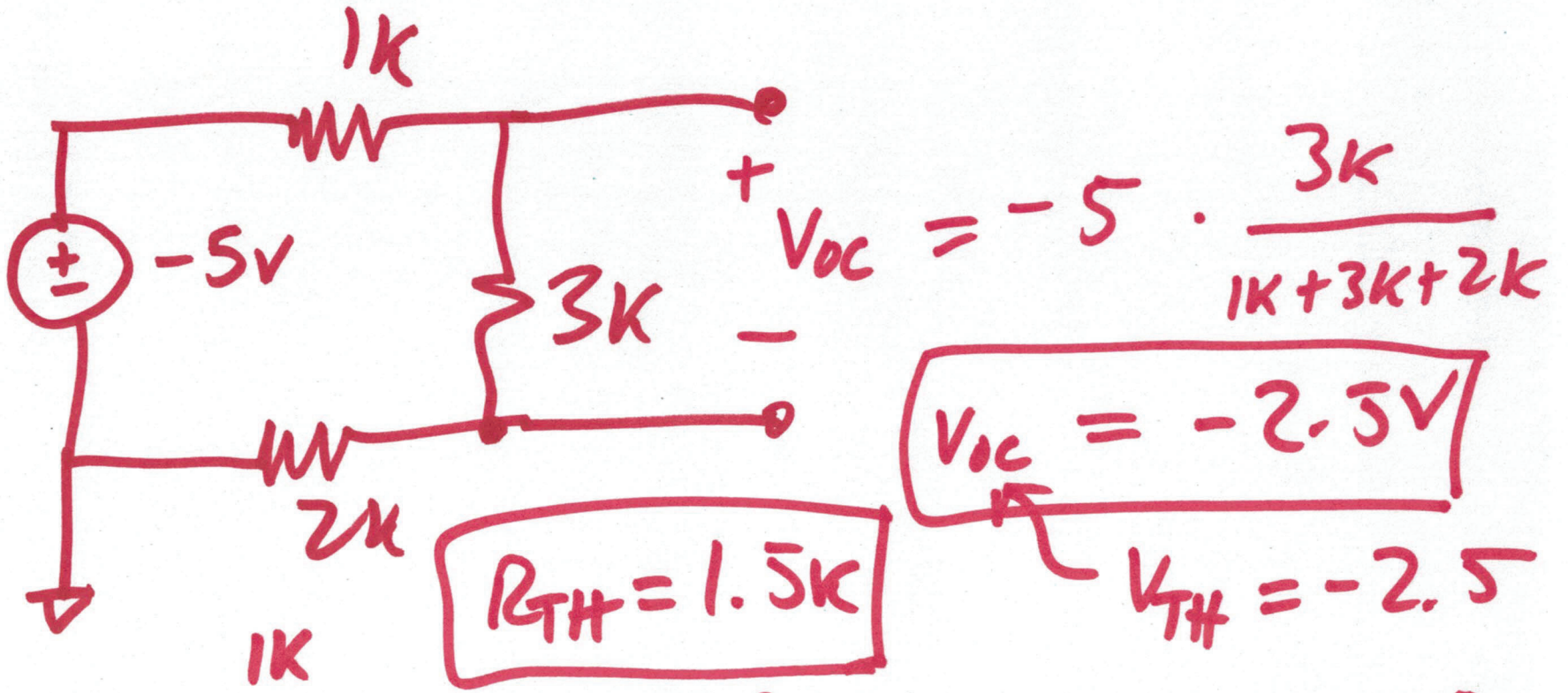


$$V_{oc} = -5 \cdot \frac{3k}{1k + 3k + 2k}$$

$$V_{oc} = -2.5V$$

$$V_{th} = -2.5$$

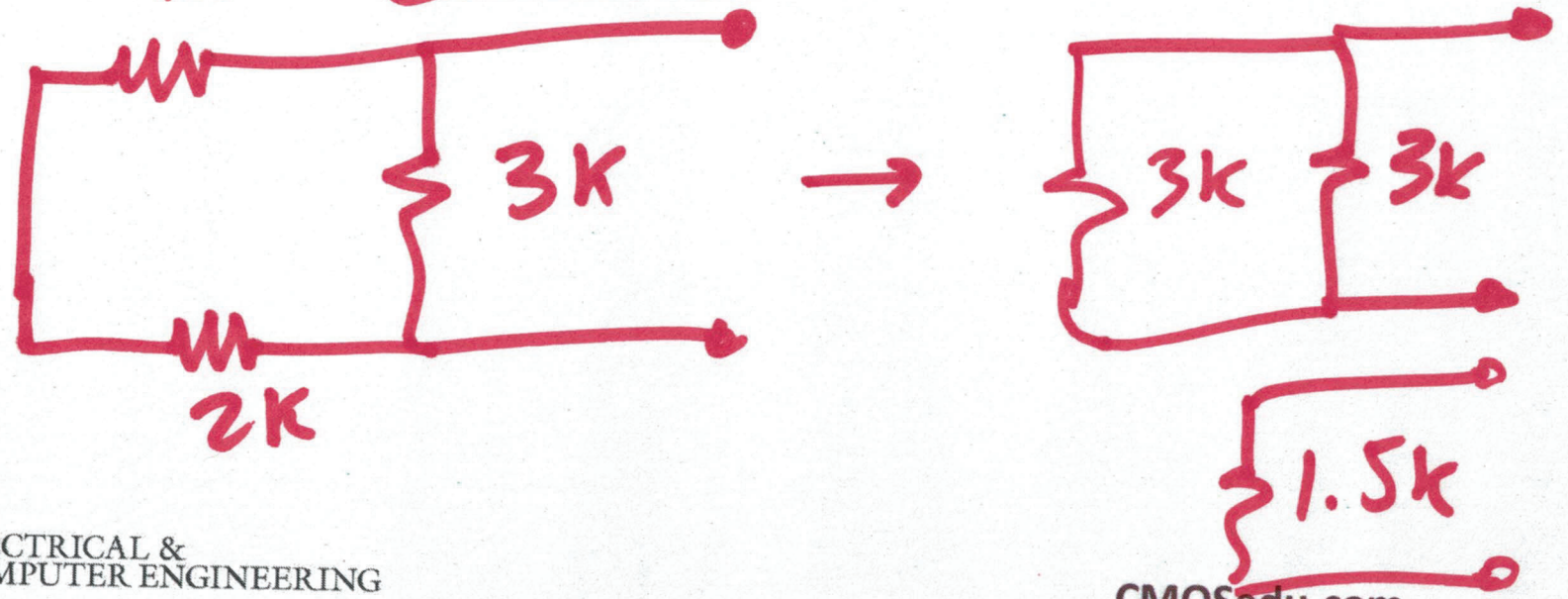


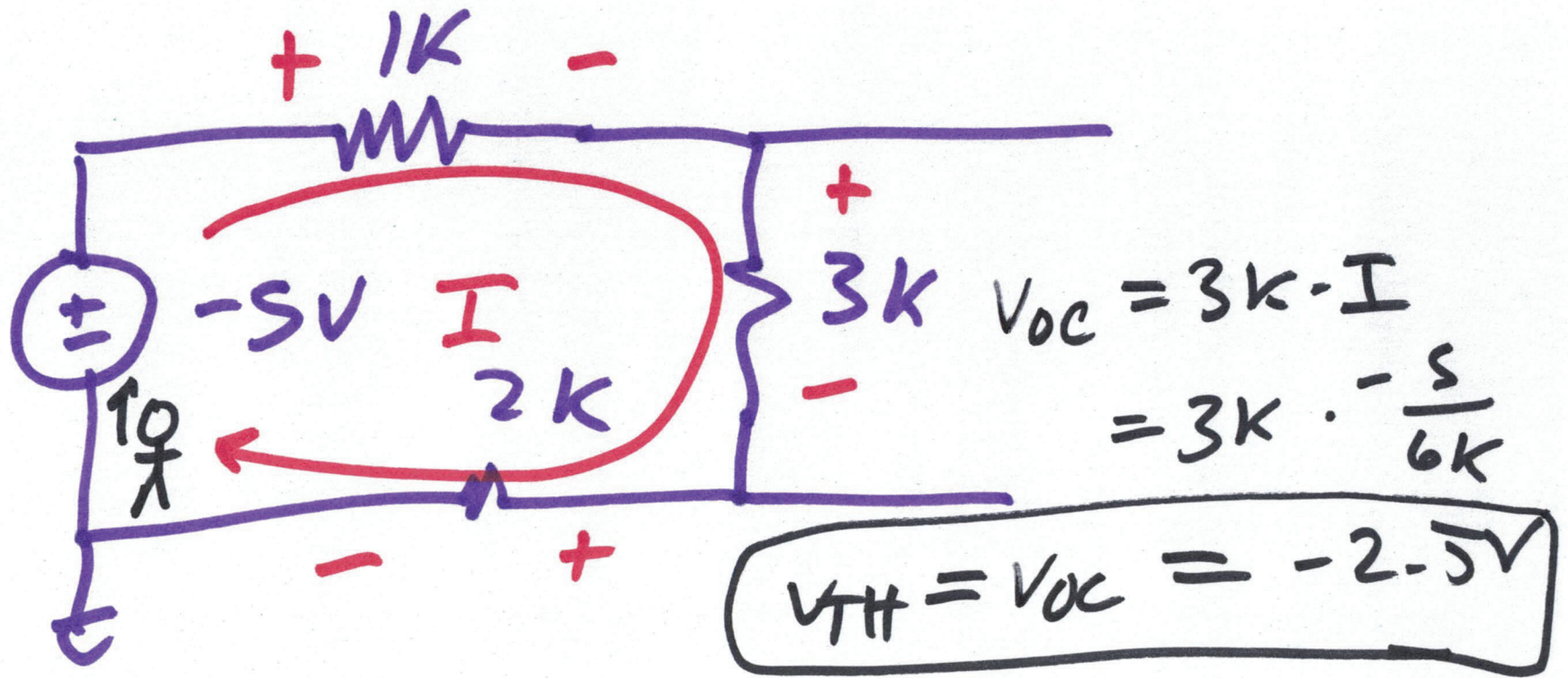

$$+(-5V) - 1kI - 3kI - 2kI = 0$$

$$6kI = -5$$


$$I = -\frac{5}{6k}$$

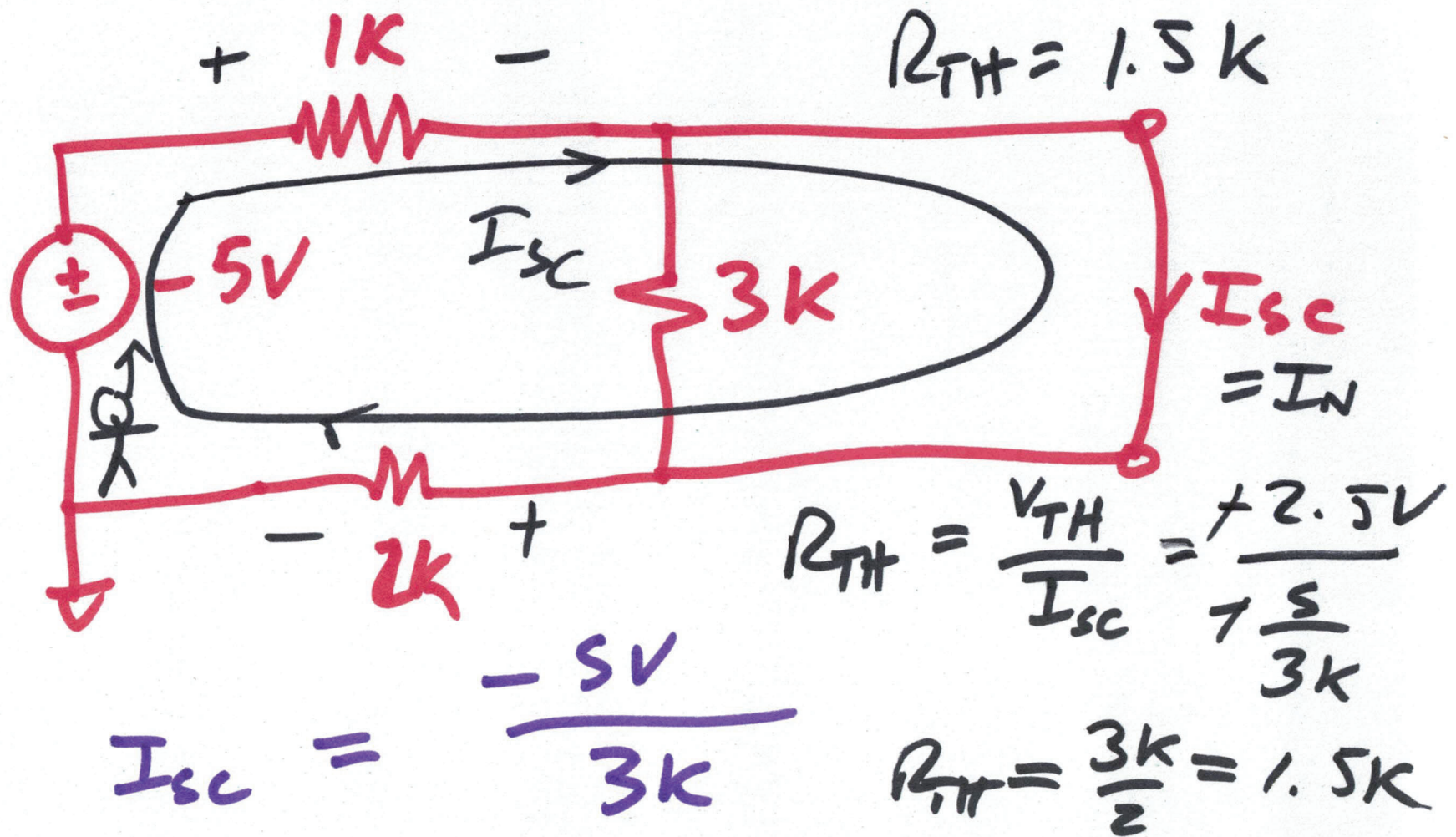

$$+(-5V) - 1k I_{sc} - 2k I_{sc} = 0$$

b)

THEVENIN

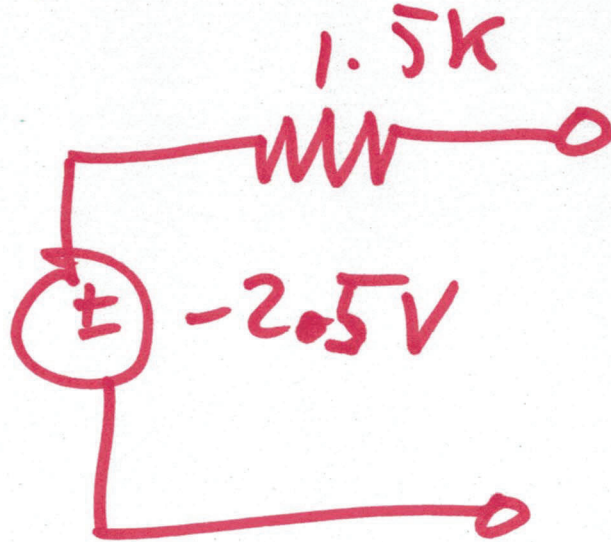

NORTON

