
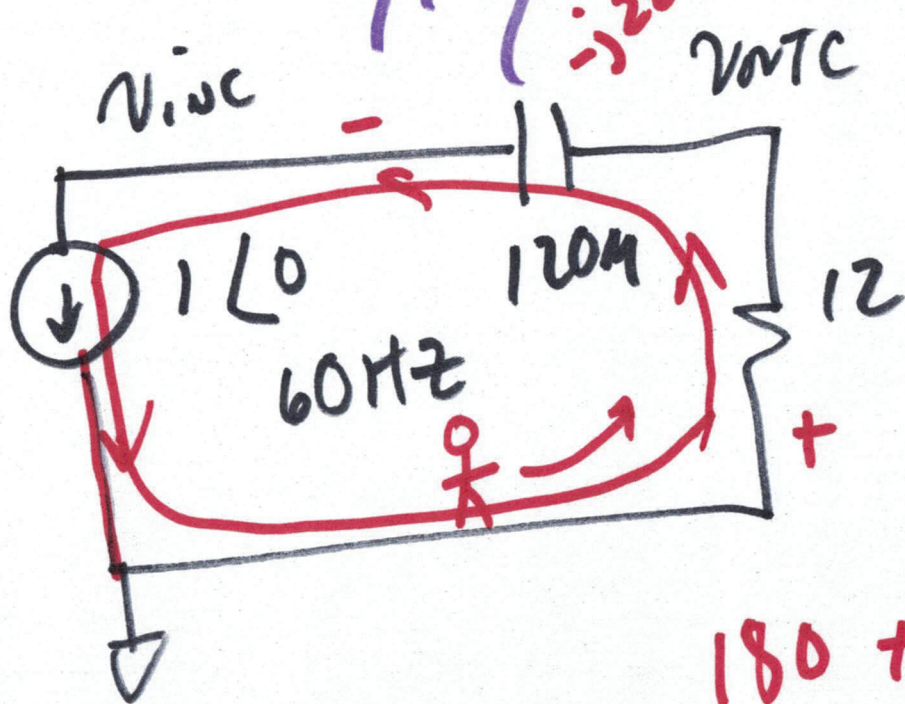


EE 221 Circuits II

Lecture 7

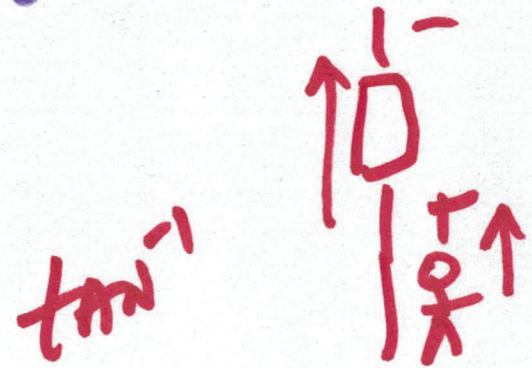

2/10/21
22.1



$$V_{INC} = \ominus (12 + (-j22.1)) \cdot 1\Omega$$


$$+ V_{INC} = 25 \angle 118.5^\circ$$



$$180 + \tan^{-1} \frac{-22.1}{12} = -61.5^\circ$$


$$v_{inc} = 25 \sin(2\pi \cdot 60 \cdot t + 118.5)$$

$$118.5 = \frac{\Delta t}{T} \cdot 360 \rightarrow \Delta t = 5.48 \text{ s}$$

\downarrow 16.67 ms

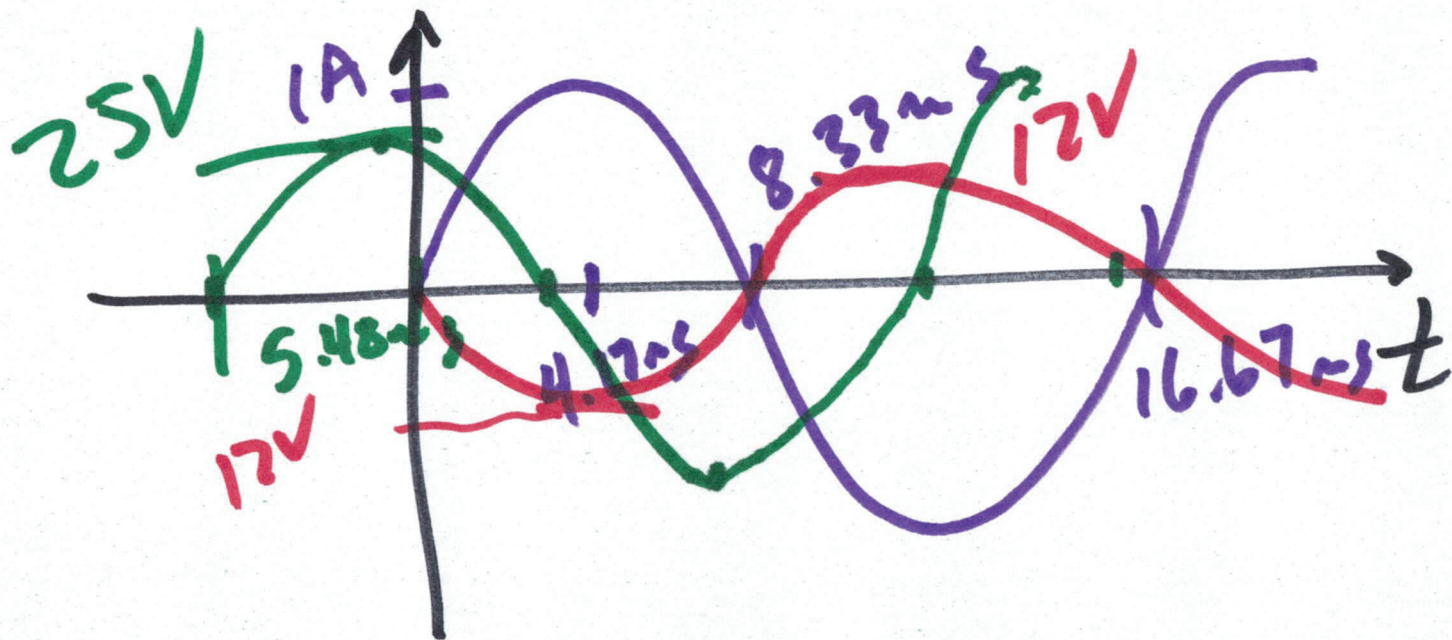

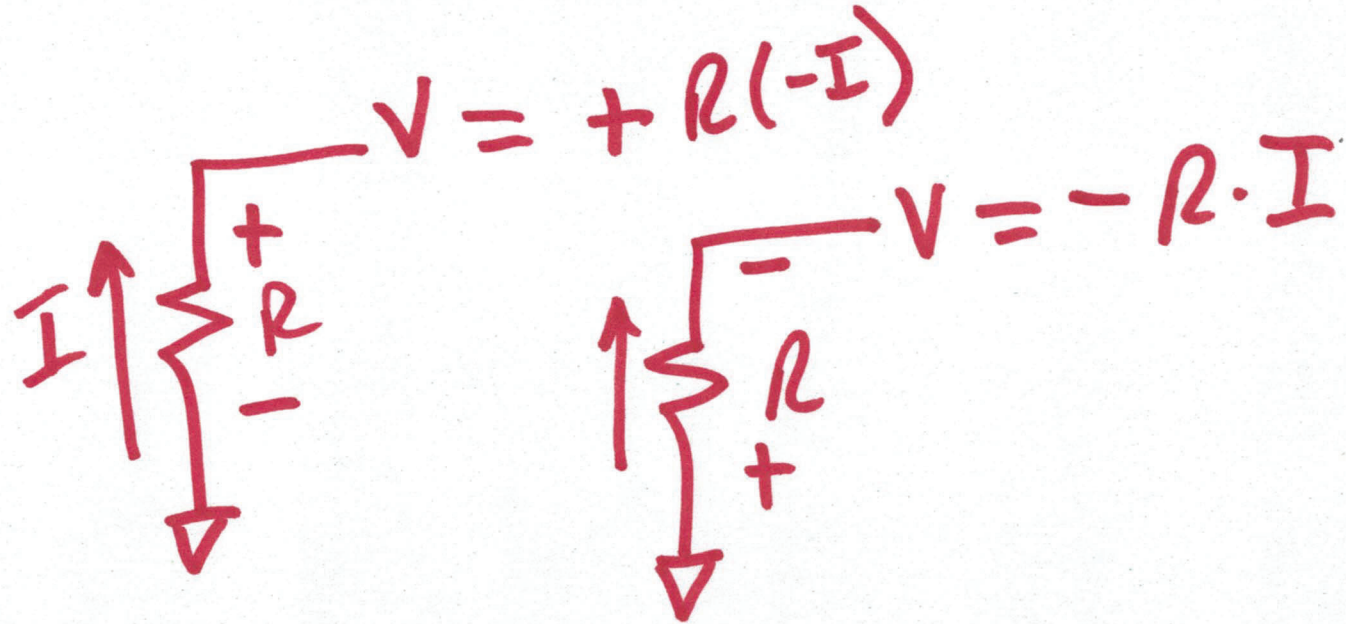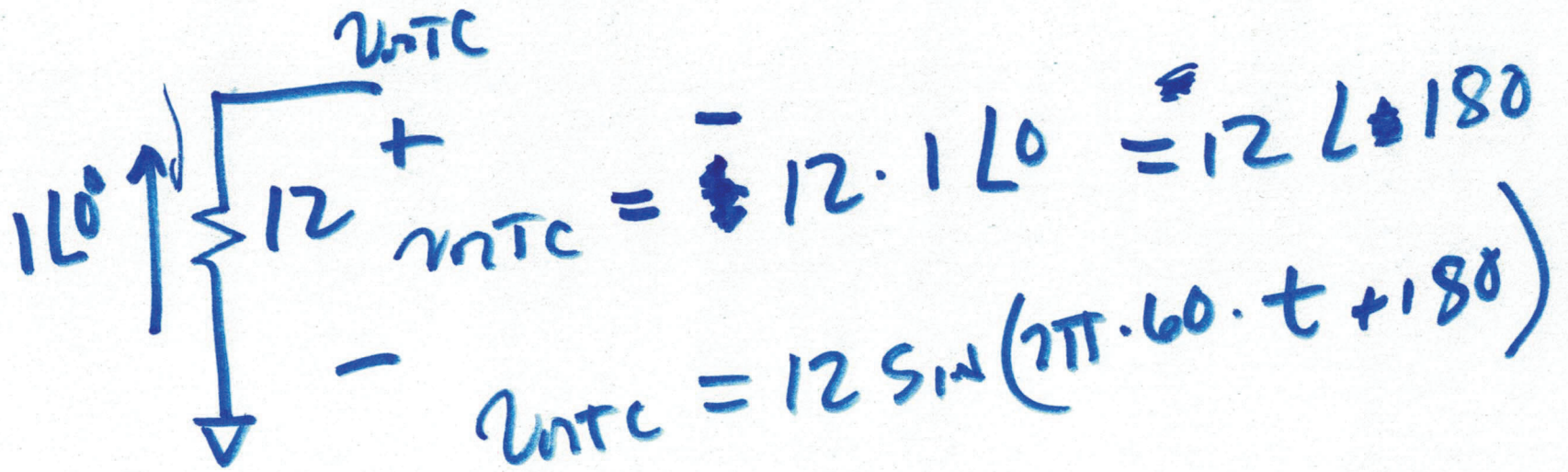

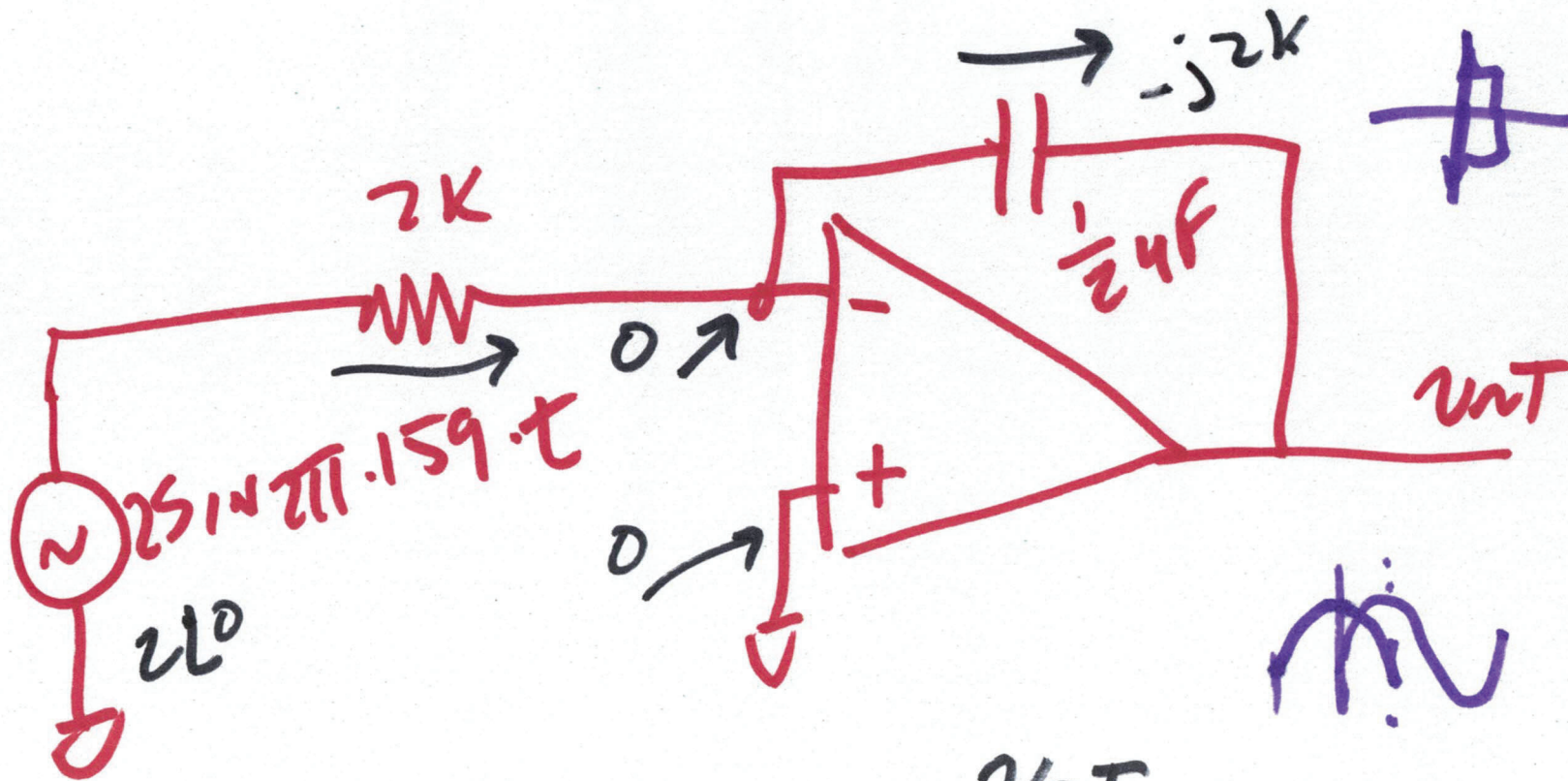


$$\frac{2L^0}{2k} = \frac{0 - V_{out}}{2k \angle -90^\circ}$$

$$2 \angle -90 = -V_{out}$$

$$V_{out} = 2 \angle 90$$

4)

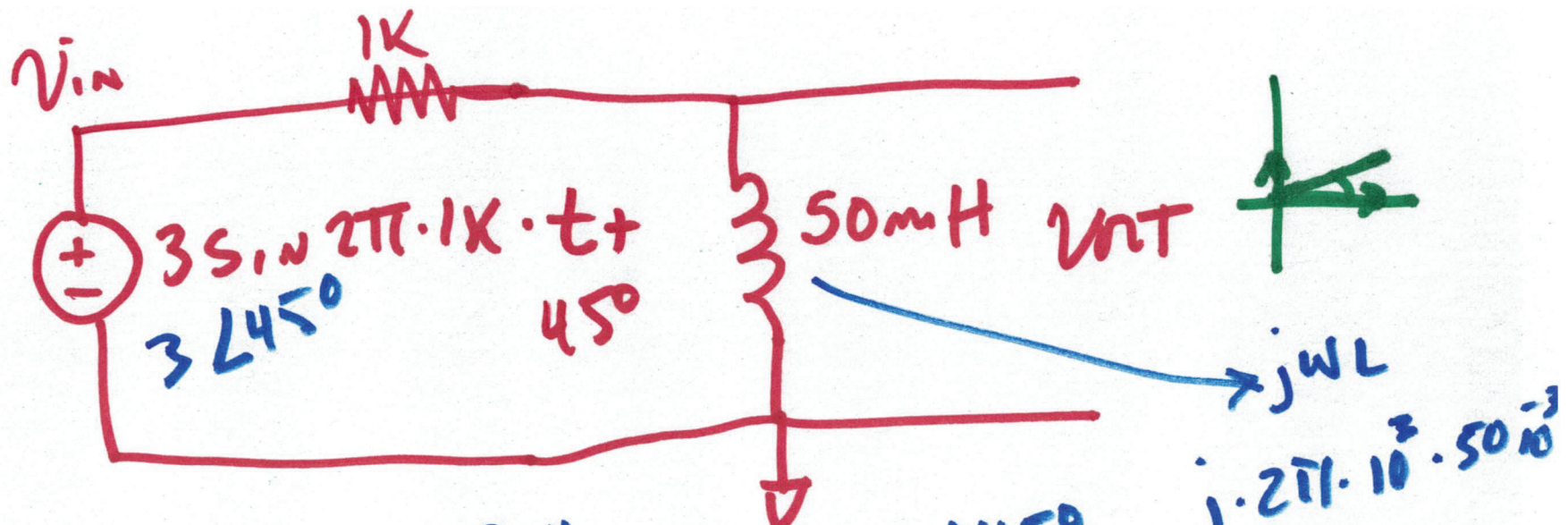

$$v_{out} = \frac{j \cdot 314 \cdot 3 \angle 45^\circ}{j \cdot 314 + 1000}$$

$$= \frac{314 \angle 90^\circ \cdot 3 \angle 45^\circ}{1048 \angle 17.43^\circ} = 0.9 \angle 117.6^\circ$$

$$\angle = 90 + 45 - 17.43$$

5)

$$v_{in} = 3 \sin(2\pi \cdot 1\text{kHz} \cdot t + 45^\circ)$$

$$v_{out} = 900\text{mV} \cdot \sin(2\pi \cdot 1\text{kHz} \cdot t + 117.6)$$


$$45 = \frac{\Delta t}{1\text{ms}} \cdot 360$$



$$f = 1\text{kHz}$$

$$T = 1\text{ms}$$

$$\frac{\Delta t}{1\text{ms}} = \frac{45}{360} = \frac{1}{8} \rightarrow \Delta t = 125\mu\text{s}$$
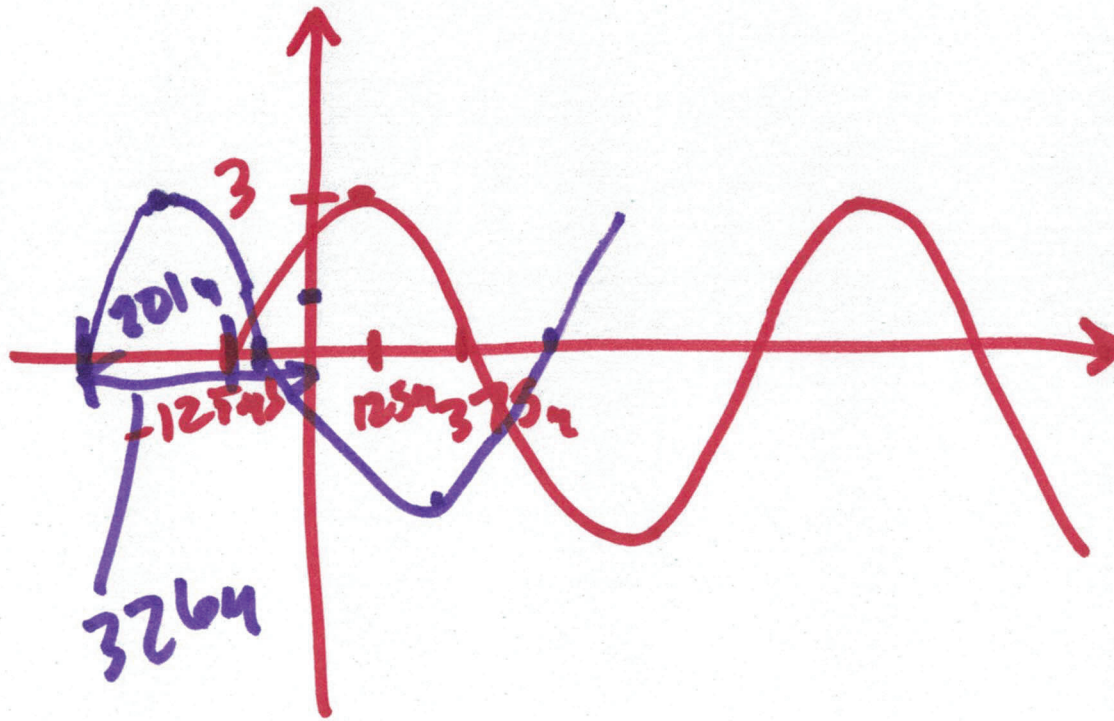
$$117.6 = \frac{\Delta t}{1\text{ms}} \cdot 360 \quad \Delta t = 326\mu\text{s}$$



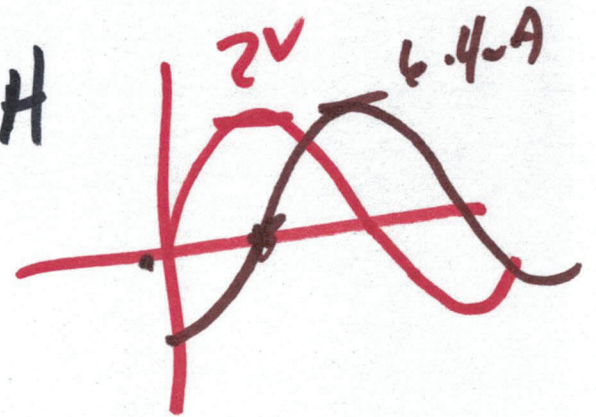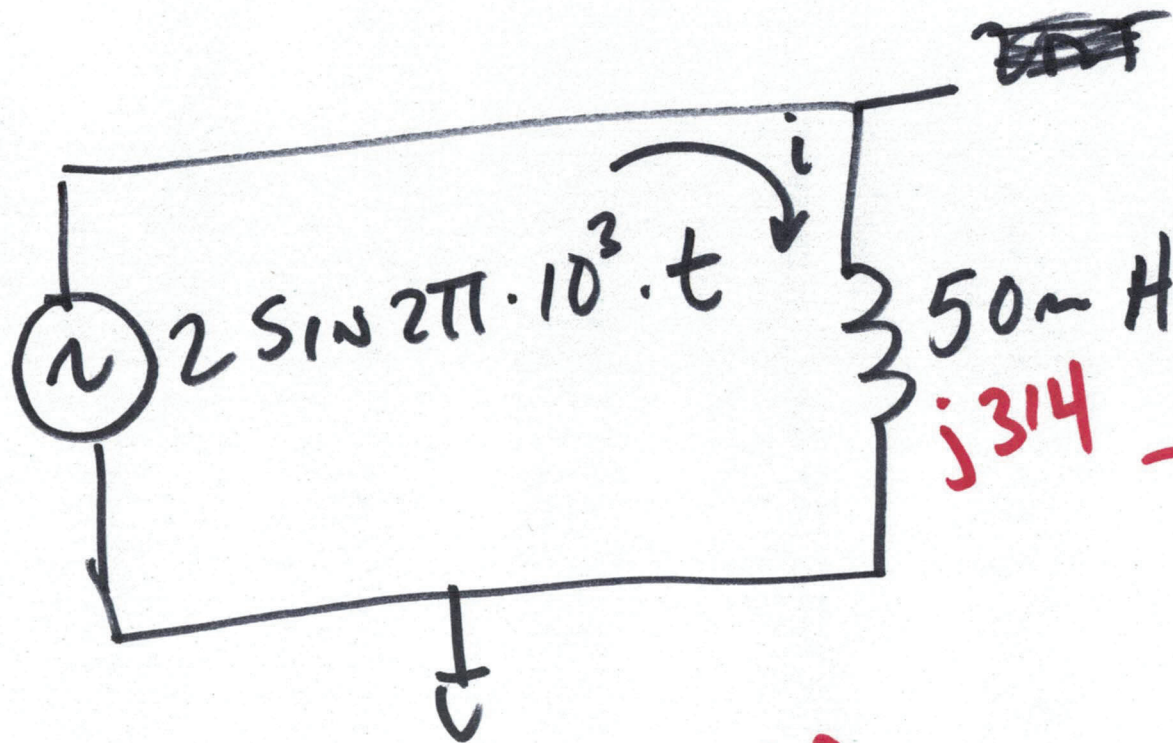

$$i = \frac{2\angle 0}{j314} = 6.4 \text{ mA} \angle -90^\circ$$

$$i(t) = 6.4 \text{ mA} \sin(2\pi \cdot 10^3 \cdot t - 90^\circ)$$

8/