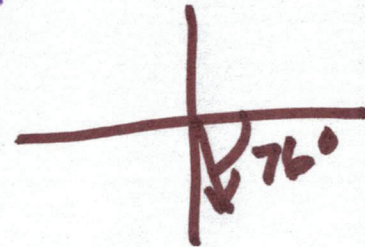


EE 221 circuits II

Feb. 22, 2021

Lecture 9




$$170 \angle 0 \cdot \frac{500}{j33.1 + 129 \angle -76}$$

$$R = 129 \cos(-76) = 31.2$$

$$I_m = 129 \sin(-76) = -125.2$$

$$\frac{170 \angle 0 \cdot 500 \angle 0}{31.2 + j(-125.2 + 33.1)}$$

7

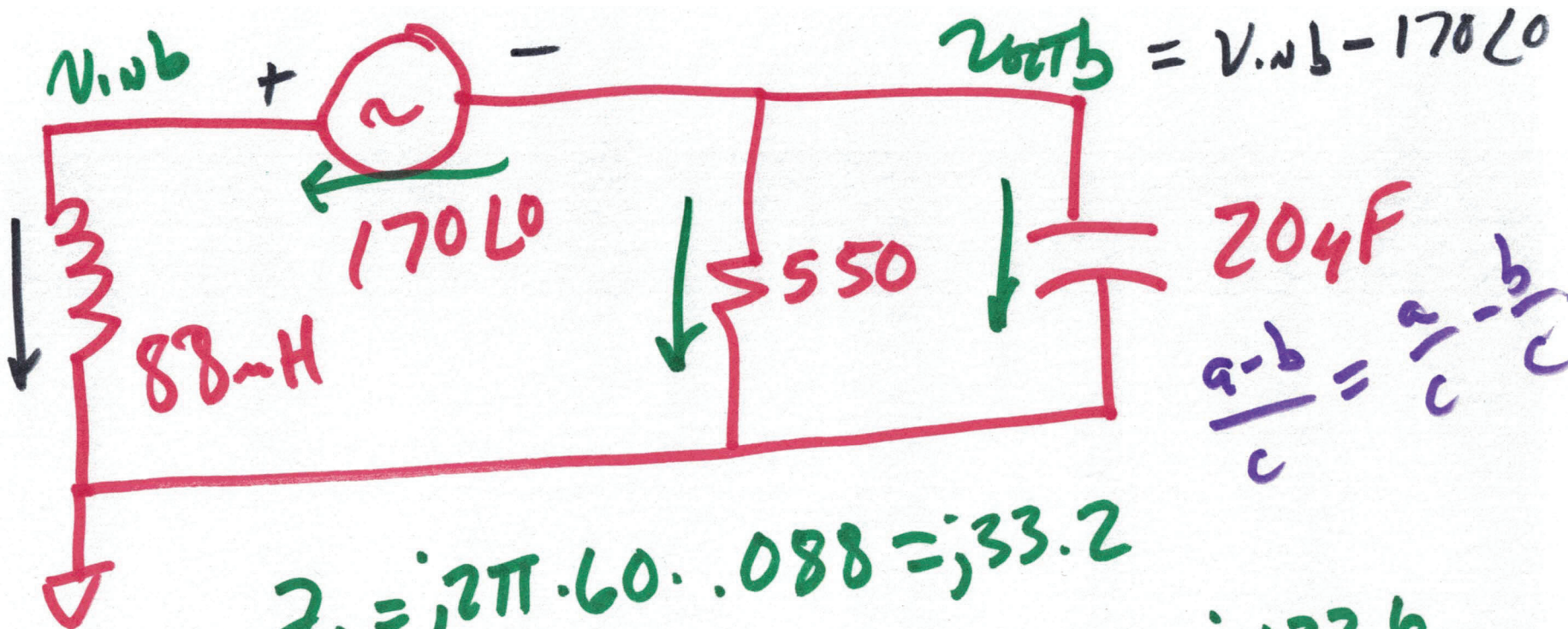


$$\frac{a-b}{c} = \frac{a}{c} - \frac{b}{c}$$

$$Z_L = j2\pi \cdot 60 \cdot 0.088 = j33.2$$

$$Z_C = -j \frac{1}{2\pi \cdot 60 \cdot 204} = -j132.6$$
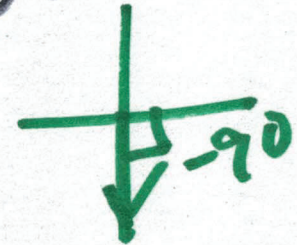
$$0 = \frac{v_{in,b}}{j33.2} + \frac{v_{in,b} - 170 \mu A}{550} + \frac{v_{out,b} - 170 \mu A}{-j132.6}$$



2)

$$0 = v_{inb} \left(\frac{1 - j(0.03)}{j33.2} + \frac{1}{550} + \frac{1 + j.001810}{-j132.6} \right)$$

Mistake

$$- \frac{170 \angle 0}{550 \angle 0}$$

$$- \frac{170 \angle 0}{132.6 \angle -90}$$

$$v_{inb} \cdot 10^{-3} (1.818 - j)(22.46)$$

↓

$$- .31 \angle 0 - 1.29 \angle 90$$

$$- .31 + j0 - j1.29$$

$$v_{inb} = -.3 - j1.26$$

$$V_{inb} = -.3 - j1.26$$




$$V_{inb} = 1.3 \angle -104$$

$$\rightarrow V_{outb} = V_{inb} - 170 \angle 0^\circ$$

$$= V_{inb} - 170 \angle 180^\circ$$

$$V_{outb} = -170.3 - j1.26$$

$$V_{outb} = 170.3 \angle 180^\circ$$

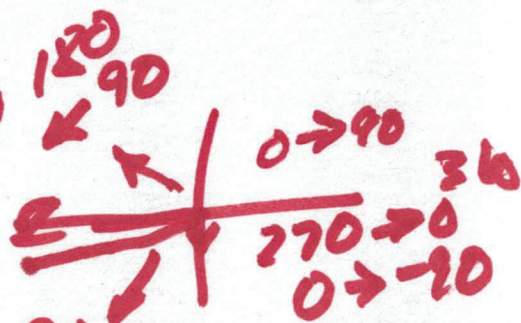

4)

$$v_{inb} = 1.3 \sin(2\pi \cdot 60 \cdot t - 104)$$

$$v_{outb} = 170.3 \sin(2\pi \cdot 60 \cdot t + 180)$$

$$T = 16.667 \mu s$$

$$t_d = 8.3 \mu s$$

~~$v_{outb} = 170.3$~~

$$v_{inb} \rightarrow$$

$$360 \cdot \frac{\Delta t}{16.67} = 104$$

$$t_d = 4.81 \mu s$$

5)

$$0 = V_{inb} \cdot 10^{-3} \left(-j \frac{30}{550} \right) + 1.81 + j7.5$$


$$+ \frac{-170 \angle 0^\circ}{550 \angle 0^\circ} + \frac{170 \angle 0^\circ}{132.6 \angle 90^\circ}$$


$$= V_{inb} \cdot 10^{-3} (1.81 + j4.5) + -0.31 + j1.25$$

$$V_{inb} = \frac{-0.31 - j1.25}{1.81 + j4.5} \cdot 10^3$$

$$= \frac{10^3 \cdot 1.28 \angle -76^\circ}{4.8 \angle 68^\circ} =$$




Root Mean Square

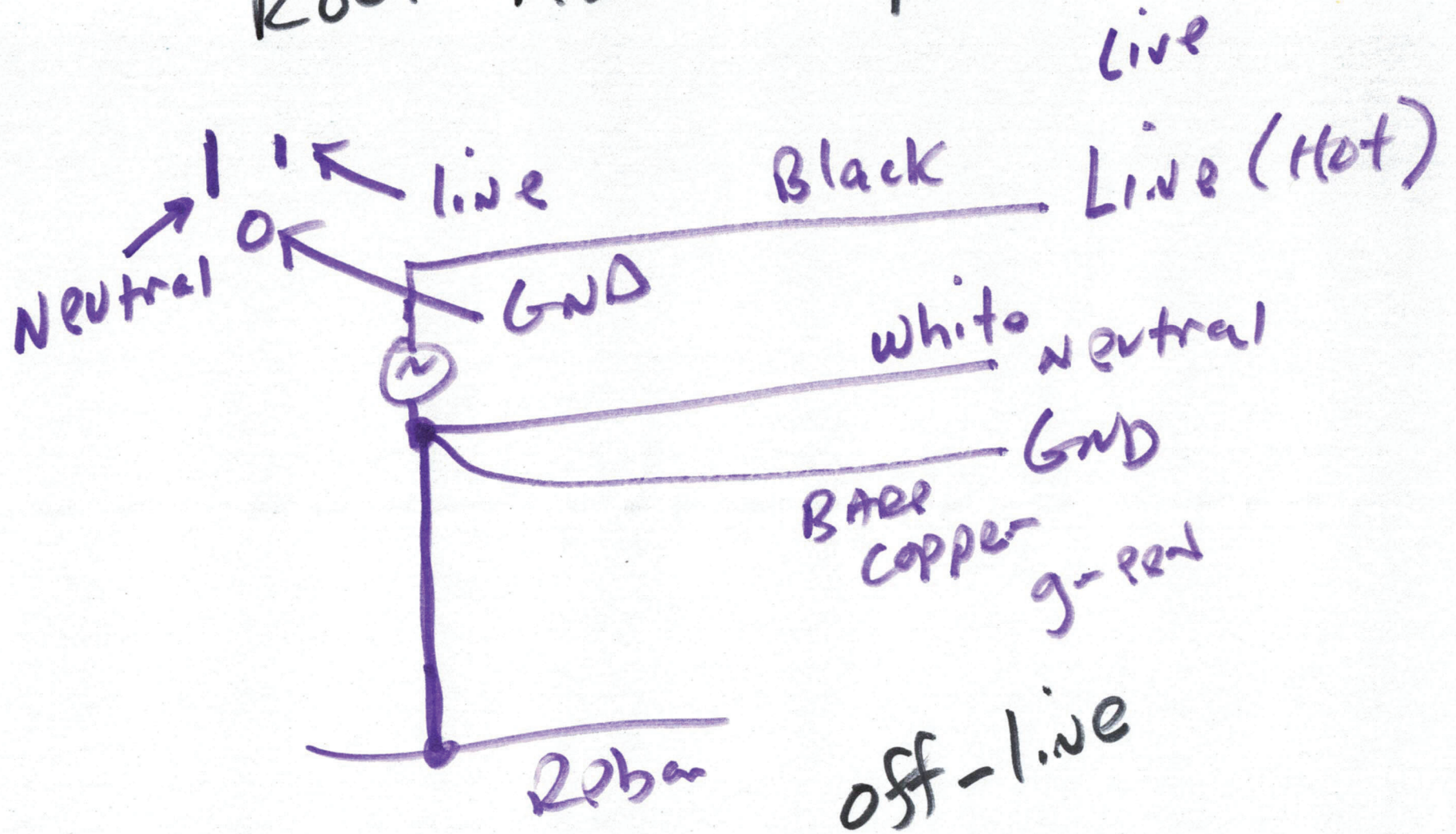

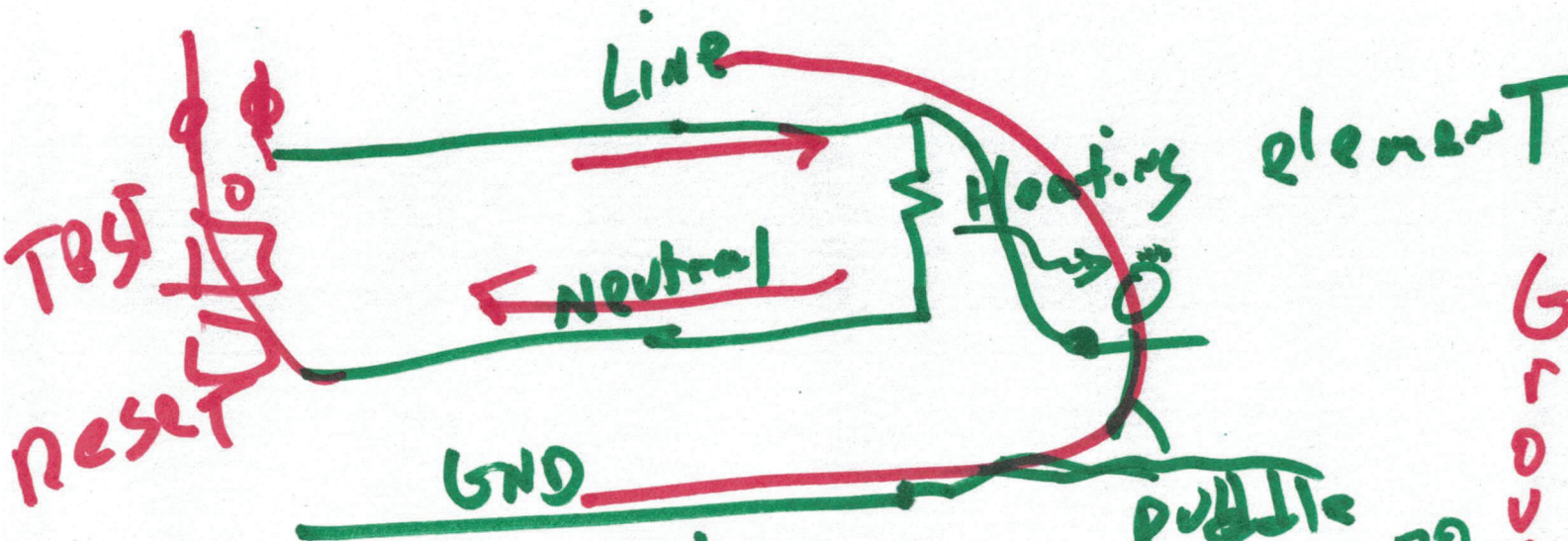

TRIP
Reset

GFCI
trip
at
120V
10A
resistor

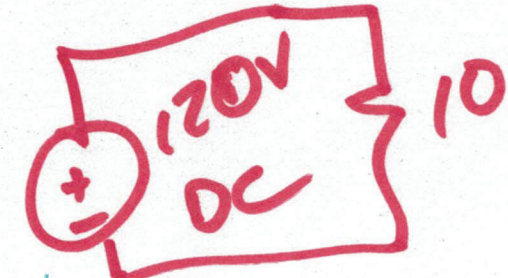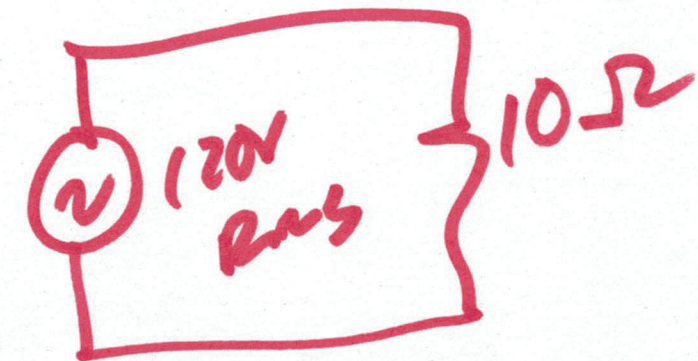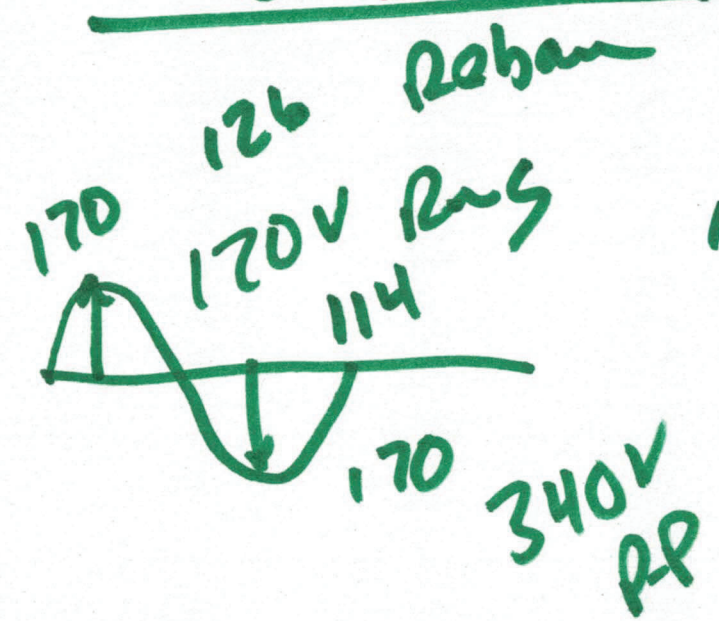

instantaneous power

$$p(t) = v(t) \cdot i(t) \quad \sim$$

$$\frac{1}{T} \int_0^T i(t) + v(t) dt$$

$$i = C \frac{dv}{dt}$$
$$v = L \frac{di}{dt}$$

$$P_{AVG} = \frac{1}{T} \int_0^T p(t) dt$$

APPARENT $P = I_{RMS} \cdot V_{RMS}$