

Closed book and notes.

Show your work for credit and place a box around each of your answers.

- In the following circuit find the currents in the directions indicated and V_2 using mesh analysis. (4 points)

