

Quiz #4 EE 221 Spring 2021

Name: _____

Closed book and notes.

Show your work for credit.

1. Find the Thevenin and Norton equivalents of the following circuit at the red terminals indicated. (4 points)

