

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Find the AC current that flows in the following circuit and sketch, along with VS, to show the magnitudes and phase shift. (4 points)

