

Quiz #8 EE 221 Spring 2021

Name: _____

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Find V_{out} and sketch in the time-domain, along with V_{in} , showing the phase shift and magnitude. (4 points)

