

EE 221 Circuits II

Lecture 11

Feb. 27, 2023

$$a \cdot b \cdot c \cdot f = \frac{f}{\frac{1}{a \cdot b \cdot c}}$$

$$2\pi R C f = \frac{f}{\frac{1}{2\pi R C}} \rightarrow \frac{f}{f_{3dB}}$$

$$f_{3dB} = \frac{1}{2\pi R C}$$

log 10


logarithms


log f

Big & small on the

0.1

10,000,000 times plot

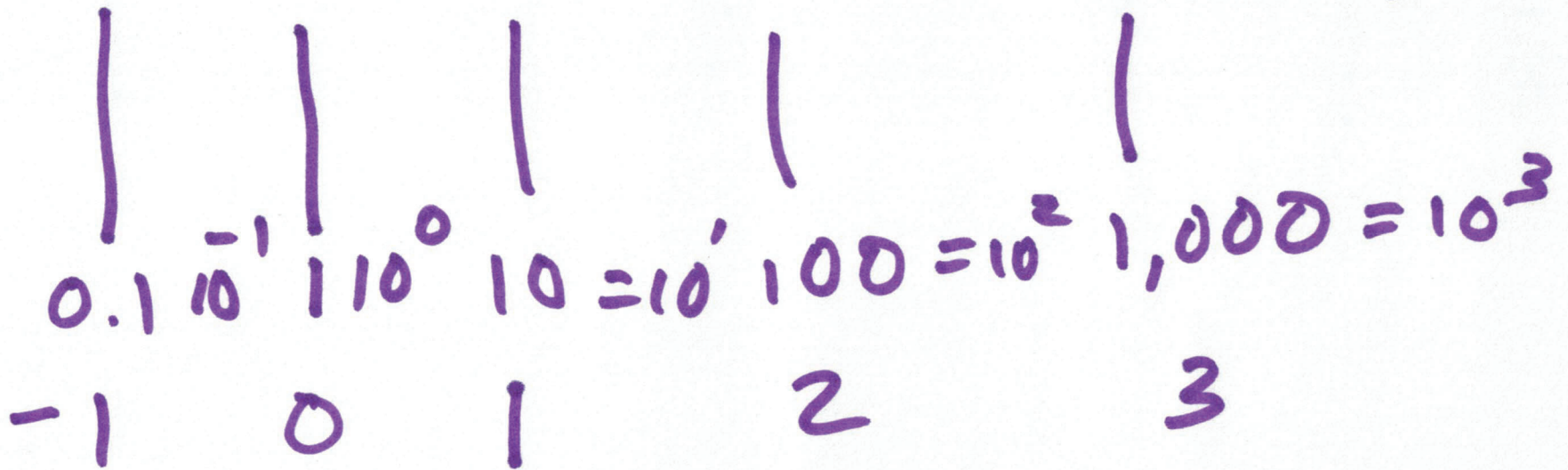


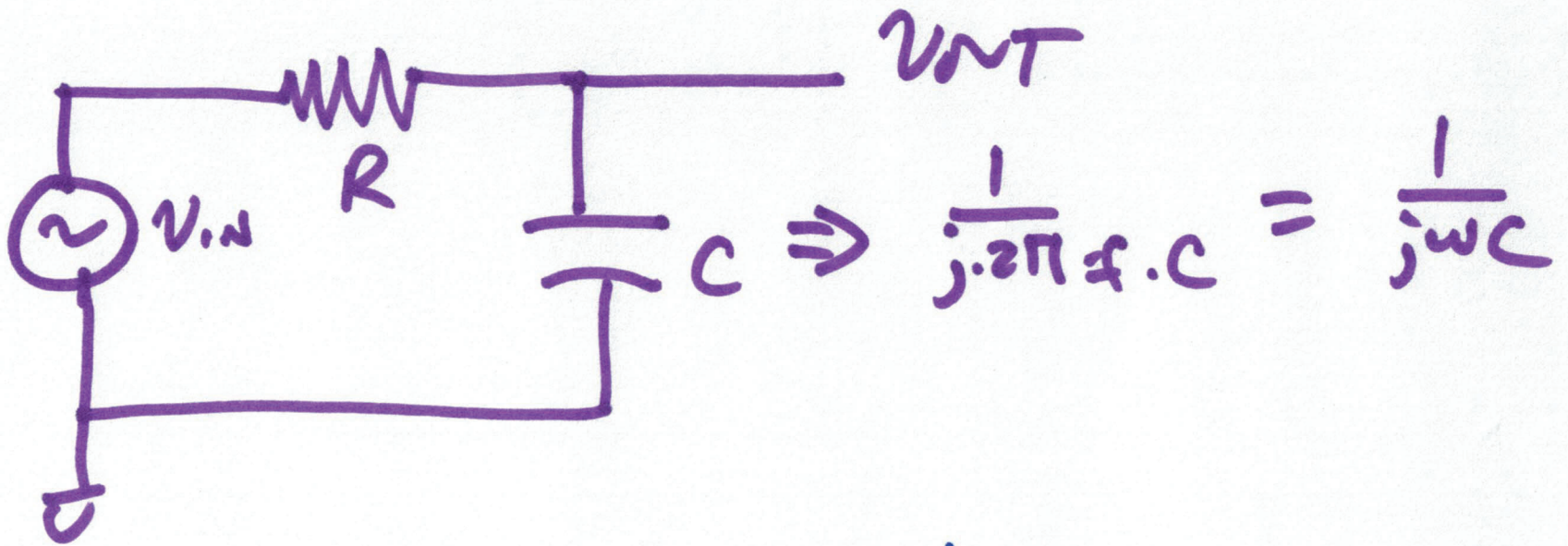

$$v_{out} = v_{in} \cdot \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R}$$

transfer function
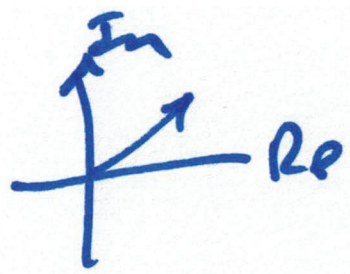
$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j\omega RC}$$



$$|a + jb| = \sqrt{a^2 + b^2}$$

$$\frac{1}{c + jd} \cdot \frac{c - jd}{c - jd}$$

Complex Conjugate

$$\frac{c}{c^2 + d^2} + j \frac{-d}{c^2 + d^2}$$

$$\left| \frac{1}{c + jd} \right| = \sqrt{\frac{c^2}{(c^2 + d^2)^2} + \frac{(-d)^2}{(c^2 + d^2)^2}}$$

$$|\frac{1}{c+jd}| = \sqrt{\frac{c^2+d^2}{(c^2+d^2)^2}} = \sqrt{\frac{1}{c^2+d^2}}$$

$$* |\frac{1}{c+jd}| = \frac{1}{\sqrt{c^2+d^2}}$$

$$\begin{aligned} * \angle \frac{1}{c+jd} &= -\tan^{-1} \frac{d}{c} \\ &= \tan^{-1} \left(-\frac{d}{c} \right) \end{aligned}$$


$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + (2\pi fRC)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{2\pi fRC}{1}$$

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}}$$
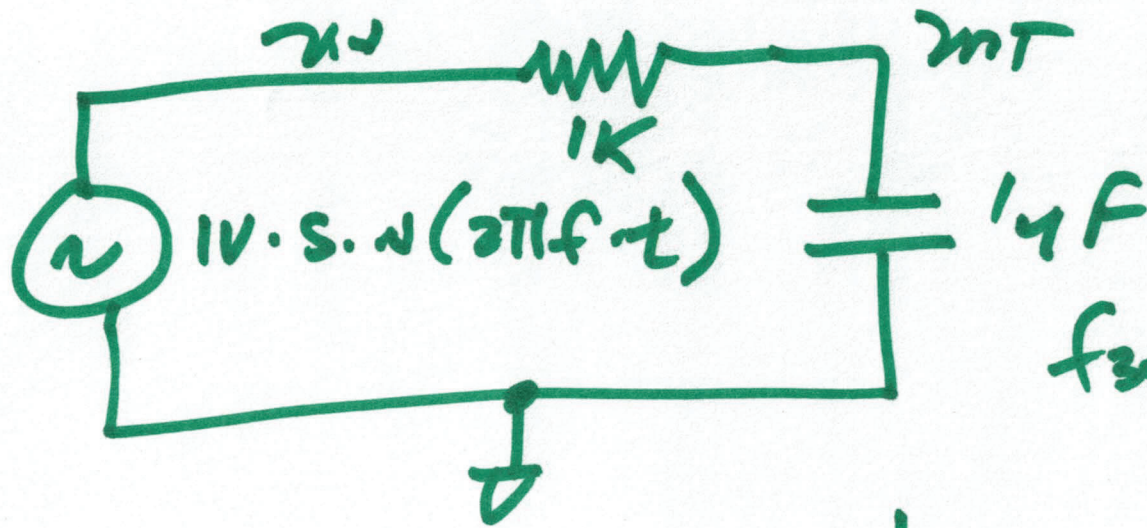
$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{f_{3dB}}$$



$$f_{3dB} = \frac{1}{2\pi \cdot 10^3 \cdot 10^{-6}} = 159 \text{ Hz}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{159}\right)^2}}$$

$$\angle \frac{v_{out}}{v_{in}} = -\tan^{-1} \frac{f}{159}$$

$$f = 159 \quad \frac{1}{\sqrt{1 + \left(\frac{159}{159}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$20 \log \left| \frac{v_{out}}{v_{in}} \right| = -3 \text{ dB}$$

10/05
 $\frac{\sqrt{2} v_{out}}{v_{in}}$
 $\frac{1}{\sqrt{2}}$

$$20 \log \frac{v_{nT}}{v_{n1}} = -36 \text{ dB}$$


$$10 \log \frac{v_{nT}}{v_{n1}} = -\frac{36}{20}$$


$$f = 10^4 = 10 \text{ kHz} \quad v_{nT} = 10^{-\frac{36}{20}}$$

$$T = 100 \mu\text{s}$$

$$v_{nT} = 15.8 \mu\text{V}$$
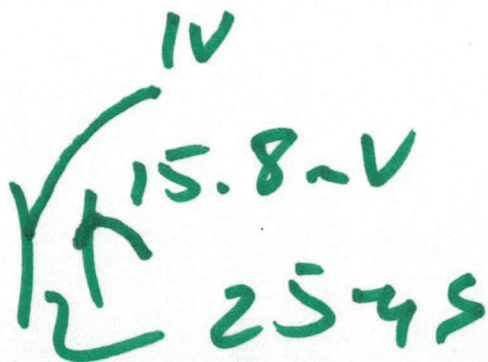
$$-90 = \frac{t_d}{100 \mu\text{s}} \cdot 360, \quad t_d = 25 \mu\text{s}$$



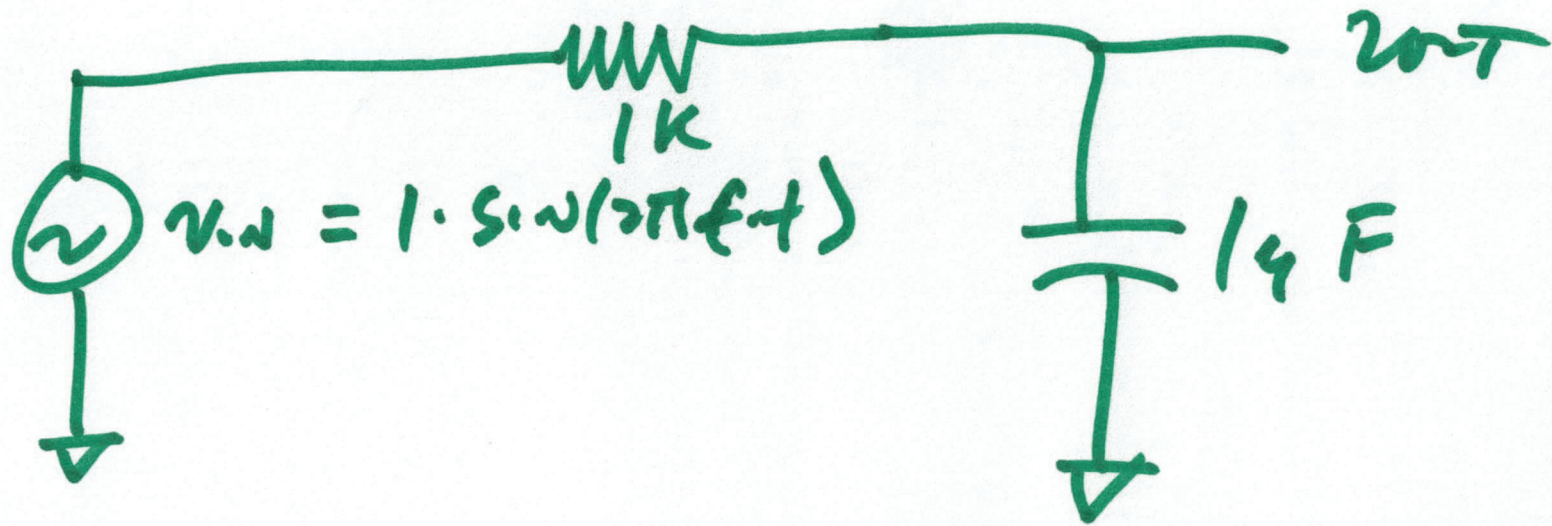

$$\frac{v_{out}}{v_s} = \frac{\frac{1}{j\omega 14}}{\frac{1}{j\omega 14} + 1k}$$


$$v_{out} = \frac{1}{1 + j\omega 10^{-3}}$$

$$= \frac{1}{1 + j \frac{f}{159}}$$

1)

$$V_{VT} = \frac{1}{1 + j \frac{f}{159}}$$

Bode Response

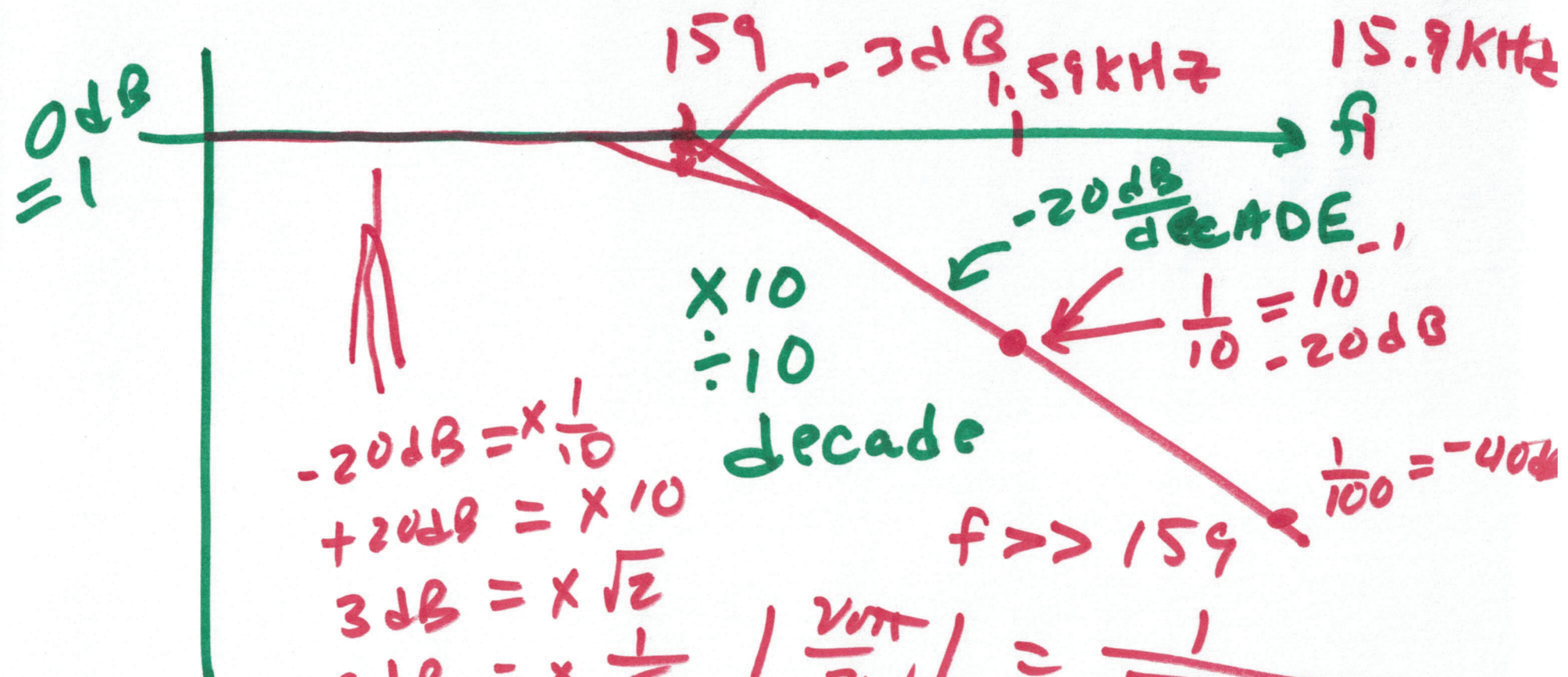


- 20 dB = x 1/10
- +20 dB = x 10
- 3 dB = x √2
- 3 dB = x 1/√2
- 6 dB = x 2
- 6 dB = x 1/2

14 dB = x 5

$$\left| \frac{V_{VT}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{cutoff}}\right)^2}}$$
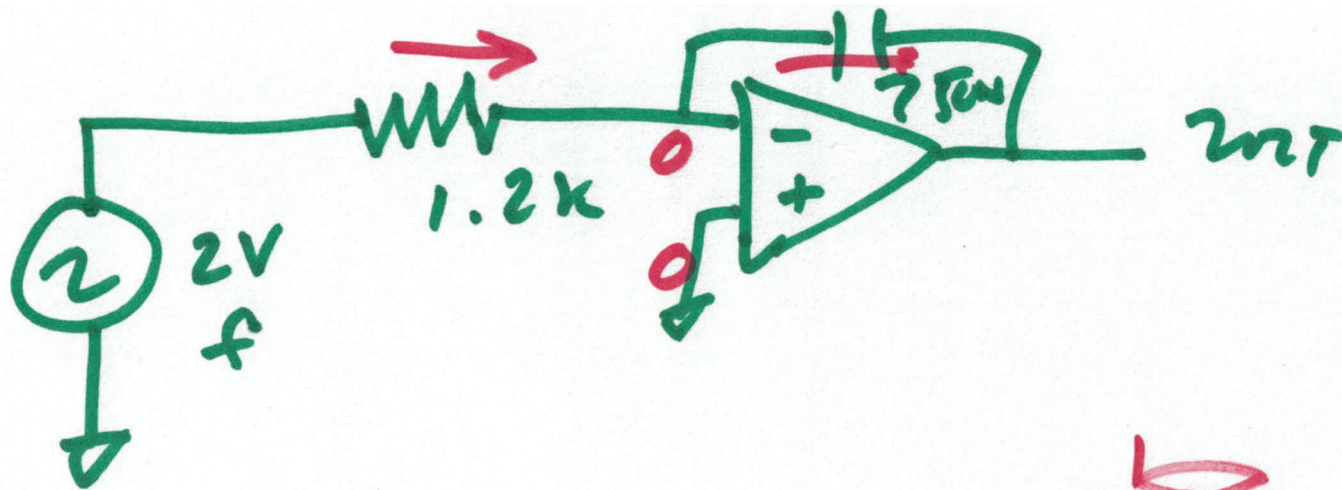
$$\frac{159}{f} = \frac{1}{\frac{f}{159}}$$



$$\frac{2-0}{1.2k} = \frac{0 - \cancel{\frac{1}{j\omega \cdot 750n}} v_{out}}{\frac{1}{j\omega \cdot 750n}}$$

$$v_{out} = - \frac{2}{j\omega \cdot 750n \cdot 1.2k} = \frac{a}{b \cdot f} = \frac{1}{f} \frac{a}{b}$$

$$v_{out} = 0 + j \frac{2}{2\pi f \cdot 750n \cdot 1.2k}$$

$$f_{bw} = \frac{2}{2\pi \cdot 750n \cdot 1.2k} = 353$$

$$V_{out} = j \cdot \frac{353}{f}$$

$$|V_{out}| = \frac{353}{f}$$

$$\angle V_{out} = \tan^{-1} \frac{353}{\cancel{f}} = 90^\circ$$