

# EE 221 Circuits II



March 20, 2023

$$CV = Q$$



$$14F \cdot 3V = 34Q$$

$$-1.6 \times 10^{-19} C$$

## Lecture 14

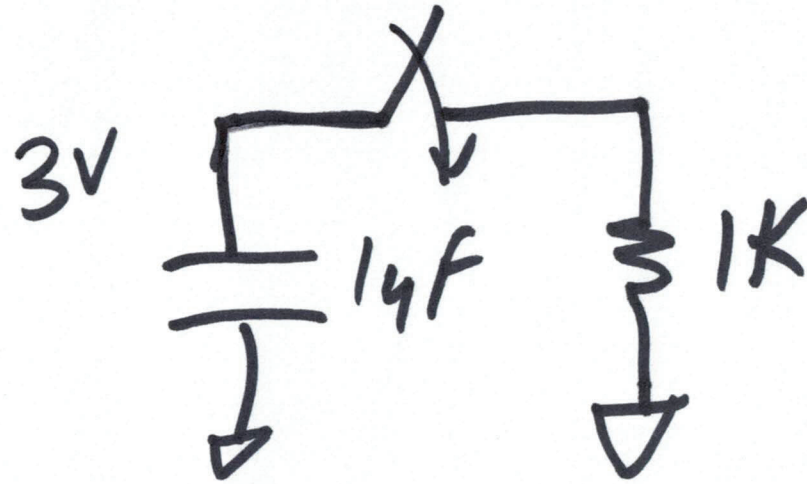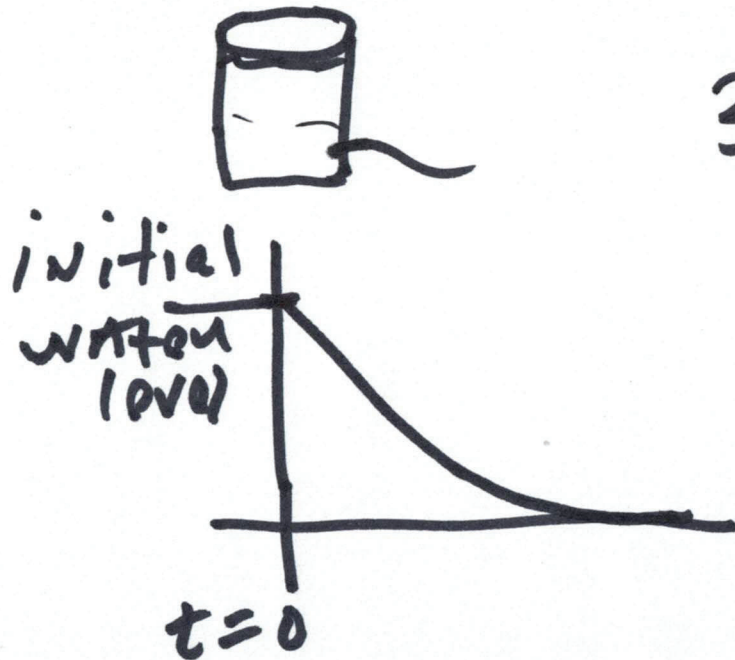
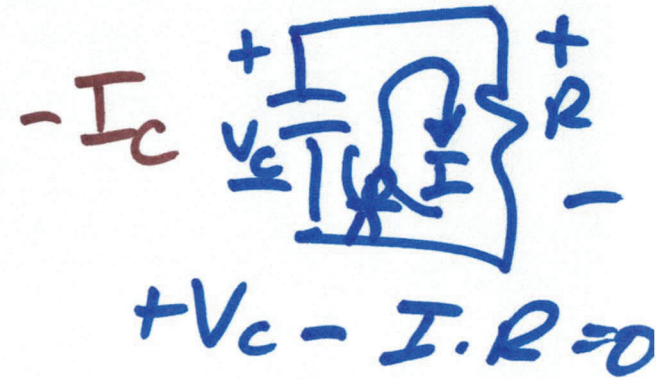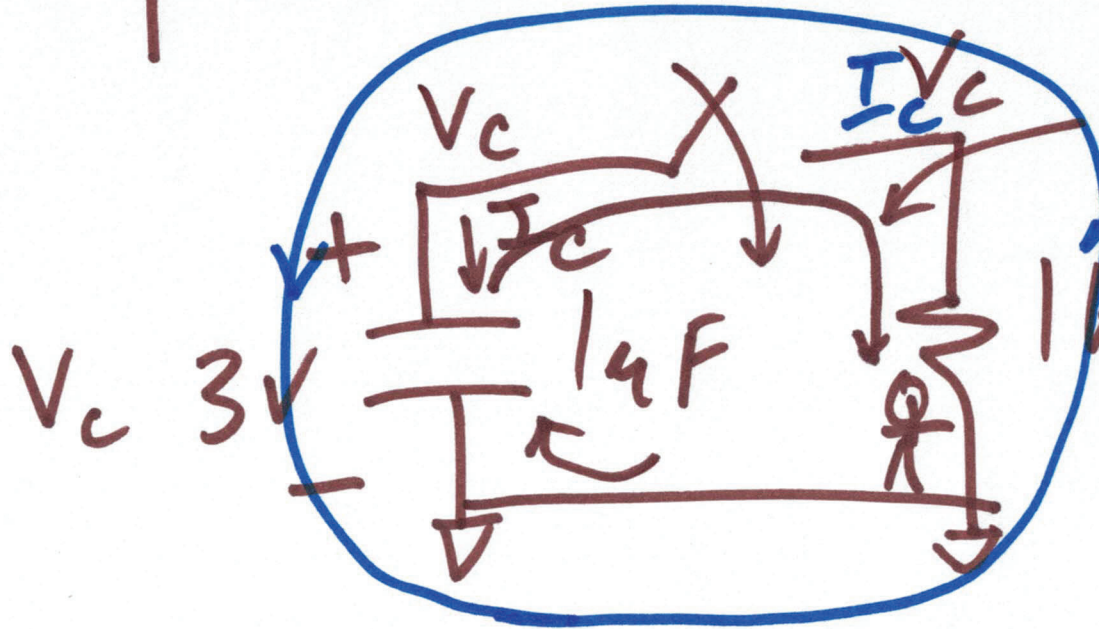
$$I_c \downarrow \frac{1}{C} \begin{matrix} + \\ - \end{matrix} V_c \quad I_c = C \frac{dV_c}{dt}, \quad V_c = \frac{1}{C} \int_0^t I_c dt$$



$$V_c - (-I_c) \cdot R = 0$$

$$V_c + I_c \cdot R = 0$$



$\int \frac{d \log e^{bi}}{\log e^{bi}}$

natural log

$$V_c + I_c \cdot R = 0$$

$$V_c = -I_c \cdot R$$

$$\int_0^t -\frac{dt}{RC} = \int_{V_{init}}^{V_c} \frac{dV_c}{V_c}$$

$$-\frac{1}{RC} t \Big|_0^t = \ln V_c \Big|_{V_{init}}^{V_c}$$

$$-\frac{t}{RC} = \ln V_c - \ln V_{init}$$

$$e^{-\frac{t}{RC}} = \ln \frac{V_c}{V_{i\text{init}}}$$

$$e^{-t/RC} = \frac{V_c}{V_{i\text{init}}}$$

$$V_c(t) = V_{i\text{init}} e^{-t/RC}$$

$$V_c(t) = 3 e^{-t/1\text{ms}}$$

$$R \cdot C = 1\text{k} \cdot 1\mu\text{F} = 1\text{ms}$$

$$V_c(t) = 3 e^{-(t-1\text{ms})/1\text{ms}}$$


$$t \geq 1\text{ms}$$



$$v_c(t) = v_f + (v_i - v_f) e^{-t/RC}$$

$$= v_f + (v_i - v_f) e^{-\frac{(t - t_{init})}{RC}}$$

$$t \geq t_{init}$$

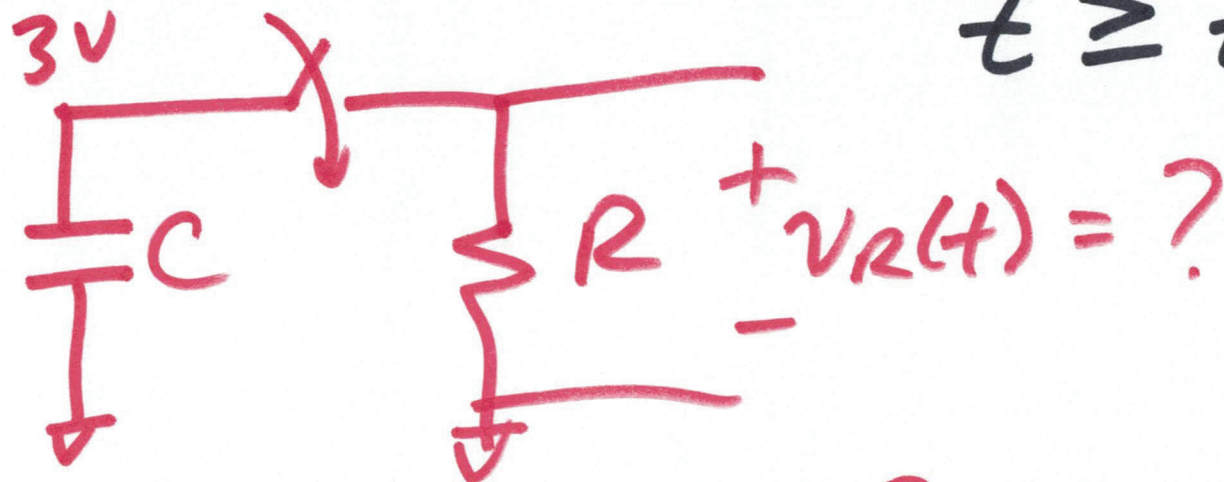

$$v_f = 0 \quad v_i = 3$$

$$v_R(t) = 3 e^{-t/RC}$$

$$v_c(t) = 3 e^{-(t-1\text{ms})/1\text{ms}}$$


1 time constant @ 1ms after  
the switch closes (2ms)

$$3 e^{-1} = 3 \cdot .37$$

↓ 1τ drops  
63%

↓  
1.89 37%



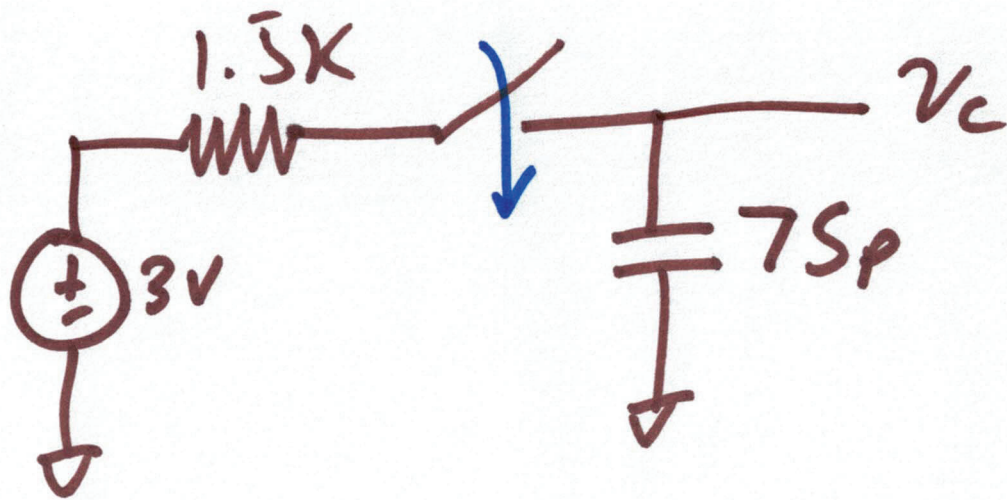

$$v_i = 0$$


$$v_f = 3V$$


$$-t / (1.5k \cdot 75p)$$

$$v_c(t) = 3 + (0 - 3)e^{-t / (1.5k \cdot 75p)}$$

$$= 3(1 - e^{-t / (1.5k \cdot 75p)})$$

$$\tau = 11.25 \mu s$$

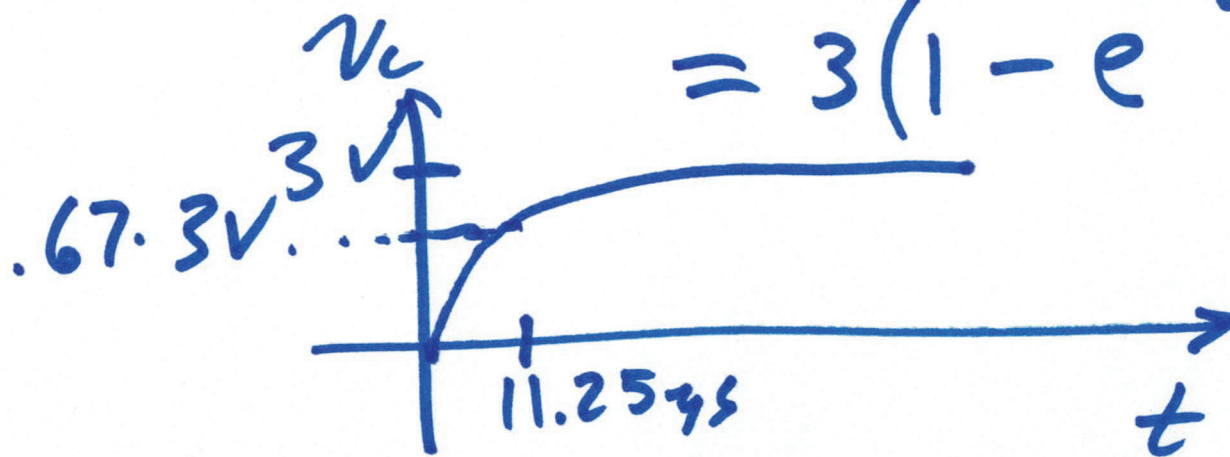

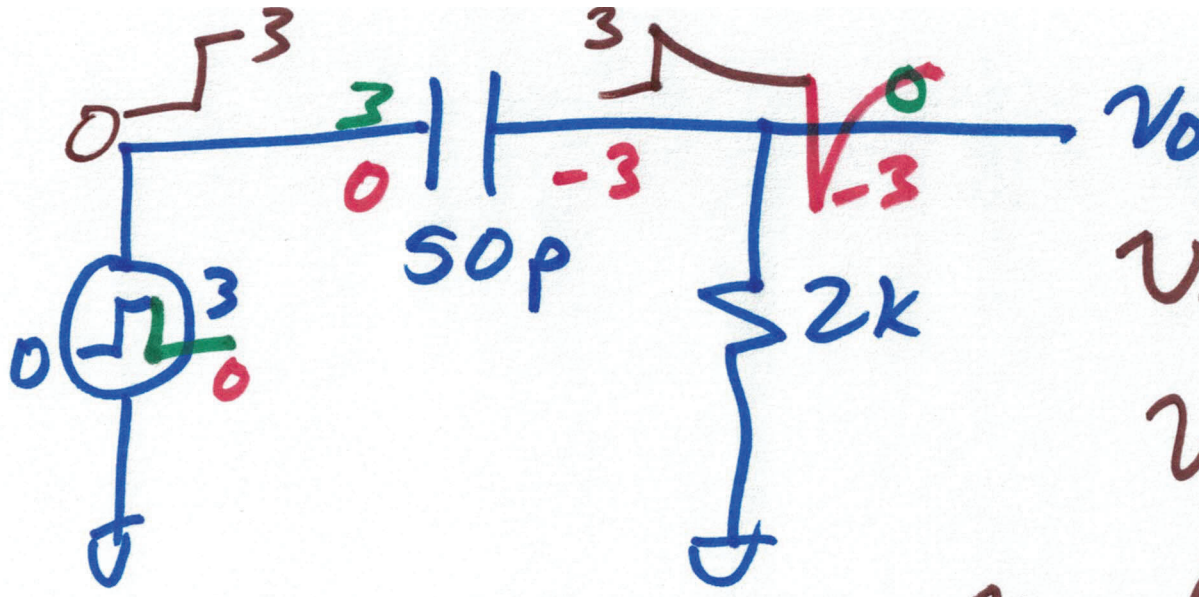

$$v_f = 0$$

$$v_i = 3$$

$$v_o = v_f + (v_i - v_f)e^{-t/\tau}$$

$$= 3e^{-t/100\text{ns}}$$

$$t > 0$$

$$v_i = -3$$

$$v_f = 0$$

$$v_o = -3(1 - e^{-t/100\text{ns}})$$