

EE 221 Circuits II

March 29, 2023


Lecture 17



$$\downarrow \left\{ \begin{array}{l} + \\ - \end{array} \right. v = IR$$

$$\downarrow \left\{ \begin{array}{l} - \\ + \end{array} \right. v = -IR$$
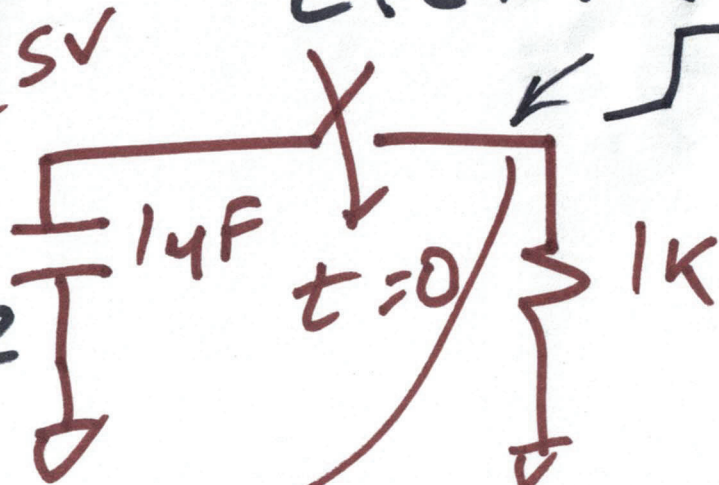
$$\uparrow \left\{ \begin{array}{l} + \\ - \end{array} \right. v = -IR$$




$$v_i = 5$$

$$v_f = 0$$

$$-t/1\mu s$$

$$v_o = 5e^{-t/1\mu s} \quad t > 0$$

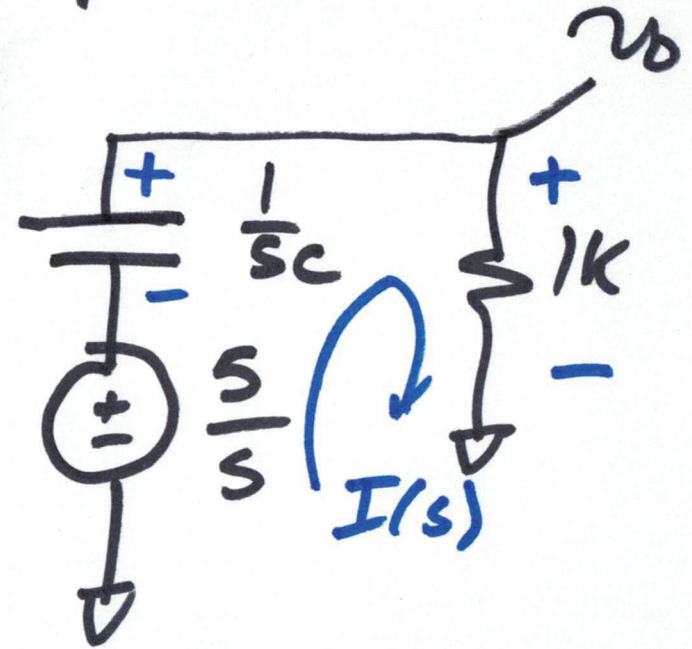

$$\frac{5}{s} + I(s) \cdot \frac{1}{sC}$$

$$- 1K \cdot I(s) = 0$$

$$\frac{5}{s} \rightarrow I(s) \cdot \frac{1}{sC} - 1K I(s) = 0$$

$$\frac{5}{s} + I(s) \left(-\frac{1}{sC} - 1K \right) = 0$$

$$I(s) = \frac{+\frac{5}{s}}{\frac{1}{sC} + 1K}$$

$$I(s) = \frac{5}{\frac{1}{14} + s \cdot 1K} \cdot \frac{1}{1K}$$
$$= \frac{5 \text{ mA}}{s + \frac{1}{1\text{m}}}$$

$$\underline{I}(s) = \frac{5 \text{ mA}}{s + \frac{1}{1 \text{ ms}}}$$

$$i(t) = 5 \text{ mA } e^{-t/1 \text{ ms}} u(t)$$

$$v_o = 1 \text{ k} \cdot i(t)$$

$$v_o(t) = 5 e^{-t/1 \text{ ms}} u(t)$$

3)

$$k \int e^x \cdot dx = k e^x$$

$$\int e^{-at} dt$$

$$\text{let } dx = d(-at)$$


$$dx = -a \cdot dt$$

$$dt = -\frac{1}{a} dx$$

$$\begin{aligned} -\frac{1}{a} \int e^x dx &= -\frac{1}{a} e^x \rightarrow x = -at \\ &= -\frac{1}{a} e^{-at} \end{aligned}$$

4)

Unit impulse function

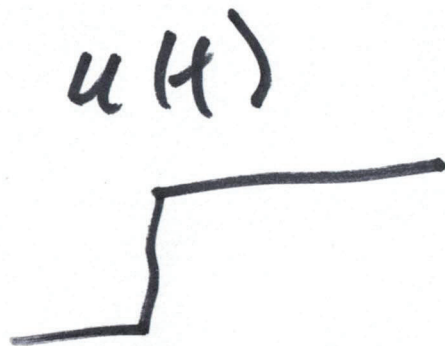

$$\frac{d u(t)}{d t} = \delta(t)$$

$$\int_{-\infty}^{\infty} \delta(t) \cdot dt = 1$$


Sampling property

$$\int_{-\infty}^{\infty} x(t) \cdot \delta(t-T) \cdot dt = x(T)$$

$$\mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} f(t) \cdot e^{-st} \cdot dt$$

$$\mathcal{L}\{u(t)\} = \int_{0^-}^{\infty} e^{-st} \cdot dt = \left. -\frac{1}{s} e^{-st} \right|_0^{\infty}$$
$$\frac{1}{s} = -\frac{1}{s} (\cancel{e^{-\infty}} - \cancel{e^{-0}})$$

$$u(t - T_d)$$


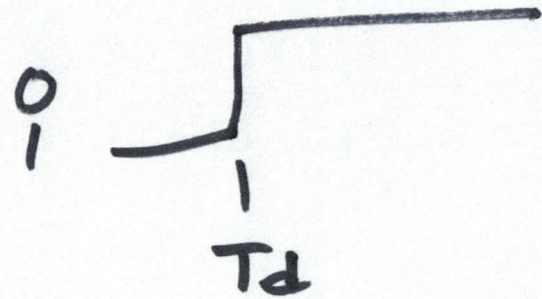


$$\mathcal{L}\{u(t - T_d)\} = \int_0^{\infty} u(t - T_d) e^{-st} \cdot dt$$

$$= \int_{T_d}^{\infty} e^{-st} \cdot dt = \frac{-1}{s} e^{-st} \Big|_{T_d}^{\infty}$$

$$\mathcal{L}\{u(t - T_d)\} = \frac{e^{-sT_d}}{s} = -\frac{1}{s} (\cancel{e^{-s \cdot 0}} - e^{-sT_d})$$

7)

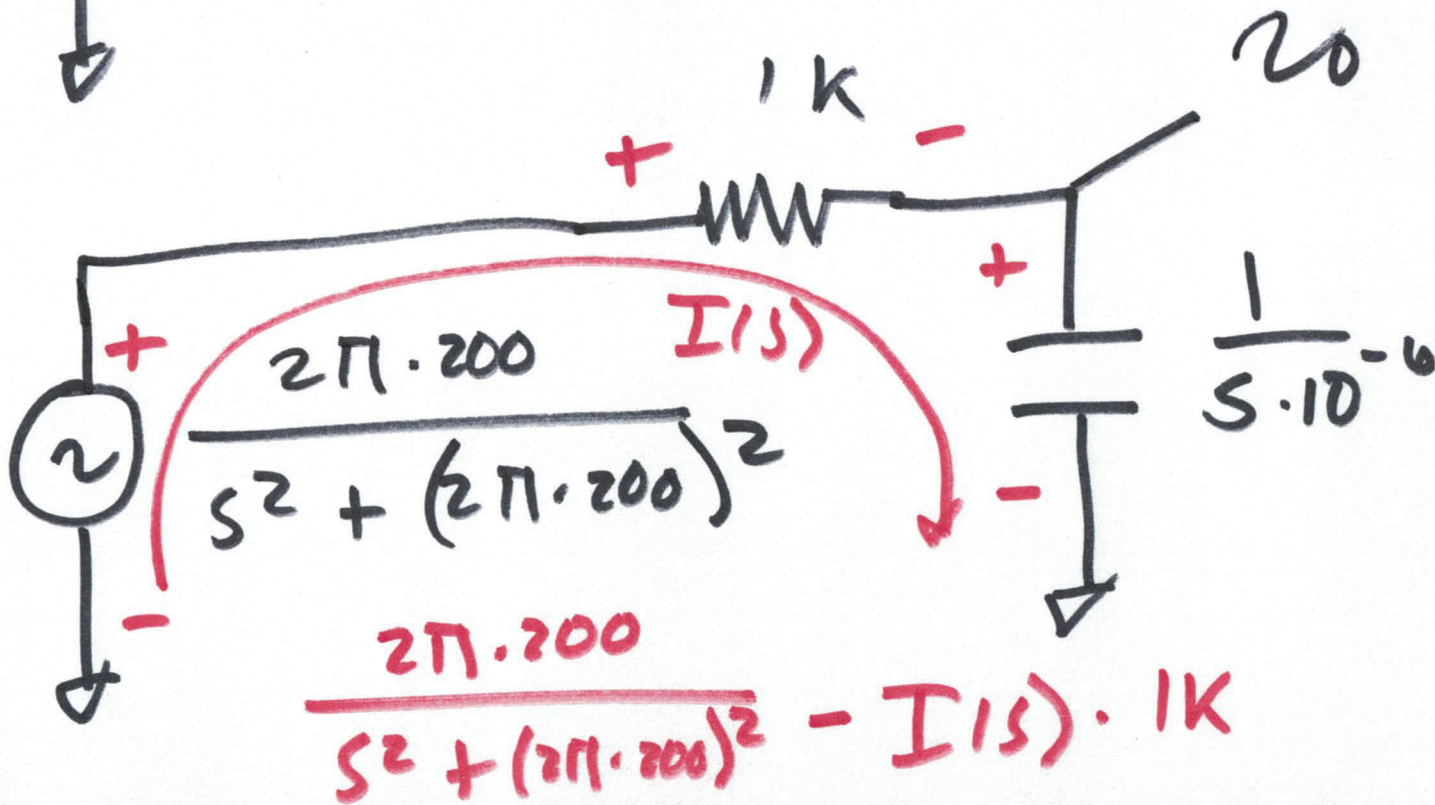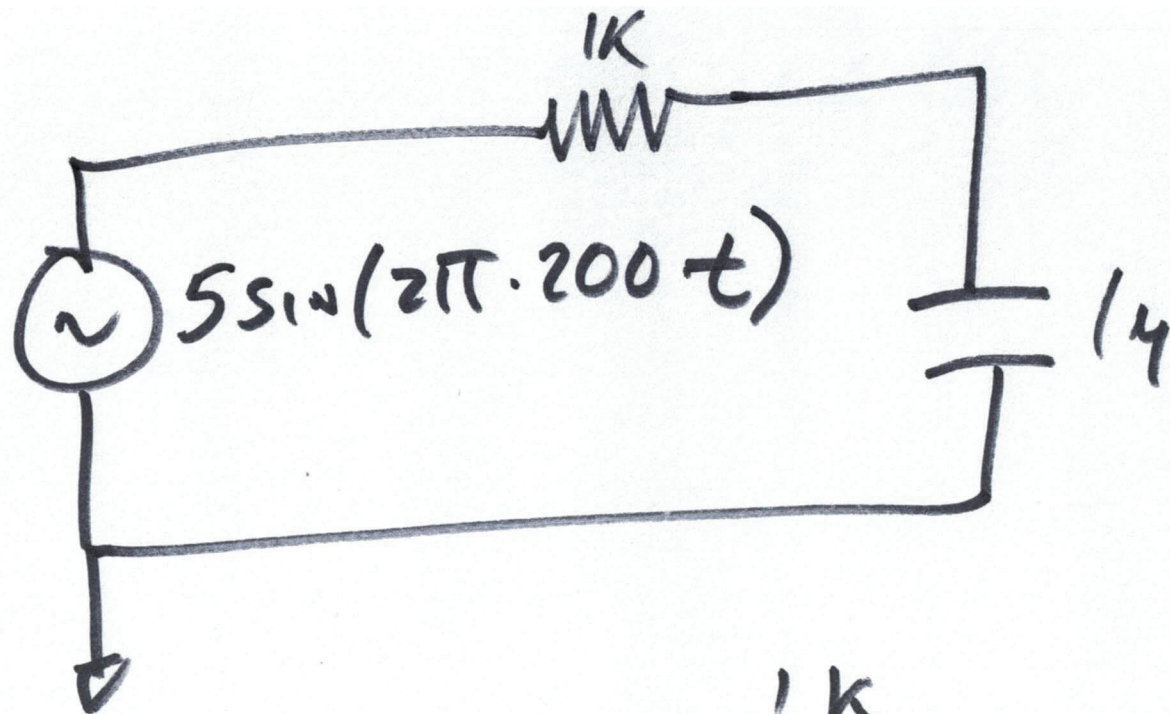

b)

$$V_o = \frac{2\pi \cdot 200}{s^2 + (2\pi \cdot 200)^2} \cdot \frac{\frac{1}{5 \cdot 10^{-6}}}{\frac{1}{5 \cdot 10^{-6}} + 1k}$$

$$= \frac{2\pi \cdot 200}{s^2 + (2\pi \cdot 200)^2} \cdot \frac{1}{10^{-3}s + 1}$$

$$= \frac{2\pi \cdot 200}{10^{-3}} \cdot \frac{1}{s^2 + (2\pi \cdot 200)^2} \cdot \frac{1}{s + 10^3}$$

$$s = \frac{\pm \sqrt{-4(2\pi \cdot 200)^2}}{2} = \pm \frac{j 4\pi \cdot 200}{2}$$

$$= \pm j 2\pi \cdot 200$$

$$V_0(s) = \frac{2\pi \cdot 200}{10^{-3}} \cdot \frac{1}{(s + j2\pi \cdot 200)(s - j2\pi \cdot 200)(s + 10^3)}$$

Partial fraction expansion

$$= \frac{A}{s + j2\pi \cdot 200} + \frac{B}{s - j2\pi \cdot 200} + \frac{C}{s + 10^3}$$

$$\frac{\cancel{A \cdot (s + 10^3)}}{\cancel{s + j2\pi \cdot 200}} + \frac{\cancel{B(s + 10^3)}}{\cancel{s - j2\pi \cdot 200}} + C$$

$$C = \frac{2\pi \cdot 200}{10^{-3}} \cdot \frac{1}{s^2 + (2\pi \cdot 200)^2}$$

$$C = \frac{2\pi \cdot 200}{10^{-3} \cdot (10^6 + (2\pi \cdot 200)^2)}$$

$$A \Big|_{s = -j2\pi 200} = \frac{2\pi \cdot 200}{10^{-3}} \cdot \frac{1}{(s - j2\pi \cdot 200)(s + 10^3)}$$

$$A = \frac{2\pi \cdot 200}{10^{-3}} \cdot \frac{1}{(-j4\pi \cdot 200)(-j2\pi 200 + 10^3)}$$

$$B = \frac{2\pi \cdot 200}{10^{-3}} \cdot \frac{1}{(j4\pi 200) \cdot (j2\pi 200 + 10^3)}$$

11)

$$\frac{1}{s^2} \rightarrow \frac{A \cdot s^2}{s} + \frac{B \cdot s^2}{s^2}$$

$$\frac{A \cdot s}{s} + \frac{B \cdot s}{s^2}$$