


EE 221 CIRCUITS II

Lecture 1

JANUARY 18, 2023

$$I \downarrow \begin{array}{c} | \\ \text{---} \\ | \\ R \\ \text{---} \\ | \end{array} \begin{array}{c} + \\ V \\ - \end{array} = IR$$

$$I \uparrow \begin{array}{c} | \\ \text{---} \\ | \\ R \\ \text{---} \\ | \end{array} \begin{array}{c} + \\ V \\ - \end{array} = (-I) \cdot R$$

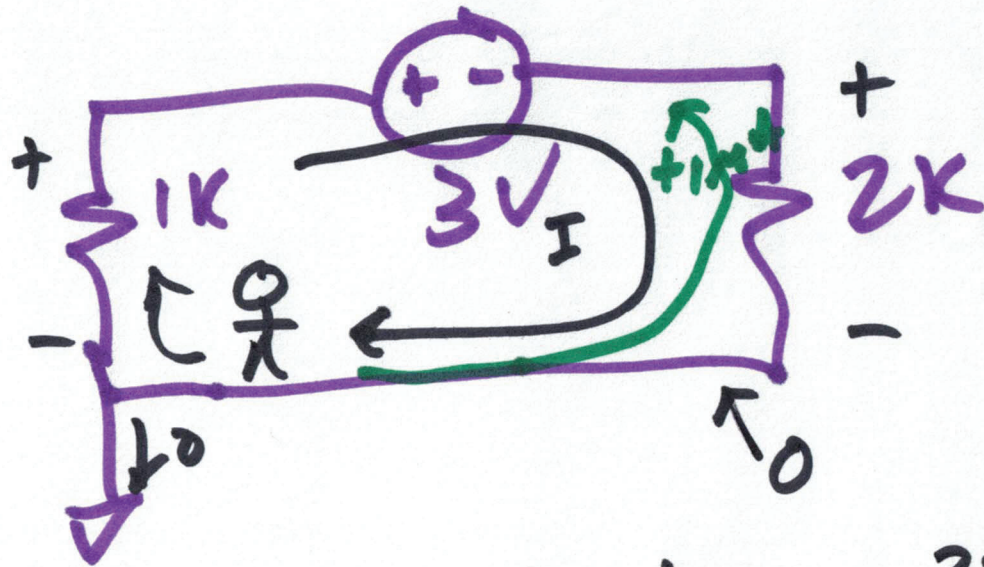


$$I = -1 \mu A$$


$$1V + (-1 \mu A) \cdot 1k + (-I) \cdot 1k - 3V - I \cdot 2k = 0$$

$$V = (-1 \mu A) \cdot 2k = -2V$$

$$-3kI = 3$$

$$I = -1 \mu A = \frac{-3V}{3k}$$

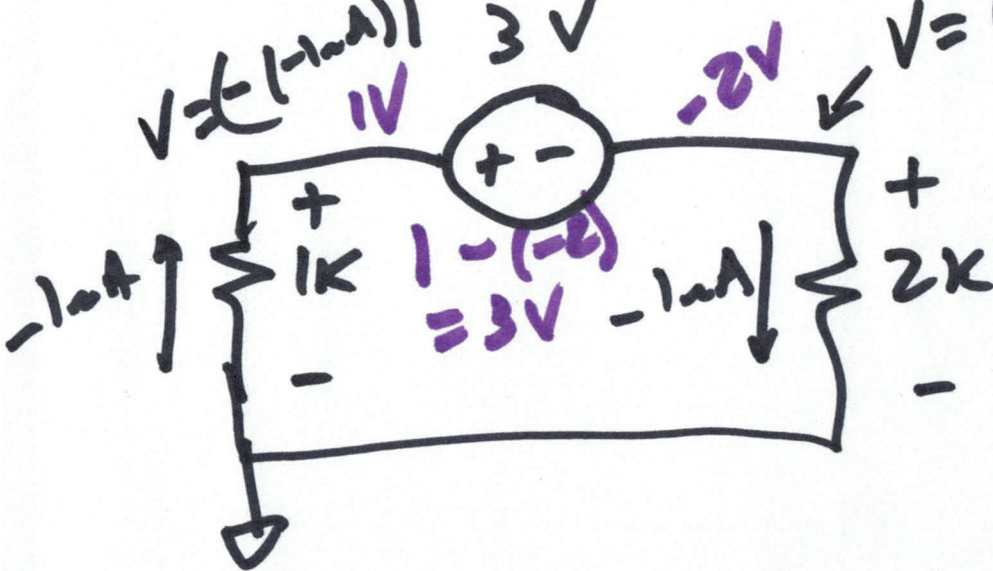

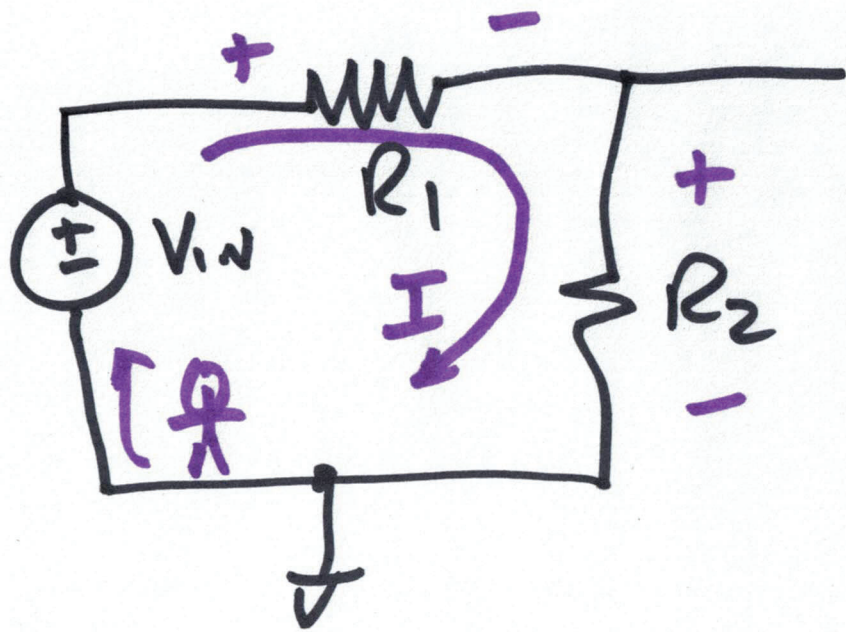

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$


$$+V_{in} - I R_1 - I \cdot R_2 = 0$$

$$I = \frac{V_{in}}{R_1 + R_2}$$


$$V_{out} = 3 \cdot \frac{2k}{2k + 1k}$$

$$= 2V$$

$$V_{out} = I \cdot R_2$$

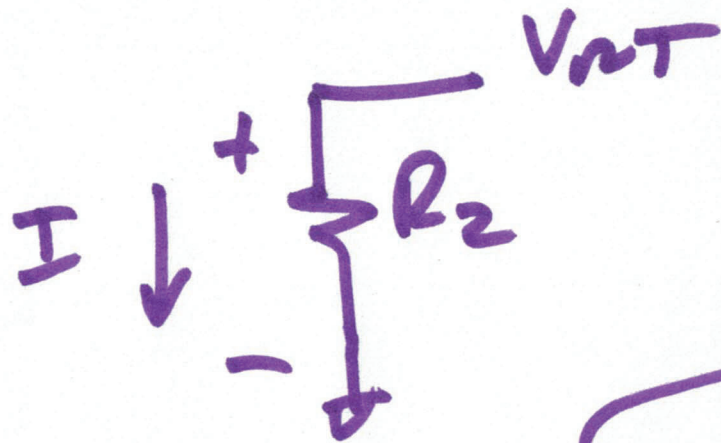
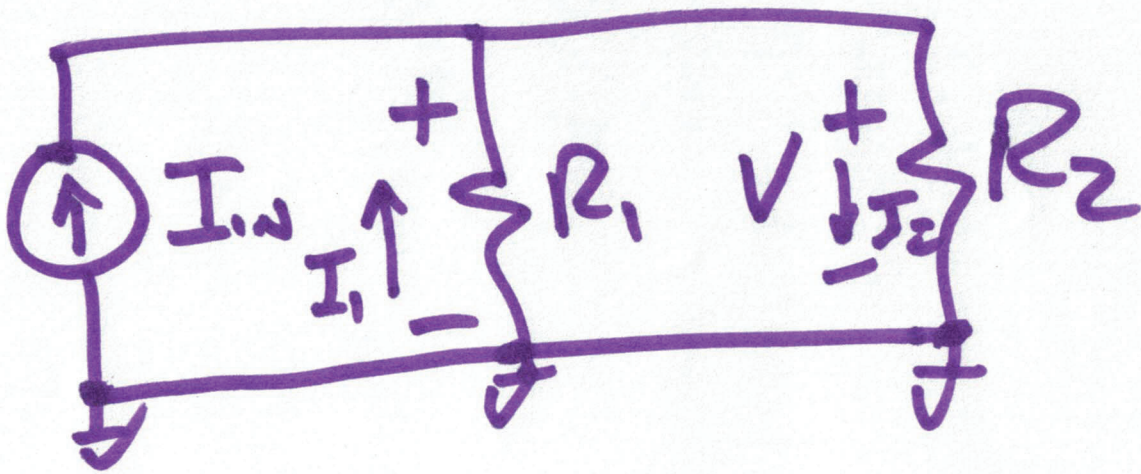
$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$



$$V = I_2 R_2$$

$$I_{in} + I_1 = I_2$$

$$I_{in} - \frac{V}{R_1} = \frac{V}{R_2}$$


$$I_{in} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$I_{in} = I_2 \cdot R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$I_2 = I_{IN} \cdot \frac{1}{R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}$$

$$= I_{IN} \cdot \frac{1}{\frac{R_2}{R_1} + 1} \cdot \frac{R_1}{R_1}$$
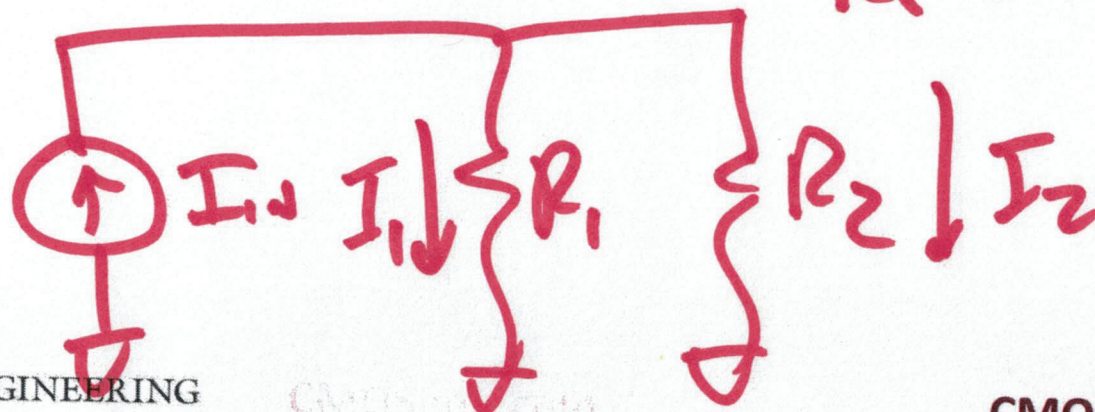
$$I_2 = I_{IN} \cdot \frac{R_1}{R_1 + R_2}$$



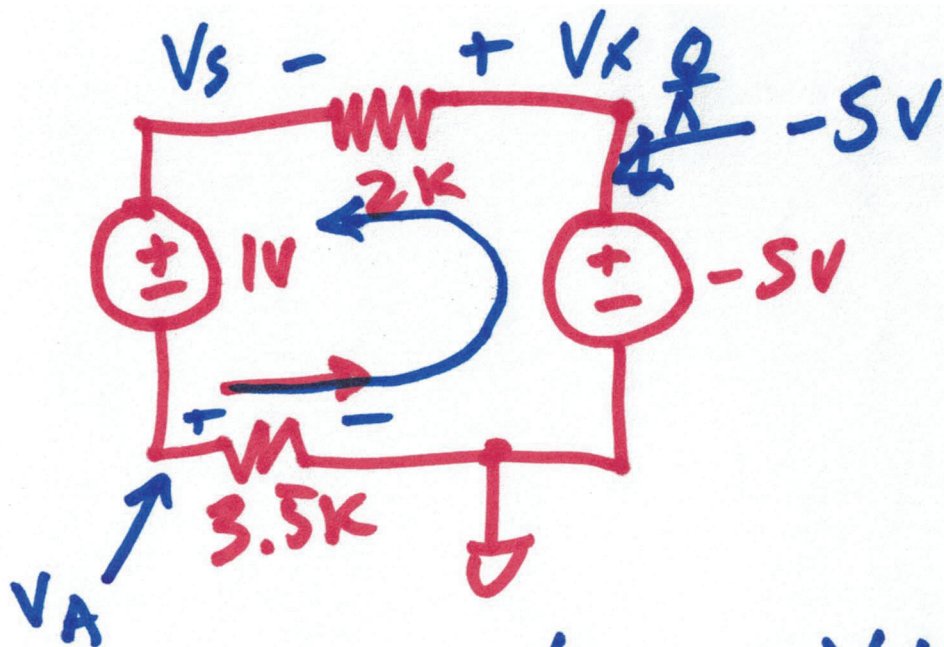

$$-(-5) + 3.5kI + 1 + 2k \cdot I = 0$$

$$6 + 5.5kI = 0$$


$$3.5k \cdot -\frac{6}{5.5k} = V_A = -\frac{7.6}{11} \quad I = -\frac{6}{5.5k}$$

$$= -\frac{42}{11} = -1\frac{1}{11} \text{ mA}$$

$$V_S = -3\frac{9}{11} + 1 \quad -3\frac{9}{11} \text{ V}$$


$$= -2\frac{9}{11} \text{ V}$$

$$= -2.818 \text{ V}$$

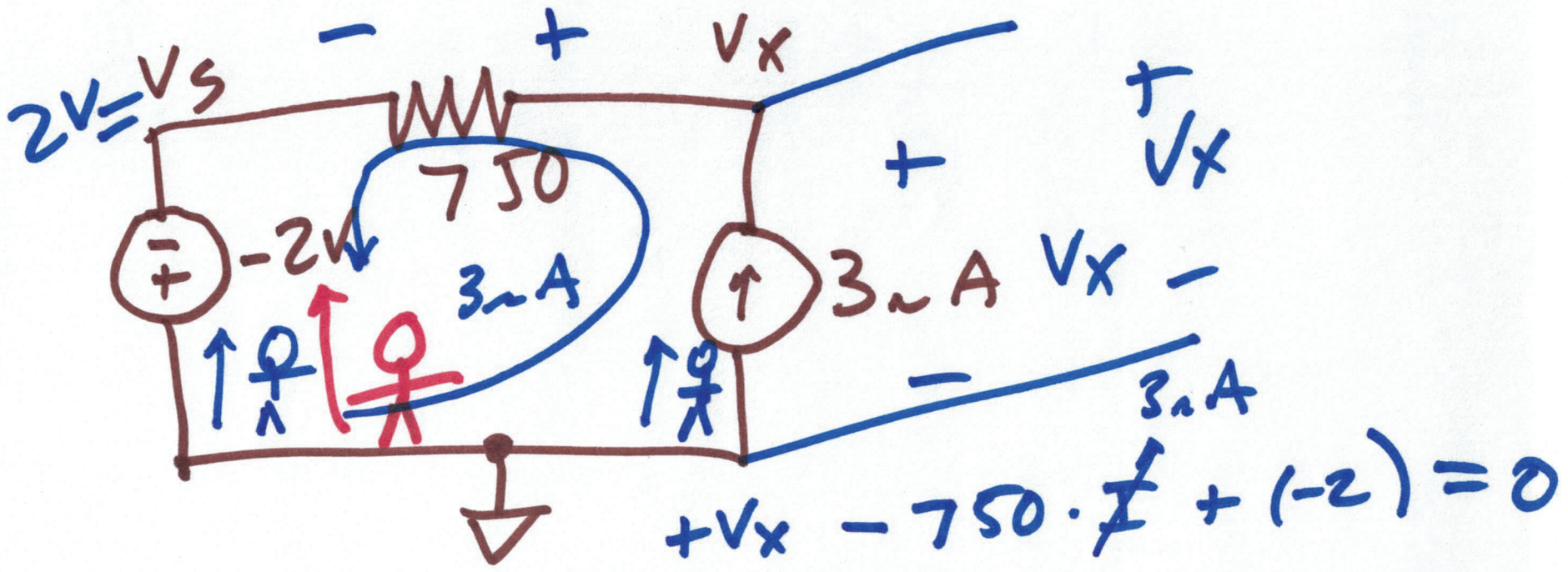

$$-(-2) = \boxed{V_s = 2V}$$

$$-(-2) + 750 \cdot 3mA = V_x$$

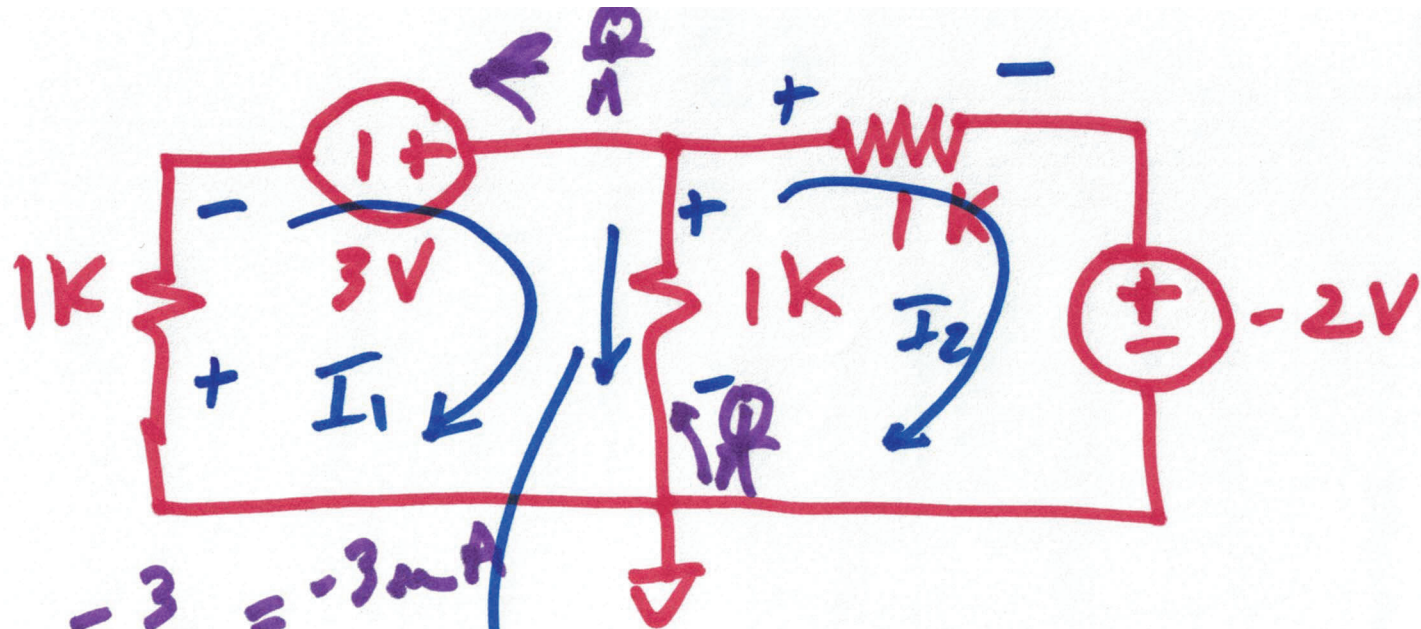

$$-\frac{3}{1k} = -3\mu A$$

$$I_1 - I_2$$

$$-3 + 1kI_1 + 1k(I_1 - I_2) = 0$$

$$+1k(I_1 - I_2) - I_2 \cdot 1k - (-2) = 0$$

$$-3\mu A + 2I_1 - I_2 = 0$$

$$I_2 = 2I_1 - 3\mu A$$

$$I_1 - 2\overset{\downarrow}{I_2} + 2A = 0$$

$$I_1 - 2(2I_1 - 3A) + 2A = 0$$

$$I_1 - 4I_1 + 6A + 2A = 0$$

$$-3I_1 = -8A$$

$$I_2 \quad \boxed{2\frac{1}{3} \mu A}$$

$$\boxed{I_1 = \frac{8}{3} \mu A = 2\frac{2}{3} \mu A}$$

$$I_2 = 2\left(\frac{8}{3} \mu A\right) - 3 \mu A$$

$$\frac{7 \mu A}{3} = \frac{16}{3} - \frac{9}{3}$$

$$= \frac{16}{3} \mu A - 3 \mu A$$