

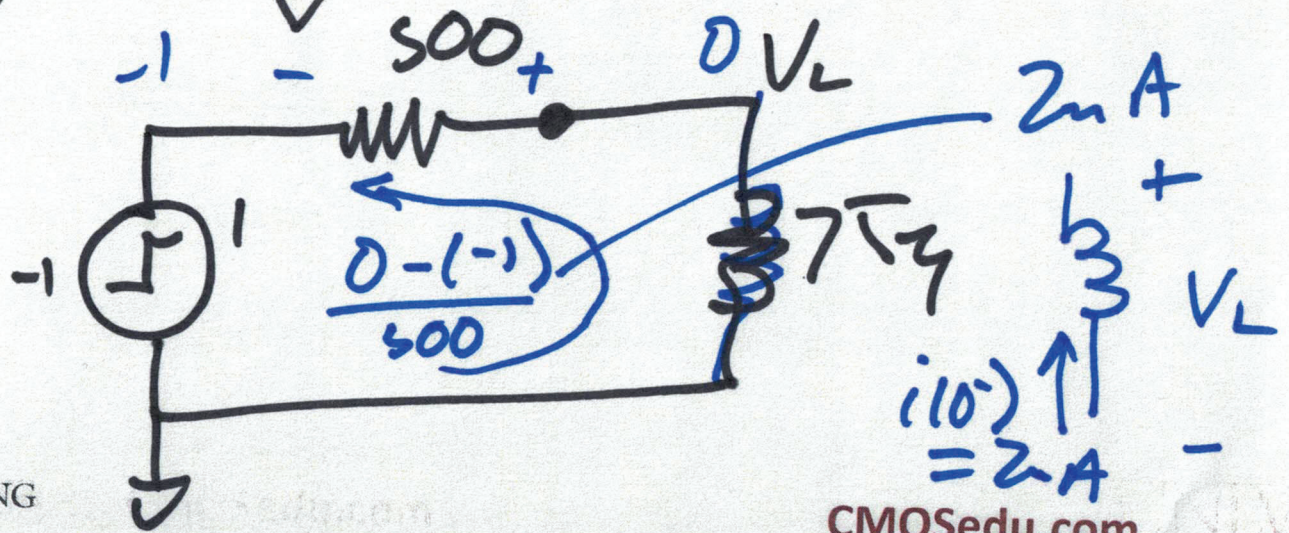
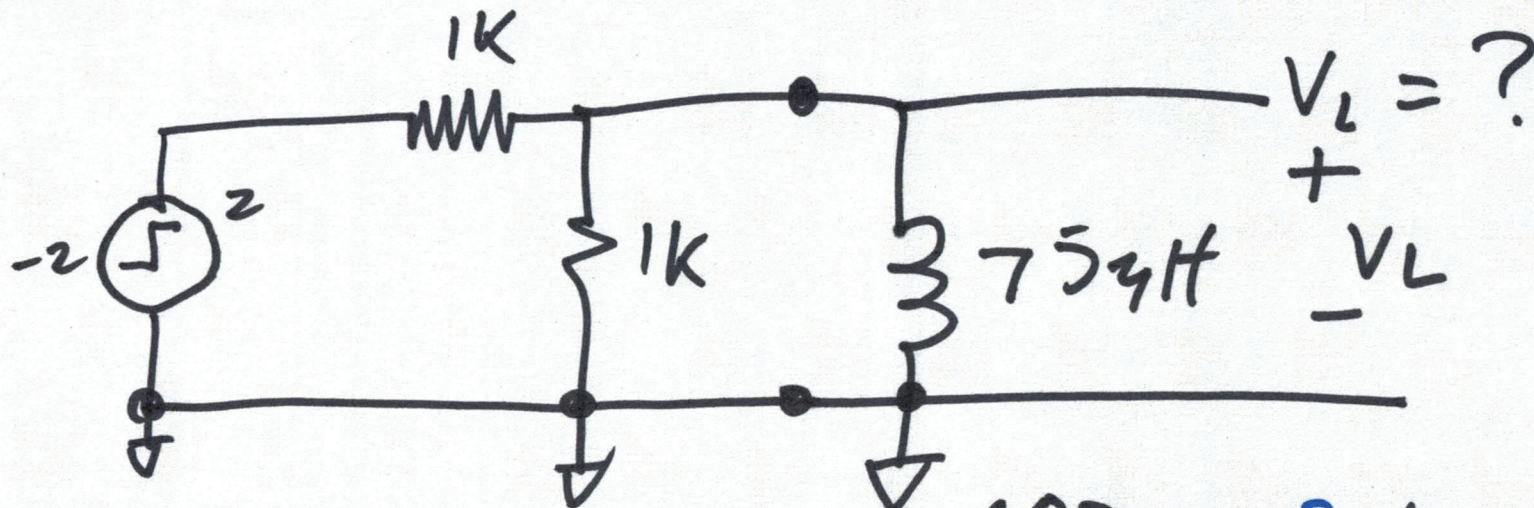



EE 220 CIRCUITS II

Lecture 22

April 17, 2023

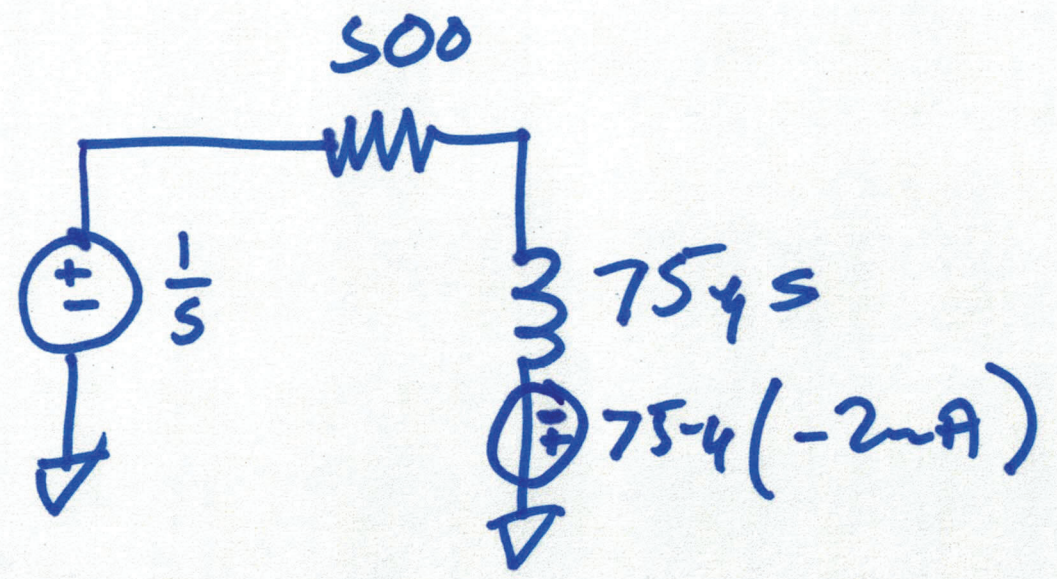

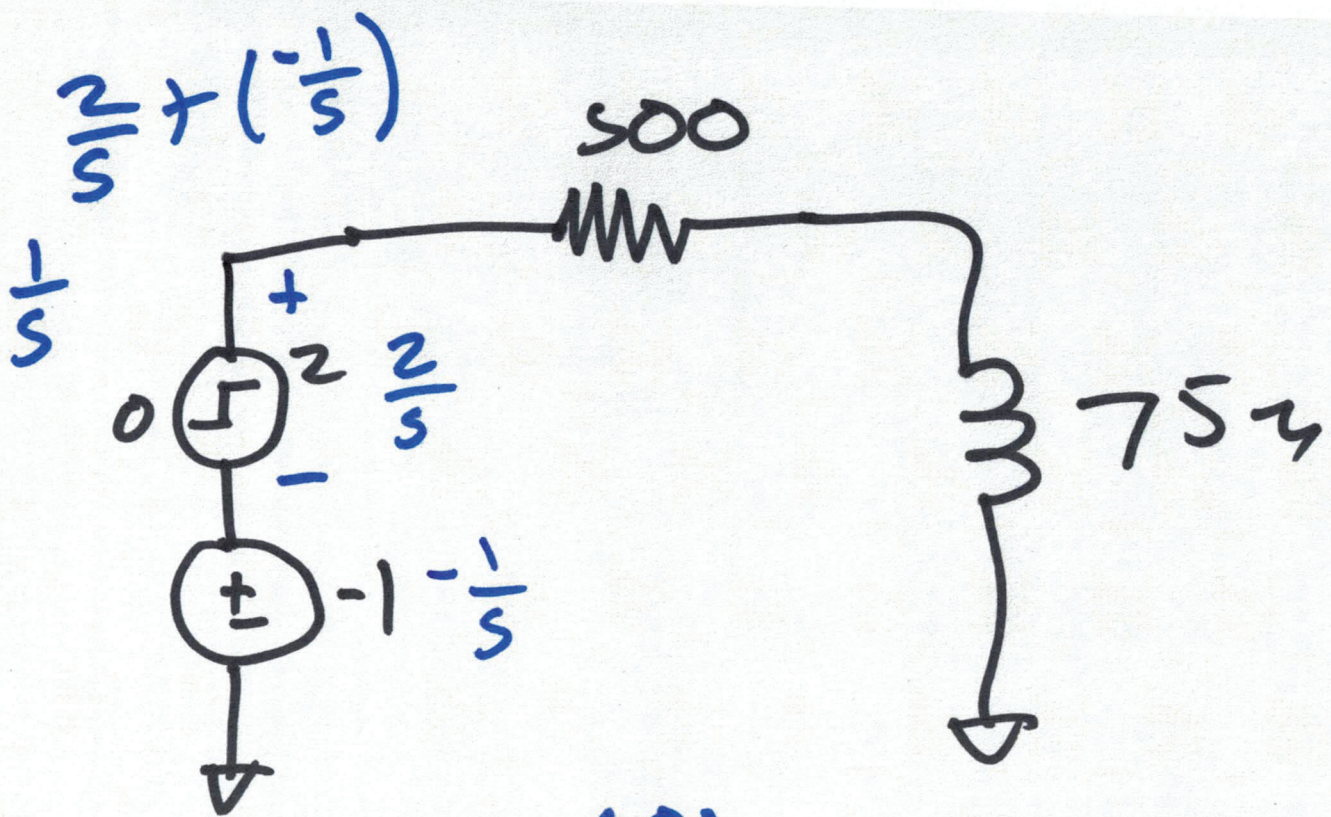

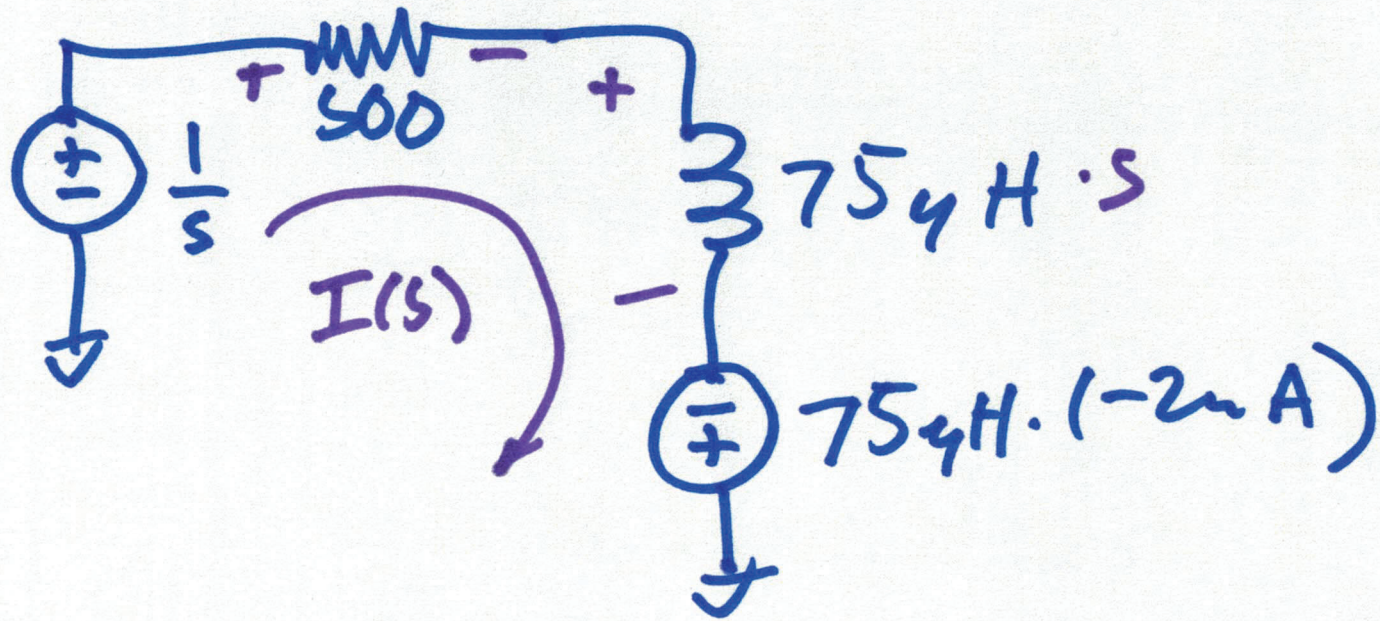

$$\frac{1}{s} - I(s) \cdot 500 - I(s) \cdot s \cdot 75\text{ m} + 75\text{ m} \cdot (-2\text{ mA}) = 0$$

$$I(s)(500 + s \cdot 75\text{ m}) = \frac{1}{s} - 75\text{ m} \cdot 2\text{ mA}$$

$$I(s) = \frac{\frac{1}{s} - 75\text{ m} \cdot 2\text{ mA}}{s \cdot 75\text{ m} + 500}$$

$$\left(\frac{\frac{1}{754} - 2m \cdot s}{s \left(s + \frac{500}{754} \right)} \right) = \frac{A \cdot \left(s + \frac{500}{754} \right)}{s} + \frac{B \cdot \left(s + \frac{500}{754} \right)}{s + \frac{500}{754}}$$

$$\frac{\frac{1}{754} - 2m \cdot s}{s} = \frac{A \cdot \left(s + \frac{500}{754} \right)}{s} + B$$


$s = -\frac{500}{754}$


$$\frac{\frac{1}{754} - 2 \times 10^{-3} \cdot \left(-\frac{500}{754} \right)}{-\frac{500}{754}} = B = \frac{1 + 1}{-500} = -\frac{4}{1000}$$

$$B = -4m A$$

$$I(s) = \frac{2\text{mA}}{s} + \frac{-4\text{mA}}{s + \frac{1}{\frac{75\Omega}{500}}}$$
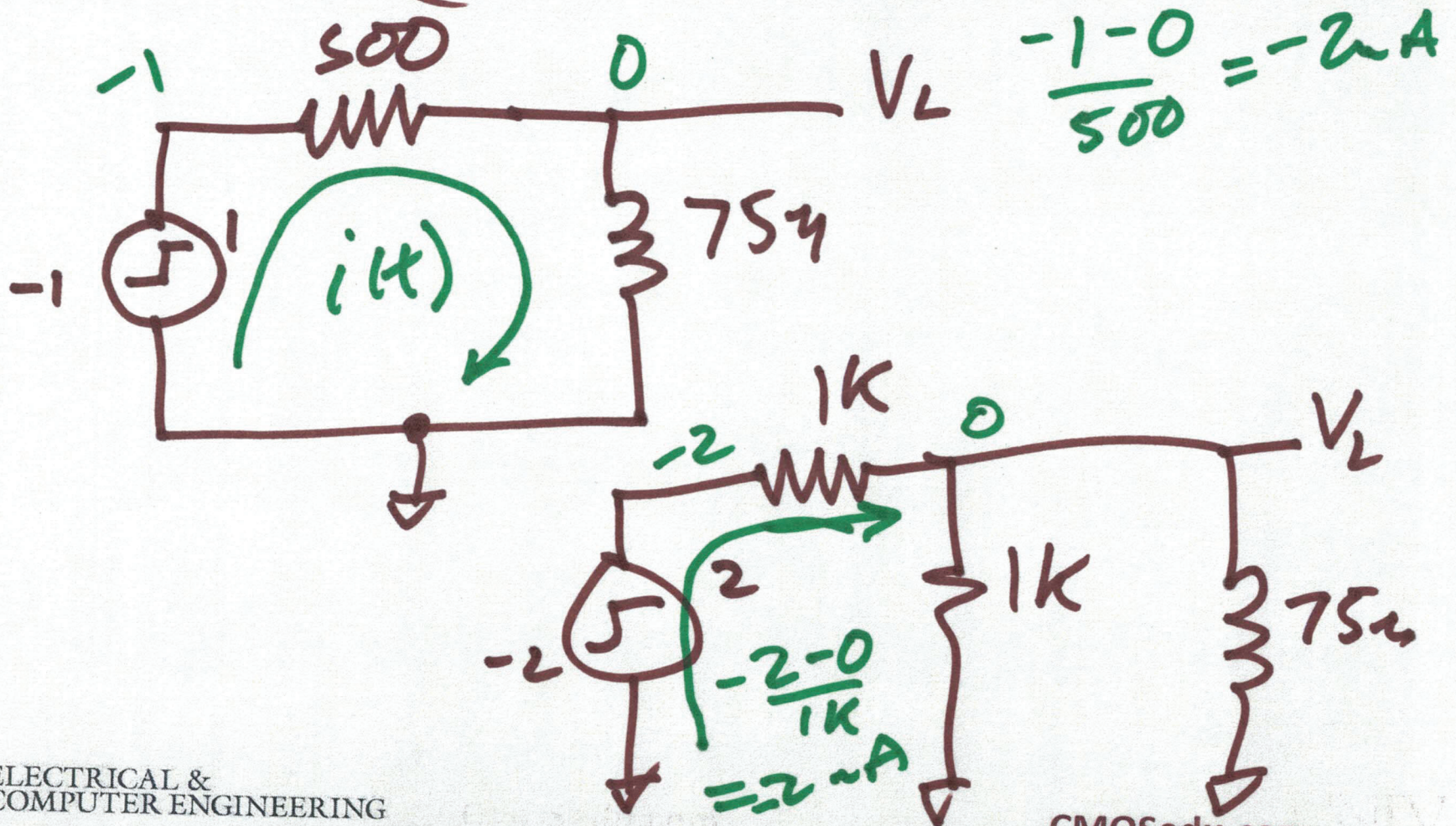
$$i(t) = (2\text{mA} - 4\text{mA}e^{-\frac{t}{75\Omega/500}})u(t)$$



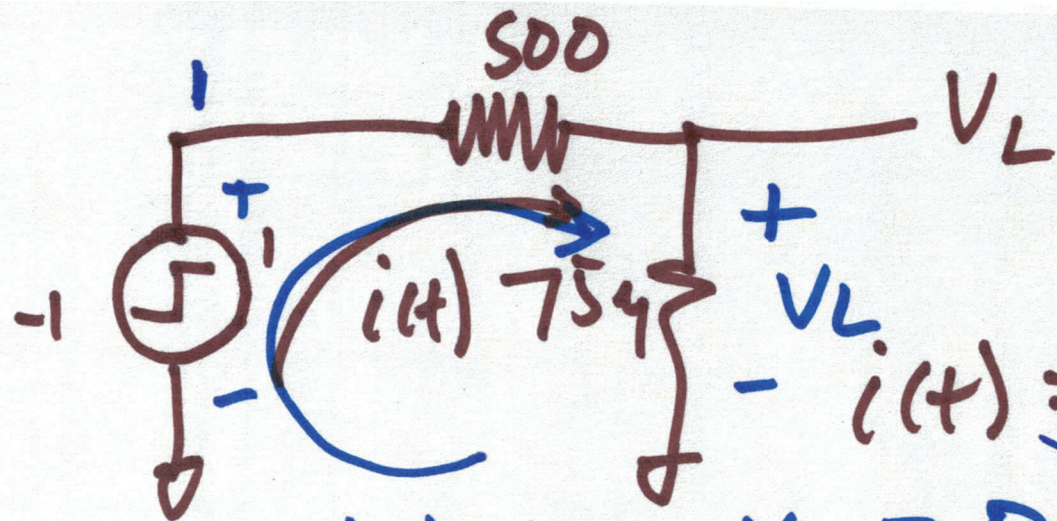

$$1V - i(t) \cdot 500 - v_L = 0$$

$$v_L = 1 - 500 \cdot i(t)$$

$$i(t) = (2A - 4e^{-t/\tau}) \mu A$$



$$\tau = \frac{L}{R} = \frac{75 \mu H}{500} = 150 \text{ ns}$$

$$v_L(t) = 1 - \frac{1}{2} \mu A \left(+2 \mu A - 4e^{-t/\tau} \right)$$

$$= 1 - 1 + 2e^{-t/\tau}$$

$$v_L(t) = 2e^{-t/\tau} \cdot 4 \mu A$$

7)

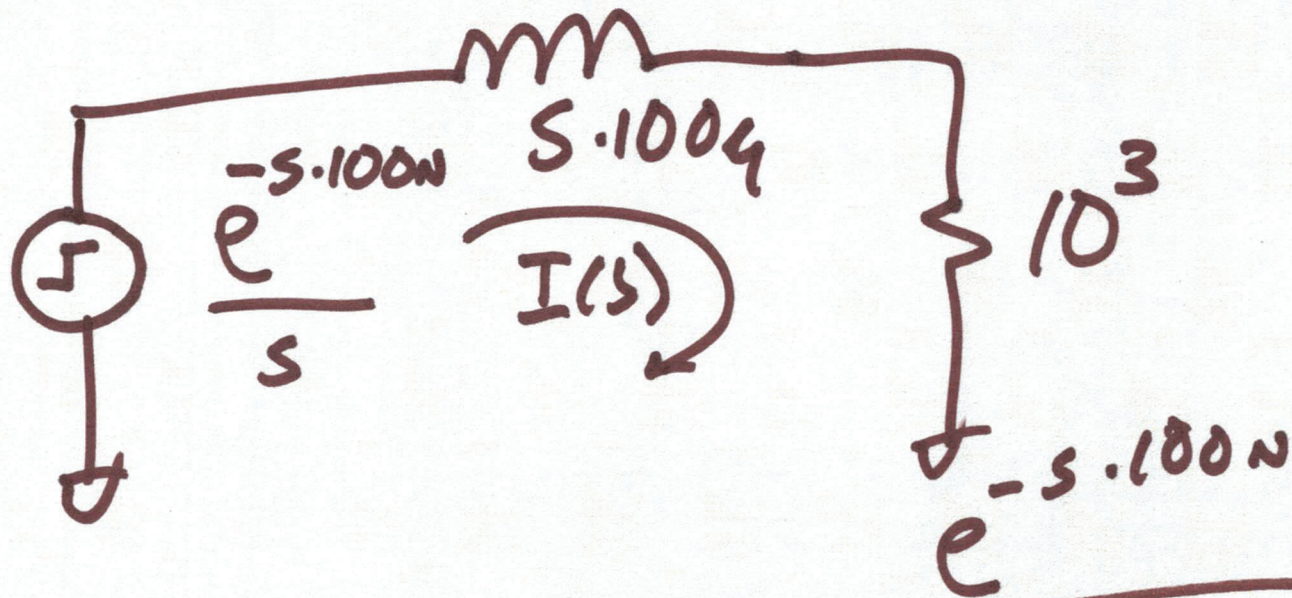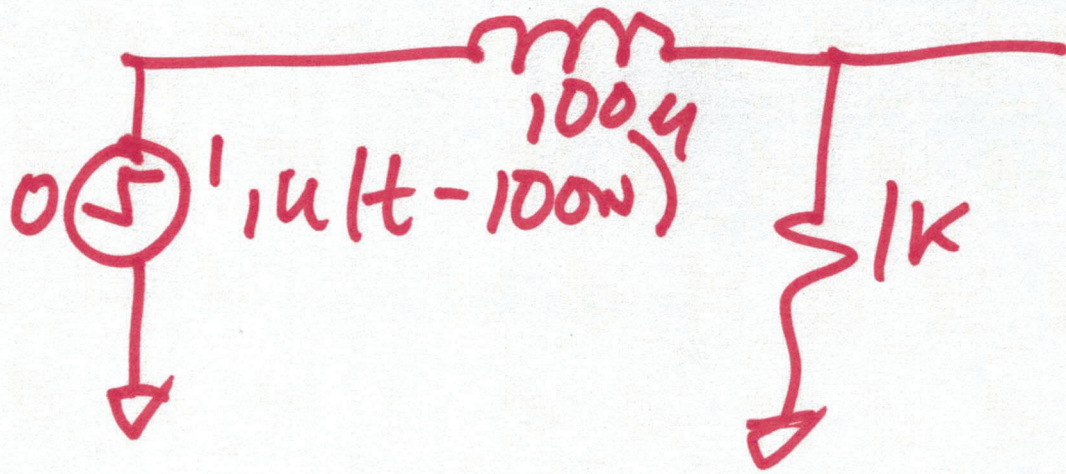

$$I(s) = \frac{\frac{e^{-s \cdot 100n}}{s}}{s \cdot 100 \cdot 10^{-6} + 10^3}$$

$$I(s) = \frac{e^{-s \cdot 100\mu} \cdot \frac{1}{10^{-4}}}{s(s \cdot 10^{-4} + 10^3)} \cdot \frac{1}{10^{-4}}$$

$$= \frac{\frac{1}{10^{-4}} e^{-s \cdot 100\mu}}{s(s + 10^7)} \quad \tau = \frac{L}{R} = \frac{100\mu}{1k} = 10^{-7} = \frac{1}{10^7}$$

$$\frac{\frac{1}{10^{-4}} e^{-s \cdot 100\mu}}{s(s + 10^7)} = \frac{A \cdot e^{-s \cdot 100\mu}}{s} + \frac{B \cdot e^{-s \cdot 100\mu}}{s + 10^7}$$

$$A = \frac{1}{10^{-4}} \cdot \frac{1}{10^7}$$

$$\frac{\frac{1}{10^{-4}}}{s(s+10^7)} = \frac{\frac{1}{10^{-4}} \cdot e^{-s \cdot 100\mu\text{s}}}{s(s+10^7)}$$

$$= B = \frac{-1}{10^{-4}} \frac{1}{10^7}$$

$$\frac{Ae^{-(s+10^7)t}}{s} + \frac{Be^{-(s+10^7)t}}{s+10^7}$$

$$\frac{\frac{1}{10^{-4}}}{-10^7}$$

$$= \boxed{B = \frac{-1}{10^7} \cdot \frac{1}{10^{-4}}}$$

$$I(s) = \frac{+ \frac{1}{10^7} \cdot \frac{1}{10^{-4}} e^{-5100s}}{s} - \frac{\frac{71}{10^7} \cdot \frac{1}{10^{-4}} e^{-5100s}}{s + 10^7}$$

$$i(t) = \frac{1}{10^7} \cdot \frac{1}{10^{-4}} \left(u(t-100\text{ns}) - e^{-\frac{(t-100\text{ns})}{10^{-7}}} u(t-100\text{ns}) \right)$$

$$= 1\text{mA} \left(1 - e^{-\frac{(t-100\text{ns})}{10^{-7}}} \right) u(t-100\text{ns})$$

100ns

