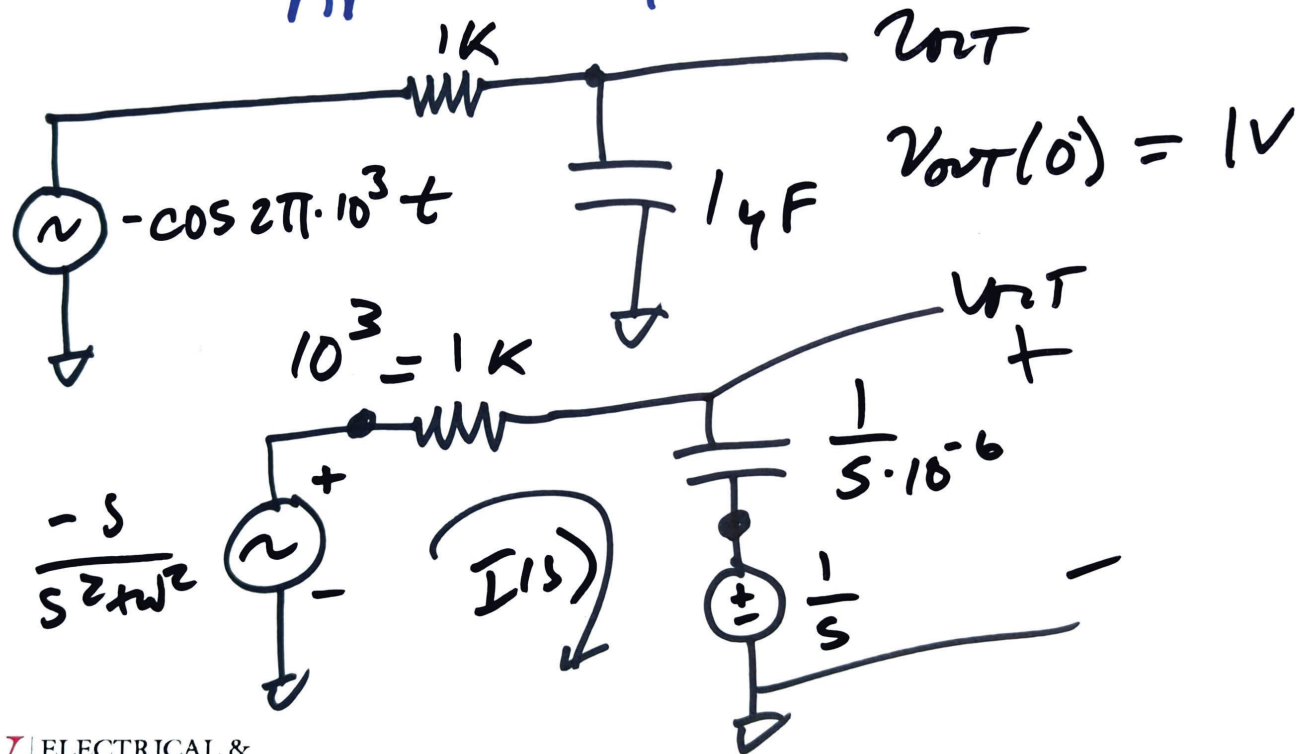


EE 221 Circuits II

Lecture 23

April 19, 2023



$$I(s) = \frac{-\frac{s}{s^2 + \omega^2} - \frac{1}{s}}{10^3 + \frac{1}{s \cdot 10^{-6}}} \quad \omega = 2\pi \cdot 10^3$$

$$= \frac{\left(-s - \frac{1}{s}(s^2 + \omega^2)\right) s}{(s^2 + \omega^2) \left(10^3 + \frac{1}{s \cdot 10^{-6}}\right) s}$$

$$= \frac{\left(-s^2 - (s^2 + \omega^2)\right) \cdot 10^3}{(s + j\omega)(s - j\omega) \left(s \cdot 10^3 + \frac{1}{10^{-6}}\right) 10^{-3}}$$

$$= \frac{-10^{-3} \left(s^2 + (s^2 + \omega^2)\right)}{(s + j\omega)(s - j\omega) \left(s + \frac{1}{10^{-3}}\right)}$$

$$I(s) = -10^{-3} \cdot \frac{(2s^2 + \omega^2)}{(s + j\omega)(s - j\omega)(s + \frac{1}{10^{-3}})}$$

$$\frac{A}{s + j\omega} + \frac{B}{s - j\omega} + \frac{C}{s + \frac{1}{10^{-3}}}$$

$$A = \frac{-10^{-3} \cdot (2(-j\omega)^2 + \omega^2)}{(-j\omega - j\omega)(-j\omega + \frac{1}{10^{-3}})} \left\{ \begin{array}{l} j^2(-\omega)^2 \\ -\omega^2 \end{array} \right.$$

$$= \frac{-10^{-3} (-2\omega^2 + \omega^2)}{-2j\omega(-j\omega + \frac{1}{10^{-3}})}$$

$$\begin{aligned}
&= \frac{-10^{-3}(-\omega^2)}{-2\omega^2 + \frac{-2j\omega}{10^{-3}}} \\
&= \frac{-10^{-3}(-\omega^2)}{-2\omega^2 - \frac{2j\omega}{10^{-3}}} \\
&= \frac{10^{-3} \cdot (2\pi \cdot 10^3)^2}{-2(2\pi \cdot 10^3)^2 - \frac{2j \cdot 2\pi \cdot 10^3}{10^{-3}}} \\
&= \frac{(2\pi)^2 \cdot 10^3}{-2(2\pi)^2 \cdot 10^6 - j 2 \cdot 2\pi \cdot 10^6}
\end{aligned}$$

4)

$$= \frac{(2\pi)^2 \cdot 10^{-3} / (2\pi)^2}{\frac{-2(2\pi)^2}{(2\pi)^2} - j \cdot \frac{2 \cdot 2\pi}{(2\pi)^2}}$$

$$= \frac{10^{-3}}{-2 - j2/2\pi}$$

$$= -\frac{1}{2} \left(\frac{10^{-3}}{1 + j/2\pi} \right)$$

$$1 e^{j\theta} = \cos \theta + j \sin \theta \quad a + jb \rightarrow \sqrt{a^2 + b^2} \angle \tan^{-1} \frac{b}{a}$$

$\sqrt{a^2 + b^2}$ $e^{j \tan^{-1} \frac{b}{a}}$

$$\begin{aligned}
 &= \frac{-10^{-3}}{2} \left(\frac{1}{1 + j/2\pi} \right) e^{-j \tan^{-1} \frac{1}{2\pi}} \\
 &= -\frac{10^{-3}}{2} \cdot \frac{1}{\sqrt{1^2 + \left(\frac{1}{2\pi}\right)^2}} e^{-j \tan^{-1} \frac{1}{2\pi}} \\
 \angle \frac{1}{a + jb} &= -\tan^{-1} \frac{b}{a} \Rightarrow \theta = .16^\circ \approx 0
 \end{aligned}$$

$$\begin{aligned}
 \frac{10^{-3}}{.078} &= -78.6 \\
 &540\mu - j.16 \\
 A &= -\cancel{78.6} e^{j.16} \\
 B &= -\cancel{78.6} e^{j.16} \\
 &540\mu
 \end{aligned}$$

$$\frac{\sqrt{49+144}}{\sqrt{324+36}} = \frac{13.9}{18.97} = .73$$

$$\mathcal{L}\{I(s)\} \Rightarrow A \cdot e^{-\frac{1}{2} \omega t} + B e^{\frac{1}{2} \omega t} + C e^{-\frac{1}{10} \omega t} + e^{-j \cdot 16}$$

↑ from book
12.70b

$$A = -540m$$

$$540 e^{j(\omega t + \theta)} + 540 e^{-j(\omega t + \theta)}$$