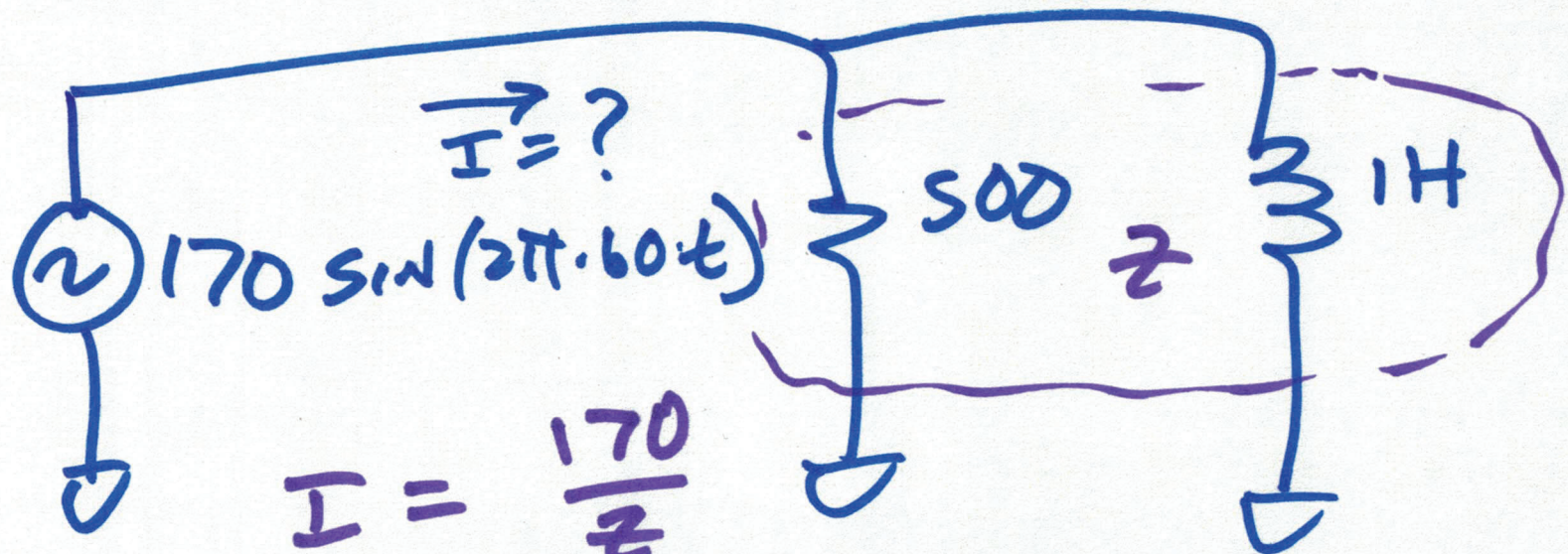


EE 221 CIRCUITS II

Lecture 25

~~April~~ April 26, 2023




$$I = \frac{170}{Z}$$

$$Z = \frac{500 \cdot j\omega \cdot 1}{500 + j\omega \cdot 1}$$

Closed book and notes.

Show your work for credit and place a box around your answer.

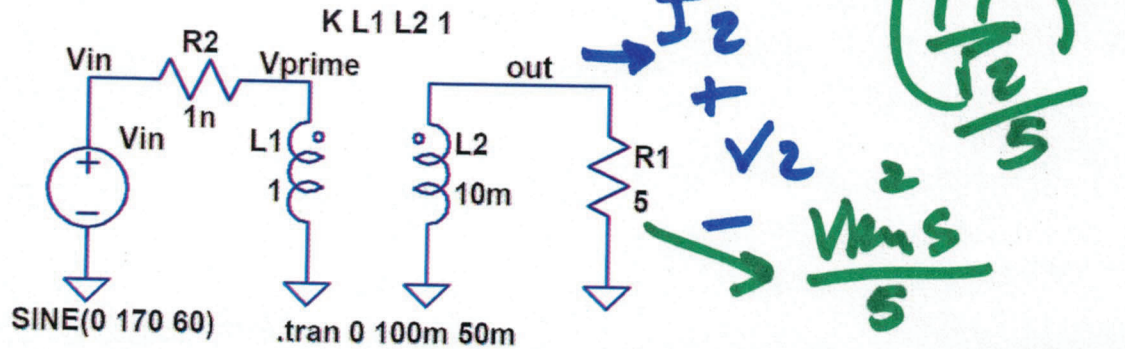1. Find the current flowing in V_{in} (write an equation in the time domain). (5 points)



$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} = \frac{1}{N}$$

$$S = \frac{V_2}{I_2} = \frac{V_1 \cdot \frac{N_2}{N_1}}{I_1 \cdot \frac{N_1}{N_2}} = \frac{V_1}{I_1} \left(\frac{N_2}{N_1}\right)^2$$

$$S = \frac{V_1}{I_1} \cdot \left(\sqrt{\frac{L_2}{L_1}}\right)^2 = \frac{V_1}{I_1} \left(\sqrt{\frac{1}{100}}\right)^2$$

$$\frac{V_1}{I_1} = 500$$

2)

$$I = \frac{170 \angle 0}{500 \cdot j\omega \cdot 1} \cdot \frac{500 + j\omega \cdot 1}{500 + j\omega \cdot 1}$$

$$I = \frac{170(500 + j\omega)}{0 + 500 \cdot j\omega}$$

$$|I| = \frac{170 \cdot \sqrt{500^2 + (2\pi 60)^2}}{\sqrt{0^2 + (500 \cdot 2\pi \cdot 60)^2}}$$

$$\angle I = \tan^{-1} \frac{2\pi 60}{500} - \tan^{-1} \infty \approx 0 - 90^\circ = -90^\circ$$

$$= \frac{88,760}{188,400} = 0.47 \cdot 56$$

$$i(t) = 560 \text{ mA} \sin(2\pi 60 t - 53^\circ)$$

3)

$$V_1 = 170$$


$$V_2 = \sqrt{\frac{L_2}{L_1}} \cdot V_1$$

$$\sqrt{\frac{10\mu}{1}} \cdot 170 = \sqrt{\frac{1}{100}} \cdot 170$$

$$V_2 = 17$$

$$I_2 = \frac{17}{5} = 3.4 \text{ A}$$

4)

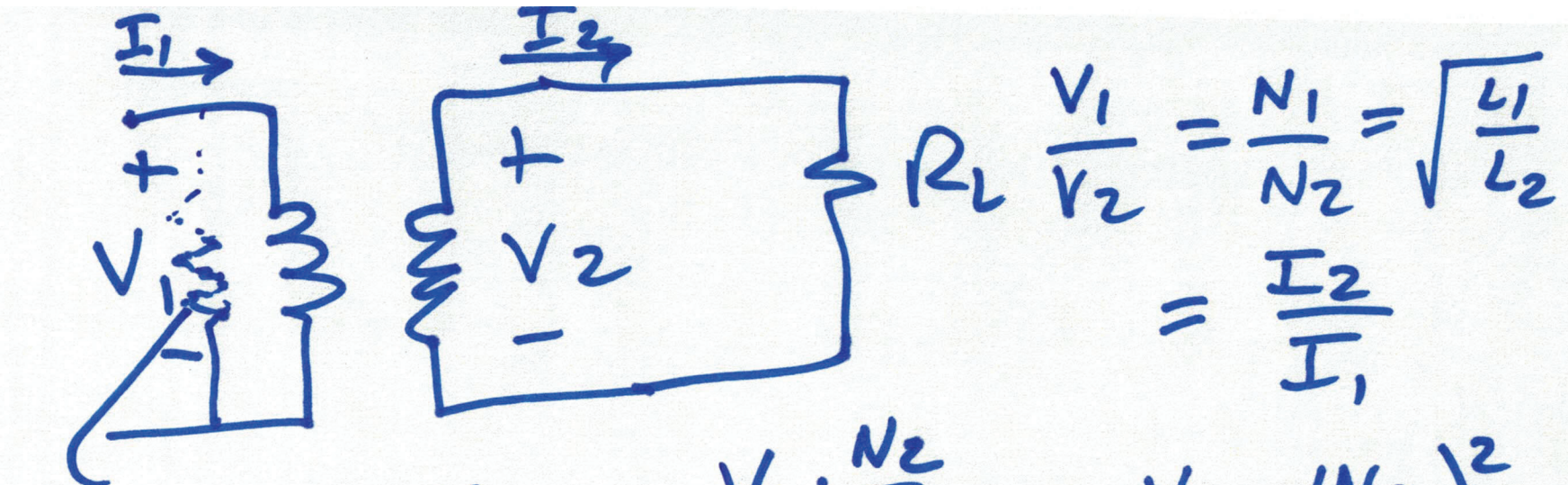


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$

$$= \frac{I_2}{I_1}$$


R_{in}

$$R_L = \frac{V_2}{I_2} = \frac{V_1 \cdot \frac{N_2}{N_1}}{I_1 \cdot \frac{N_1}{N_2}} = \frac{V_1}{I_1} \cdot \left(\frac{N_2}{N_1}\right)^2$$
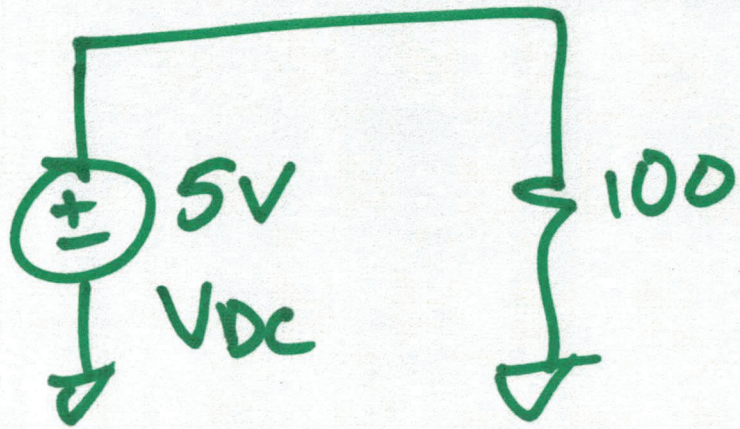
$$R_{in} = R_L \cdot \left(\frac{N_1}{N_2}\right)^2 = R_L \cdot \frac{L_1}{L_2}$$



$$V_{OC} = V_{R-S}$$

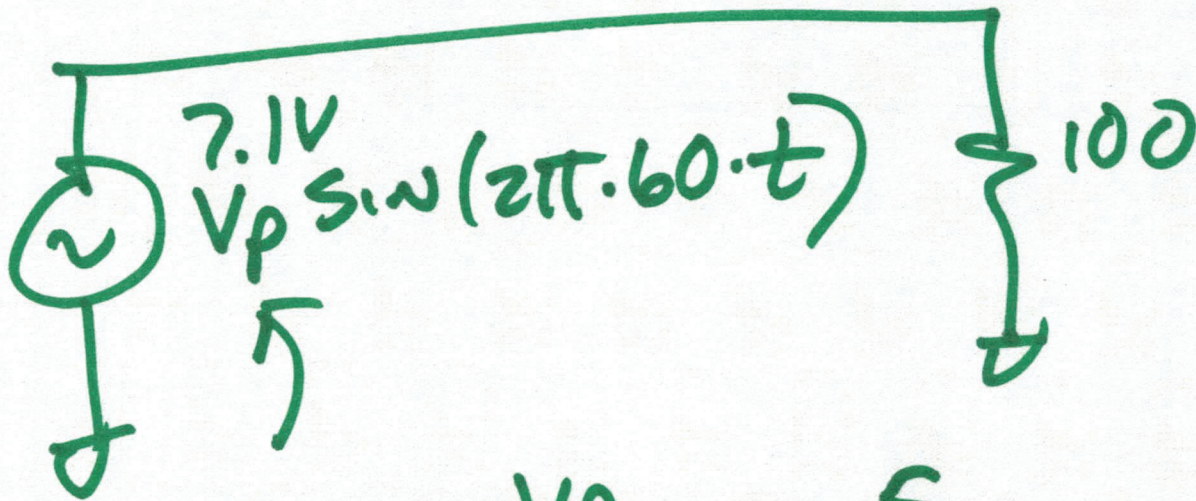


$$\frac{V_p}{\sqrt{2}} = 5$$

$$V_p = \sqrt{2} \cdot 5 = 7.1V$$

instantaneous


$$p(t) = i(t) \cdot v(t)$$

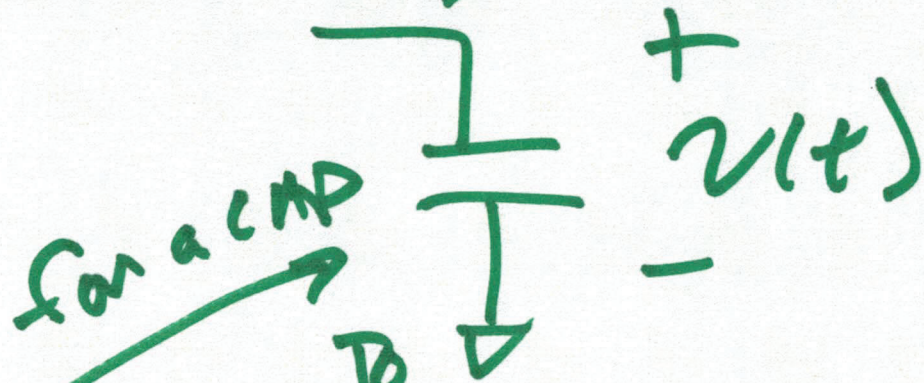

$$P_{AVG} = \frac{1}{T_0} \int_0^{T_0} p(t) \cdot dt = 0$$



12.5V = constant

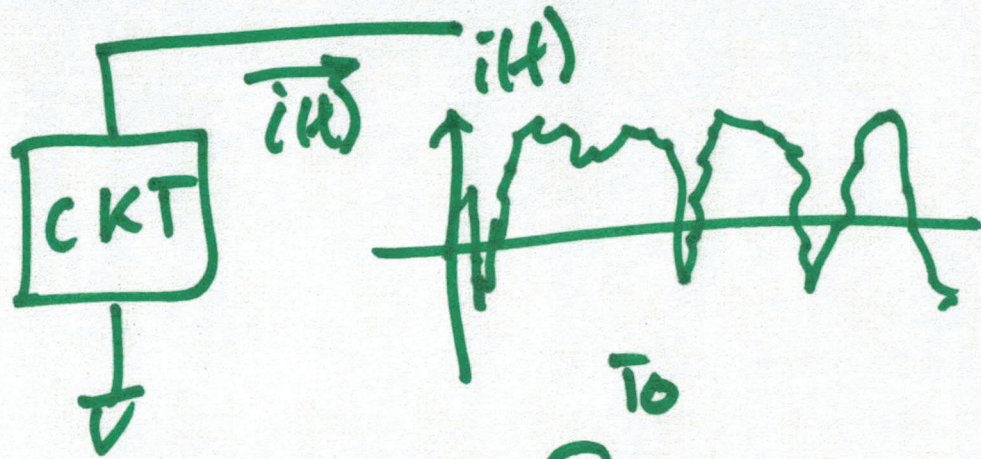

$$P_{AVG} = \frac{1}{T_0} \int_0^{T_0} 12.5 \cdot i(t) \cdot dt$$

