
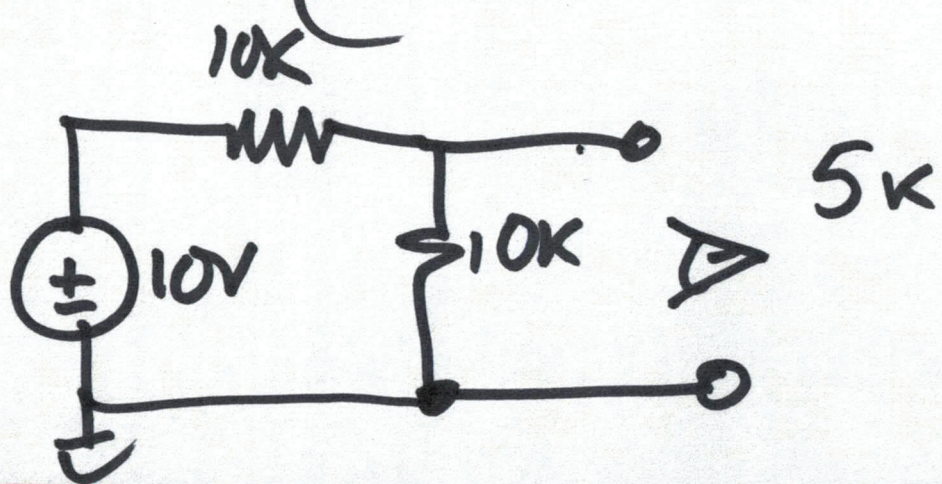


2)

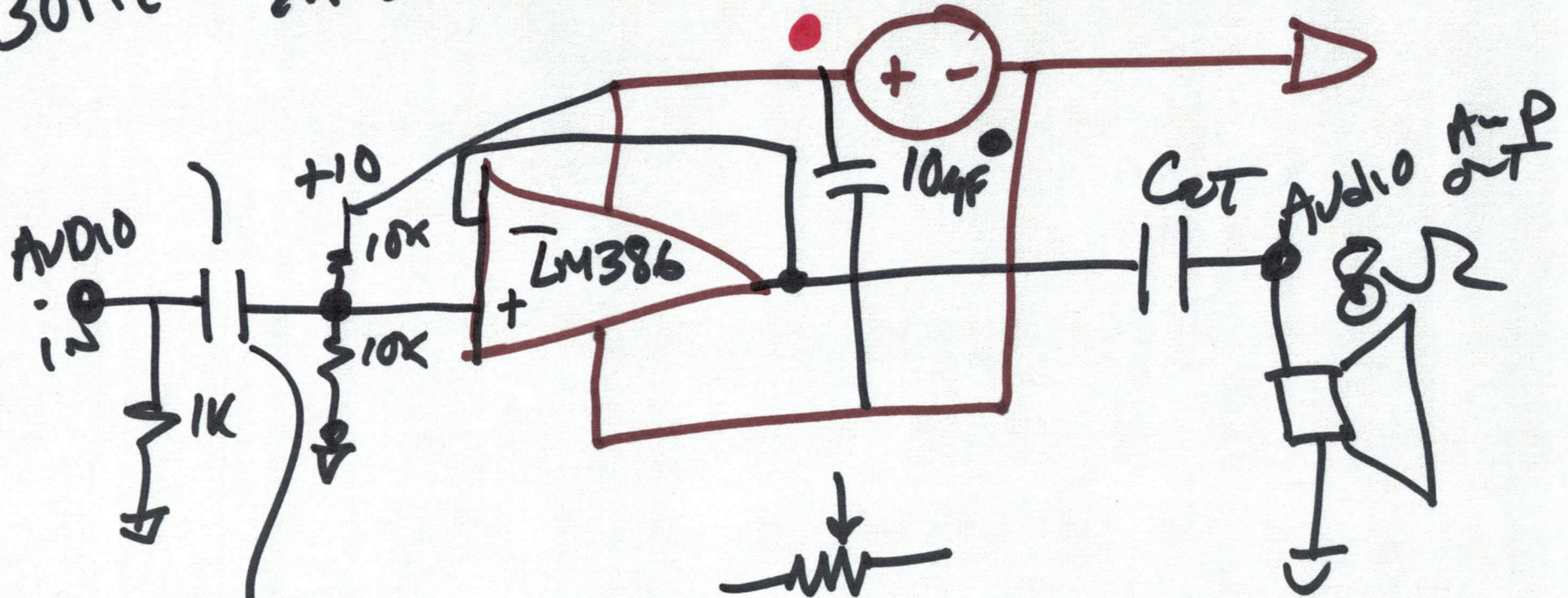

$30\text{Hz} = \frac{1}{2\pi \cdot 5\text{k} \cdot C}$  AC coupling 18V




$f_{3dB} = \frac{1}{2\pi RC}$   
 $f_{3dB} \approx 30\text{Hz}$




555


Monostable

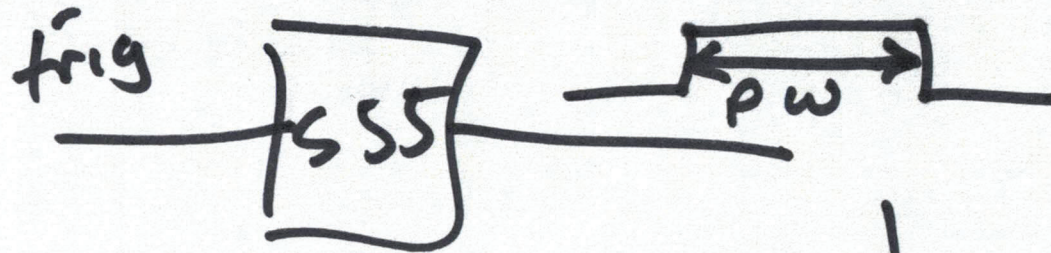

Astable

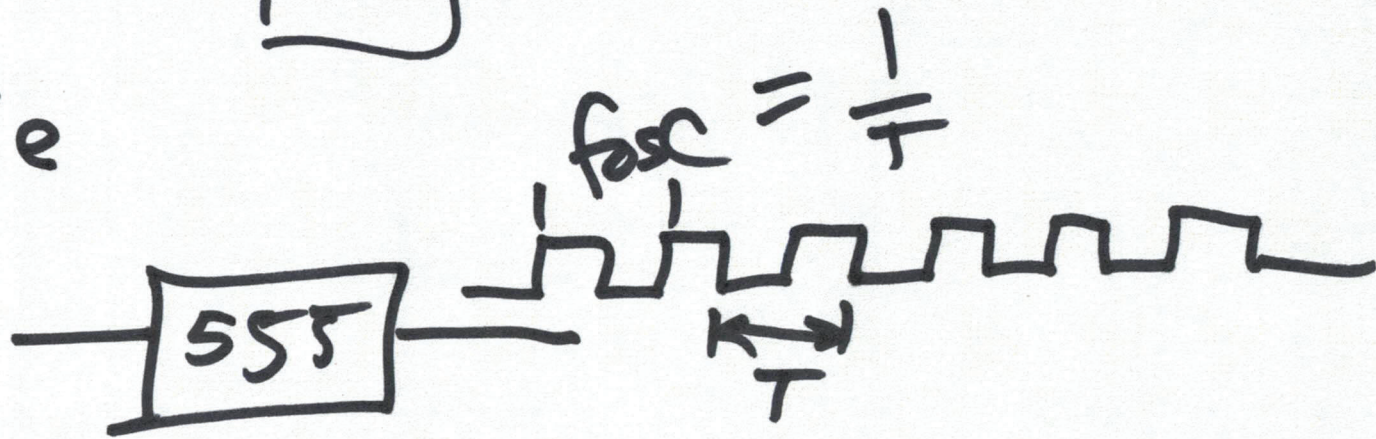


Bi stable

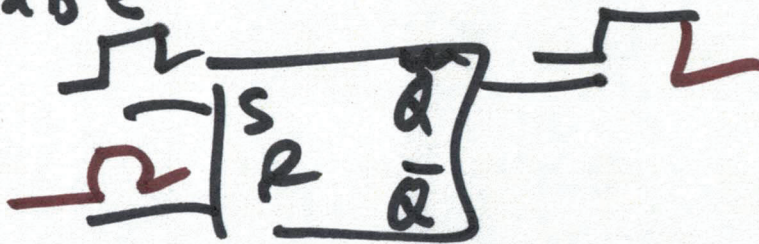



# MAXimum power

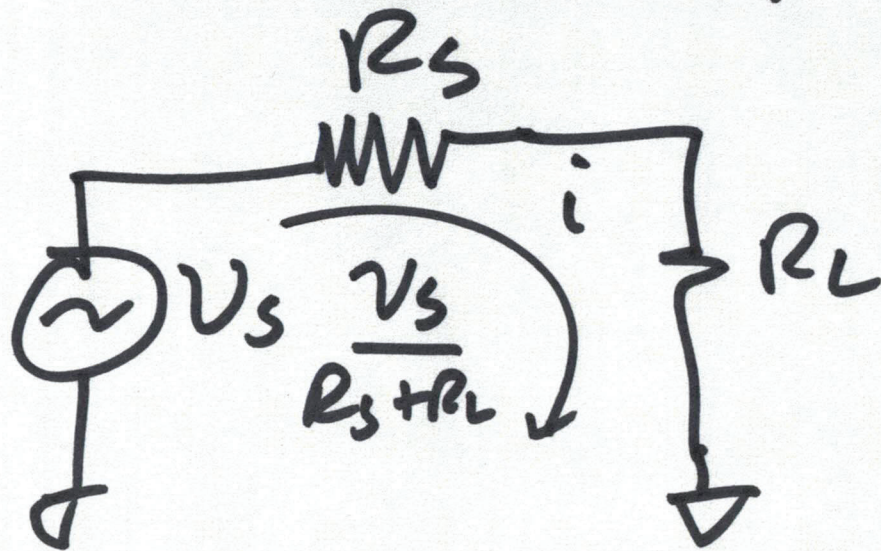

$$P_L = i^2 R_L = \left( \frac{V_s}{R_s + R_L} \right)^2 \cdot R_L$$

$$= \frac{V_s^2 \cdot R_L}{(R_s + R_L)(R_s + R_L)}$$



$$P_L = \frac{v_s^2 \cdot R_L}{R_s^2 + 2R_s R_L + R_L^2}$$

$$P_L = \frac{v_s^2}{R_s^2 \cdot R_L^{-1} + 2R_s + R_L}$$

Minimum

$$\frac{d}{dR_L} (R_s^2 R_L^{-1} + 2R_s + R_L) = 0$$


$$(-1)R_s^2 R_L^{-2} + 0 + 1 = 0$$

$$1 = \frac{R_s^2}{R_L^2}$$

MAX power  
transfer

$$R_s = R_L$$



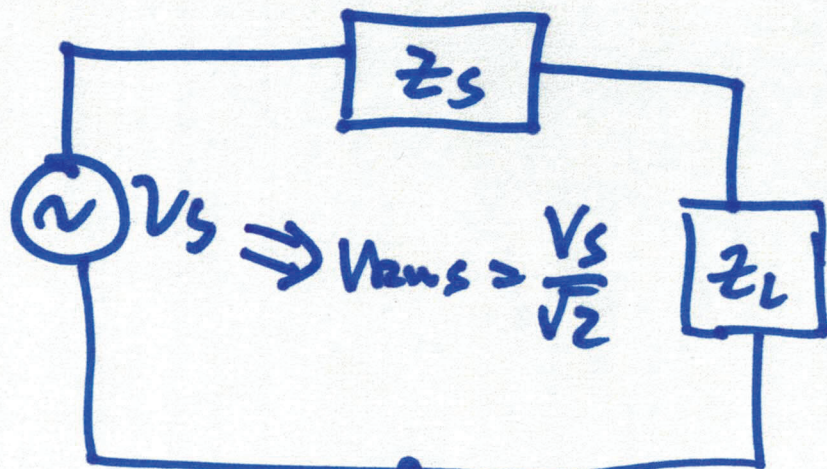


$$Z_s = R_s + jX_s$$

$$Z_L = R_L + jX_L$$

$$P = \frac{V^2}{R} = I^2 R$$

$$P_L = \frac{1}{2} \left| \frac{|V_s|}{|Z_s + Z_L|} \right|^2 \cdot R_L$$

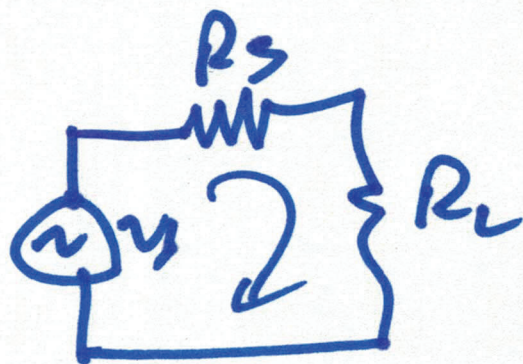

$$\frac{V_s}{R_s + R_L}$$

current  $i$

$$P = I^2 \cdot R$$

$$\frac{\frac{V_s}{\sqrt{2}}}{(R_s + R_L)^2}$$



$$P_L = \frac{1}{2} \frac{|V_s|^2 \cdot R_L}{|(R_s + R_L) + j(X_s + X_L)|^2}$$

MAX. power xfer

$$X_s = -X_L$$

→ 
$$\frac{1}{2} \frac{|V_s|^2 \cdot R_L}{|(R_s + R_L)|^2}$$

maximum power transfer

$$Z_s = R_s + j \cdot X_s \rightarrow Z_L = R_s + j(-X_s)$$

Load to be the complex conjugate of the source impedance