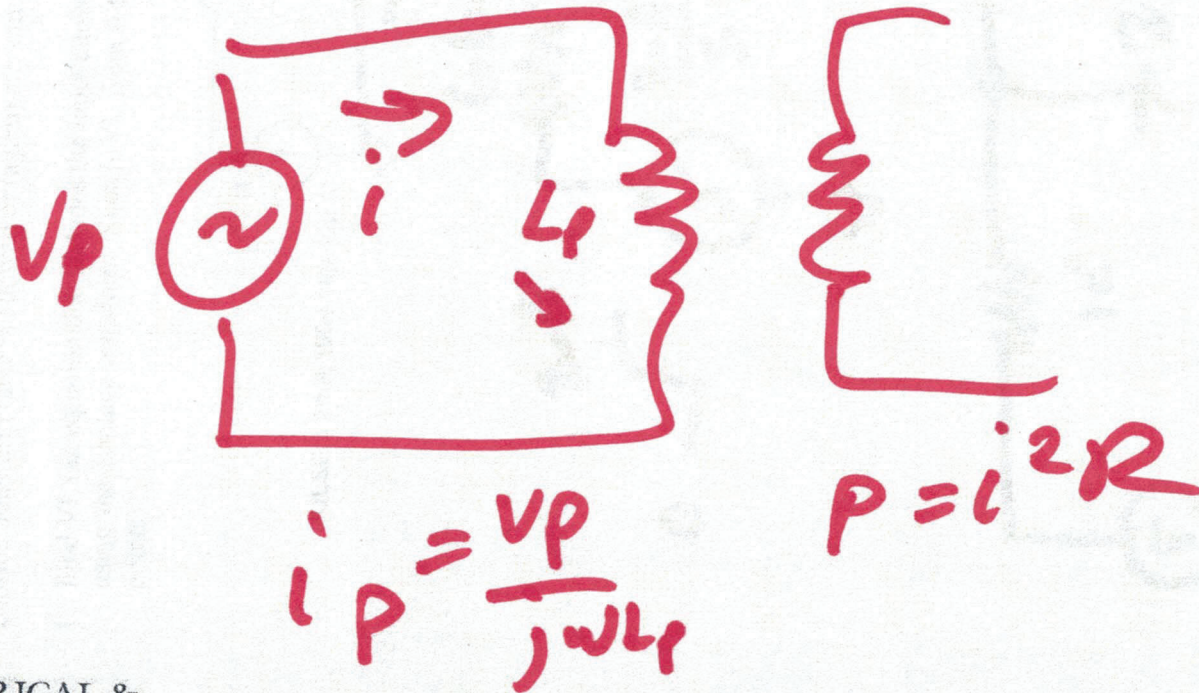


EE 221

Circuits II





May 3, 2023



Lecture 27



Closed book and notes. No extra paper, do your work on this exam, use the back if needed.
Show your work for credit and be neat! Place a box around each of your answers. No
 Laplace transform table is allowed or (again) any other extra material (scratch paper).

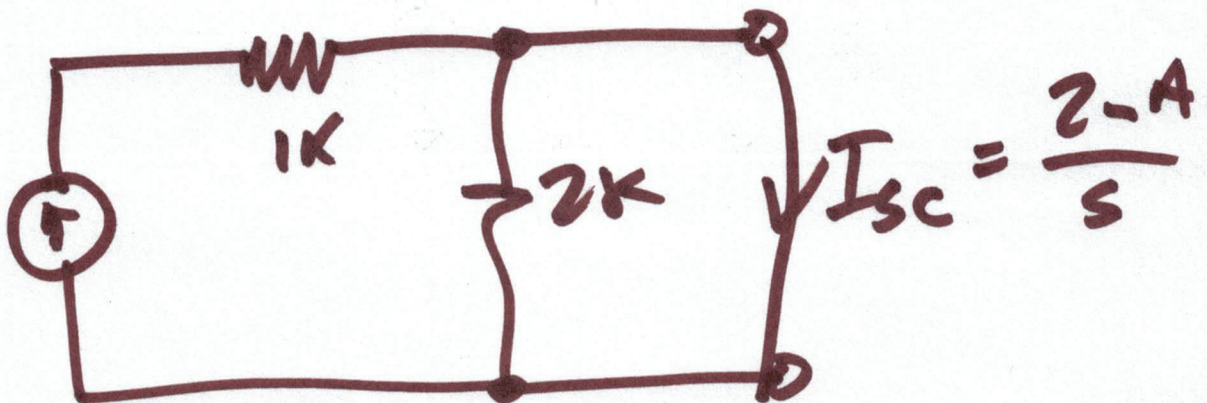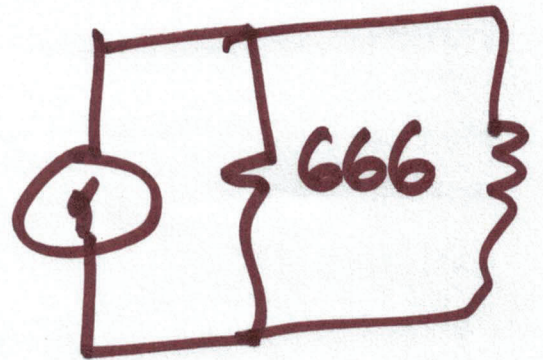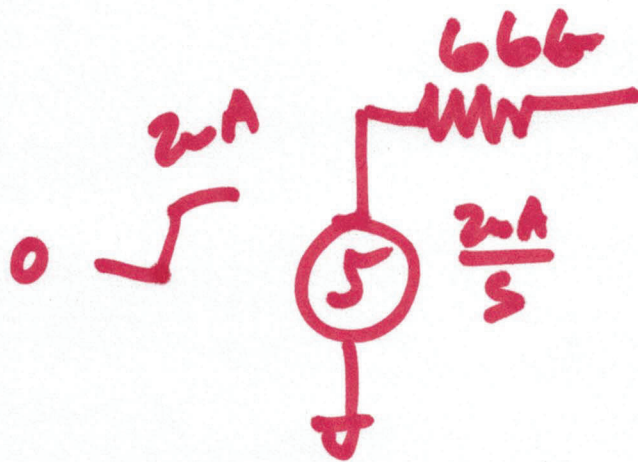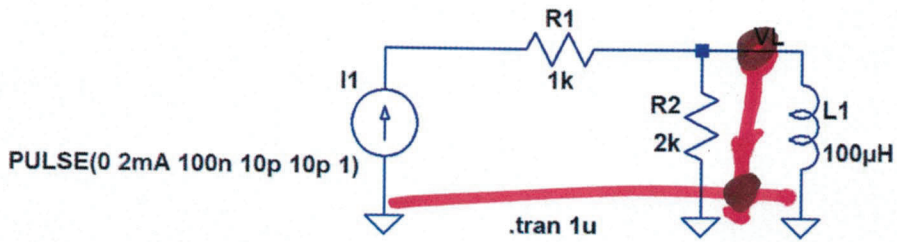- Find V_L (an equation that includes the input current pulse's delay) in the following circuit using the Laplace transform. Sketch V_L from 0 to 1 us ensuring you label the axis. (15 points)



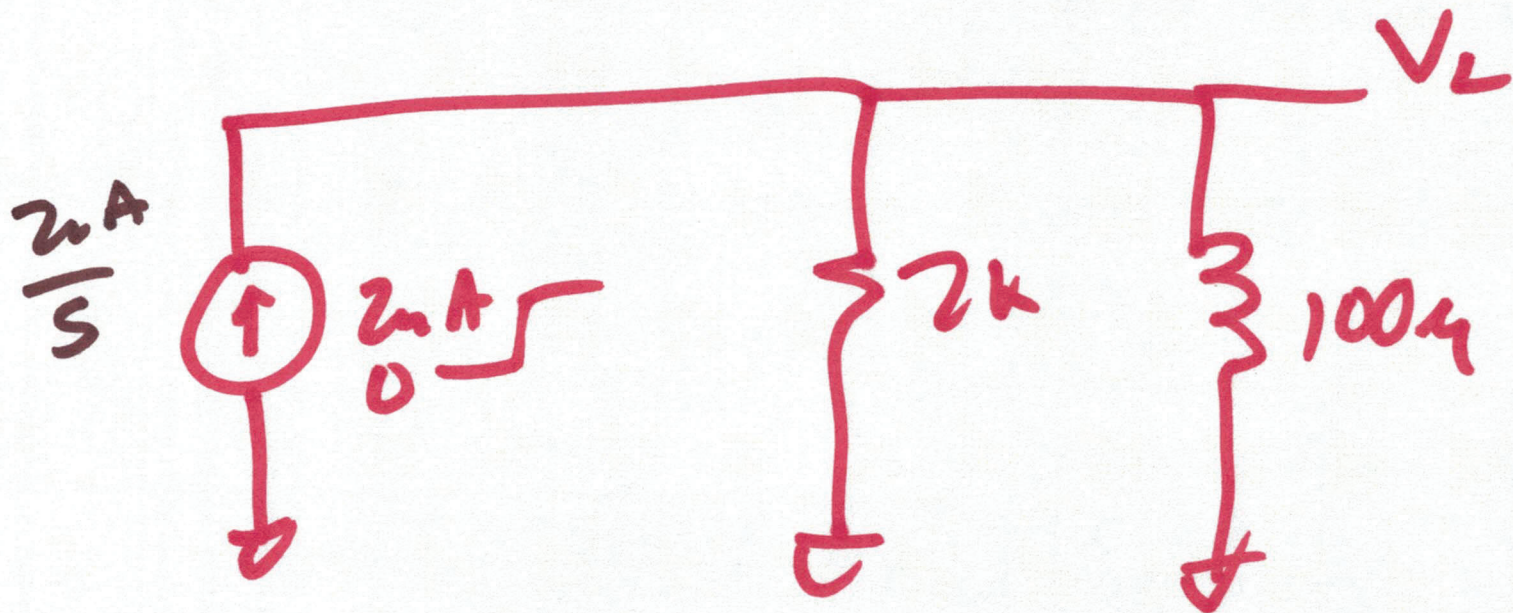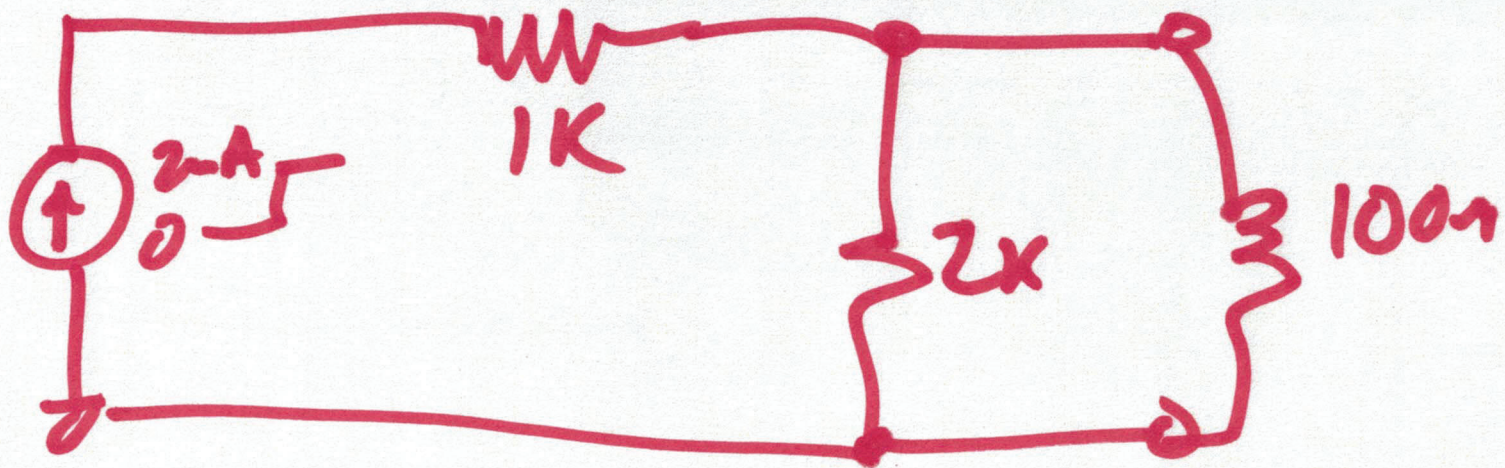

$$V_L = \frac{2mA}{s} \cdot \frac{2k \cdot \cancel{s} \cdot 100\Omega}{2k + s \cdot 100\Omega}$$


3)



$$V_L = 2\text{mA} \cdot \frac{2\text{k}}{5 + \frac{2\text{k}}{100\text{n}}}$$

$$V_L(t) = 4\text{V} e^{-t / \frac{100\text{n}}{2\text{k}}} u(t)$$

$$V_L(t) = 4 e^{-(t-100\text{n}) / \frac{100\text{n}}{2\text{k}}} \cdot u(t-100\text{n})$$

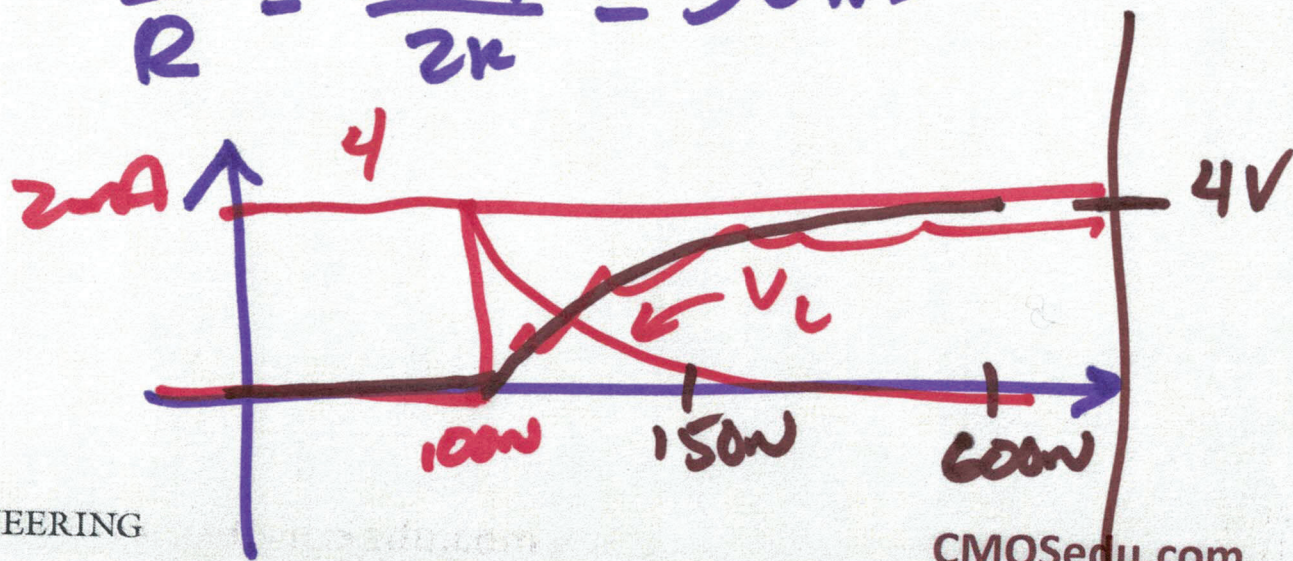
$$\frac{L}{R} = \frac{100\text{n}}{2\text{k}} = 50\text{ns}$$



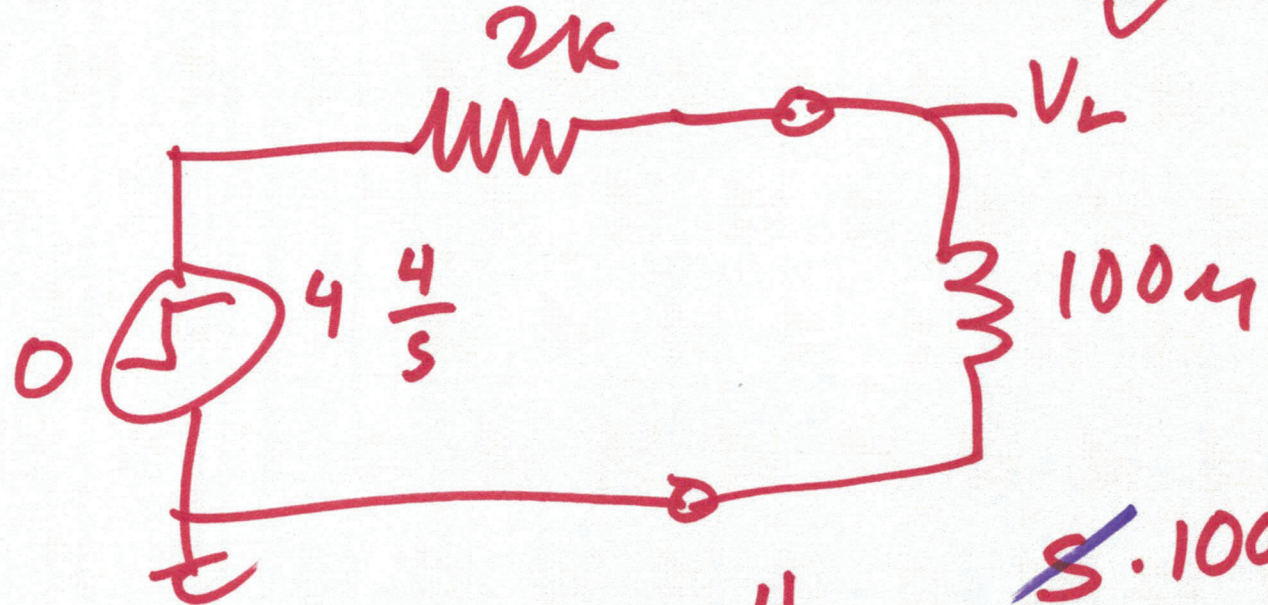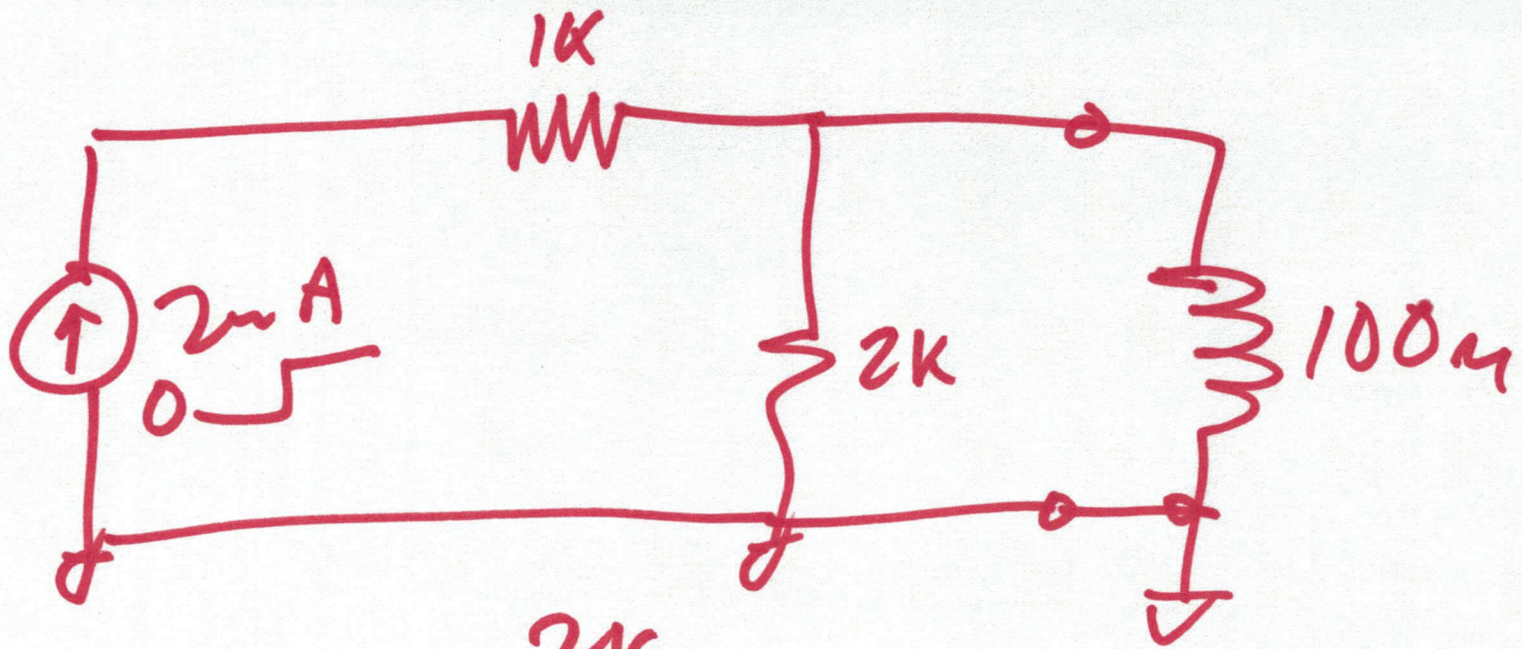

$$V_L = \frac{4}{8} \cdot \frac{\cancel{8} \cdot 100\mu}{5100\mu + 2k}$$

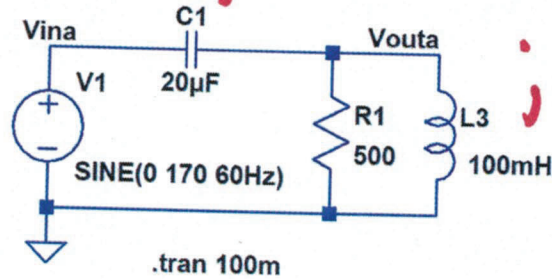2. Assuming the circuit seen below is operating in steady-state, use AC analysis to determine V_{out} . Sketch V_{out} and V_{in} on the same plot ensuring to label times (phase shift) and voltages. (15 points)



$$V_{out} = 170 \angle 0^\circ$$

$$= 170 \angle 0^\circ \cdot \frac{500 \cdot 2\pi \cdot 60 \angle 90^\circ}{500 \cdot 2\pi \cdot 60 \angle 90^\circ + \frac{500 + j2\pi \cdot 60 \cdot 0.1}{j2\pi \cdot 60 \cdot 20 \times 10^{-6}}}$$

$$500 \cdot 2\pi \cdot 60 = 18.84 \text{ k} \angle 90^\circ$$

$$V_{out} = 170 \angle 0^\circ \cdot \frac{18.84 \text{ k} \angle 90^\circ}{18.84 \text{ k} \angle 90^\circ + 66.8 \text{ k} \angle 85.7^\circ} = \frac{500 \angle 4.3^\circ}{7.5 \cdot 10^3 \angle 90^\circ} \cdot 6.8 \text{ k} \angle -85.7^\circ$$

7)

$$j18.84k + 5k - j66.6k$$


$$V_{outa} = \frac{170 \angle 0 \cdot 18.84k \angle 90}{j18.84k + 5k - j66.6k}$$
$$5k - j47.8k$$

$$V_{outa} = \frac{170 \angle 0 \cdot 18.84 \angle 90}{48.1 \angle -84}$$

$$V_{outa} = 66.6 \angle 174^\circ$$

$$= 66.6 \sin(2\pi \cdot 60 \cdot t + 174^\circ)$$

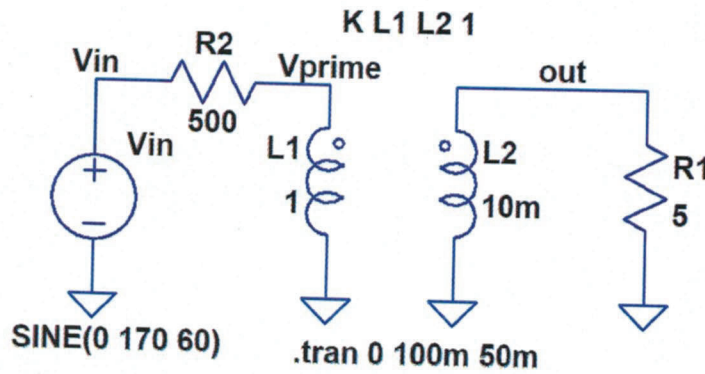3. Find the voltages and currents in the following circuit. How much power does R1 dissipate?
(20 points)





$$\frac{V_2}{I_2} = \frac{5 V_1 \cdot \frac{N_2}{N_1}}{I_1 \cdot \frac{N_2}{N_1}}$$

$$\frac{V_1}{I_1} = 5 \left(\frac{N_1}{N_2} \right)^2 = 500$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} = \frac{1}{N}$$

$V_p = 170V$ peak or $120V_{rms}$

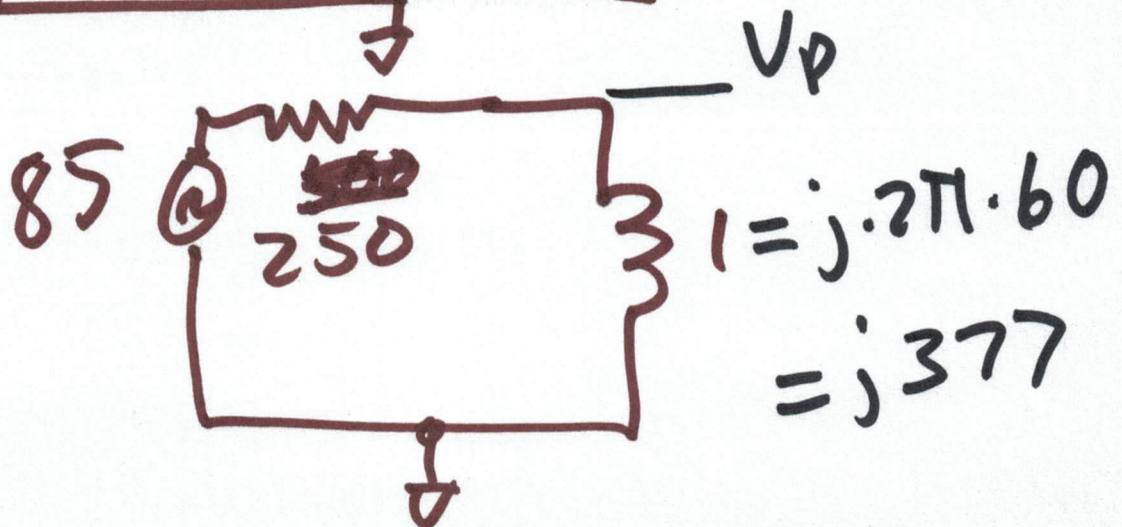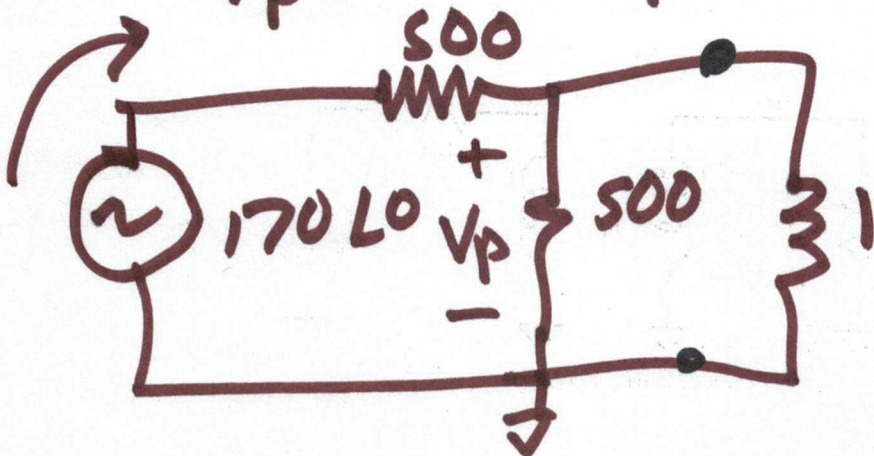

i)

$$V_p = 85 \cdot \frac{j377}{250 + j377}$$

$$= 85 \cdot \frac{377 \angle 90^\circ}{452 \angle 56.5^\circ}$$


$$V_1 = V_p = 70.9 \angle 33.5^\circ$$

$$I_p = \frac{70.9 \angle 33.5^\circ}{377 \angle 90^\circ}$$

$$V_2 = V_s = V_p \cdot \sqrt{\frac{L_2}{L_1}} = \frac{70.9 \angle 33.5^\circ}{10}$$

$$I_2 = \frac{V_s}{5} = \frac{70.9 \angle 33.5^\circ}{50}$$

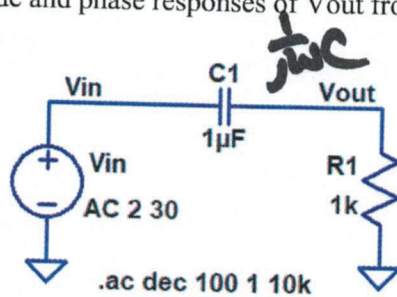4. In the following circuit the input voltage is 2V with a phase shift of 30 degrees. If the input frequency is swept determine equations for the magnitude and phase of the output voltage $V_{out}(f)$. Plot the magnitude and phase responses of V_{out} from 1 Hz to 10 kHz. (15 points)




$$\begin{aligned}
 V_{out} &= 2 \angle 30^\circ \cdot \frac{10^3 / 10^3 \cdot 10^3}{\frac{10^3}{10^3} + \frac{1}{j 2\pi \cdot 10^{-6} f}} \\
 &= \frac{2 \angle 30^\circ}{1 + \frac{1}{j 2\pi 10^3 f}} \\
 &= \frac{2 \angle 30^\circ \cdot j 2\pi 10^3 f}{1 + j 2\pi \cdot 10^3 f}
 \end{aligned}$$

$$|V_{out}| = 2 \cdot 2\pi \cdot 10^3 \cdot f$$

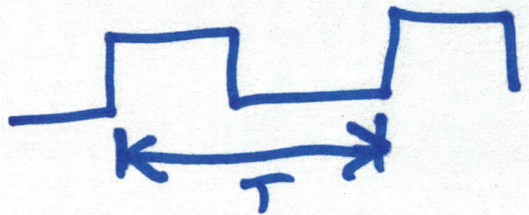11)

$$2 \angle 30 (0 + j 2\pi \cdot 10^{-3} \cdot f)$$

$$\frac{2 \angle 30 (0 + j 2\pi \cdot 10^{-3} \cdot f)}{1 + j 2\pi \cdot 10^{-3} \cdot f}$$



$$f = \frac{1}{T}$$

$$f_{3dB} = \frac{1}{2\pi \cdot 10^{-3}}$$

$$= 159$$


$$20\pi T =$$

$$\frac{2 \angle 30 (0 + j \frac{f}{159})}{1 + j \frac{f}{159}}$$



$$1 + j \frac{f}{159} \quad 20 \text{ dB}$$

$$|20\pi T| = \frac{2 \cdot \frac{f}{159}}{\sqrt{1 + (\frac{f}{159})^2}}$$
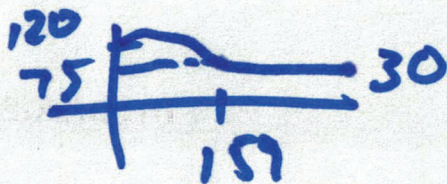
$$\angle 20\pi T = 30 + 90 - \tan^{-1} \frac{f}{159}$$



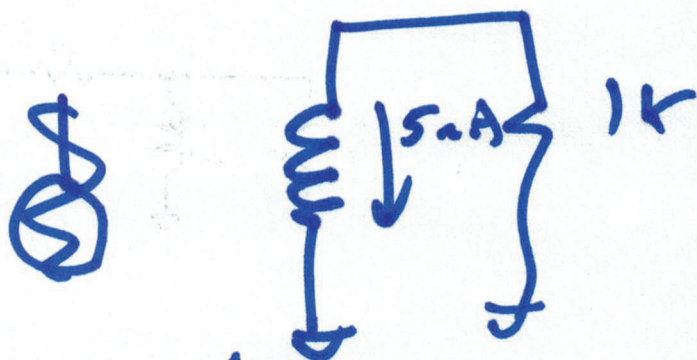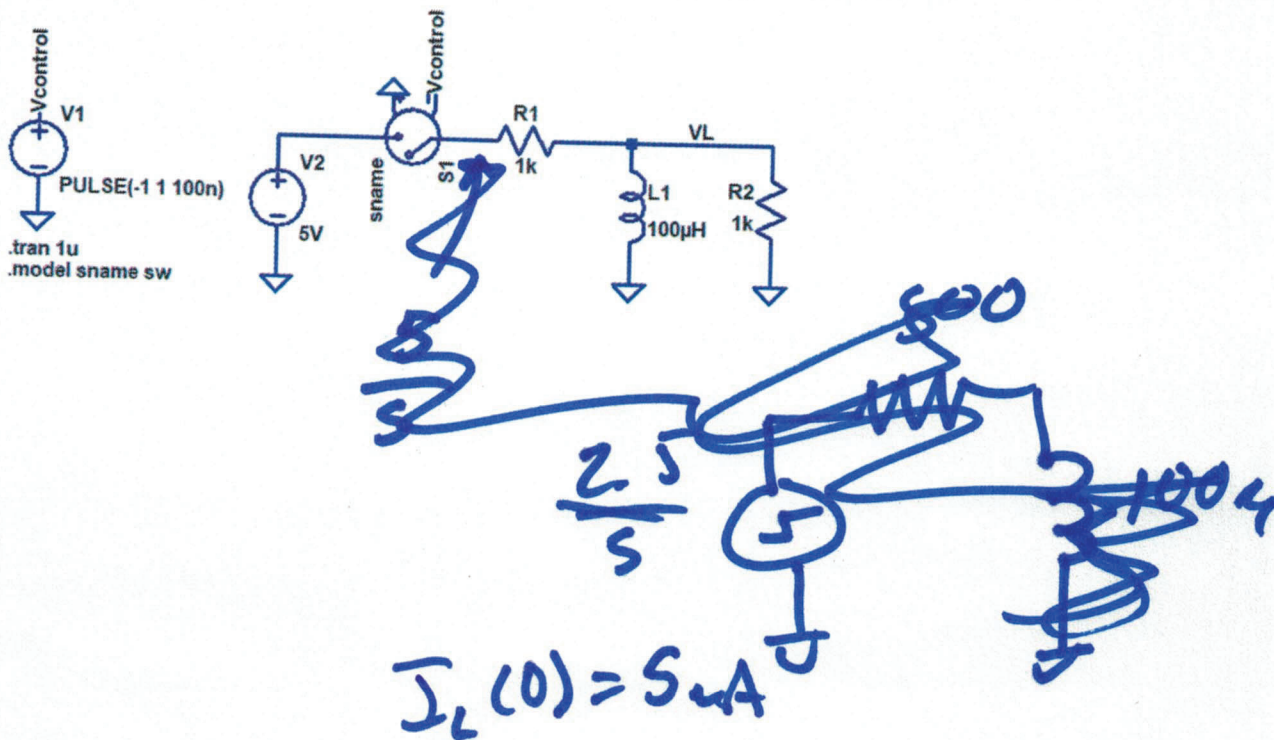5. Using the Laplace transform show how to find the current through L1 in the following circuit. Ensure you place a box around your answer (the equation in the time domain you've derived using the Laplace transform). Plot this current in the time domain. (15 points)




$$-I(s) \cdot 1k - I(s) \cdot s \cdot 100\mu - 100\mu \cdot 5\mu A = 0$$

$$I(s) (1k + s \cdot 100\mu) = 100\mu \cdot 5\mu A$$

$$I(s) = \frac{100\mu \cdot 5\mu A}{1k + s \cdot 100\mu}$$

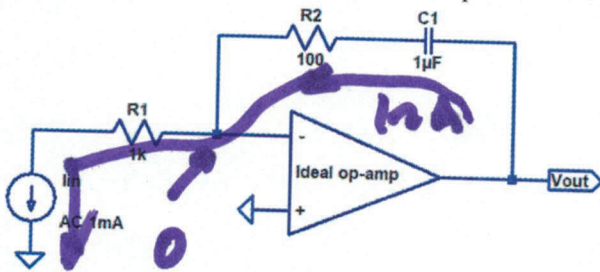6. Determine the frequency when the output voltage is 1V peak in the following integrator circuit. Again, show your work and place a box around your answer. (20 points)



$$1 = V_{out} = 1 \text{ mA} \cdot \left(100 + \frac{1}{j \cdot 2\pi \cdot f \cdot 10^{-6}} \right)$$

$$1 = 1 \text{ mA} \cdot \left(100 + \frac{1}{j \cdot 2\pi \cdot f \cdot 10^{-6}} \right)$$

$$1 \text{ k} = 100 + \frac{1}{j \cdot 2\pi \cdot f \cdot 10^{-6}}$$

$$1 \text{ k} = 100 + j \left(-\frac{1}{2\pi \cdot f \cdot 10^{-6}} \right)$$

$$1 \text{ k} = \sqrt{100^2 + \left(\frac{1}{2\pi \cdot f \cdot 10^{-6}} \right)^2}$$