

EE 221 Circuits II

Lecture 6



Feb 6, 2023

$$V_{rms} = 120V \text{ AC}$$



$$114 \rightarrow 126 \quad 240V$$

$$V_{rms} \cdot \sqrt{2} = V_p = 169.7$$

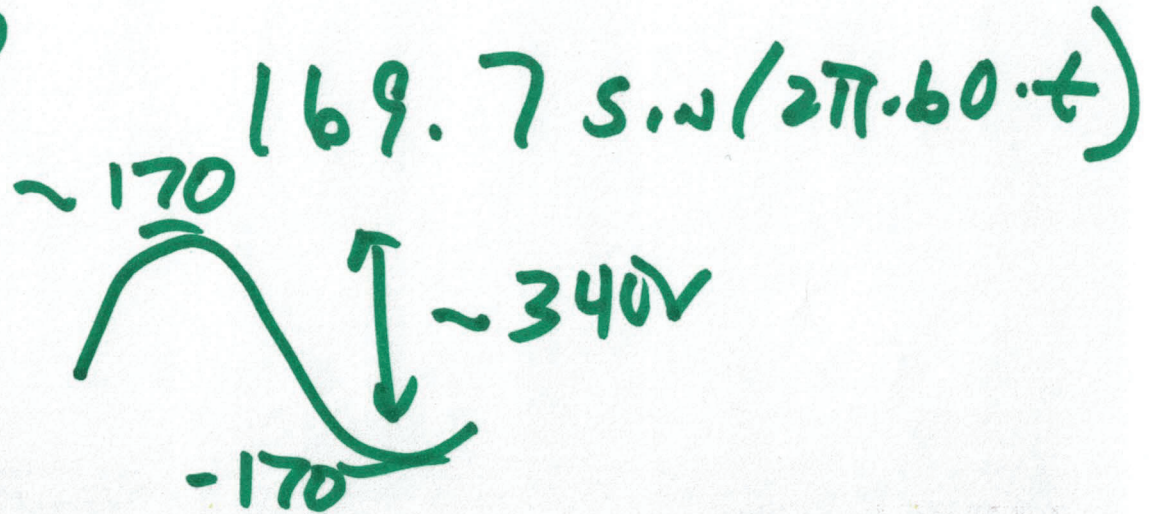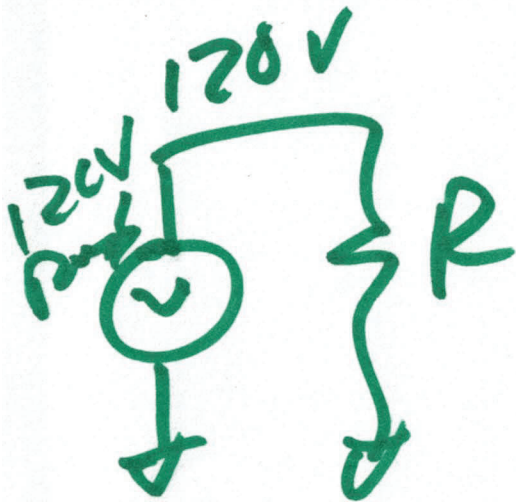


IMAGINARY

NUMBERS
SIGNALS


Represent delay
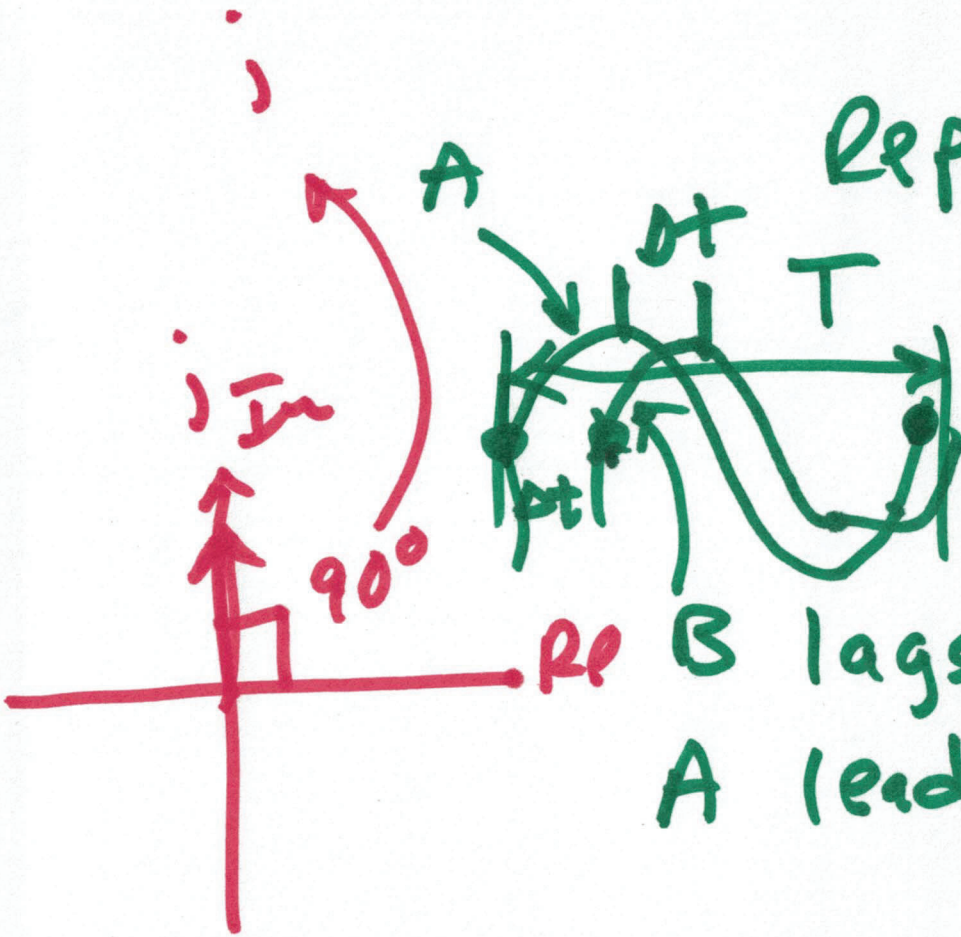
$$\theta = \frac{\Delta t}{T} \cdot 360$$



B lags A → phase shift is negative
A leads B → phase shift is positive

$i = ?$

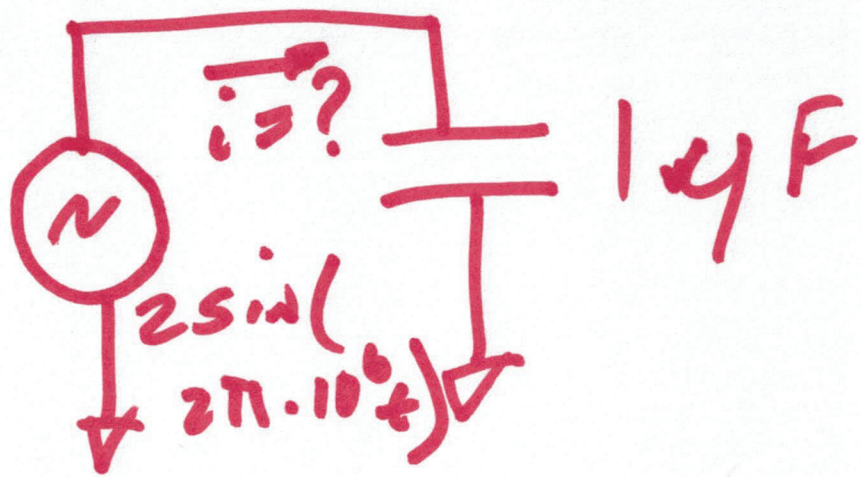


$$v_c = 2 \sin(2\pi 10^6 \cdot t)$$

$$1 \text{ MHz} = 10^6$$

$$i = 1 \mu F \cdot \frac{d(2 \sin(2\pi 10^6 t))}{dt} = C \cdot \frac{dv_c}{dt}$$


$$= 1 \mu F \cdot 2 \cos(2\pi 10^6 t) \cdot 2\pi 10^6$$

$$= 4\pi \sin(2\pi 10^6 t - 90^\circ)$$

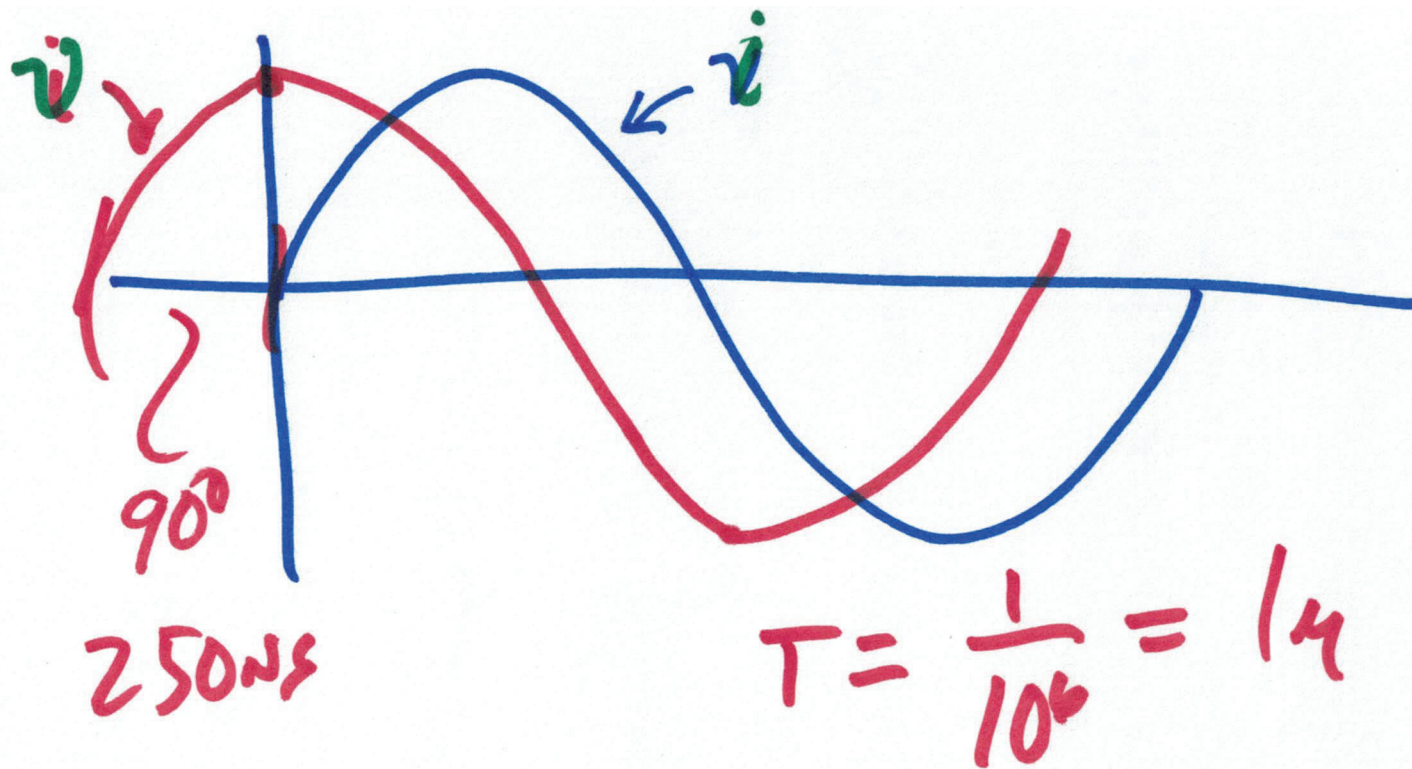

$$Z_c = \frac{1}{j \cdot 2\pi \cdot f \cdot C} = \frac{V_c}{I_c}$$
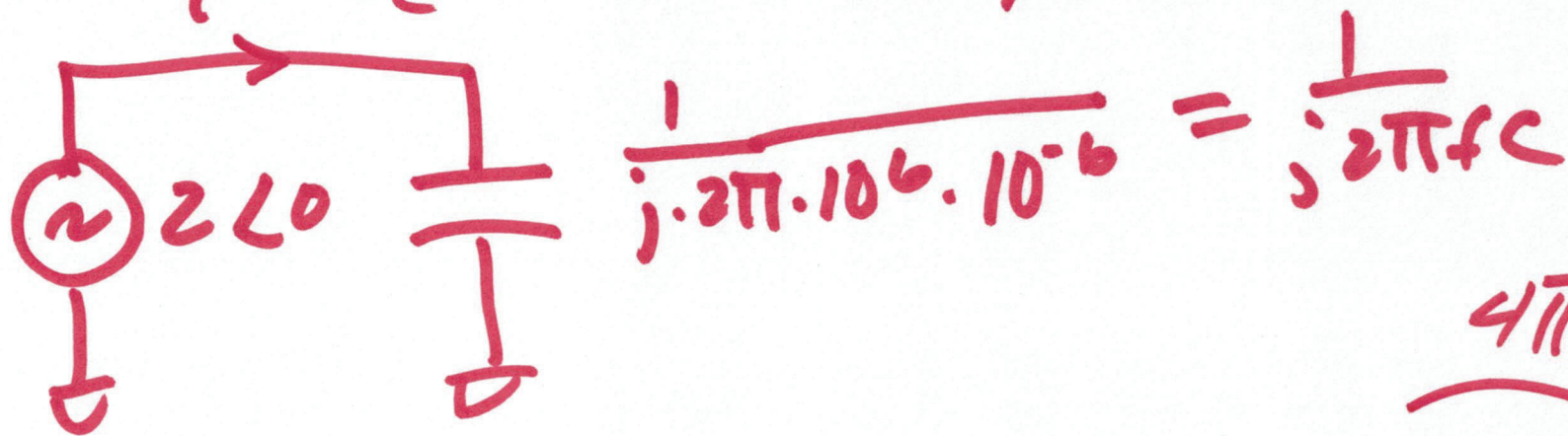
$$V_c = I_c \cdot Z_c, \quad I_c = j \cdot 2\pi \cdot f \cdot C \cdot V_c$$




$$I_c = \frac{V_c}{Z_c} = \frac{2L0}{\frac{1}{j \cdot 2\pi \cdot f \cdot C}} = \frac{2 \cdot 2\pi \cdot f \cdot C \cdot V_c}{1}$$

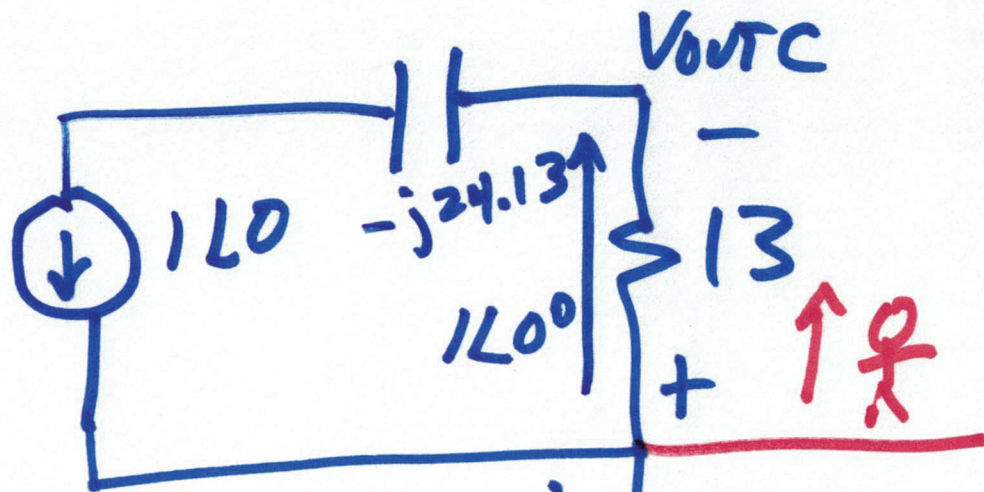5)

$$i_c = 4\pi \cdot i \Rightarrow 4\pi \angle 90$$

$$i_c = 4\pi \sin(2\pi \cdot 10^6 \cdot t + 90)$$



$$\frac{1}{j} \cdot \frac{j}{j} = \frac{j}{-1} = -j$$


$$j \cdot j = \sqrt{-1} \cdot \sqrt{-1} = -1 = 13 \sin(2\pi \cdot 60t + 180)$$

$$= 13 \sin(2\pi \cdot 60t - 180)$$

$$Z_C = -j \cdot \frac{1}{2\pi \cdot 60 \cdot 1104}$$

$$-1L0 \cdot 13 = V_{outC}$$
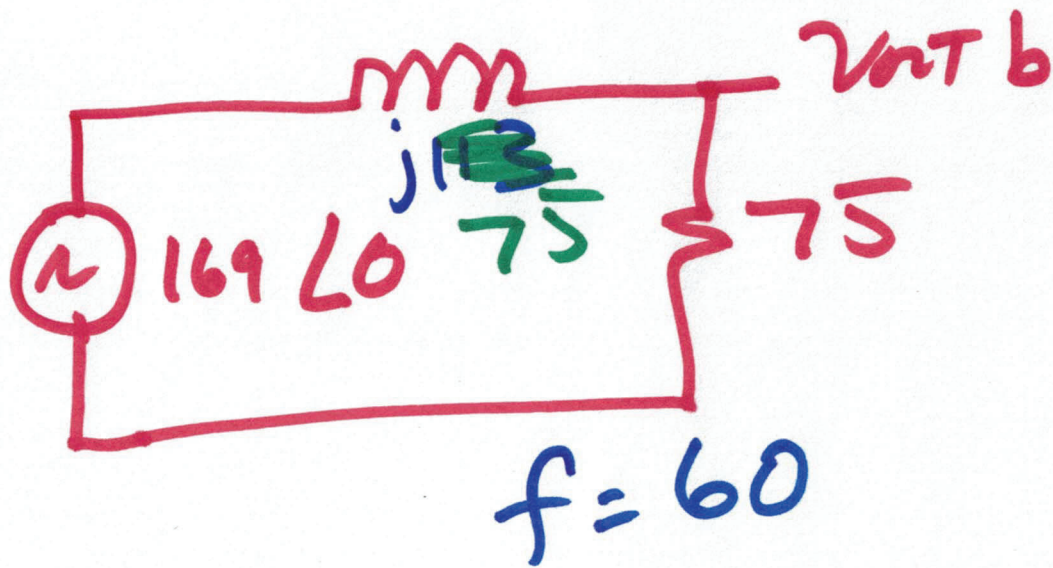
$$V_{outC} = 13 \sin(2\pi \cdot 60 \cdot t)$$



$$Z_L = j \cdot 2\pi \cdot f \cdot L$$

$$= j \cdot 2\pi \cdot 60 \cdot 0.2$$

$$v_{out b} = 169 \angle 0 \cdot \frac{75}{75 + j\omega L}$$

$$= 169 \angle 0 \cdot \frac{75 \angle 0}{75 \angle 0 + j75 \angle 90}$$

$$|x + jy| = \frac{\sqrt{x^2 + y^2}}{\sqrt{x^2 + y^2}} \angle \tan^{-1} \frac{y}{x}$$

$$\frac{\sqrt{(75)^2 + (75)^2}}{75\sqrt{2}} \angle \tan^{-1} \frac{75}{75}$$

$$Z_{inTb} = \frac{169 \angle 0 \quad \cancel{75 \angle 0}}{\cancel{75} \sqrt{2} \cdot \angle 45^\circ}$$

$$Z_{inTb} = \frac{169}{\sqrt{2}} \angle -45^\circ$$