


360 = 2π EE 2201 Circuits II

120 = $\frac{2}{3}\pi$

240 = $\frac{4}{3}\pi$

Lecture 9

Feb. 15, 2023

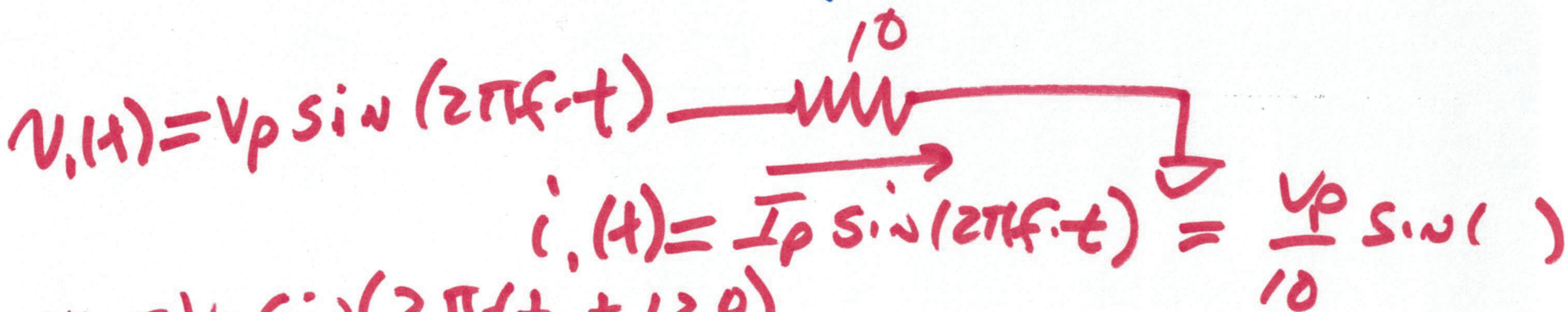

$P_1(t) = v_1(t) \cdot i_1(t)$

$^+ P_2(t) = v_2(t) \cdot i_2(t)$


$^+ P_3(t) = v_3(t) \cdot i_3(t)$

$$e^{jx} = \cos x + j \sin x$$

Euler's formula

$$\cos x = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin x = \frac{e^{jx} - e^{-jx}}{2j}$$

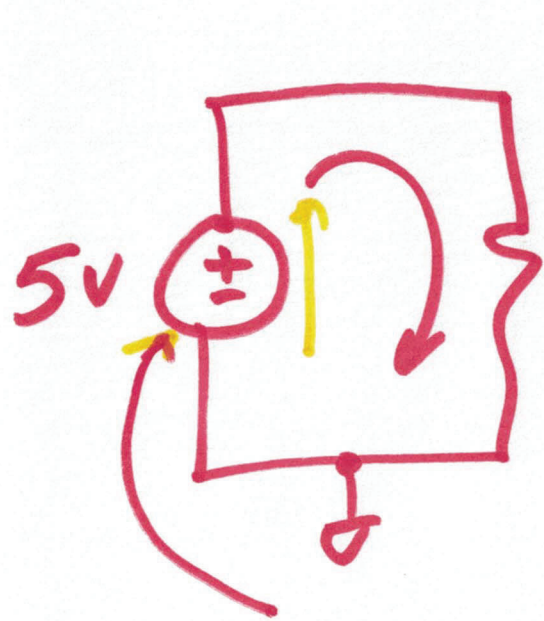



$$5\text{mA} \cdot V_I = 5.5\text{mA} = 25\text{mW}$$


$$- \frac{V^2}{R} = \frac{5^2}{1\text{k}} = 25\text{mW}$$

$$I^2 R = (5\text{mA})^2 \cdot 1\text{k} = 25\text{mW}$$

$$5 \cdot \sqrt{2} \sin(2\pi f \cdot t)$$

V_p

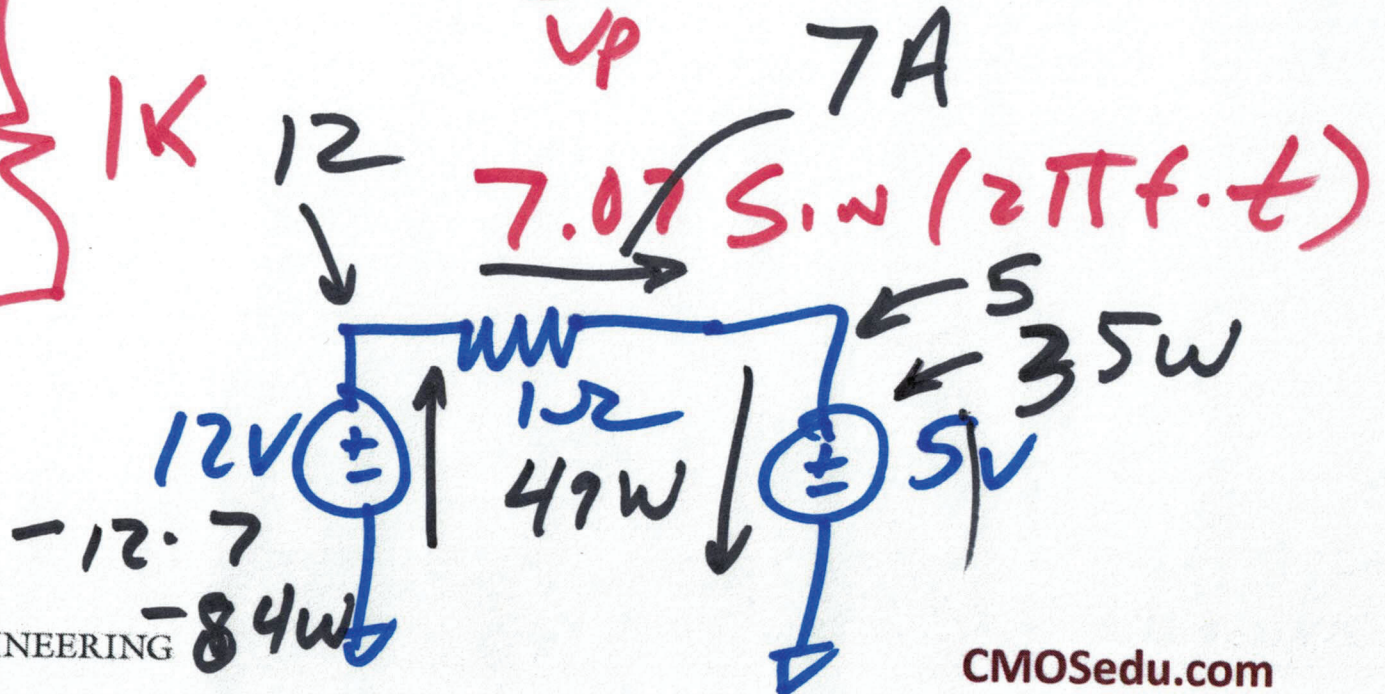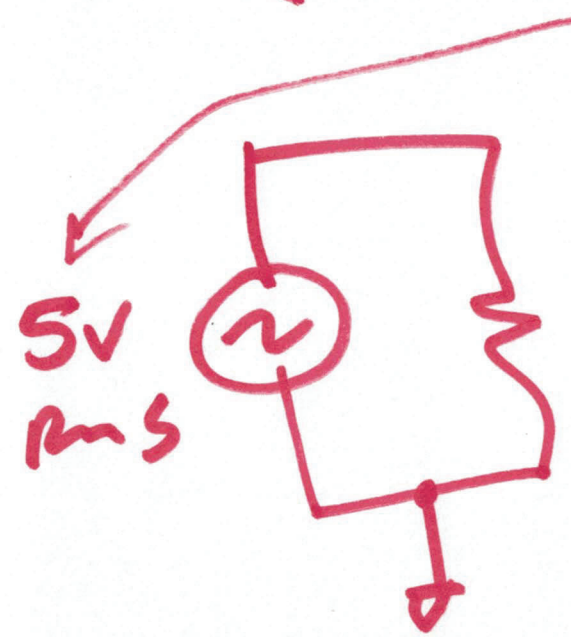

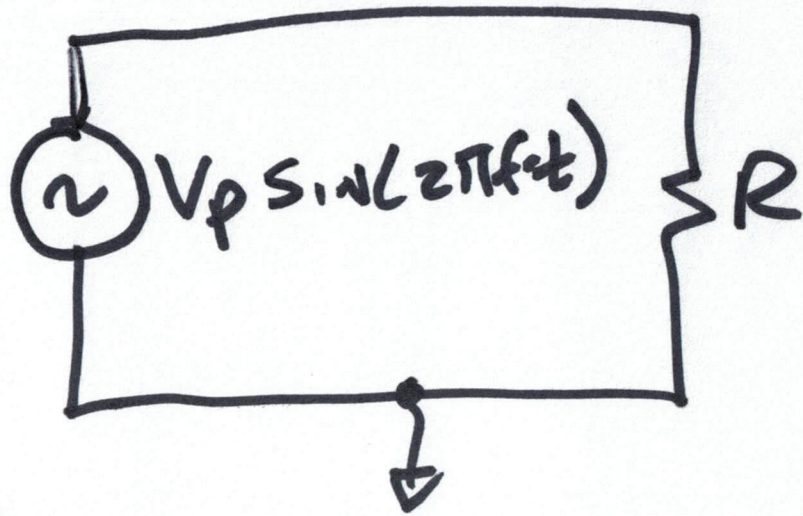

$$P(t) = V(t) \cdot I(t)$$

INSTANTANEOUS
POWER



MEAN

SQUARE
ROOT

$$\sqrt{\frac{1}{T} \int_0^T V_p^2 \sin^2(2\pi ft) dt}$$

$$V_{RMS} =$$



$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

$$\sqrt{\frac{V_p^2}{T} \int_0^T \frac{1 - \cos 4\pi f \cdot t}{2} dt}$$


$$\sqrt{\frac{V_p^2}{T} \left[\int_0^T \frac{1}{2} dt - \int_0^T \frac{\cos 4\pi f t}{2} dt \right]}$$


$\frac{1}{2}(T-0)$

$f = \frac{1}{T}$
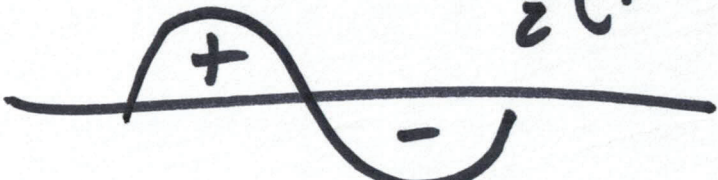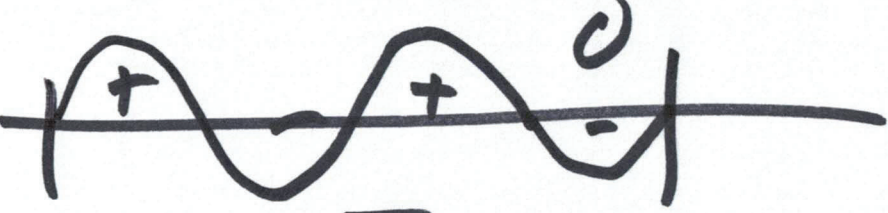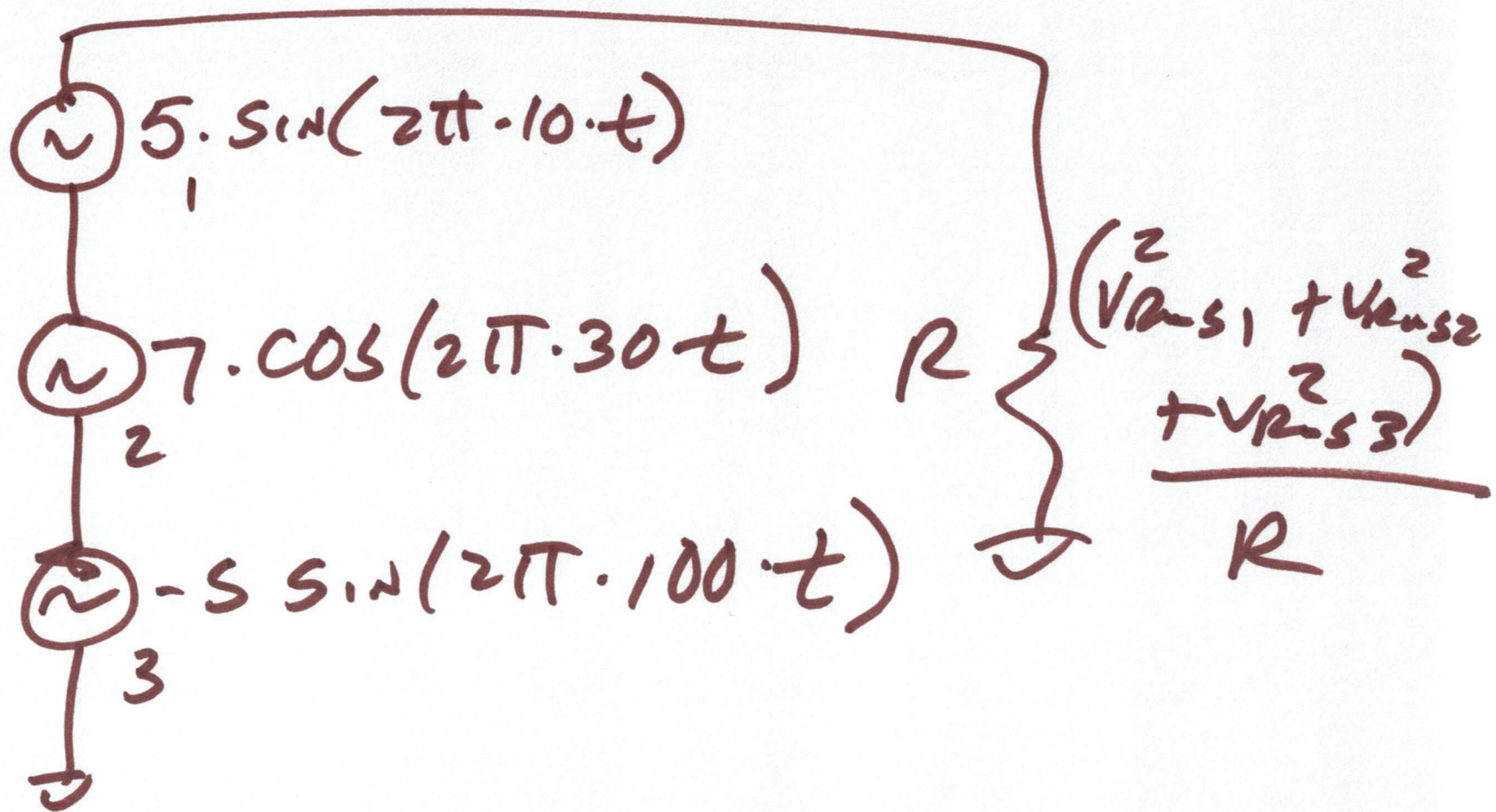
$$\sqrt{\frac{V_p^2}{T} \cdot \frac{T}{2}} = \frac{V_p}{\sqrt{2}} = V_{RMS}$$




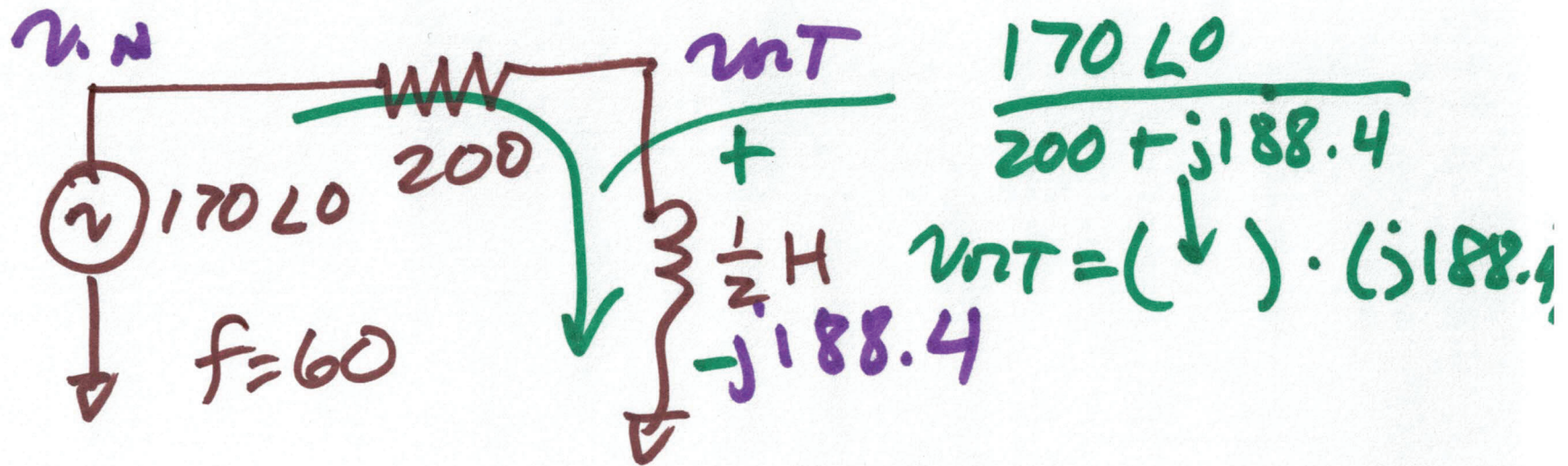
$$\begin{aligned}
 v_L &= 170 L_0 \cdot \frac{j188.4}{200 + j188.4} \\
 &= \frac{170 L_0 \cdot 188.4 \angle 90^\circ}{275 \angle 43.3^\circ}
 \end{aligned}$$

$$v_L = 116.5 \angle 46.7^\circ$$

$$46.7 = 360 \cdot \frac{+1}{16.67\%}$$

$$t_d = 2.16 \mu s, T = 16.67 \mu s$$

$$v_{out} = 116.5 \sin(2\pi \cdot 60 \cdot t + 46.7^\circ)$$

