Quiz #2 EE 221 Spring 2023
 Name:

 Closed book and notes.
 Show your work for credit and place a box around each of your answers.

1. In the following circuit find the currents in the directions indicated and V2 using mesh analysis. (4 points)

