

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Find the AC **current** (an equation in the time-domain) that flows in the following circuit and V_{out} (again an equation in the time-domain) and sketch both, along with V_S , to show the magnitudes and phase shift. (4 points)

