

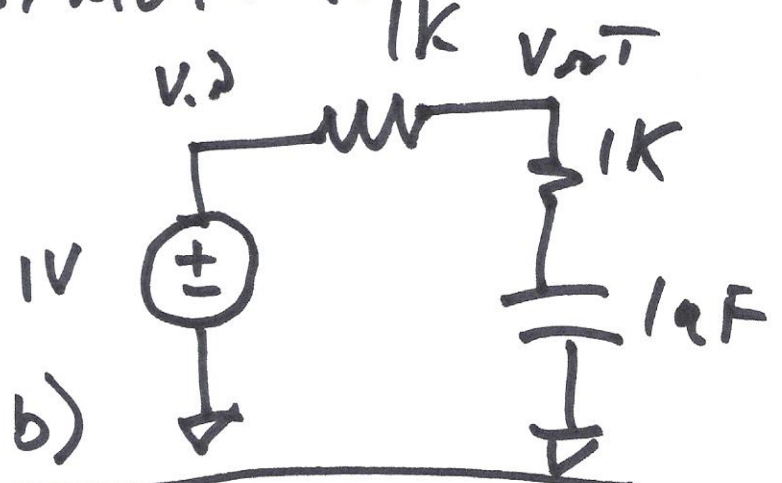


For the following circuits

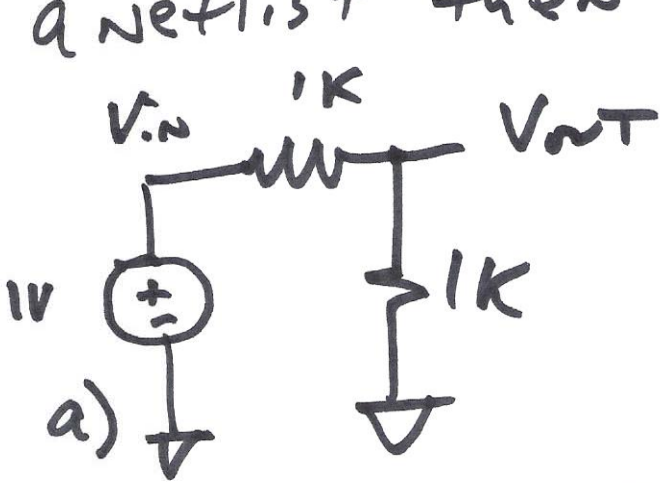use a text editor to hand-write a netlist then simulate.



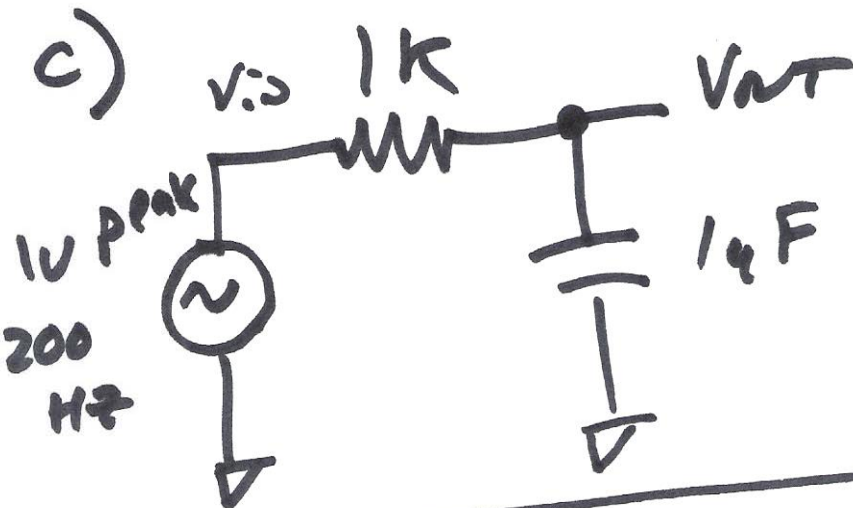a) & b) are DC circuits so use .op or .tran 1



$$\frac{1}{200} = 5\text{ms}$$

$$= 5 \times 10^{-3}$$

for c) use .tran 20us
 ↗
 4 cycles