

# H.W. # 4

For the following problems assume  $A_{OL} = 750 \frac{V}{V}$  and  $V_{OS} = \pm 15mV$ .

1) Find  $V_{OUT}$  in each circuit.  
Show your hand calculations  
Verify your answer with LTSpice

