
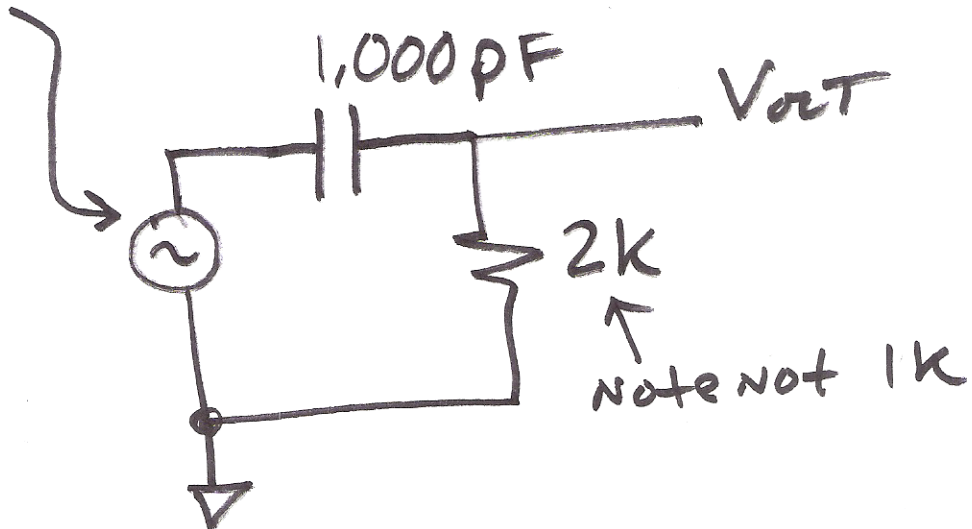


H.W. #5 EE 320 Spring 2013

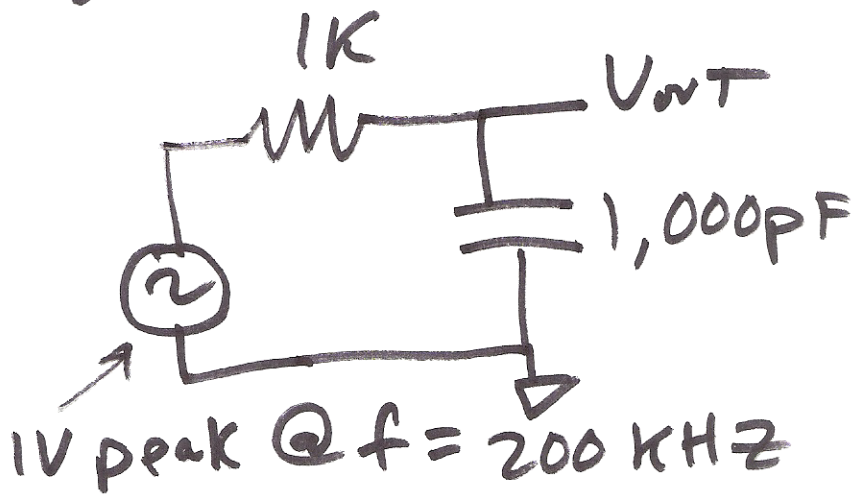1) find V_{out} and plot with V_{in}
 verify your hand calculation with LTSPICE.
 plots are in the time domain.



2) What is the BW of the following circuit. Assume op-amp Gain.BW = 1 MHz.

