


Feb. 26, 2014

Lecture 10

EE 320

Electronics

$$\Delta t < \frac{1}{60}$$

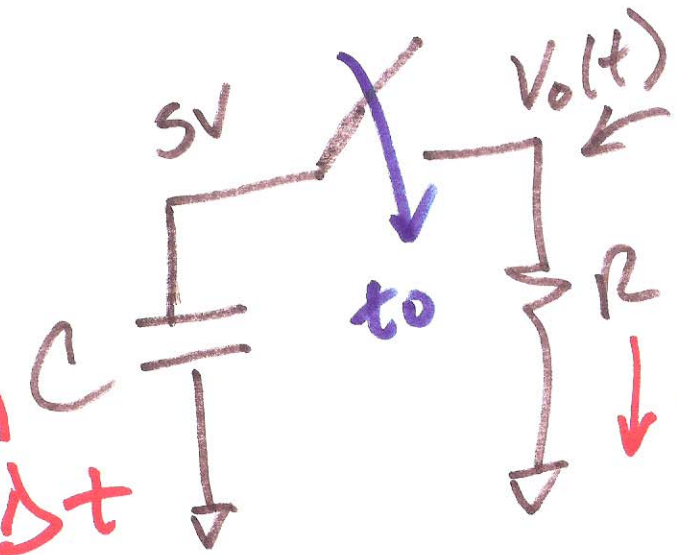


$$\Delta V_o = \frac{V_{OOC}}{RC} \cdot \Delta t$$

$$\frac{5}{R} = I_{CONST}$$


$$\Delta V_o = \frac{V_{OOC}}{RC} \cdot \Delta t$$

$$I = C \frac{dV}{dt}$$
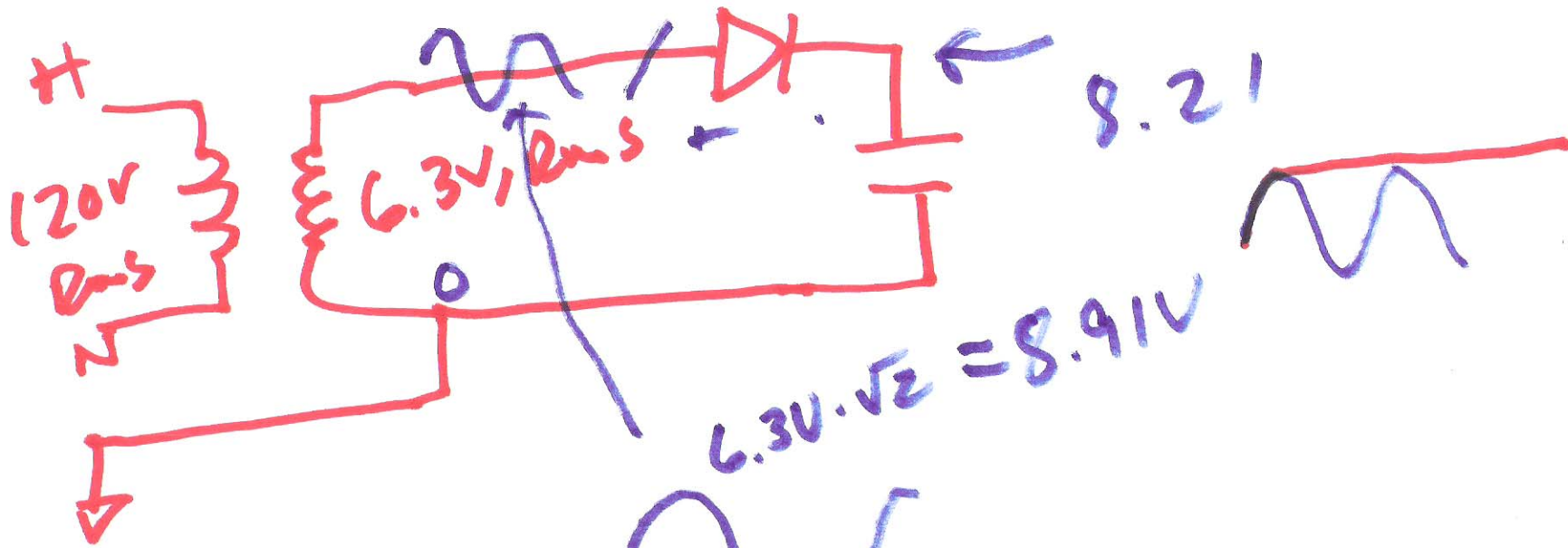
$$\frac{V_{OOC}}{R} = C \frac{\Delta V_o}{\Delta t}$$




$$6.3V \cdot \sqrt{2} = 8.91V$$

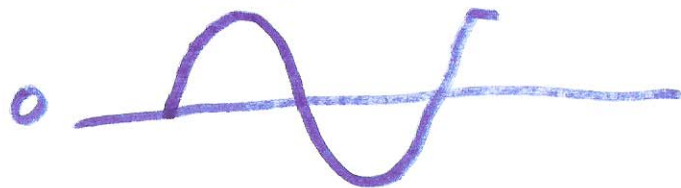

$$V_{pp} = 2 \cdot 6.3V \cdot \sqrt{2} = 17.82$$

$$T = 16.67ms \quad f = 60Hz$$

2)

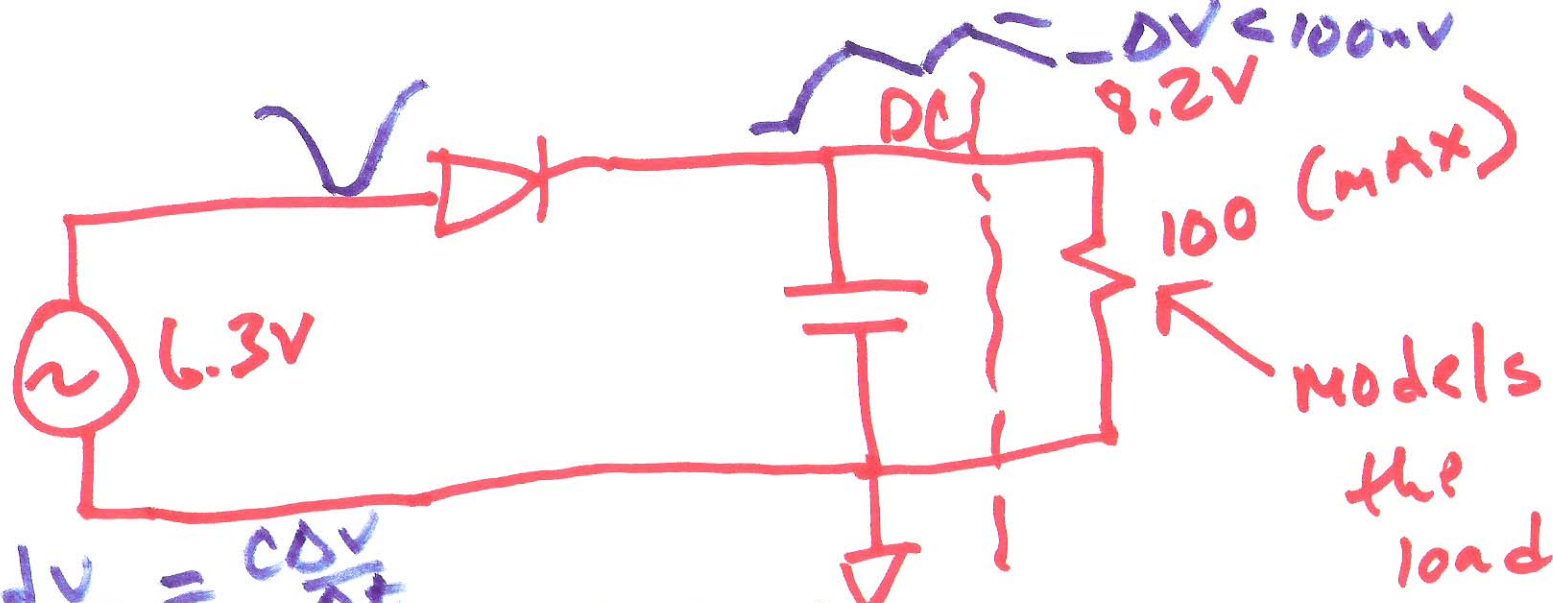

$$I = C \frac{dv}{dt} = \frac{C \Delta V}{\Delta t} \quad \Delta V < 100 \text{mV}$$



$$\frac{8.2}{100} \cdot \frac{\Delta t}{C} = \Delta V$$

$$C \geq \frac{8.2 \text{V} \cdot \frac{16.67 \text{ms}}{100 \Omega}}{100 \text{mV}} = 13.7 \text{mF}$$

↓
milliFarad
10⁻³


$$\Delta t = 16.67 \text{ms}$$
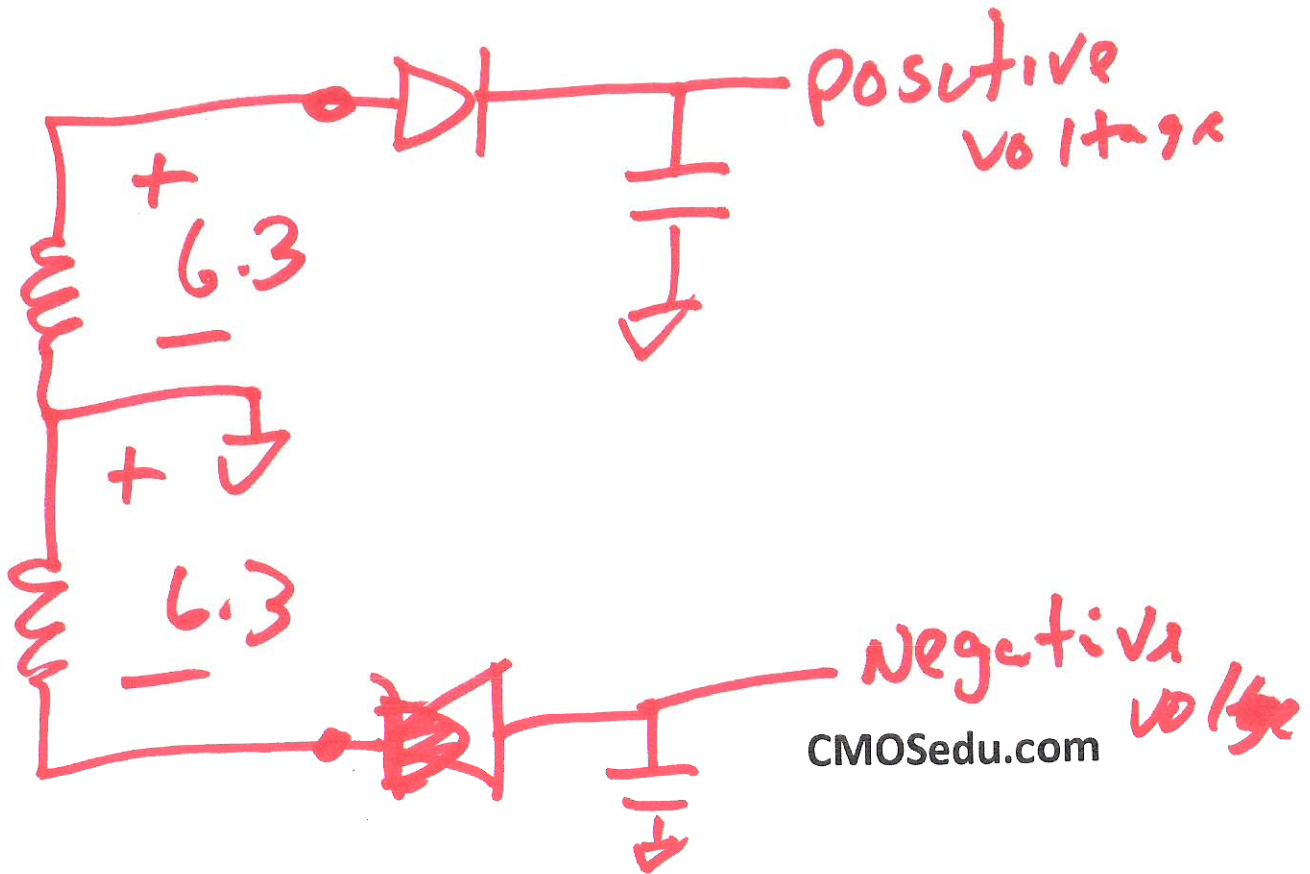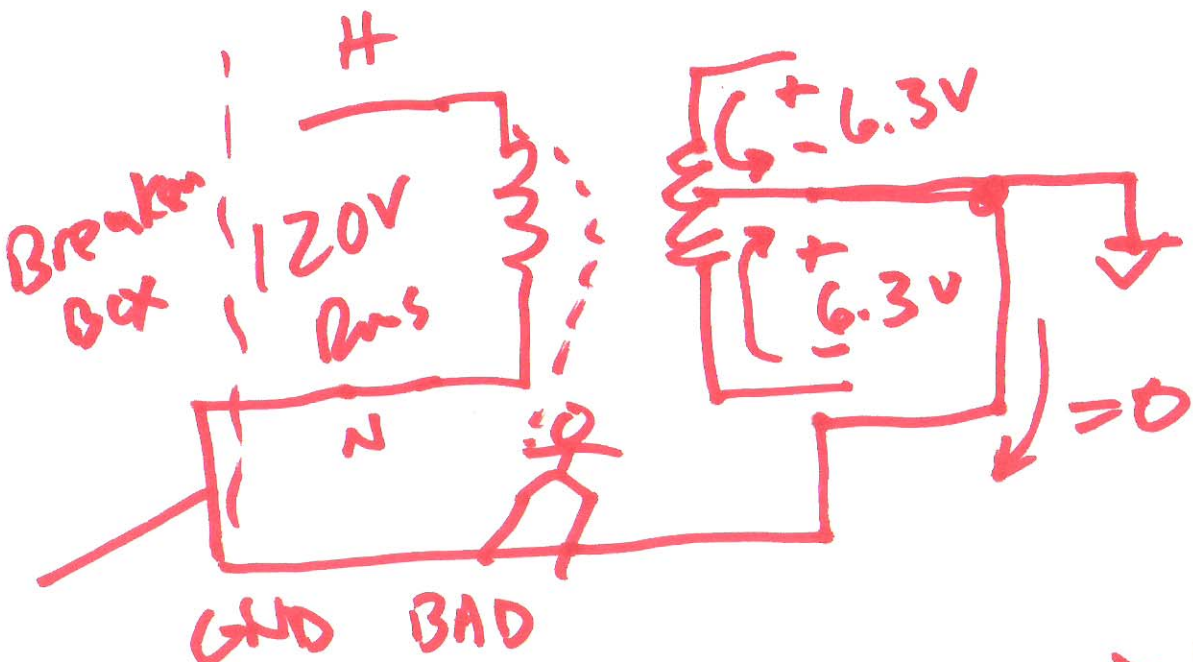
$$\frac{8.2}{100} = I_{\text{max}} = 82 \text{mA}$$



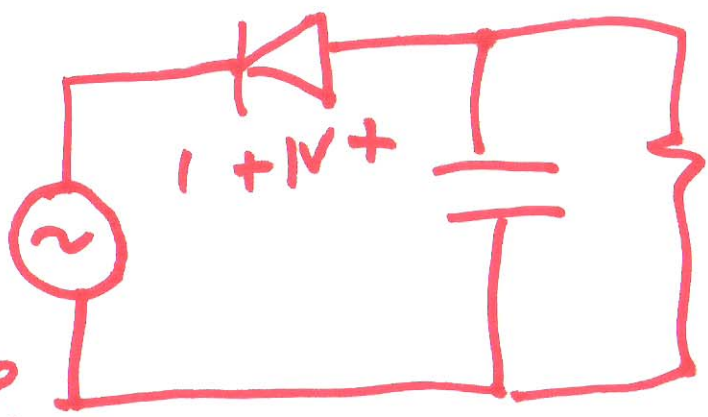4)

$12.6V \pm 10\%$
 $12.6 + 1.26 = 13.86$
 $12.6 - 1.26 = 11.34V$




$\underline{\underline{-18.6V}}$
 $\underline{\underline{-15.03}}$

$\text{peak} = 19.6 \rightarrow 18.6$

$M.V = 16.03 \rightarrow 15.03$

5)

Full-wave rectifier

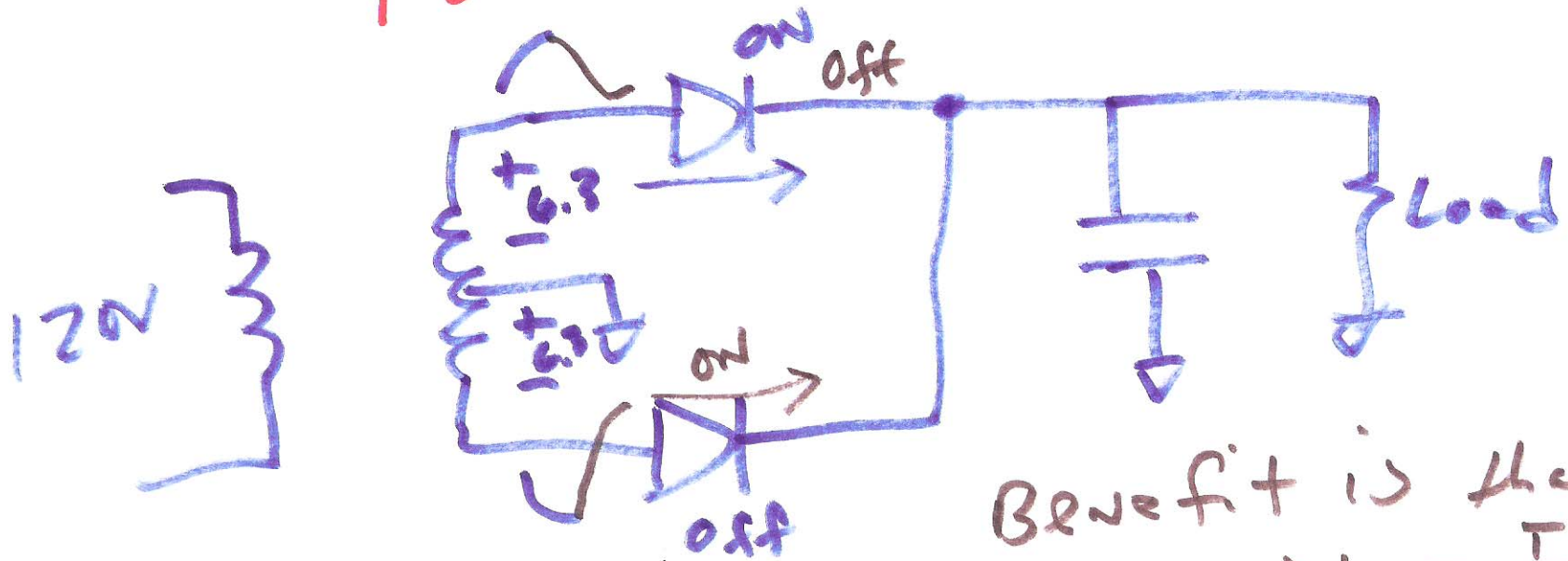


Benefit is that
now $\Delta t = \frac{T}{2}$

$$\Delta t = \frac{16.67 \text{ ms}}{2}$$
$$= \underline{\underline{8.35 \text{ s}}}$$


6)

Full-wave rectifier

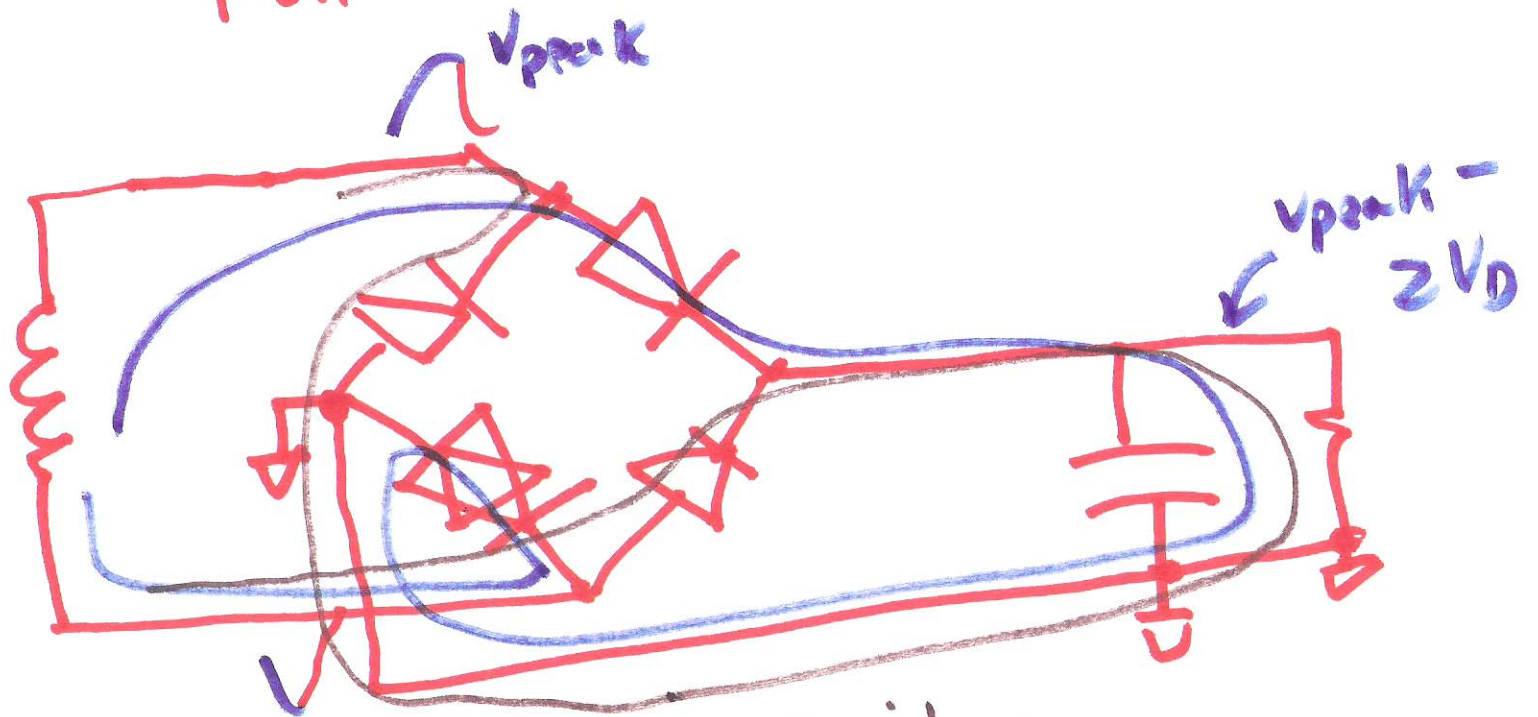


Diode Bridge




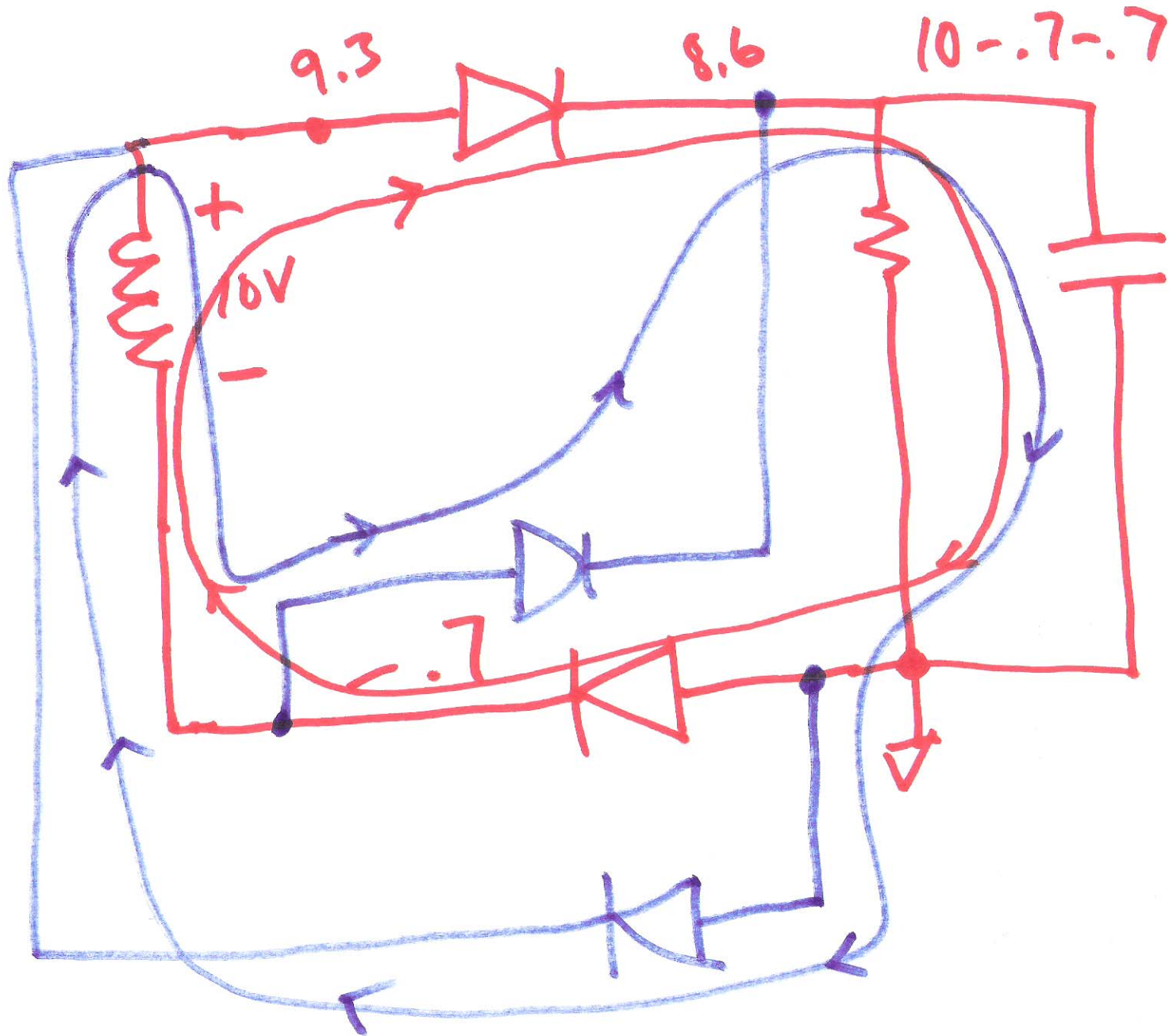

8)

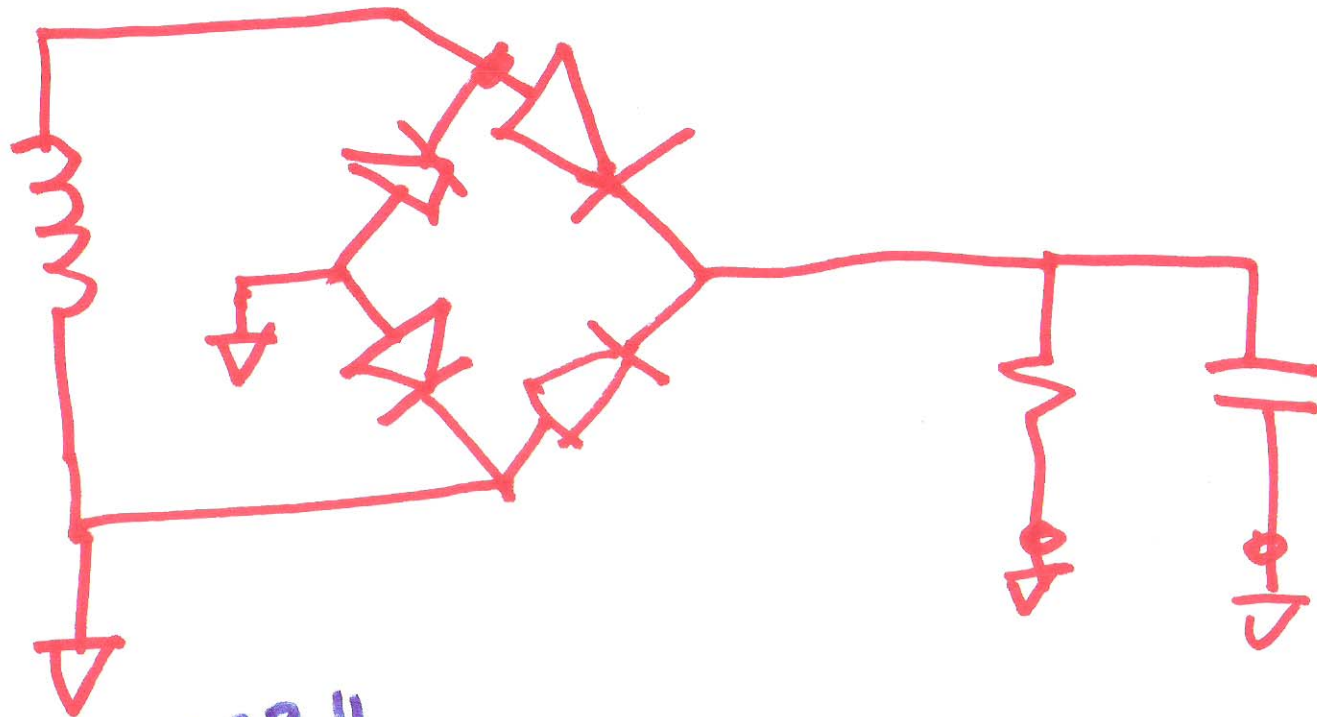


SUMMER 4

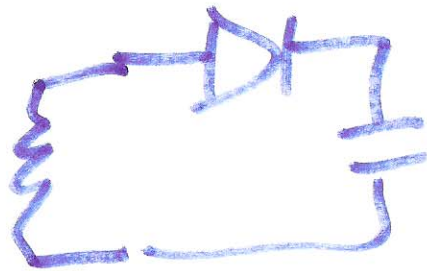

Half-wave
no-center tap
needs bigger cap

only one
diode
drop

Full-wave with center tap

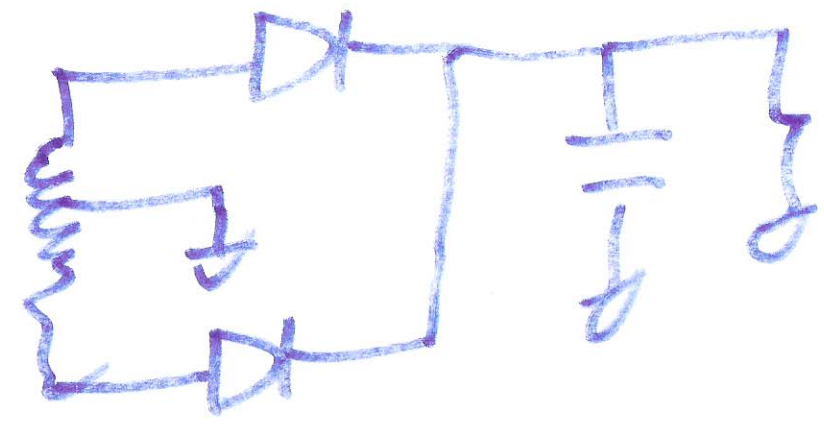


ONLY one diode drop

Need center tap

smaller cap

Bridge, 2 diode drops


no center tap XFR

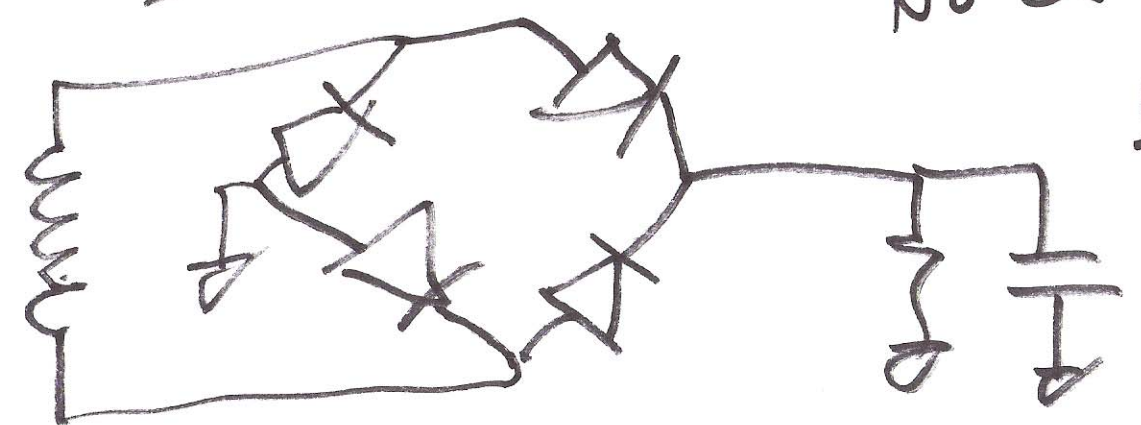

full-wave

10)

3.113

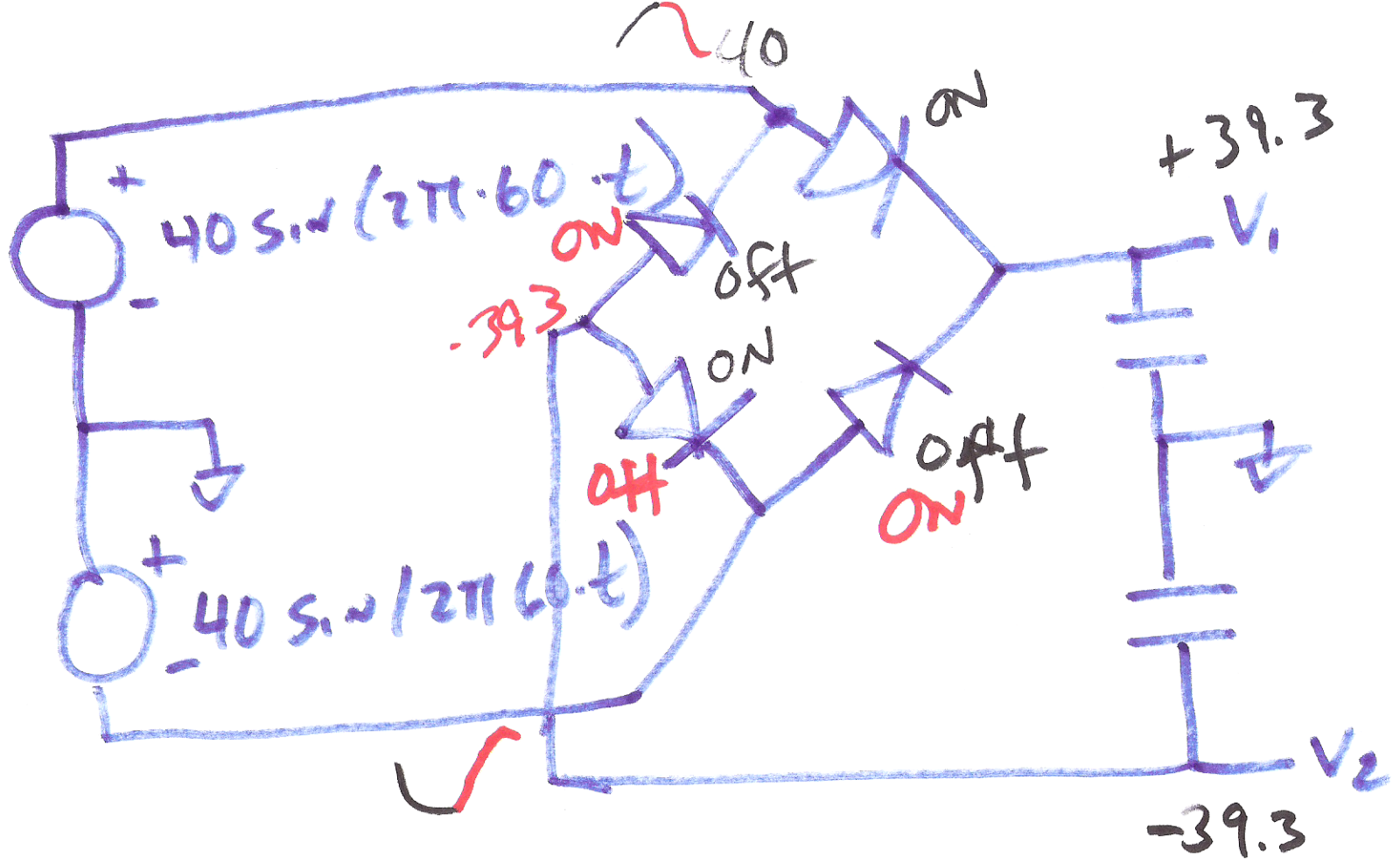

11)