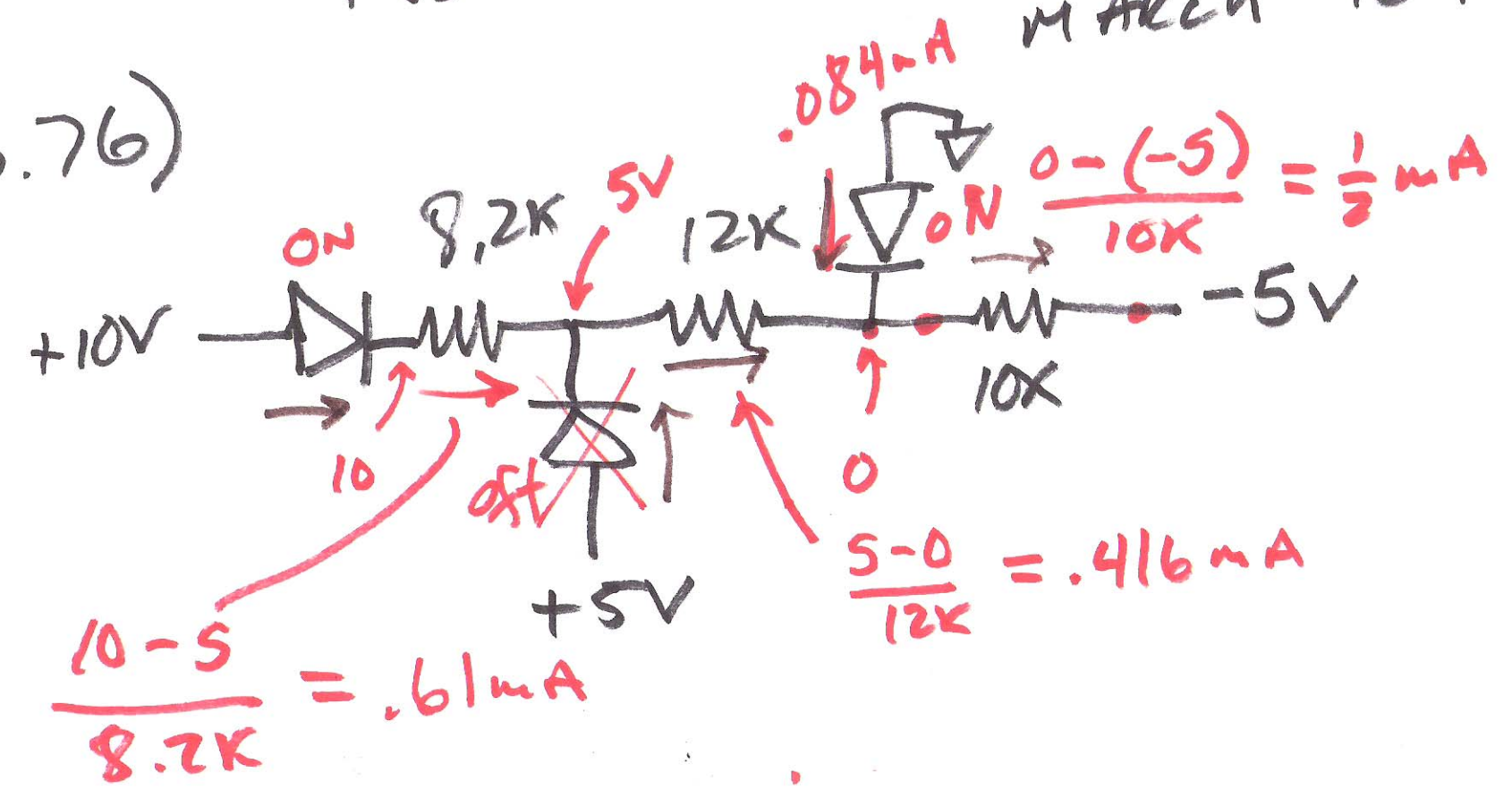



Lecture 12,
EE 320

March 5, 2014
Electronics

TEST ON MONDAY
MARCH 10!


3.76)



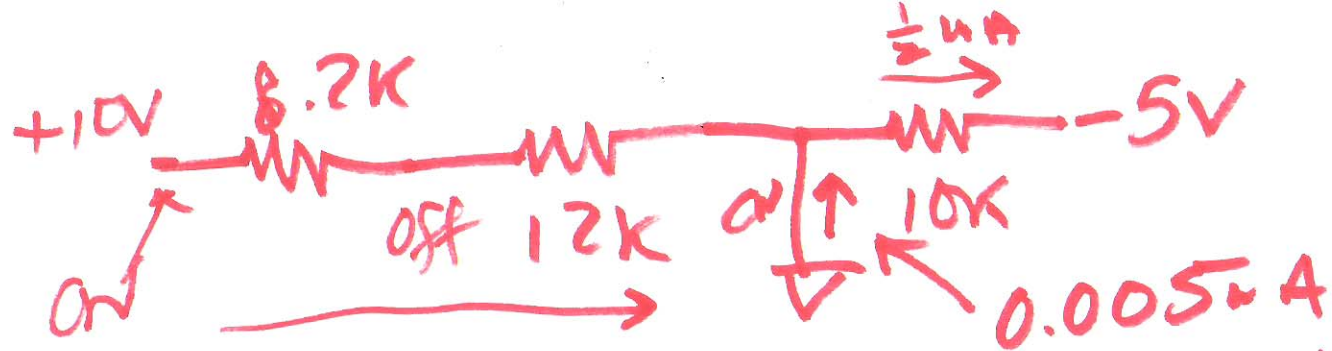

$$\frac{10 - 0}{20.2K} = .495 \text{ mA} = 5.941$$

$$10 - .495 \cdot 8.2K = 5.941$$

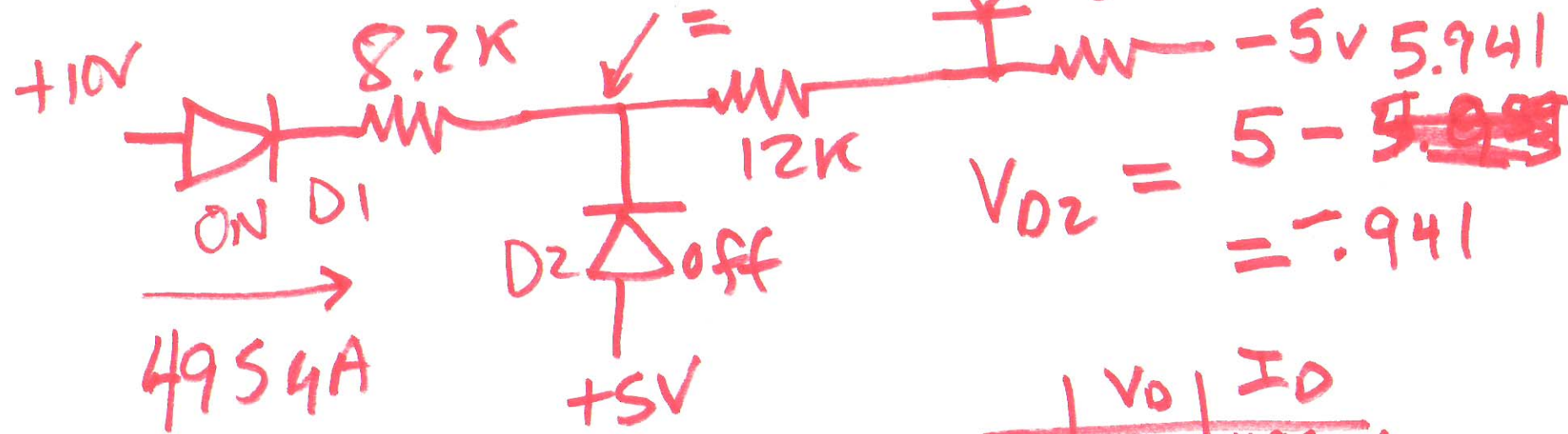


	V_0	I_0
D1	0	495 uA
D2	-0.941	0
D3	0	54 uA

2)



RC circuits

$$\theta = \frac{t_d}{T} \cdot 360$$

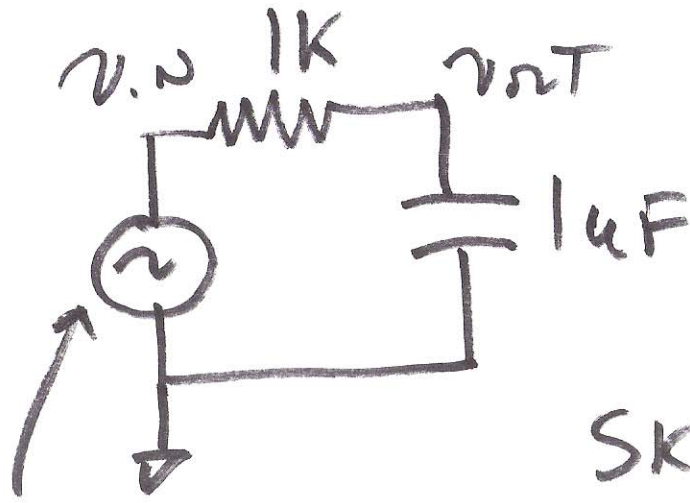



1V-peak
@ 175 Hz

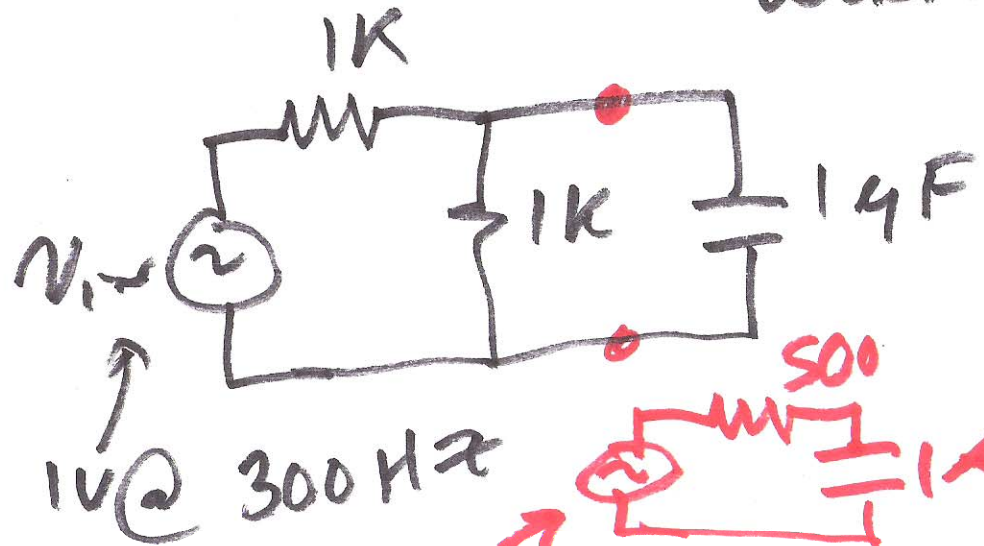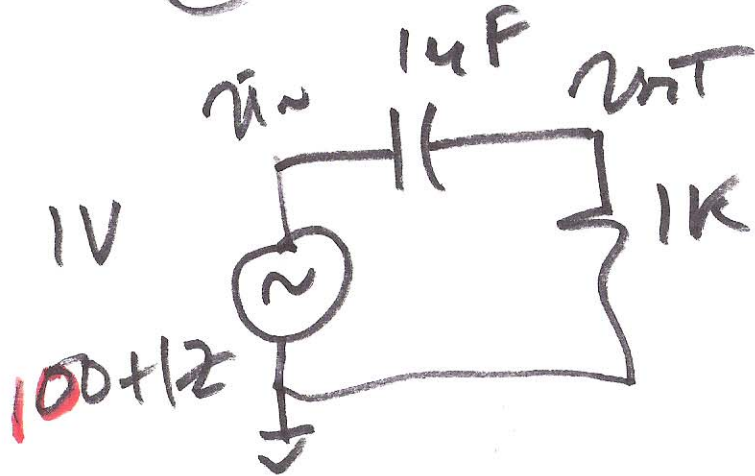Sketch v_{oT} & v_i on
the same plot
Show your
work!



1V @ 300 Hz

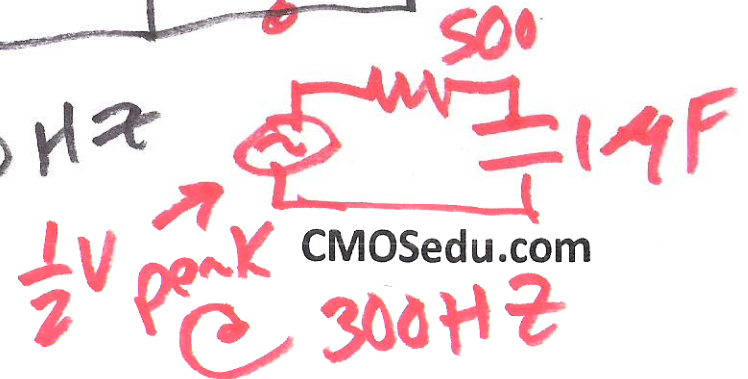

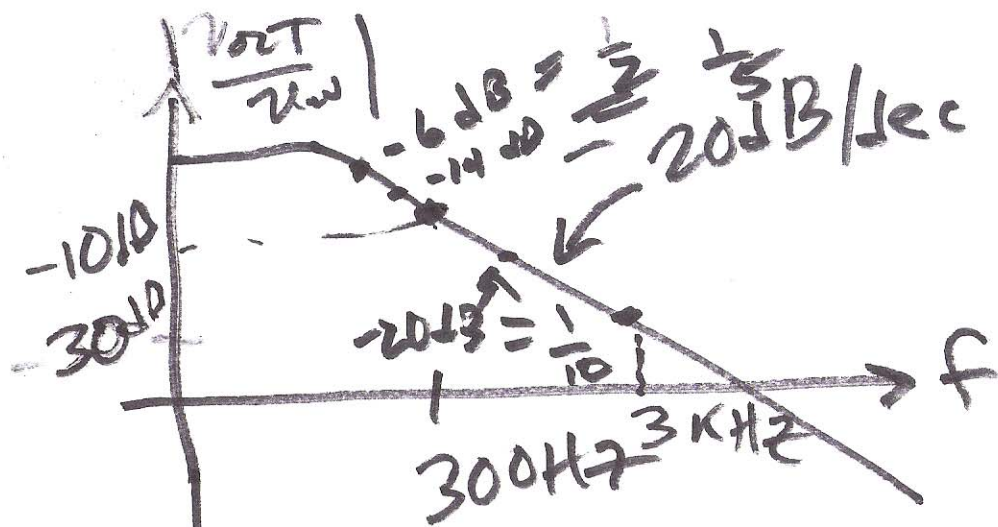

write a spice netlist



$$20 \text{ dB} \times 10$$

$$-20 \text{ dB} \div 10$$

$$1 \text{ dec.} \times 10$$

$$\text{Lower dec} \div 10$$

$$1.2 \text{ kHz}$$

↓ 1 decade above

$$12 \text{ kHz}$$

$$6 \text{ dB} \times 2$$

$$1 \text{ octave} \times 2$$

$$14 \text{ dB} \times 5$$

OP-Amp Circuits


Calculate $\frac{v_{out}}{v_{in}}$ for:

$A_{OL} = 250$

$V_{OS} = \pm 10 \mu V$

Calculate v_{out}


ideal op-amp
show your work

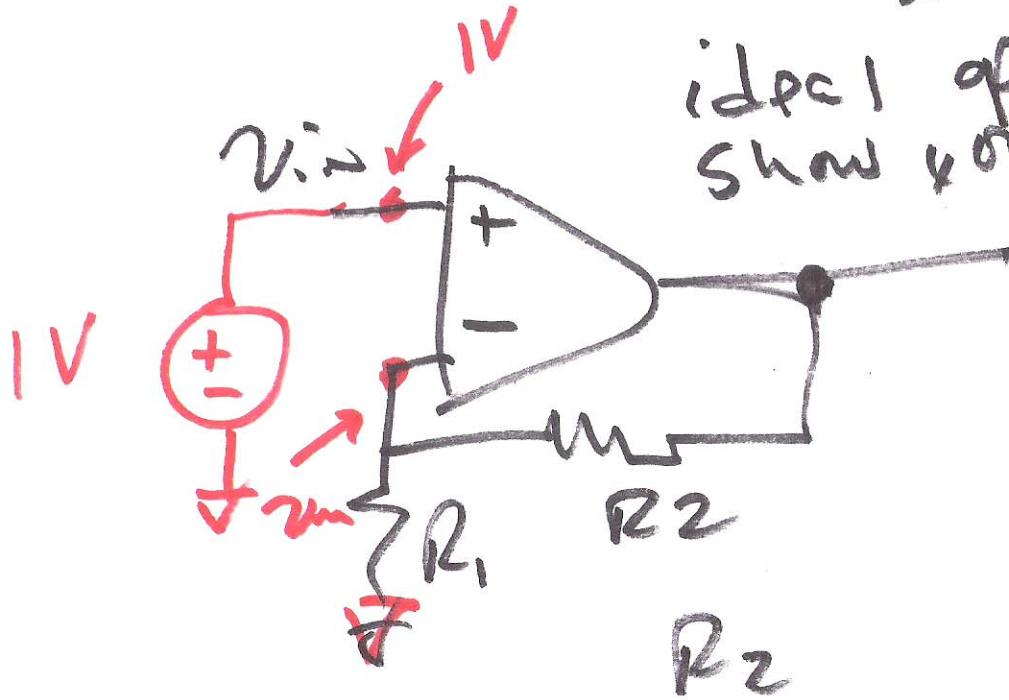


$v_{out} = A_{OL}(1 - \mu)$

$\frac{v_{out}}{v_{in}} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$

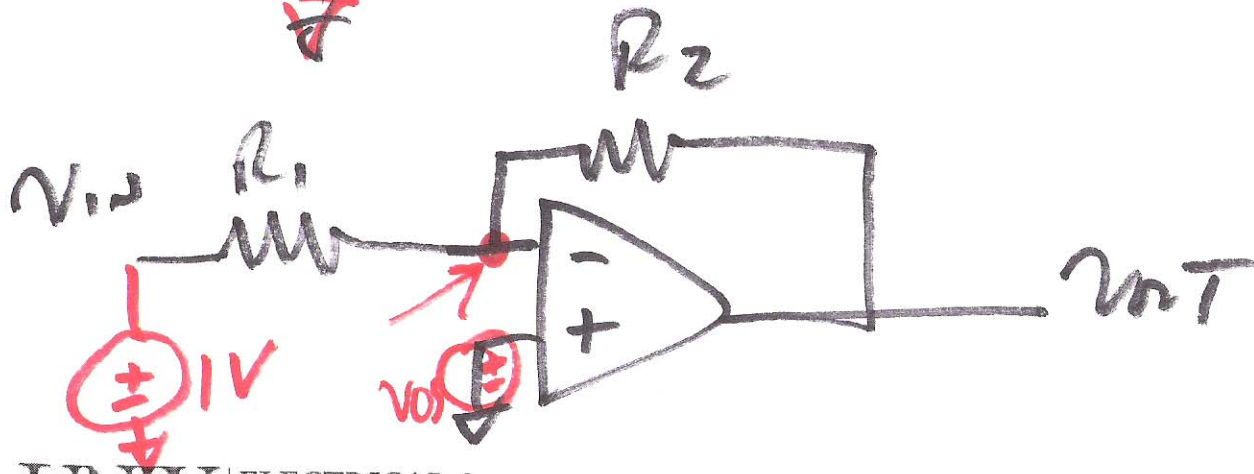$\frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1}$



5)

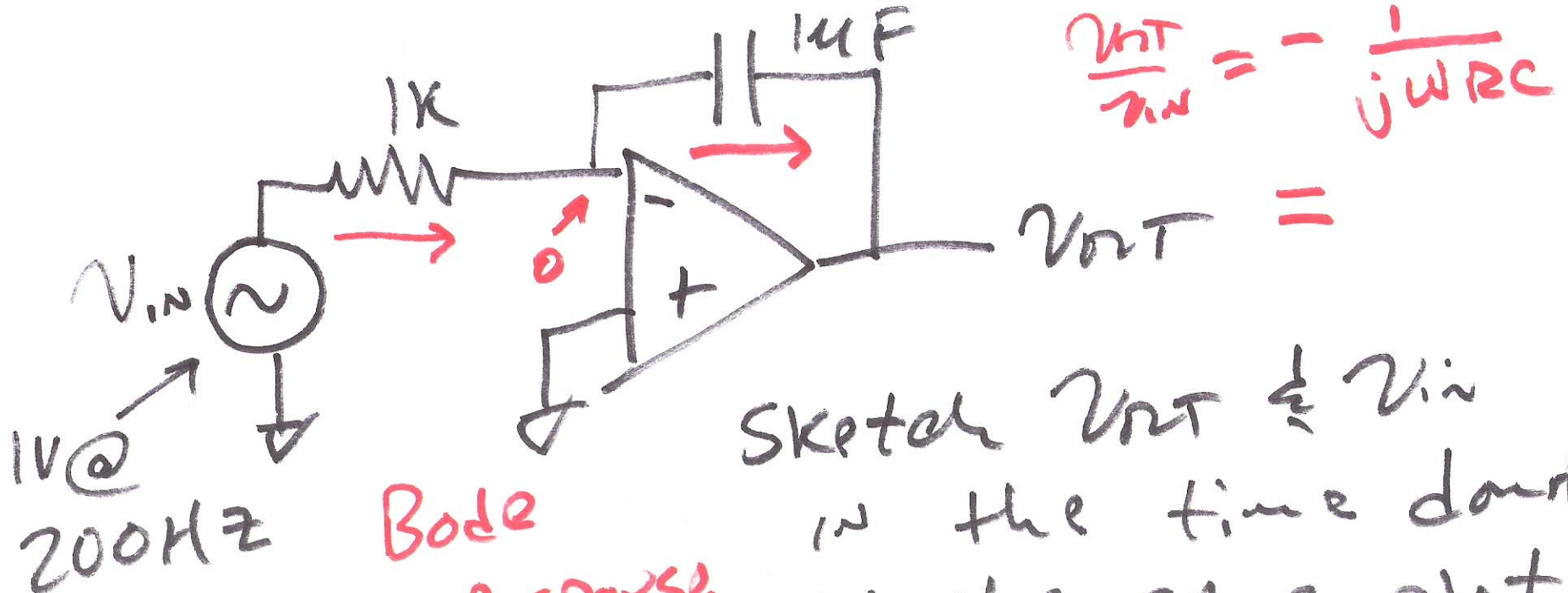

$$\frac{v_{OUT}}{v_{IN}} = -\frac{1}{j\omega RC}$$

v_{IN}
1V @
200kHz

Bode
Response

Sketch v_{OUT} & v_{IN}
in the time domain
on the same plot.

$$\frac{v_{IN} - 0}{1k} = \frac{0 - v_{OUT}}{\frac{1}{j\omega 10^{-6}}} = \frac{1}{2\pi f RC} = \frac{1}{\omega RC}$$

$$\left| \frac{v_{OUT}}{v_{IN}} \right| = \left| \frac{1 + j0}{0 + j \cdot 2\pi \cdot 200 \cdot 10^{-3}} \right| = \frac{\sqrt{1^2 + 0^2}}{\sqrt{0^2 + (1.256)^2}}$$

$$\left| \frac{v_{OUT}}{v_{IN}} \right| = 0.634$$

$$\textcircled{1} \frac{v_{out}}{v_{in}} = -\frac{1}{j\omega RC} \cdot \frac{j}{j} = 0 + j \cdot \frac{1}{\omega RC}$$

$$\angle a + jb \Rightarrow \tan^{-1} \frac{b}{a} \quad \angle \frac{v_{out}}{v_{in}} = \tan^{-1} \frac{1}{0} = 90^\circ$$

$$\angle \frac{1}{a + jb} \Rightarrow -\tan^{-1} \frac{b}{a}$$



$\textcircled{2}$

$$\frac{j}{\omega RC} \quad \begin{array}{c} \uparrow \\ 90^\circ \end{array}$$

$\textcircled{3}$

$$\frac{-1}{j\omega RC}$$


$$\Rightarrow \frac{180}{1 + j0} \quad \Rightarrow \frac{180 - 90}{0 + j\omega RC}$$

$$180 - 90 = 90^\circ \quad 90^\circ$$

$$= \tan^{-1} \frac{-1}{0} \Rightarrow -\tan^{-1} \frac{\omega RC}{0}$$

Semiconductors

→ H.W. & Quizzes

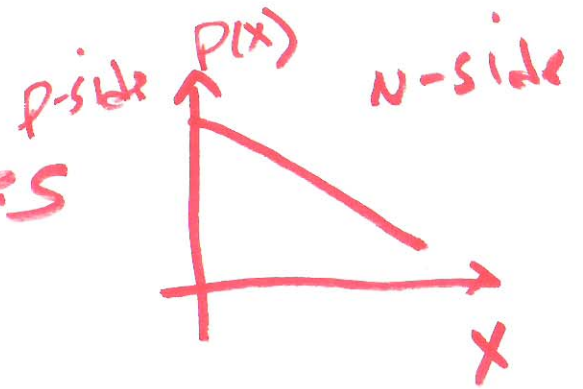


$Q = \frac{\text{Coulombs}}{\text{cm}^2}$
 $J = \frac{A}{\text{cm}^2}$
 $NA = 10^{16} \frac{\text{Atoms}}{\text{cm}^3}$

$\rho = \frac{1}{q \cdot p \cdot \mu_p + q \cdot n \cdot \mu_n}$
 $\rho = 10^{16} \text{ holes/cm}^3$
 Assuming complete ionization

$I_{\text{for applied } v}$
 $\mu_p = \frac{\text{Velocity, cm/s}}{E, \frac{V}{\text{cm}}}$
 $N = \frac{N_i^2}{P}$
 R
 $J = \frac{\text{cm}^2}{V \cdot s}$

8)

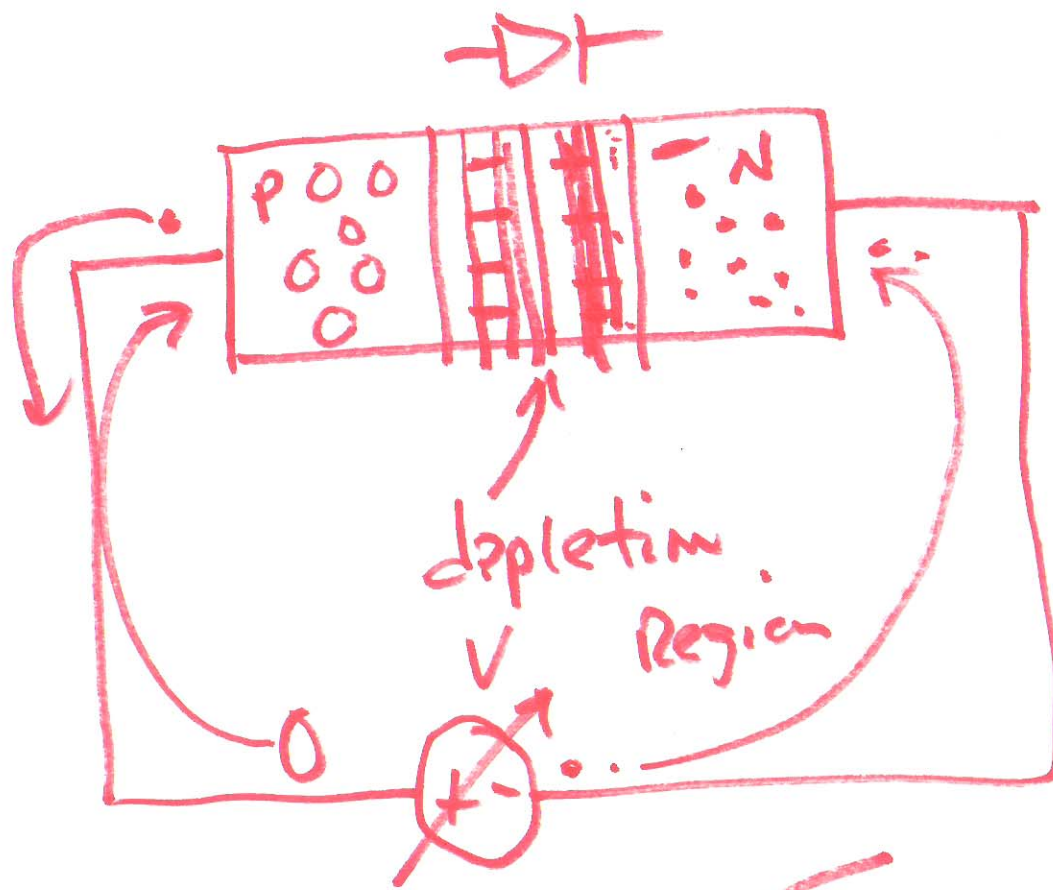

$$J_{p,diff} = q \cdot D_p \cdot \frac{dp}{dx}$$




diffusion
curr.

9)

Diodes


Study H.W. & Quizzes

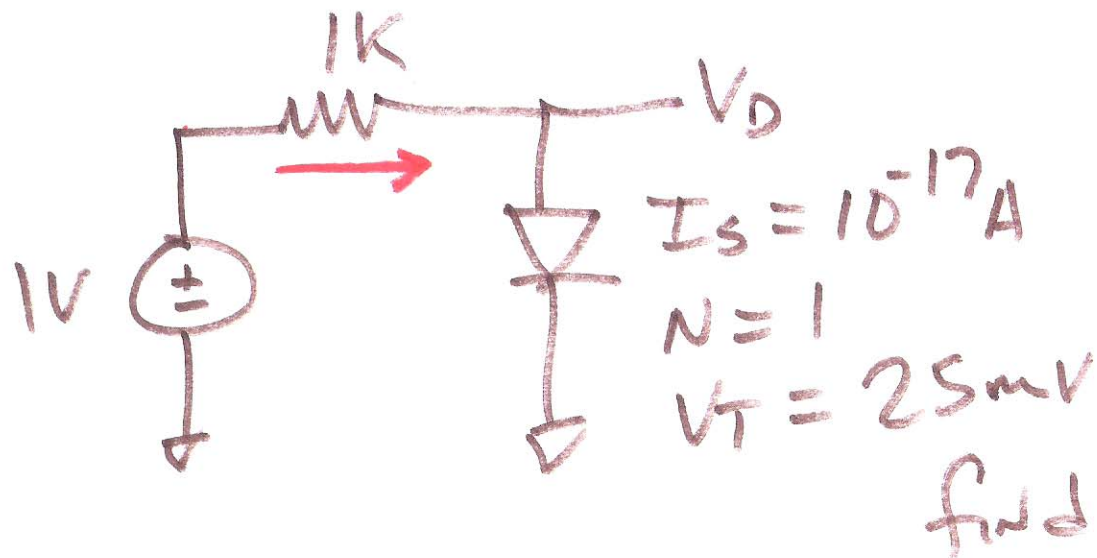

on the test:

$$I = \frac{1 - V_D}{1k}$$

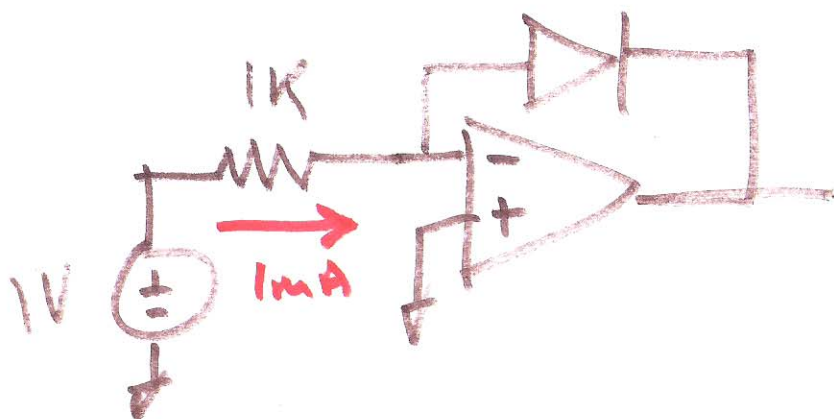
$$V_D = \frac{KT}{q} N \ln \frac{I_D}{I_S}$$



$$V_D = - \frac{KT}{q} \cdot N \cdot \ln \frac{I_D}{I_S}$$

$$= -25 \text{ mV} \cdot \ln \frac{10^{-3}}{10^{-17}}$$


=

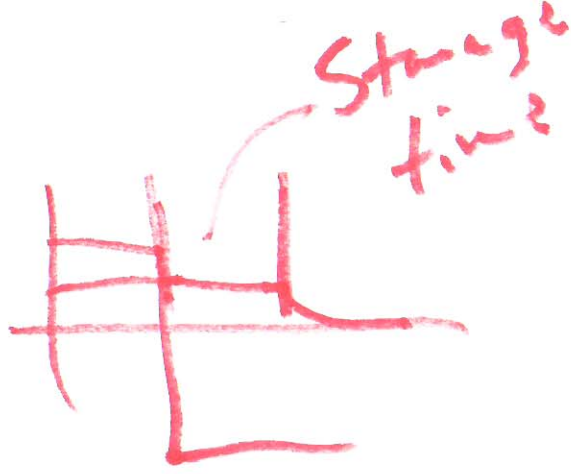

Rectifiers Basic operation

Selecting the

filter OAP

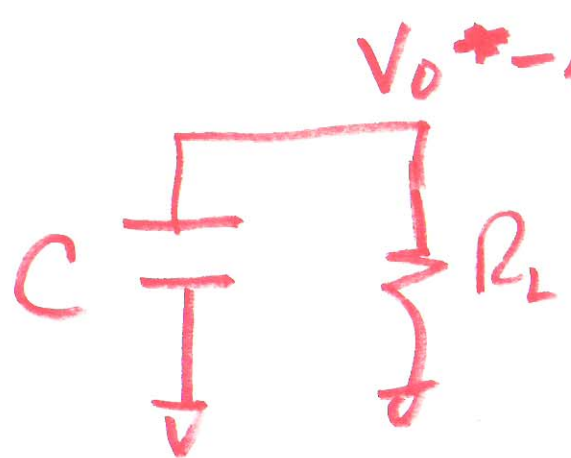

Ripple

for a
specific
Ripple

$$I = C \frac{dV}{dt} = \frac{V_0}{R_L} = C \cdot \frac{\Delta V}{\Delta T}$$

Reverse recovery time $\Delta T = \frac{1}{f} = \frac{1}{60}$

11)