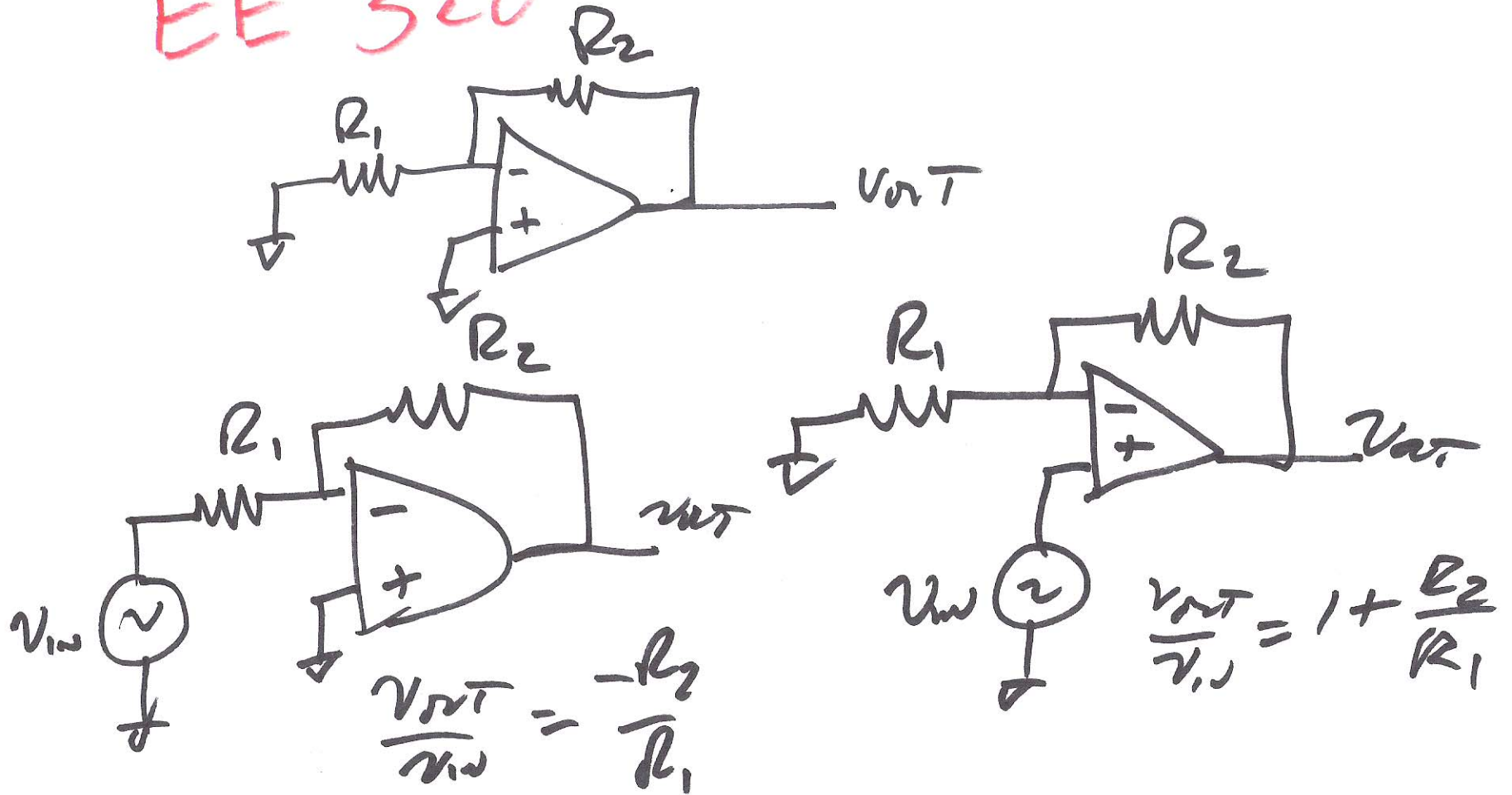



Lecture 13

3/12/14

EE 320



1)

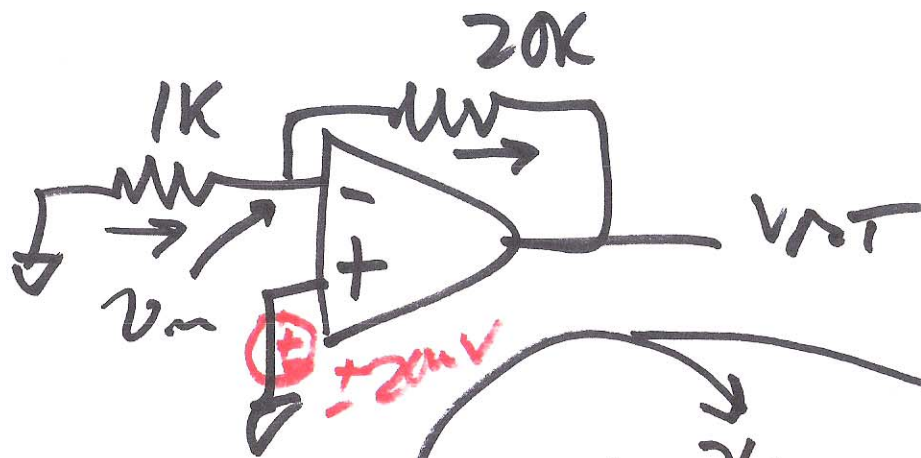

a) $V_{out} = 0$

b) $V_{out} = 0$

c) $V_{out} =$
 $\pm 20\text{mV} \left(1 + \frac{20}{1}\right)$
 $= \pm \underline{\underline{420\text{mV}}}$

$$\frac{0 - V_{in}}{1K} = \frac{V_{in} - V_{out}}{20K}$$


$$V_{out} = A_{OL}(0 - V_{in})$$

$$V_{in} = \frac{-V_{out}}{A_{OL}}$$

$$\frac{V_{out}}{A_{OL} \cdot 1K} = \frac{-V_{out}}{A_{OL} \cdot 20K} - \frac{V_{out}}{20K}$$

$$V_{out} = 0$$

2)

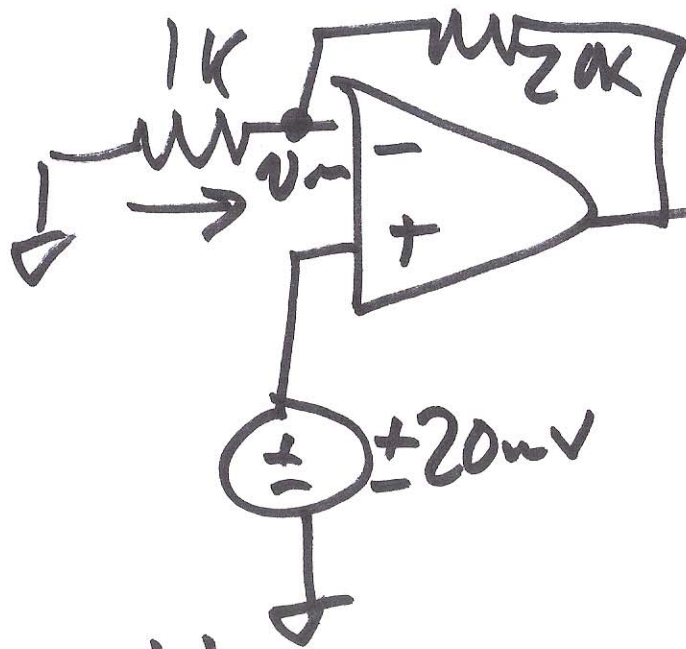

$$Z = 0.02 \times 100$$

$$v_{out} = A_{oc}(v_p - v_m)$$

$$v_{out} = 100(\pm 20\mu\text{V} - v_m)$$

$$v_m = \frac{\pm 1}{60.5}$$

$$\frac{0 - v_m}{1\text{k}} = \frac{v_m - v_{out}}{20\text{k}}$$

$$v_{out} = 100\left(\pm 0.02 \pm \frac{1}{60.5}\right) - \frac{v_m}{1\text{k}} = \frac{v_m}{20\text{k}} - \frac{100(\pm 20\mu\text{V} - v_m)}{20\text{k}}$$

$$\pm 2 \mp 1.7$$

$$\pm \underline{\underline{.3\text{V}}}$$





.347

$$-v_m \left(\frac{1}{1\text{k}} + \frac{1}{20\text{k}} + \frac{100}{20\text{k}} \right) = \frac{\pm 1}{10\text{k}}$$




$$-v_m \left(10 + \frac{1}{2} + 50 \right) = \pm 1$$

3)

Hose Bib water flow

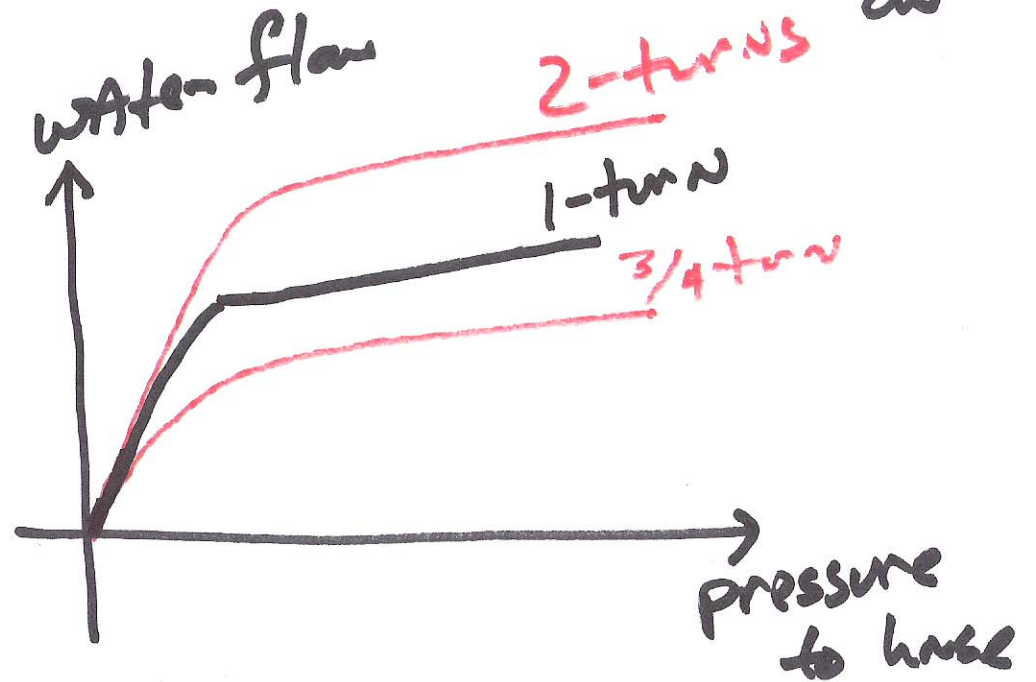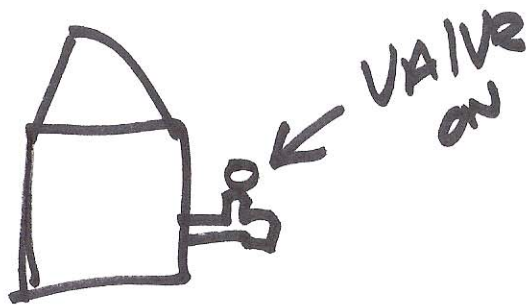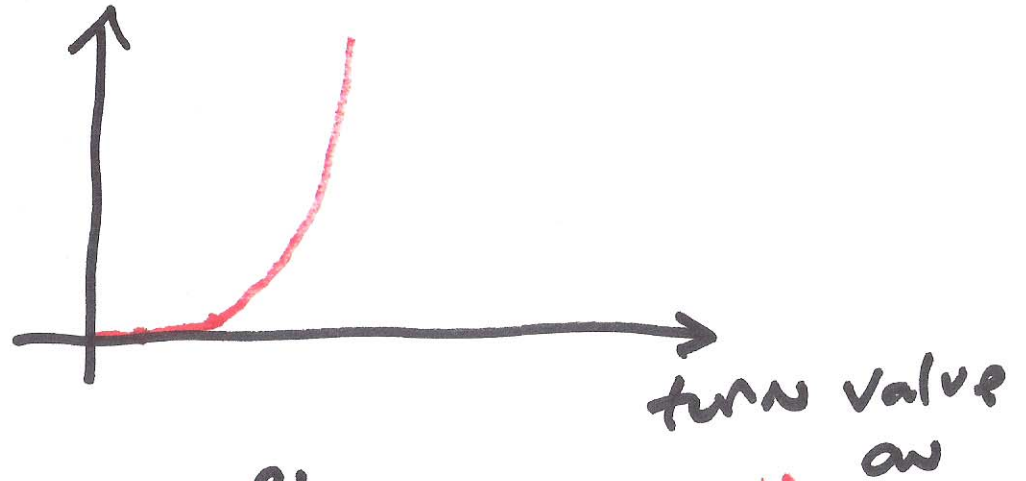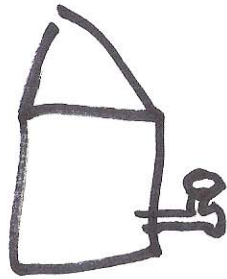

4)

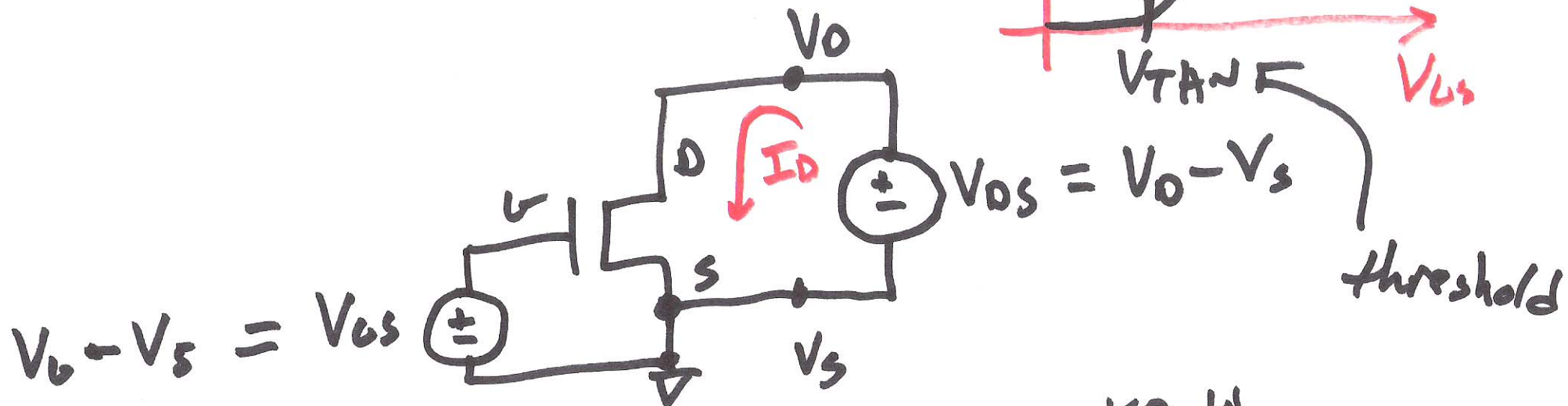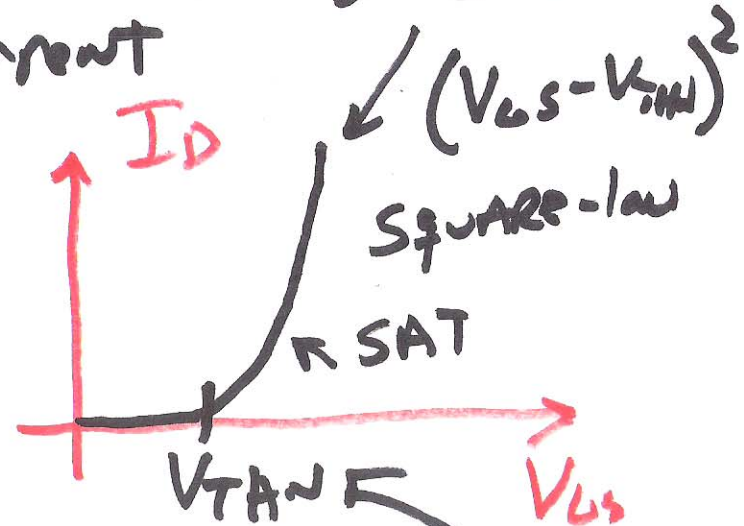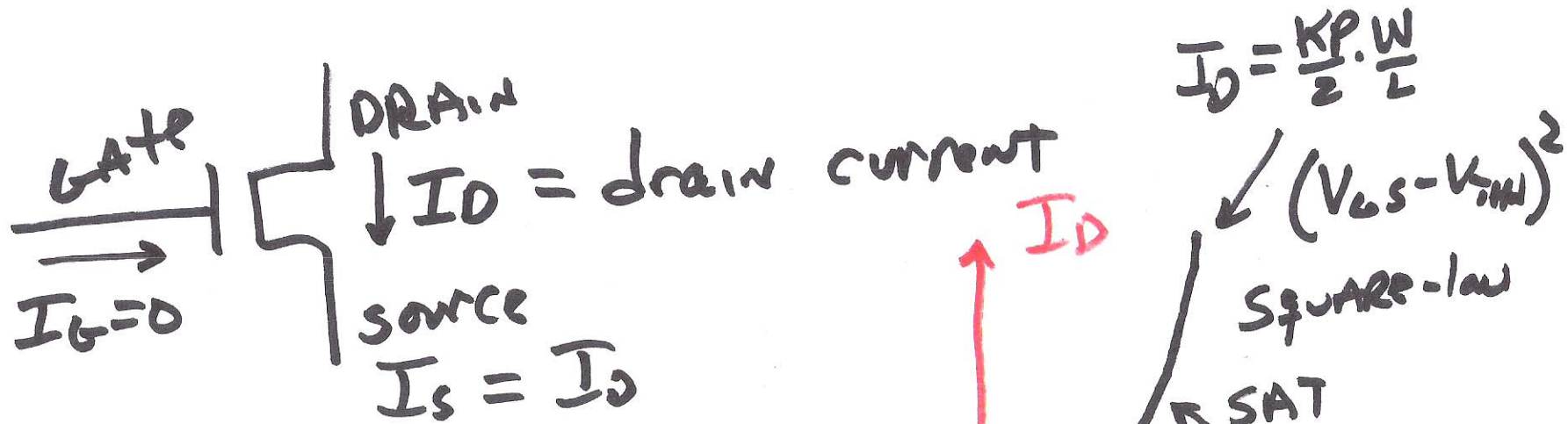


$$K_n = \frac{K_P \cdot W}{L}$$

$$K_n' = K_P \leftarrow \text{transconductance}$$

per


5)

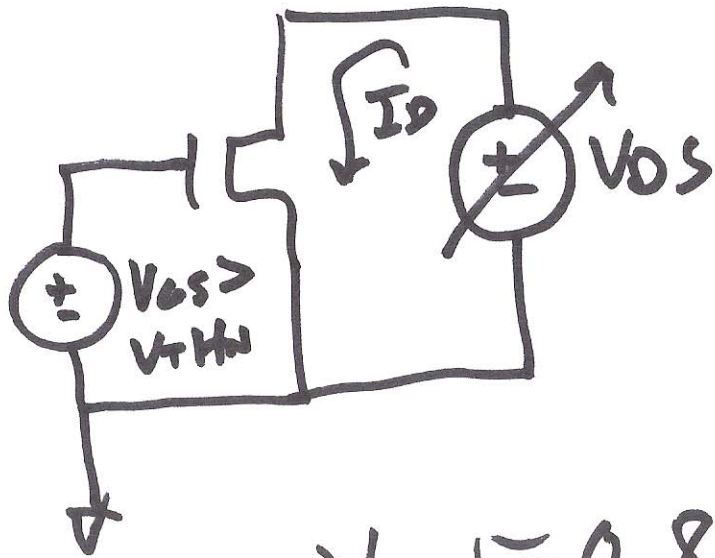

$$V_{TH} = 0.8$$

$$V_{GS1} = 1V$$






$$V_{GS2} = 2V$$

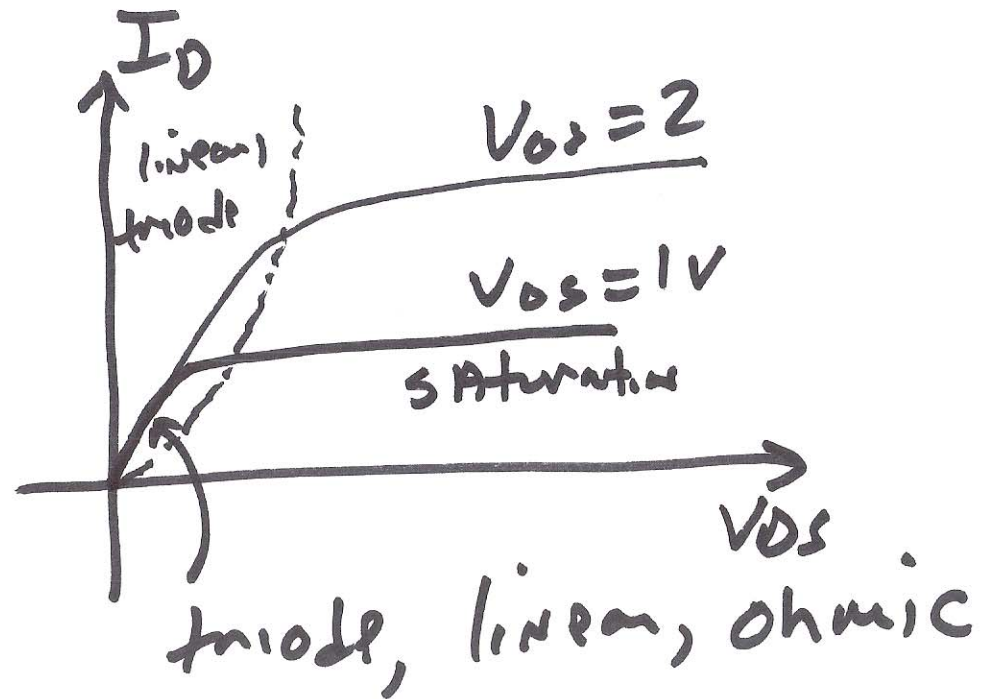

$$I_D = \frac{K_P \cdot W}{2 \cdot L} (V_{GS} - V_{TH})^2$$


$$V_{GS} > V_{TH}$$

$$V_{DS} \geq V_{GS} - V_{TH}$$

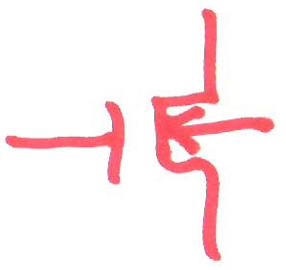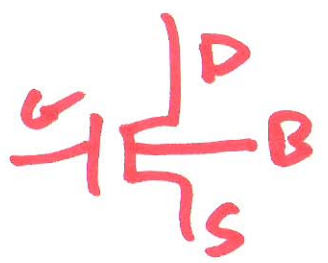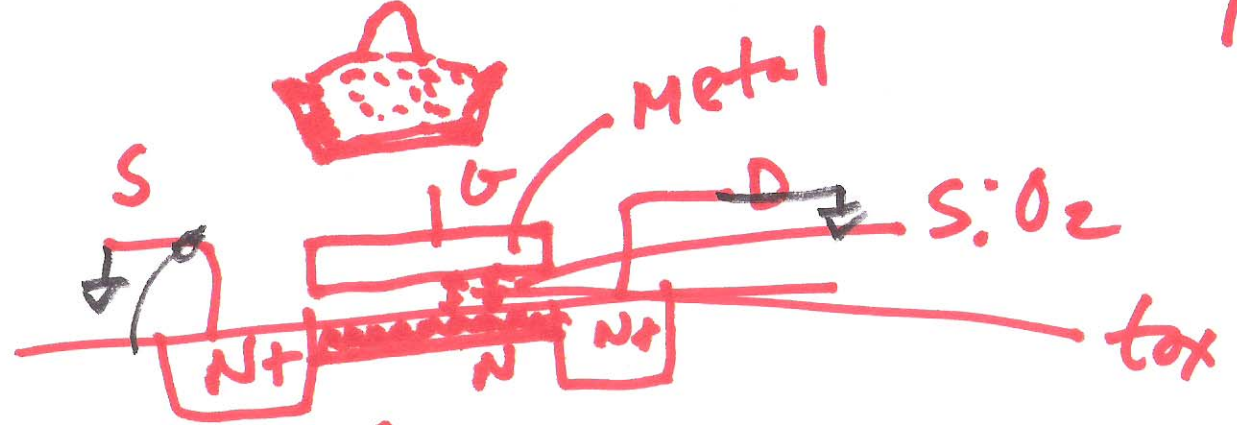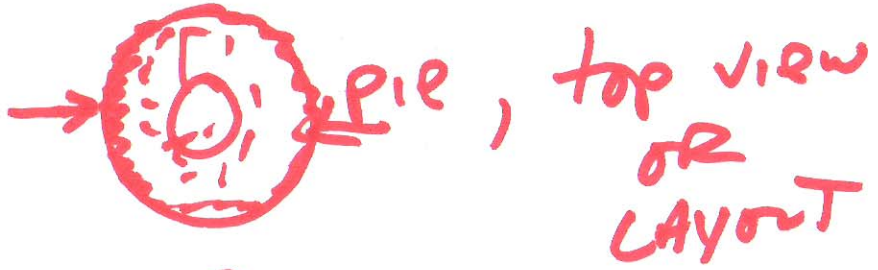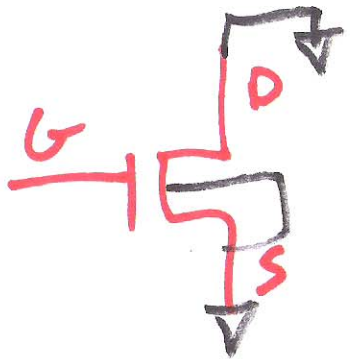


N-channel device oxide
 NMOS - semi
 N-channel metal oxide
 transistor

7)

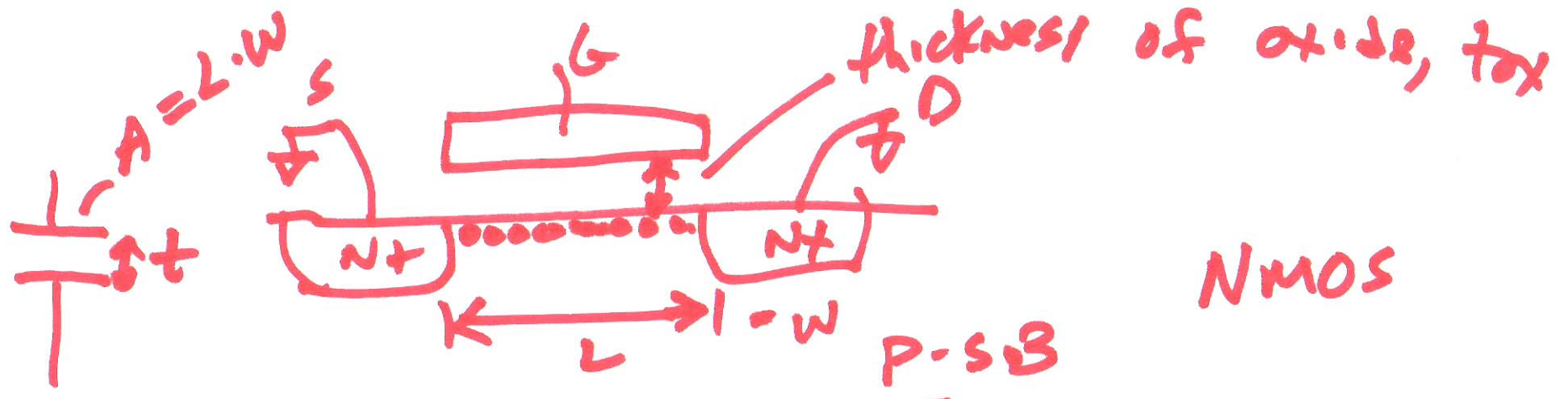


$$C = \frac{\epsilon \cdot A}{t}$$

$V_{DS} \gg V_{THW}$
Strong inversion

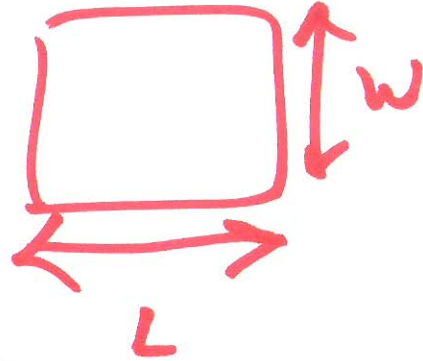


$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \cdot W \cdot L$$

$$= C_{ox}' \cdot W \cdot L$$

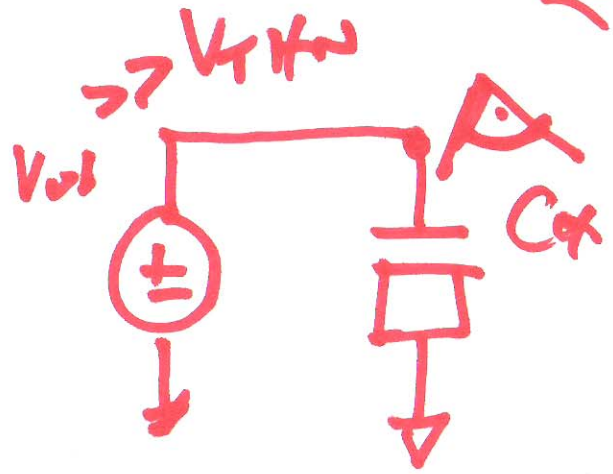

8)

$$1 \text{ \AA} = 10^{-10} \text{ m}$$

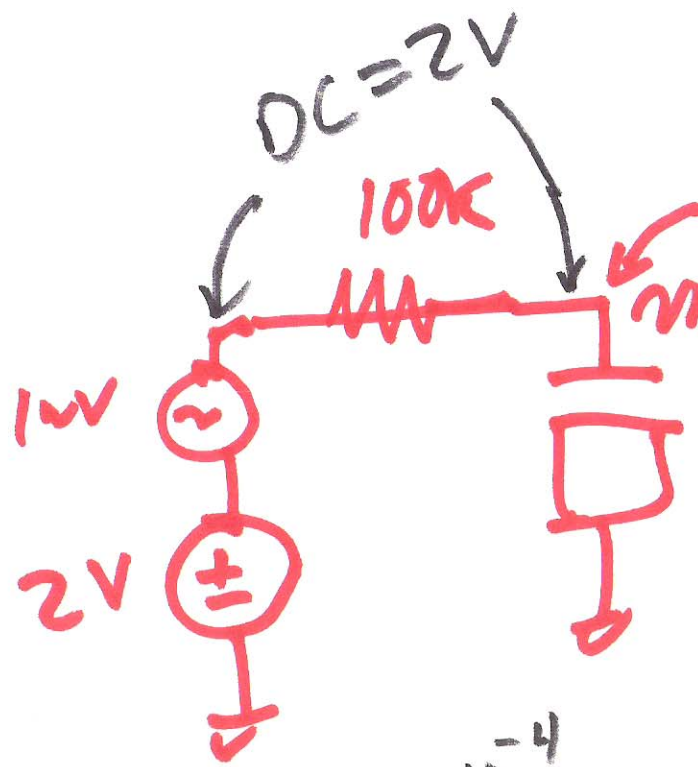

$$t_{ox} = 100 \text{ \AA} = 10 \text{ nm}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \cdot W \cdot L$$


$$\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm} \cdot \frac{10^{-4}}{10^{-4}}$$

$$\epsilon_{ox} = 3.9 \cdot \epsilon_0$$

$$\frac{8.85 \times 10^{-18} \text{ F}}{4 \mu\text{m}}$$

$$= \frac{3.9 \cdot 8.85 \cdot 10^{-18} \text{ F/cm} \cdot (100 \cdot 10^{-6})^2}{10 \cdot 10^{-9}} = \frac{3.9 \cdot 8.85 \cdot 10^{-15} \cdot 100^2}{10 \cdot 10^{-3}} = 34.5 \text{ pF}$$

9)

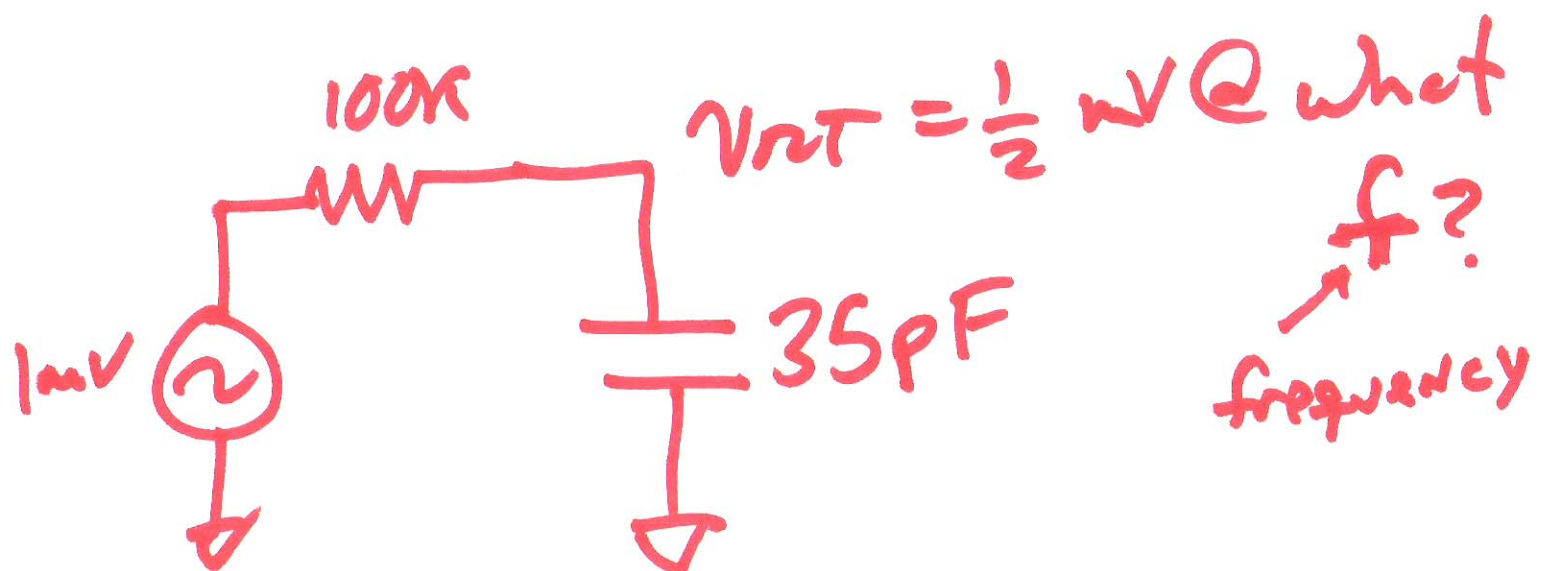

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{2} = \sqrt{\frac{1}{1 + (2\pi f \cdot 100k \cdot 35pF)^2}}$$

$$\frac{1}{4} = \frac{1}{1 + ()^2}$$

10)

$$1 + (2\pi f \cdot 100k \cdot 35pF)^2 = 4$$

$$2\pi f \cdot 100k \cdot 35pF = \sqrt{3}$$

$$f = \frac{\sqrt{3}}{2\pi \cdot 100k \cdot 35pF} = 78.9kHz$$

$$20 \log 10^{-3}$$

$$-60 \log 10 = -60dB$$

11)