
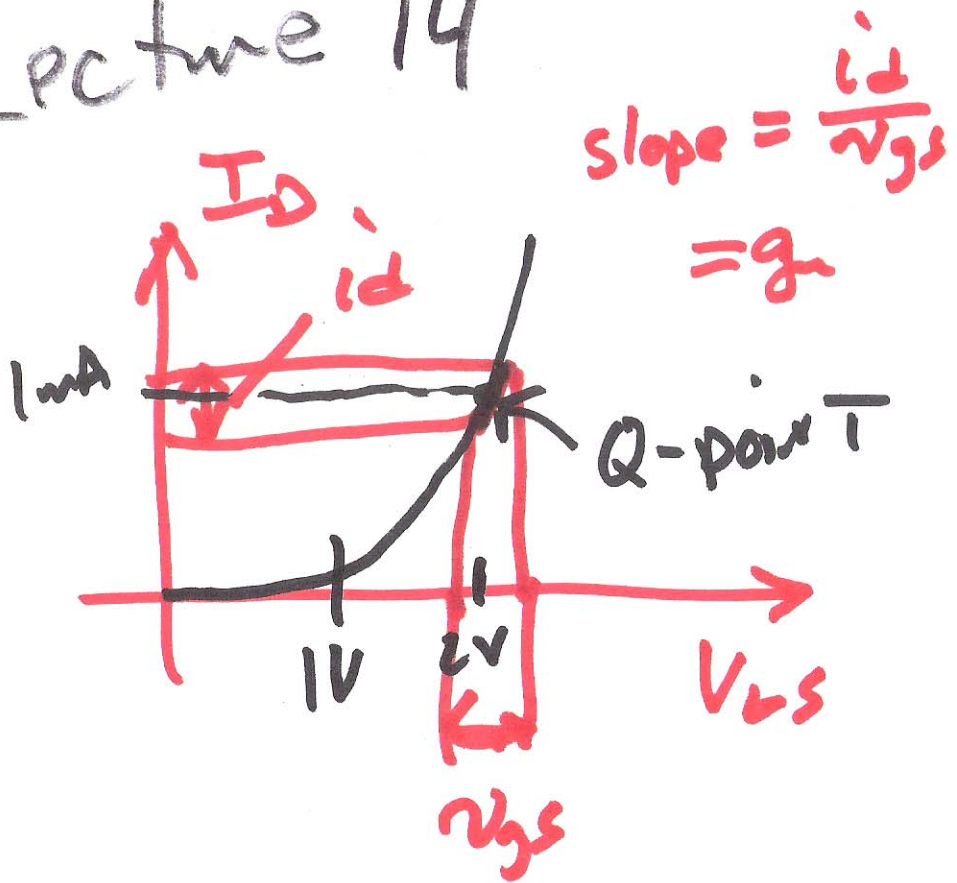


EE 320 Electronics I

3/24/14



Lecture 14

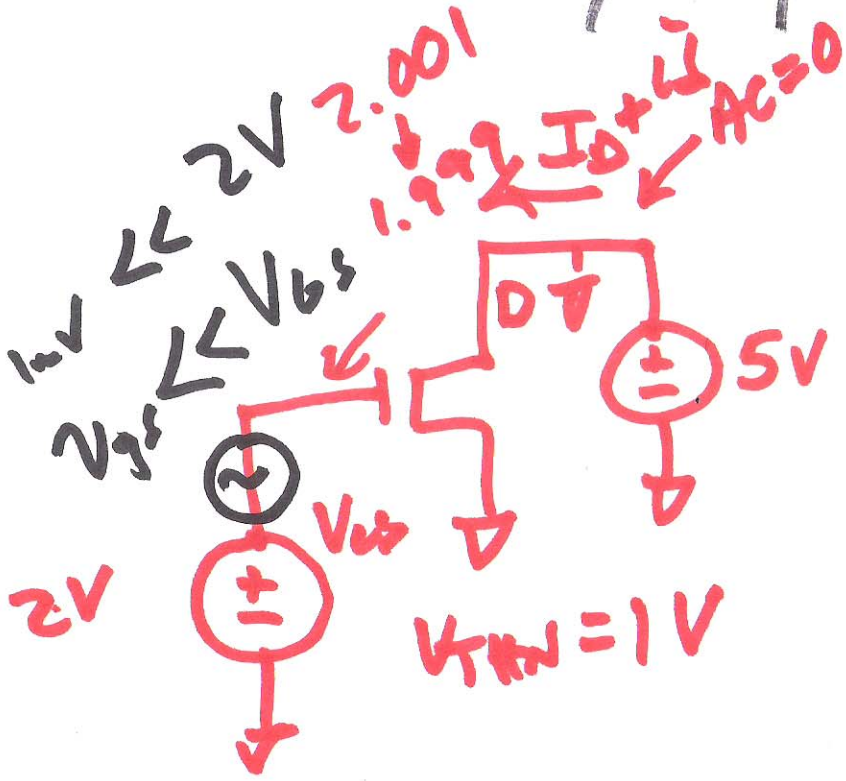


11

Closed book and notes.

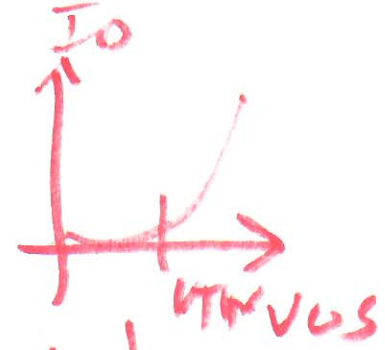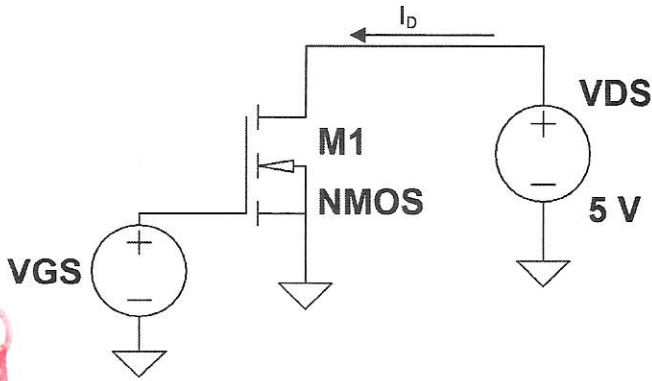1. Sketch the drain current, I_D , against V_{GS} in the following circuit. Assume the MOSFET's threshold voltage is 1 V (show the threshold voltage on your plot).





$$K_n = \frac{\mu_n C_{ox} W}{L}$$

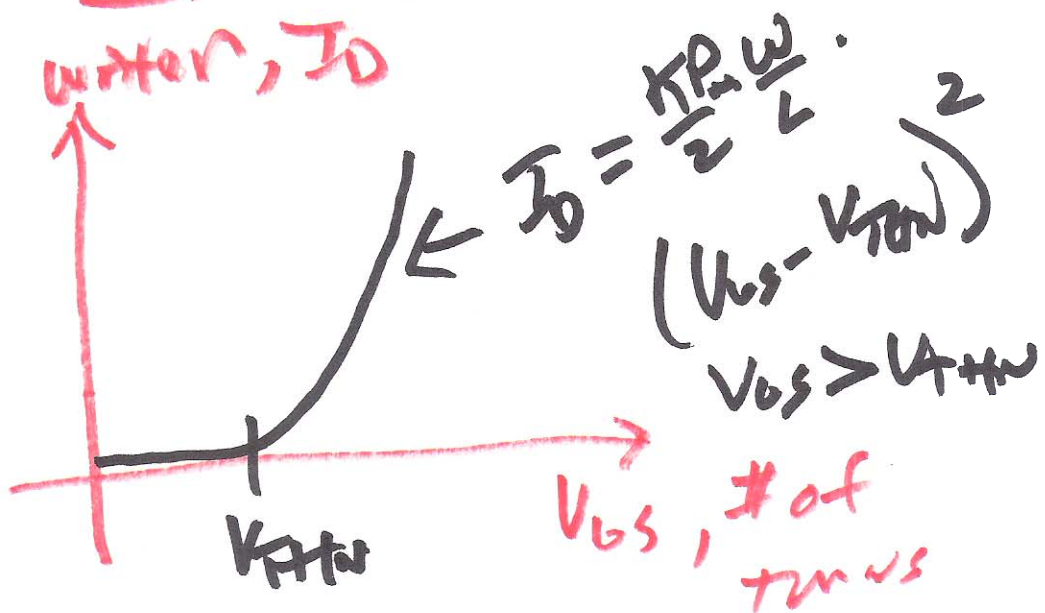

$$I_D = 0 \quad V_{GS} < V_{TN}$$

2)

$$\leftarrow I_0 + i_d = i_D$$

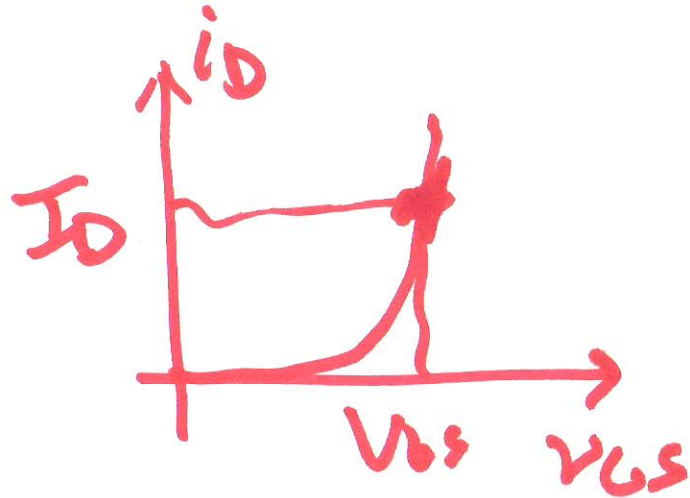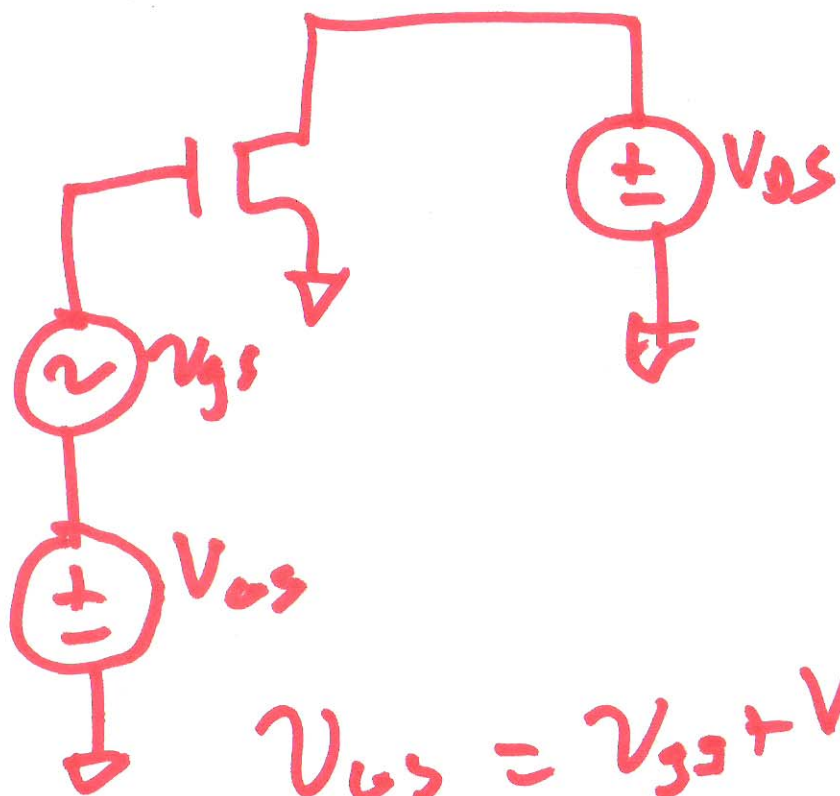

$$i_D = \frac{\mu_n \cdot C_{ox} \cdot W}{2L} (V_{GS} - V_{TH})^2$$

$$V_{GS} = V_{GS} + V_{BS} \quad g_m = \frac{\delta i_D}{\delta V_{GS}} \Big|_{\substack{I_D = \text{CONST} \\ V_{BS} = \text{CONST}}}$$

$$g_m = \frac{\delta (I_0 + i_d)}{\delta V_{GS}} \Big|_{\substack{I_D = \text{CONST} \\ V_{BS} = \text{CONST}}} = \frac{\mu_n \cdot C_{ox} \cdot W}{2L} \cdot 2 (V_{GS} - V_{TH}) \cdot \frac{\delta (V_{GS} - V_{TH})}{\delta V_{GS}}$$

3)

$$g_m = \mu_n \cdot C_{ox} \cdot \frac{W}{L} (V_{GS} + v_{gs} - V_{THN})$$

$$V_{GS} \gg v_{gs} \quad \text{Small-signal}$$

$$g_m \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN})$$

$$I_D = \frac{\mu_n C_{ox} \cdot W}{2L} (V_{GS} - V_{THN})^2$$

$$V_{GS} - V_{THN} =$$

$$\frac{2(I_D \cdot L)}{\mu_n C_{ox} \cdot W}$$

$$g_m = \sqrt{2 \cdot \mu_n C_{ox} \cdot \frac{W}{L} I_D}$$

4)

$W = 10\mu$ $L = 1\mu$

$C_{ox} = 2 \text{ fF}/\mu^2$

$K_N = 50 \mu\text{A}/\text{V}^2 = \mu_0 C_{ox} \frac{q}{2}$

$V_{THN} = 0.8 \text{ V}$


find all AC & DC voltages & currents

for saturation

$V_{GS} \geq V_{THN}$

$V_{DS,s} \geq V_{GS} - V_{THN}$

$2\text{V} \geq 1.8 - 0.8$
yes!

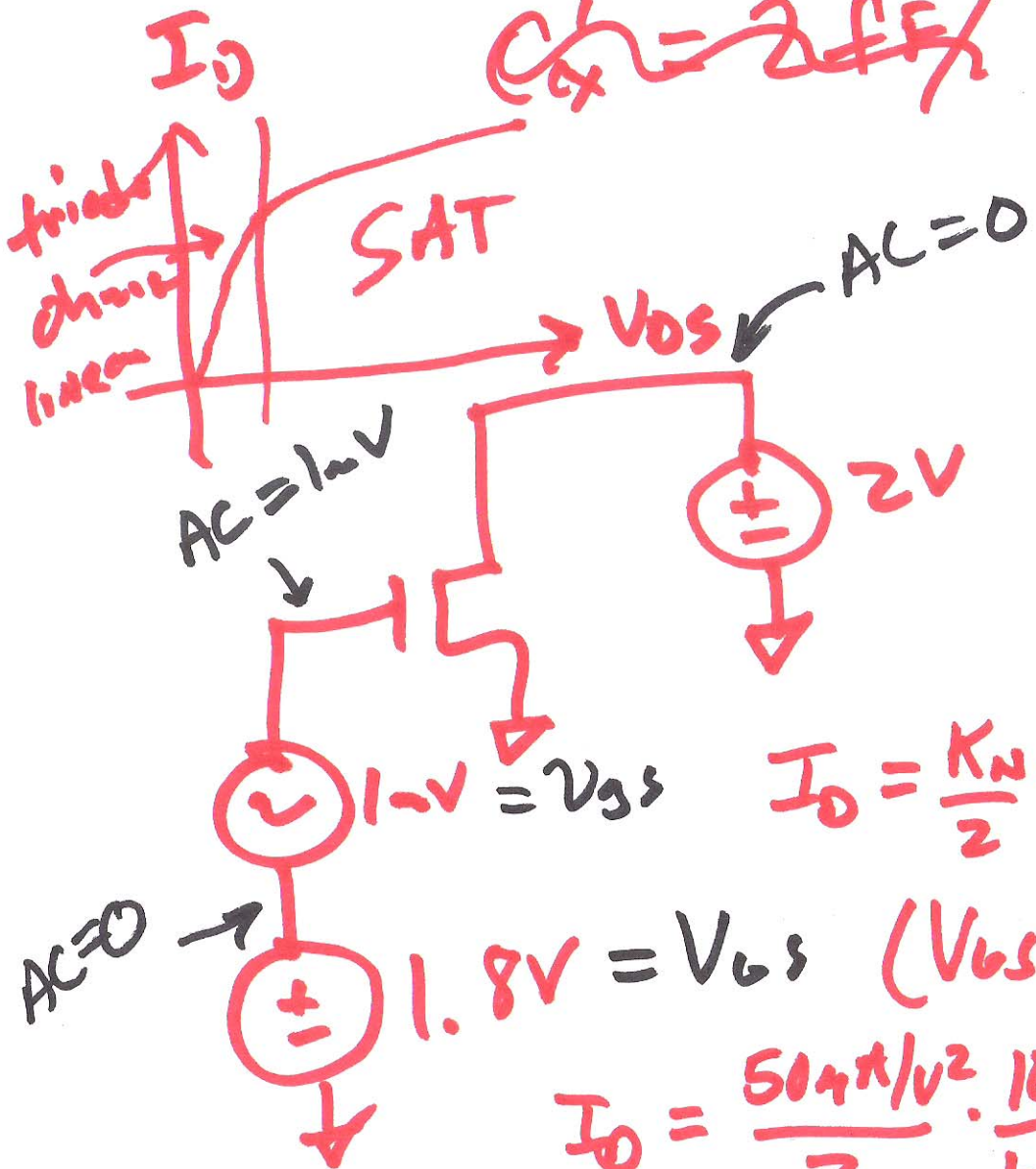

$I_D = \frac{K_N \cdot W}{2} \frac{V_{GS} - V_{THN}}{L}$


$I_D = \frac{50 \mu\text{A}/\text{V}^2 \cdot 10\mu}{2} \frac{(1.8 - 0.8)^2}{1\mu}$

$I_D = 250 \mu\text{A}$

5)

IN SATURATION!

AC CKT

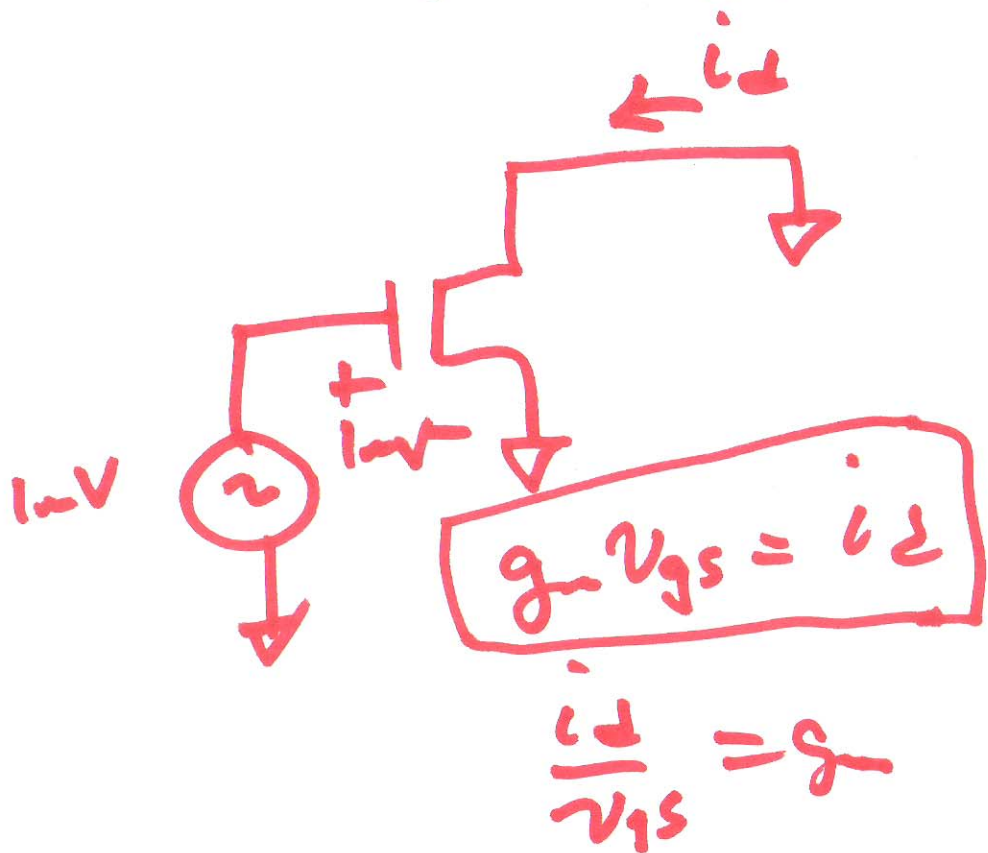

$$i_d = 500\mu\text{A} \cdot 1\text{mV}$$

$$= 500\text{nA}$$

$$K_P n = 50\mu\text{A}/\text{V}^2$$

$$W = 10\mu\text{m}$$

$$L = 1\mu\text{m}$$


$$I_D = 250\mu\text{A}$$

$$g_m = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH})$$


$$= \frac{50\mu\text{A}}{\text{V}^2} \cdot \frac{10}{1} (1)^2 \text{V}$$

$$g_m = 500\frac{\mu\text{A}}{\text{V}}$$

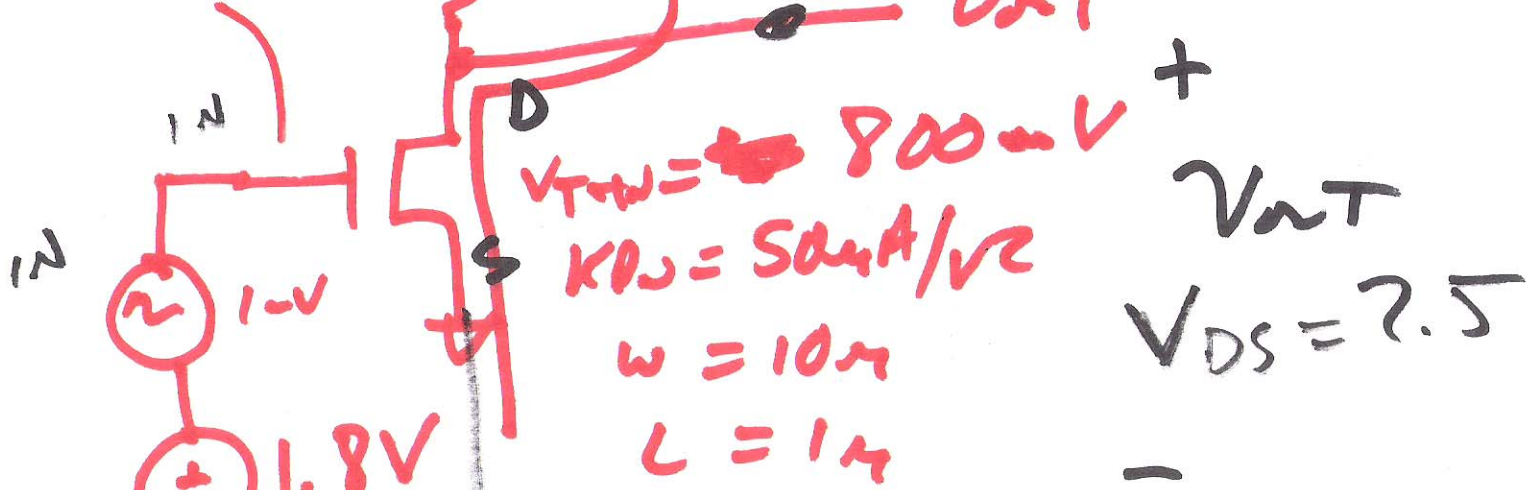DC = 1.8V
 +5V
 "our first step"
 C.S.
 10K
 250μA
 25
 V_{INT}



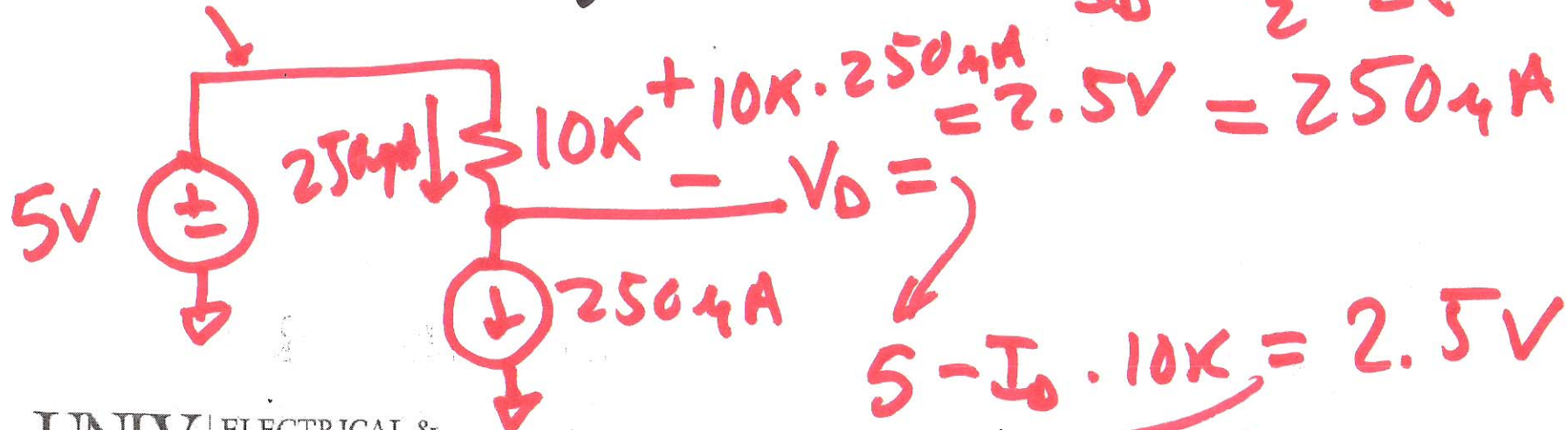
$$I_D = \frac{K_{P0}}{2} \frac{W}{L} (V_{GS} - V_{T0})^2$$



$$5 - I_D \cdot 10K = 2.5V$$


2.5V



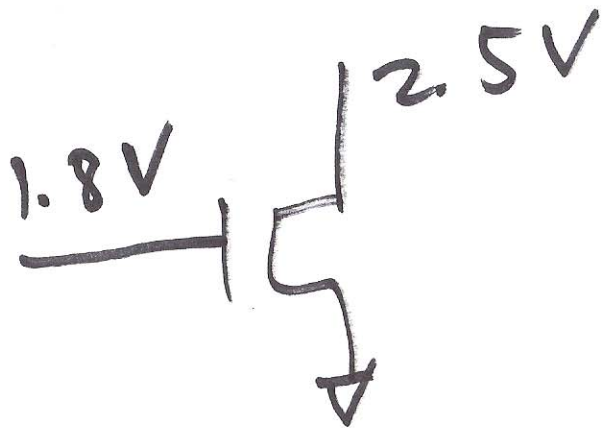

$V_{GS} > V_{THN} ?$
 $1.8 \geq .8 ?$ yes!
 $V_{DS} \geq V_{GS} - V_{THN} ?$
 $2.5 \geq 1.8 - .8 ?$
 yes!

$g_m = 500 \mu A/V$
 AC CKT

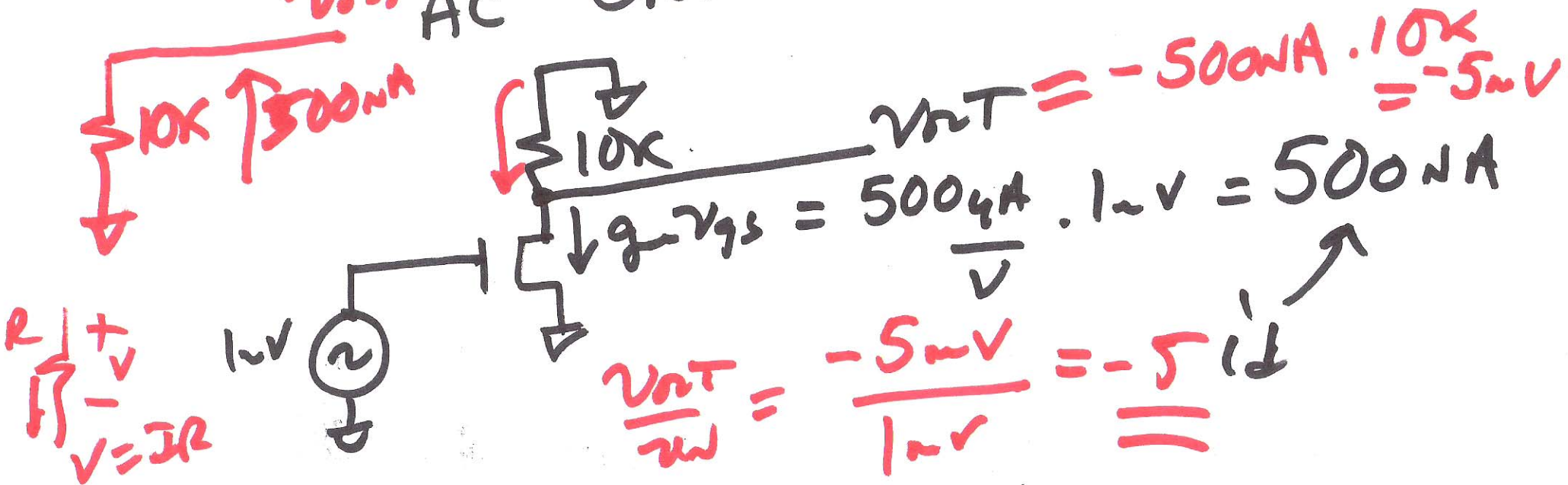

8)