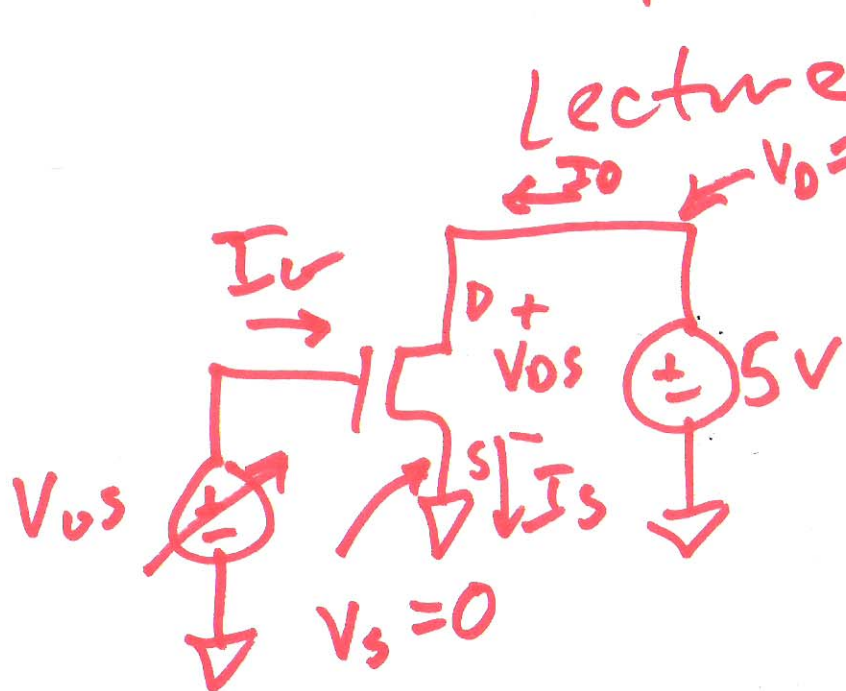


3/26/14


Lecture 15



$$V_D - V_S = V_{DS} = 5 - 0$$

$$V_G - V_S = V_{GS}$$

$$I_D = I_S, I_G = 0$$

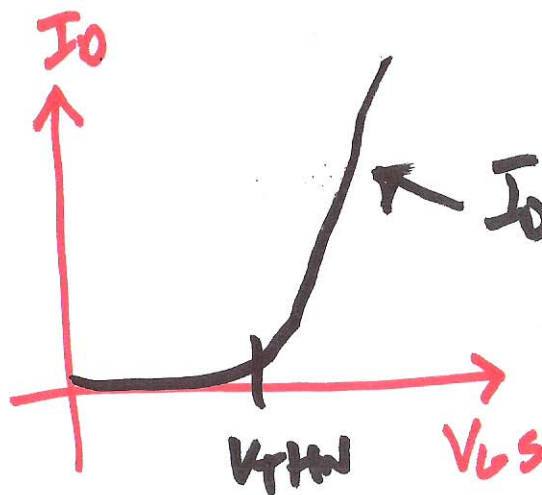

$$I_D = \frac{K_P n W}{2 L} (V_{GS} - V_{TH})^2$$


$$(V_{GS} - V_{TH})^2$$

$$V_{GS} > V_{TH}$$



$$V_{GS} \geq V_{GS} - V_{TH}$$

CMOSedu.com

for SAT!


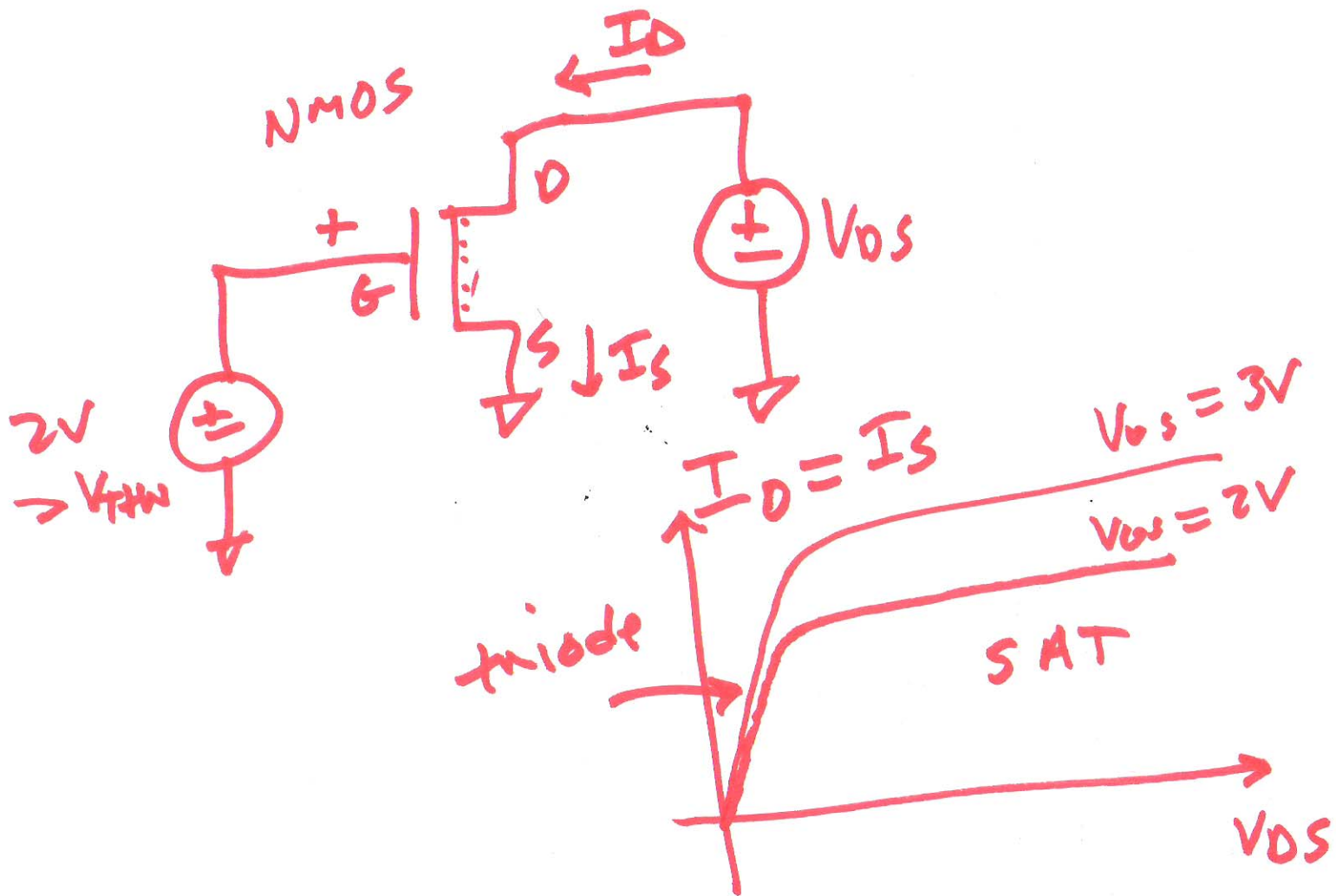


2)

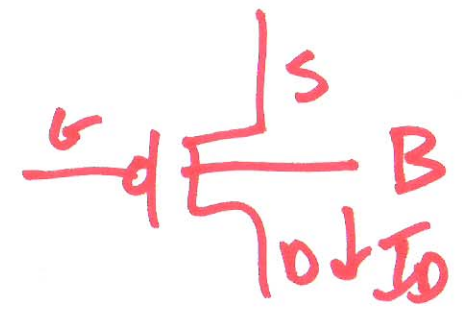
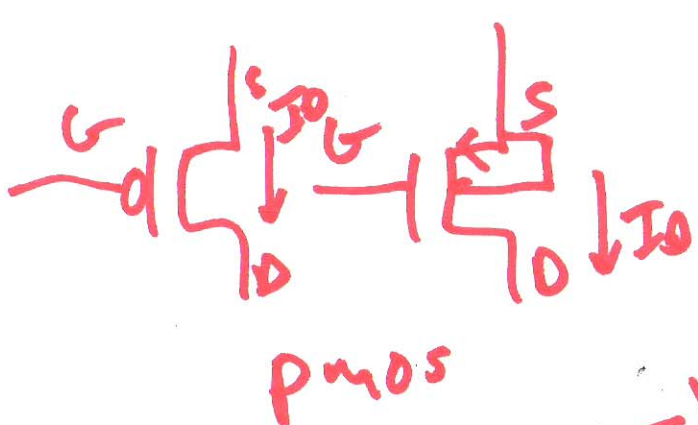


Complimentary CMOS


$$-V_{DS} = V_{SG}$$

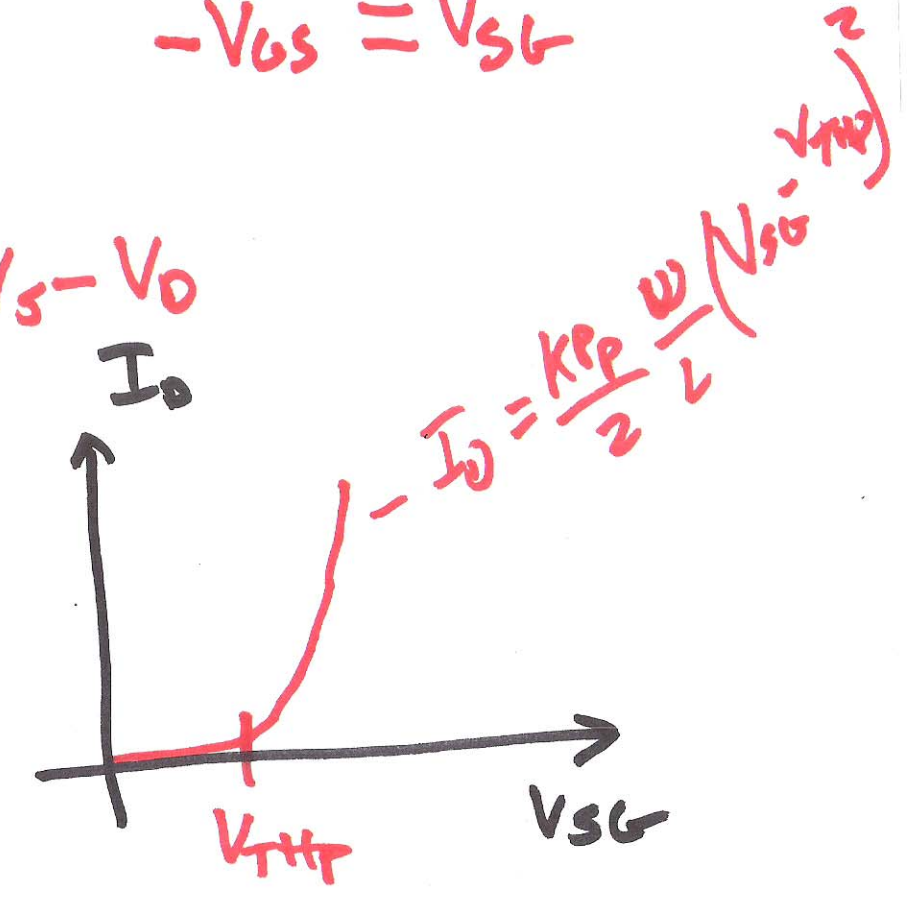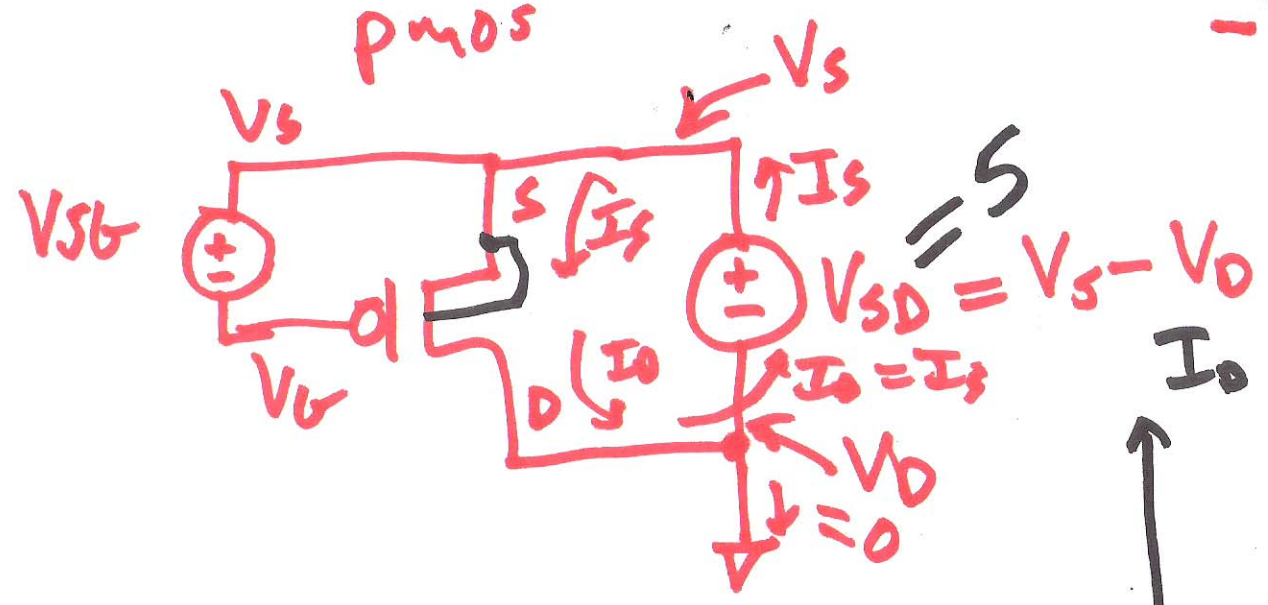


3)

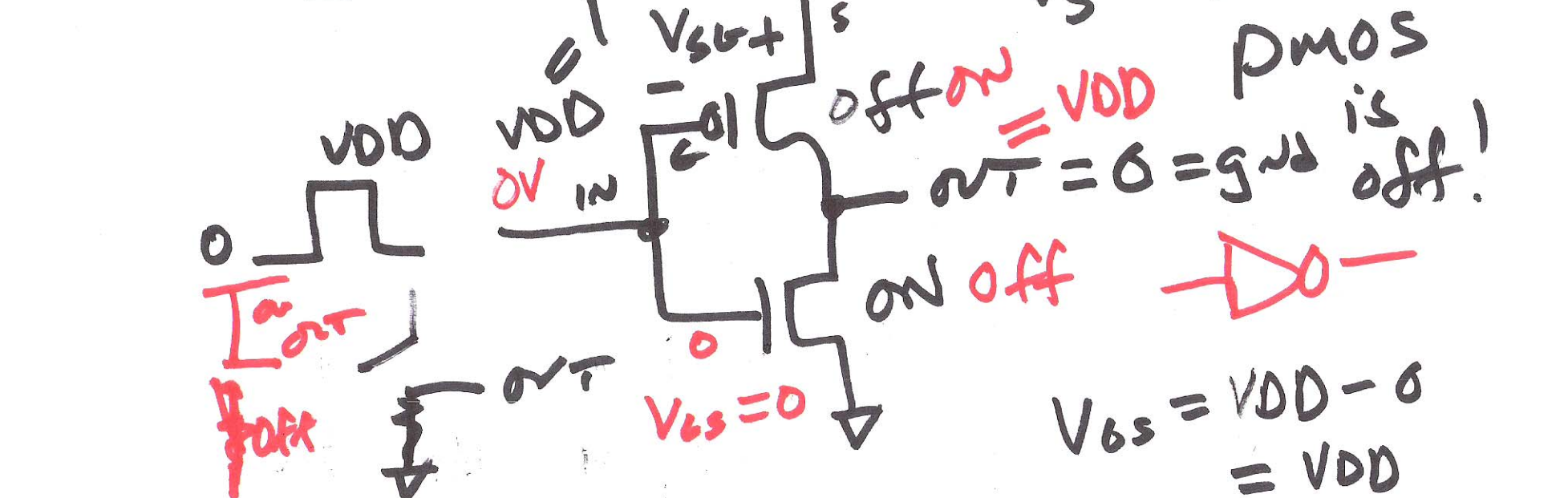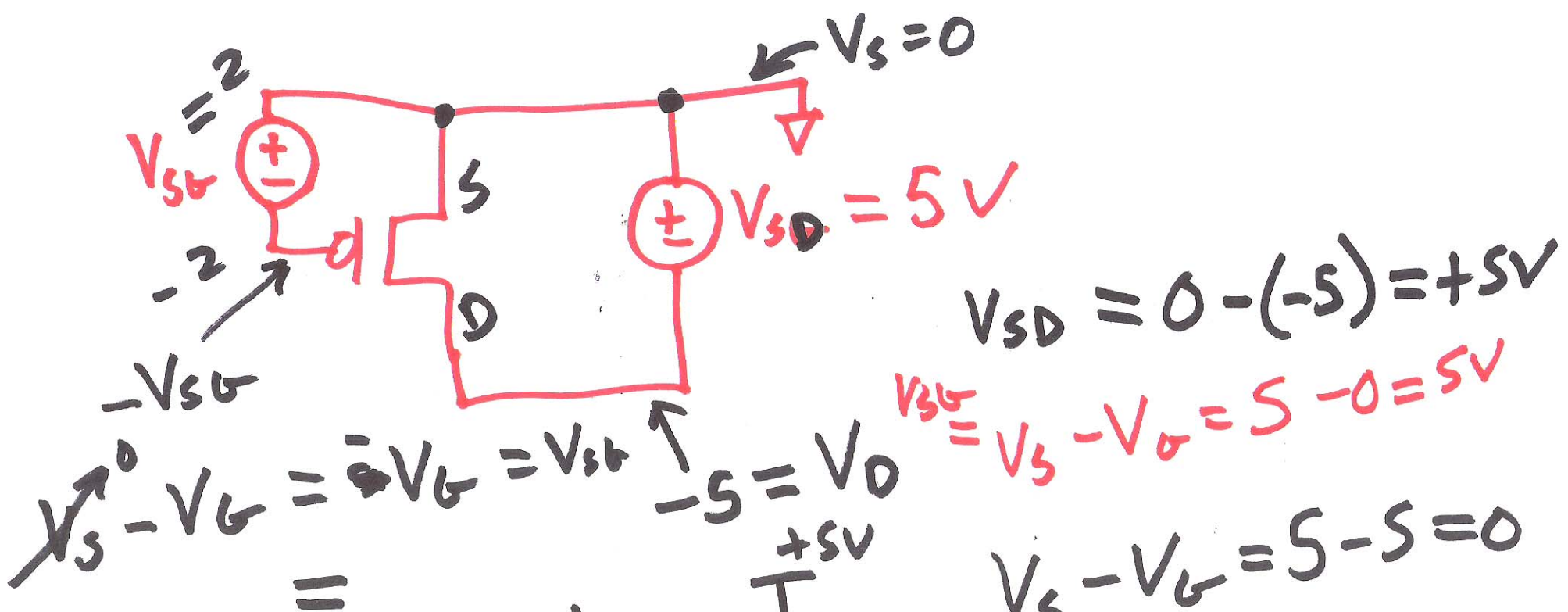

4)

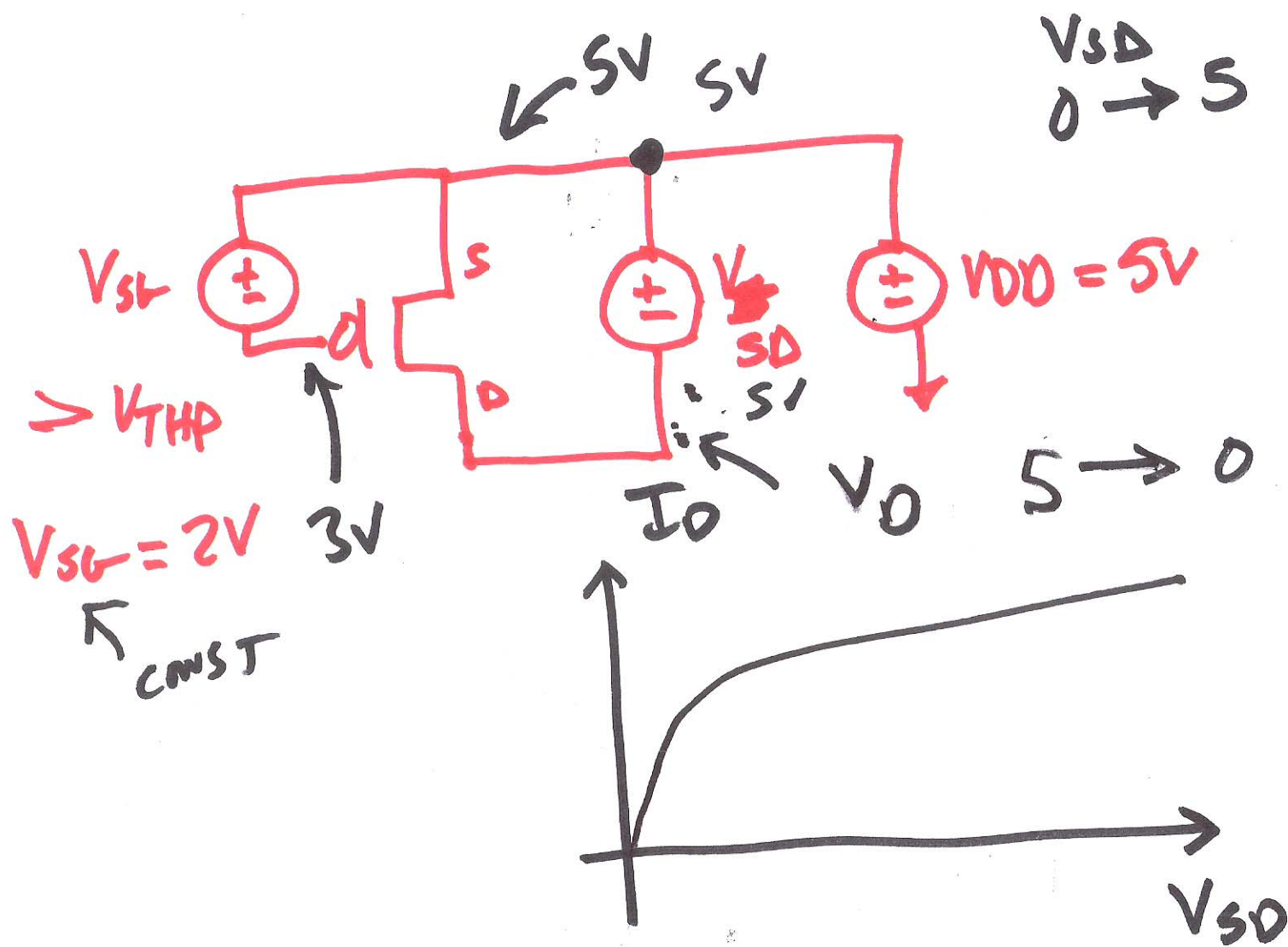

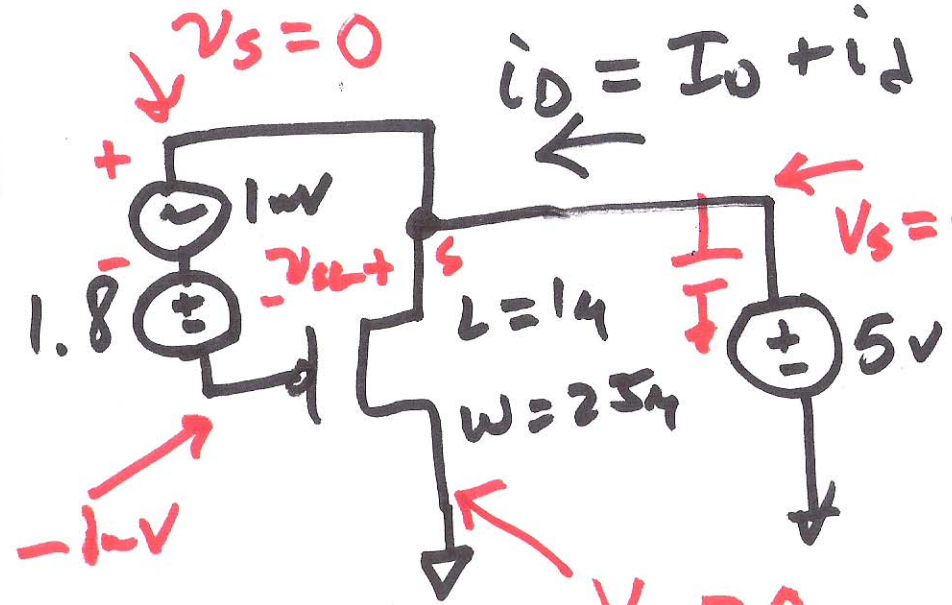$V_s = 5^-$
 $5 - 1.8 = 3.2$
 $= V_G$
 $V_s - V_G = 1.8$



$K_P = 20 \mu A/V^2$
 $V_{THP} = .8$

$V_{SD} = V_s - V_D = 5V$
 $V_{SG} = V_s - V_G = 5 - (-1) = 6V$
 $5 - 1.8 = 3.2$

$V_s - V_G = 0 - (-1\mu V)$
 $V_{SG} = 1\mu V$

$V_{SG} > V_{THP}$
 $3.2 > .8?$

$I_0 = \frac{K_P \cdot W}{2 \cdot L} (V_{SG} - V_{THP})^2$
 $= \frac{20 \mu A}{V^2} \cdot \frac{25}{1} (1.8 - .8)^2$

$3.2 - .8$
 $\geq V_{SG} - V_{THP}$
 YES


$I_0 = 250 \mu A$

6)

$$i_{in} = v_{sg}$$



$$i_d = g_m v_{sg} = 500 \mu A$$

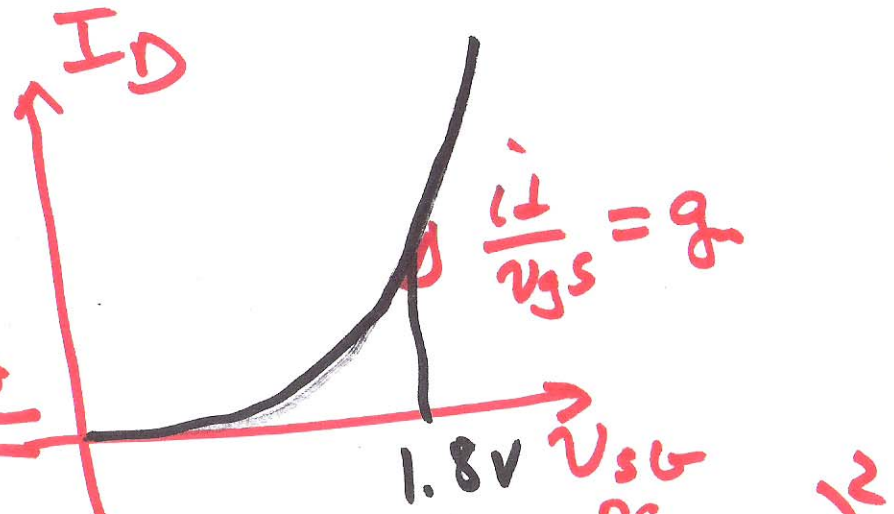

$$g_m = \left. \frac{\delta i_D}{\delta v_{GS}} \right|_{\substack{I_D = \text{const} \\ V_{DS} = \text{const}}} = \frac{\delta}{\delta v_{GS}} \frac{K_P P}{2} \frac{W}{L} \left(\underbrace{V_{GS}^{DC} + v_{sg}^{AC}}_{v_{GS}} - V_{THP} \right)^2$$

$$209 \cdot \frac{25}{1} (1.8 - 0.8) = g_m =$$

$$g_m = 500 \frac{\mu A}{V}$$

$$g_m = K_P P \cdot \frac{W}{L} (V_{GS} + v_{sg} - V_{THP}) \cdot 1$$

Small-signal approximation
 $V_{GS} \rightarrow v_{gs}$

$$g_m = K_P P \cdot \frac{W}{L} (V_{GS} - V_{THP})$$

7)