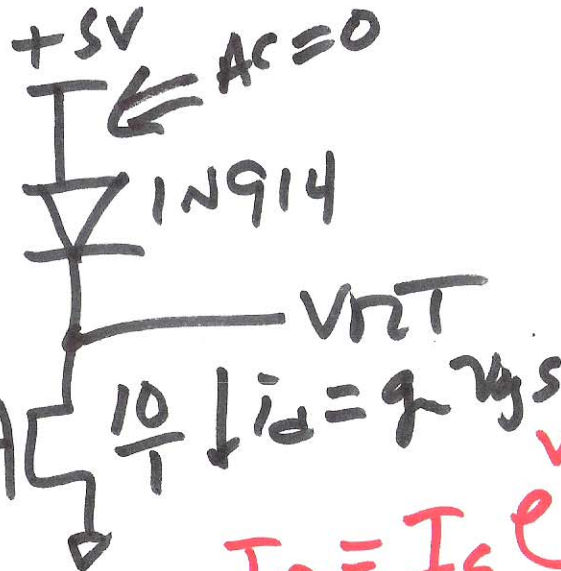


Lecture 17

April 2, 2014

$V_{DS} \geq V_{GS} - V_{THN}$
 $V_D > V_G - V_{THN}$

EE 320!



$$I_D = \frac{K_{PN} \cdot W}{2} \frac{V_{GS} - V_{THN}}{L}^2$$

$$= \frac{120 \mu A}{2} \cdot \frac{10}{1} (1.5 - .8)^2$$

$$V_D / N V_T = 600 \mu A \cdot .49$$

$$\approx \underline{\underline{295 \mu A}}$$

$$I_D = I_S e^{\frac{V_D}{N V_T}}$$


$$V_D = N V_T \ln \frac{I_D}{I_S}$$

$$I_S = 2.52 \text{ nA}$$

$$N = 1.752$$

$$V_D = 1.752 (26 \text{ mV}) \ln \frac{295 \mu A}{2.52 \text{ nA}}$$
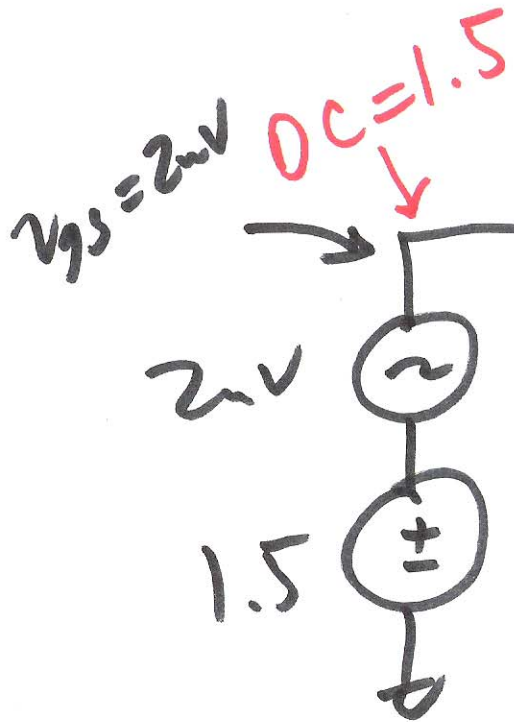
$$V_D = .568 \text{ V} \quad V_{VT} = 9 \cdot .568$$




$V_{VT} = 4.432 \text{ V}$

1)

Quiz 9 EE 320 Electronics, Spring 2014 Name: _____
 Open book and closed notes.

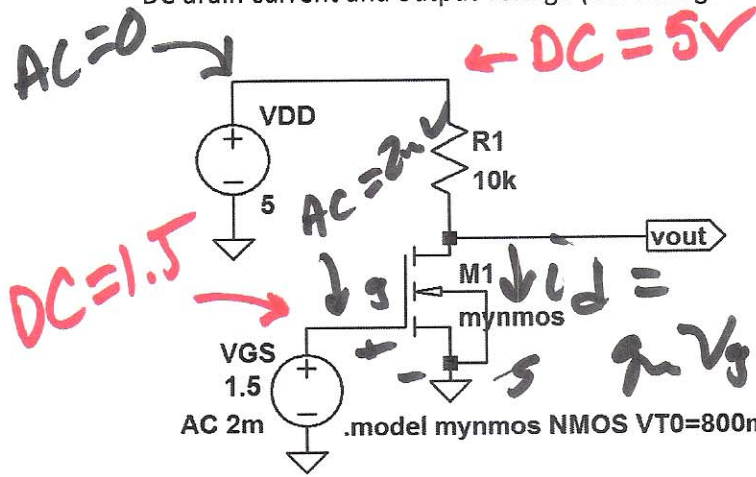1. If the transconductance, g_m , of M1 is $200 \mu\text{A/V}$ then calculate the AC drain current, i_d , and the AC output voltage, v_{out} . If the width of the MOSFET is $10 \mu\text{m}$ and the length is $5 \mu\text{m}$ calculate the DC drain current and output voltage (the voltage on the drain of M1).




$$V_{gs} = V_g - V_s = 2 - 0 = 2 \text{ V}$$

$$V_g = 2 \text{ V}$$

$$V_s = 0$$

$$I_D = \frac{KP_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{Tn})^2$$
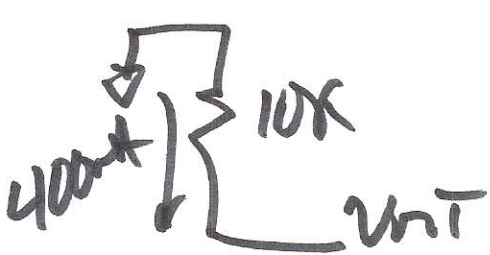
$$= \frac{50 \mu\text{A/V}^2}{2} \cdot \frac{10}{5} (1.5 - 0.8)^2$$



$$g_m = KP \cdot \frac{W}{L} (V_{GS} - V_{Tn})$$

$$i_d = g_m V_{gs} = \frac{200 \mu\text{A}}{\text{V}} \cdot 2 \text{ V}$$

$$v_{out} = -400 \text{ nA} \cdot 10 \text{ k}$$


$$v_{out} = -4 \text{ mV}$$

$$i_d = 400 \text{ nA}$$

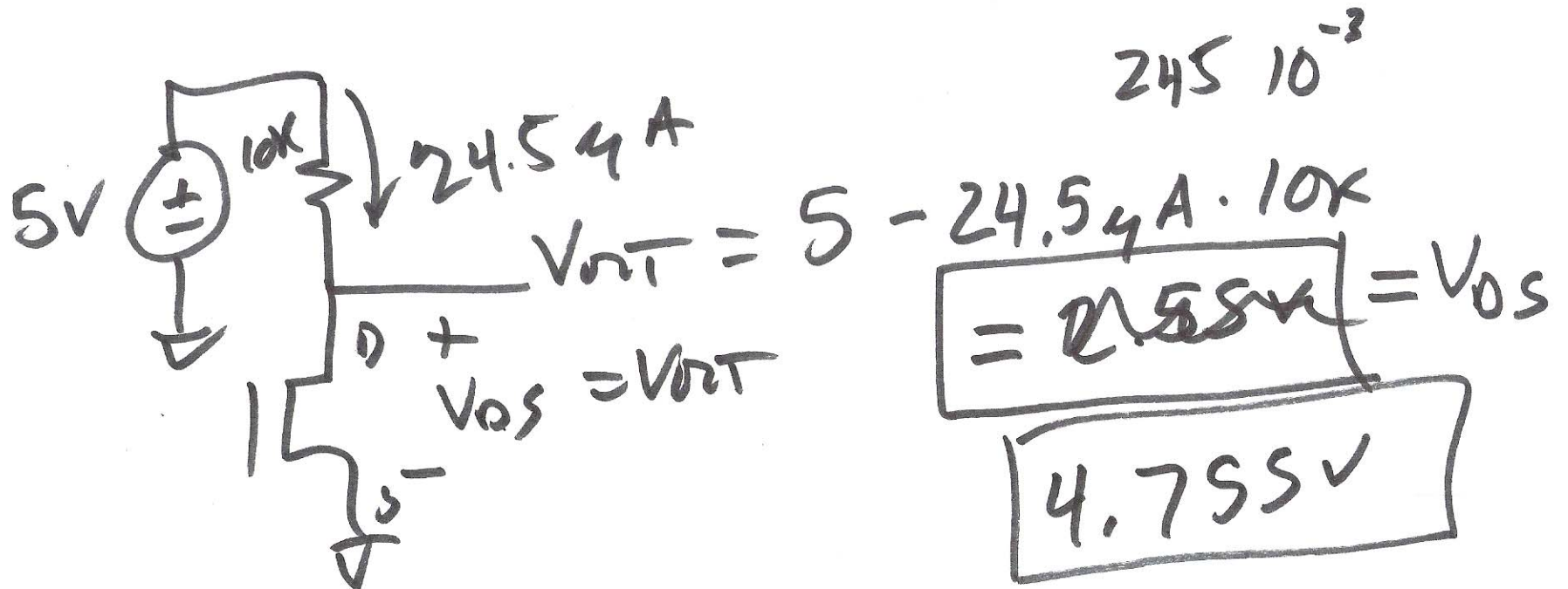2)

$$I_D = \frac{504}{2} \frac{10}{5} (1.5 - .8)^2$$



$$= 504 \cdot .49 \approx \boxed{24.54 \text{ A}}$$



$$245 \cdot 10^{-3}$$

$$= 2.55\text{V} = V_{os}$$

$$\boxed{4.755\text{V}}$$

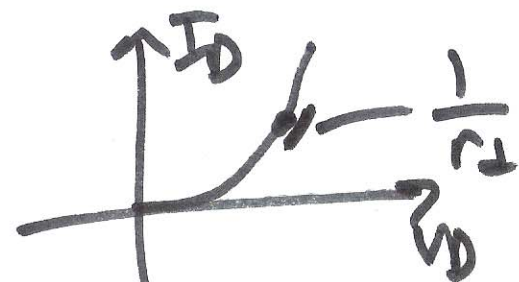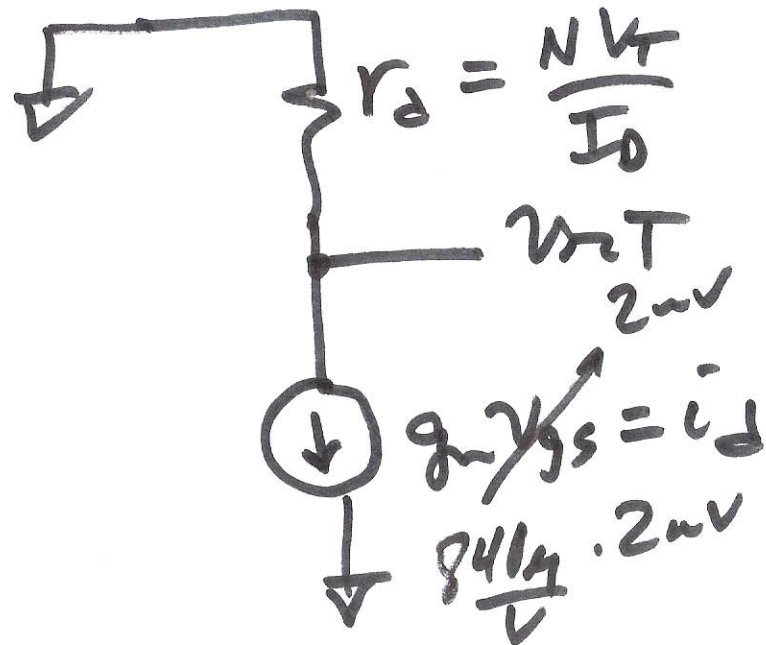

$$r_d = \frac{1.752 \cdot 26\text{mV}}{295\mu\text{A}}$$

$$r_d = 154\Omega$$

$$i_d = 1680\text{ nA} = \frac{1204 \cdot 10}{\sqrt{2}} \frac{1}{1} (1.5 - .8)\text{V}$$

$$i_d = 1.684\text{A} = 1.2 \frac{\text{A}}{\sqrt{2}} \cdot 7$$


$$= \frac{840\mu\text{A}}{\sqrt{2}}$$

$$v_{DS} = -i_d \cdot r_d$$

$$= -1.684 \cdot 154$$

$$= -258\mu\text{V}$$

4)

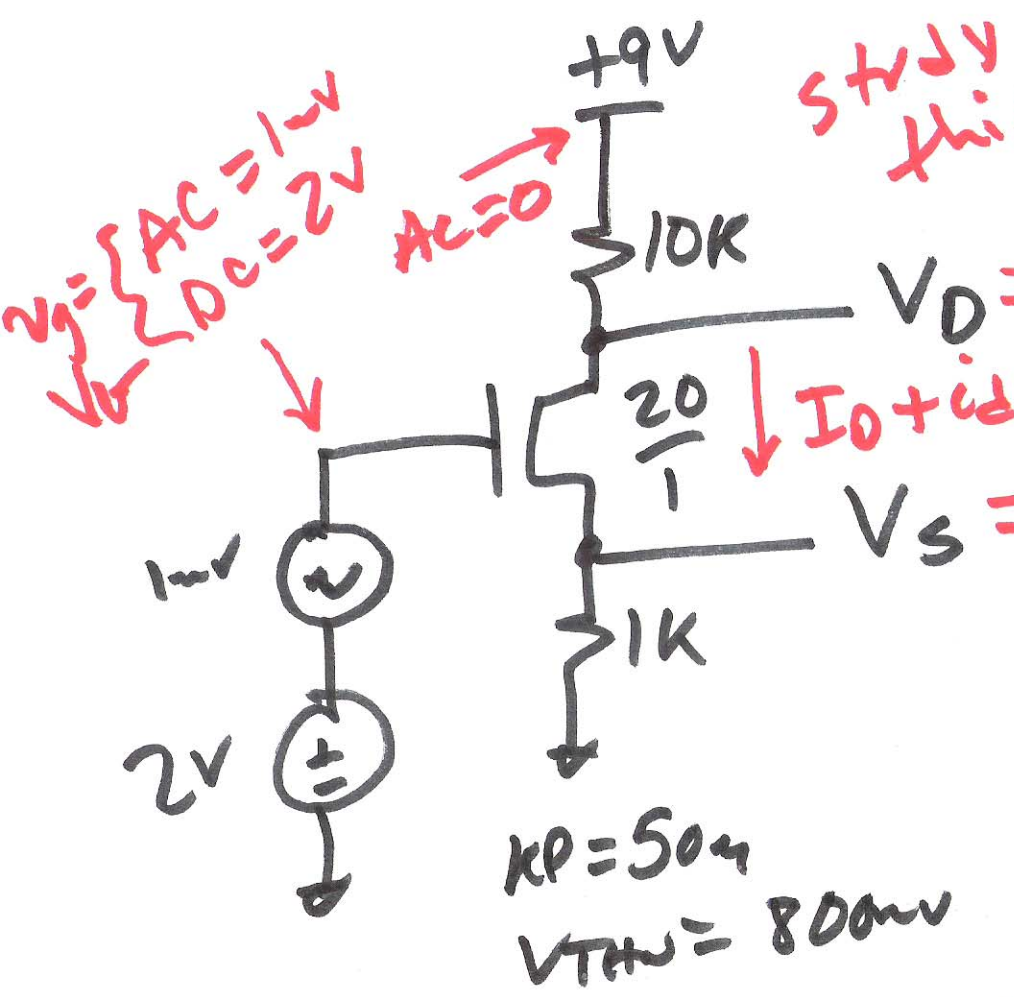

STUDY!
this!

$V_D = \overbrace{9 - I_D \cdot 10K}^{DC} + \overbrace{(-i_d \cdot 10K)}^{AC}$

$V_S = i_D \cdot 1K = \underbrace{I_D \cdot 1K}_{DC} + \underbrace{i_d \cdot 1K}_{AC}$

$I_D = \frac{K_P}{2} \cdot \frac{W}{L} (V_{GS} - V_{TH})^2$
 $\frac{25\mu}{20}$

$I_D = \frac{K_P}{2} \cdot \frac{W}{L} (V_{GS} - V_{TH})^2$
 $\frac{500\mu}{2} \cdot \frac{1\mu}{2} \cdot \frac{10}{2} = V_{GS}$
 $(1.2 - I_D \cdot 1K)^2$

5)

$$\frac{2I_D}{10^{-3}} = 2000 I_D \quad I_D = \frac{10^{-3}}{2} \cdot (1.2 - I_D \cdot 1K)^2$$

$$V_D = 9 - I_D \cdot 10K \quad 2,000 I_D = (1.2 - I_D \cdot 1K)(1.2 - I_D \cdot 1K)$$

$$= 9 - 3564 \cdot 10K \quad I_D 2 \times 10^3 = 1.44 - 2.4K I_D + I_D^2 \cdot 10^6$$

$$= 9 - 3.56V$$

$$V_D = 5.44V$$

$$V_S = 356 mV$$

$$V_{DS} = 1.644V$$

V_D

$$I_D^2 \cdot 10^6 - 4.4K I_D + 1.44 = 0$$


$$I_D^2 - 4.4m I_D + 1.444 = 0$$

$$I_D = \frac{4.4m \pm \sqrt{(4.4m)^2 - 4(1.444)}}{2} \quad \left. \begin{array}{l} \\ \end{array} \right\} 0.00368$$

$$4.04 mA$$

$$3564 A = I_D$$

6)

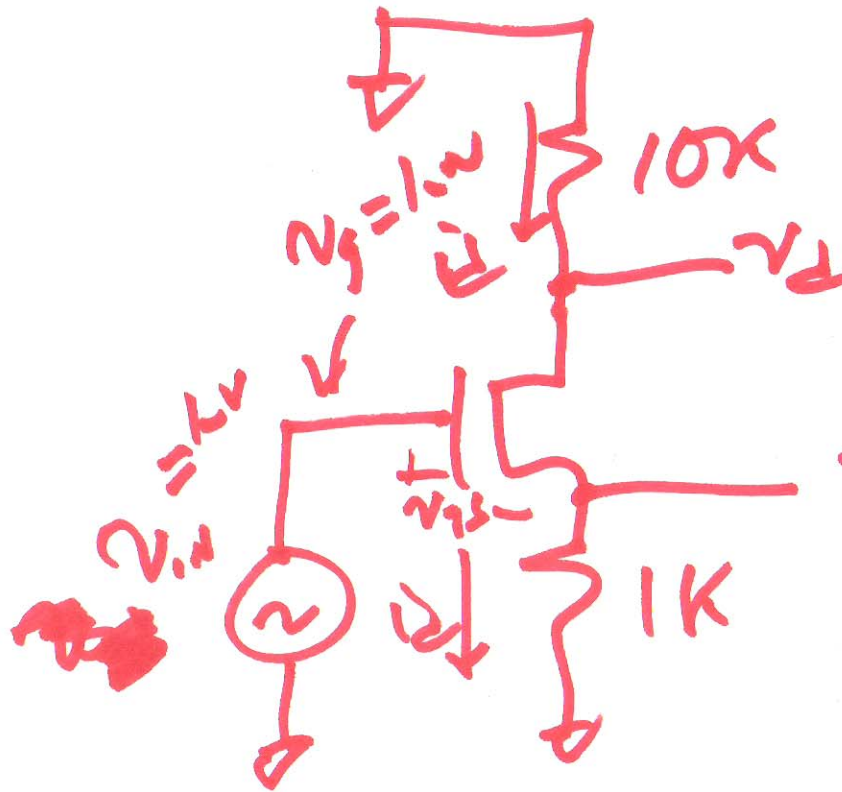

$$\frac{v_d}{v_{in}} = \frac{1K}{\frac{1}{g_m} + 1K}$$


$$v_d = -i_d \cdot 10K \leftarrow$$

$$v_d = i_d \cdot 1K$$

$$i_d = g_m v_{gs} \leftarrow$$


$$v_{in} = v_{gs} + i_d \cdot 1K$$
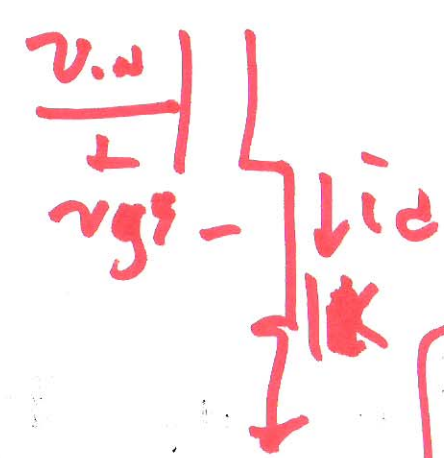
$$= i_d \left(\frac{1}{g_m} + 1K \right)$$



$$\frac{v_d}{v_{in}} = \frac{-10K}{\frac{1}{g_m} + 1K}$$

(11)

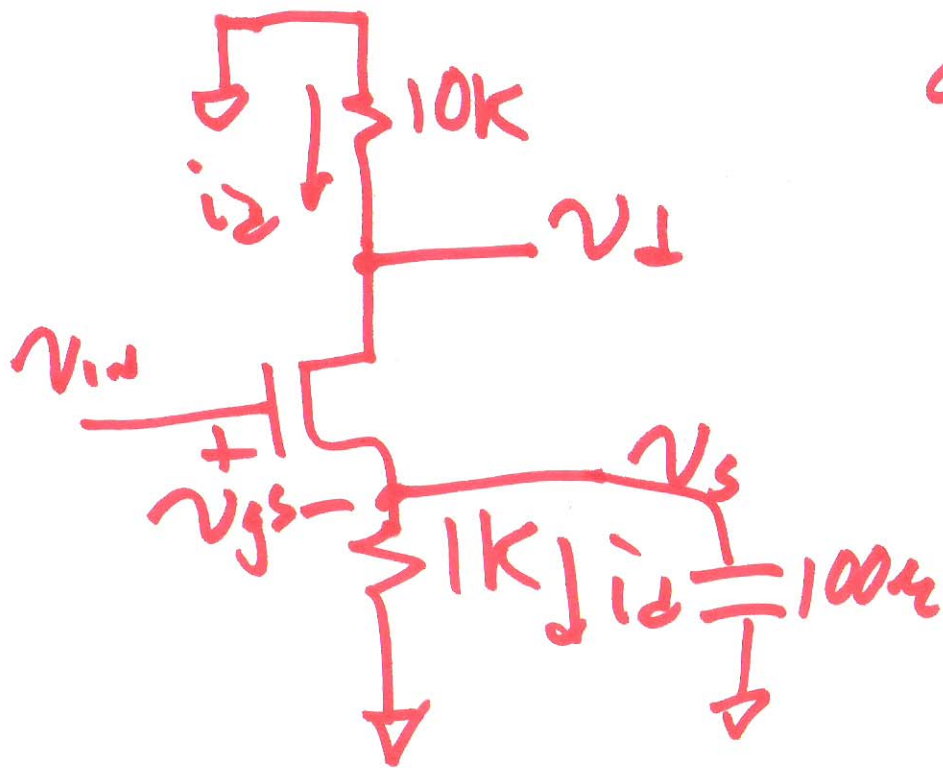

$$g_m = k_p \cdot \frac{W}{L} (V_{GS} - V_{TH})$$

$$= 120 \mu \frac{20}{1} (1.644 - 0.8)$$

$$g_m = 2.02 \mu A$$

$$v_d = -i_d \cdot 10k$$

$$v_w = v_{gs} + 1k \cdot i_d$$

$$i_d = g_m v_{gs}$$

$$\frac{v_d}{v_w} = \frac{-10k}{\frac{1}{2\mu A} + 1k}$$

$$= \frac{-10k}{1500} = i_d \left(\frac{1}{g_m} + 1k \right)$$

$$\approx -6.66 v_s = i_d \cdot 1k$$

$$\frac{v_s}{v_w} = \frac{1k}{1.5k} = .666$$

8)