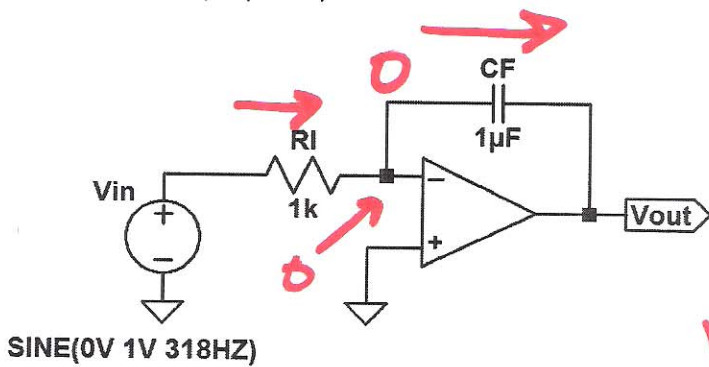


# Lecture 19, April 14, 2014

Midterm2 EE 320 Electronics, Spring 2014 Name: \_\_\_\_\_

- Closed notes, open book, **show your work** (hand calculations, including algebra) for credit.
- No scratch paper is allowed.
- Unless otherwise indicated use  $KP_N = 120 \mu\text{A}/\text{V}^2$ ,  $KP_P = 40 \mu\text{A}/\text{V}^2$ ,  $V_{THN} = 800 \text{ mV}$ ,  $V_{THP} = 900 \text{ mV}$ ,  $W = 10 \mu\text{m}$ ,  $L = 1 \mu\text{m}$ , and  $C_{ox} = 1.75 \text{ fF}/\mu\text{m}^2$ .

1. The input to the integrator seen below is a sinusoid having a peak amplitude of 1 V and a frequency of 318 Hz. Calculate the amplitude and phase shift of the output voltage assuming an ideal op-amp is used. Sketch the circuits' input and output voltage on the same plot in the time domain. (20 points)



$$\frac{V_{in}}{1k} = \frac{0 - V_{out}}{j\omega C}$$

$$\frac{V_{out}}{V_{in}} = \frac{-1}{j\omega 10^{-6} \cdot 10^3}$$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{2\pi \cdot 318 \cdot 10^{-3}}$$

$$\left| \frac{1}{0 + ja} \right| = \frac{1}{\sqrt{0^2 + a^2}}$$

$\uparrow +90^\circ$


$$\boxed{\frac{V_{out}}{V_{in}} = 0.5}$$
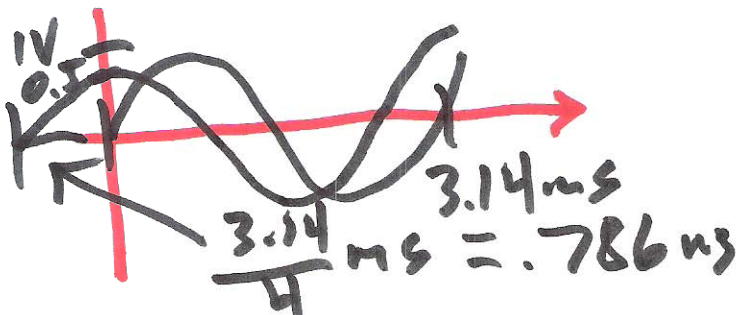
$$\angle \frac{V_{out}}{V_{in}} = \angle \frac{j}{j} \cdot \frac{-1}{j\omega 10^{-3}} = 2\pi \cdot 318 \cdot \tan^{-1} \frac{1}{\pi \cdot 318}$$



$$\boxed{\angle \frac{V_{out}}{V_{in}} = +90^\circ}$$

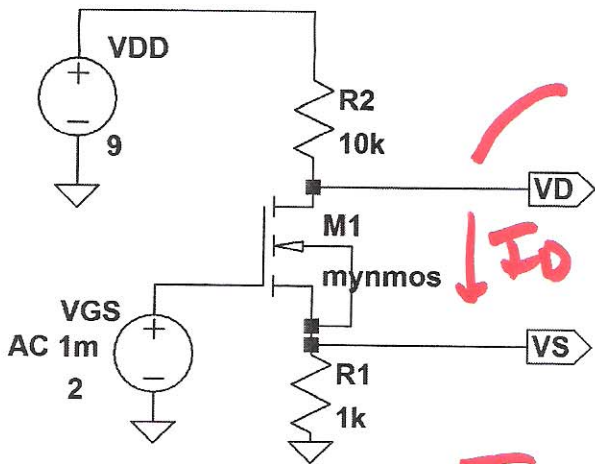2. Calculate the AC and DC voltages on the gate, drain, and source of the NMOS transistor in the following circuit. Show your work for credit. (20 points)



$$V_D = 9 - 10k \cdot I_D$$

$$V_G = 2V$$

$$V_S = 1k \cdot I_D$$

$$I_D = \frac{120\mu A/V^2}{2} \cdot \frac{10}{1} \cdot (V_{GS} - 0.8)^2$$

$$I_D = 600\mu (2 - I_D \cdot 1k - 0.8)^2$$

$$= 600\mu (1.2 - I_D \cdot 1k)^2$$

$$I_D = 600\mu (1.44 - 2.4kI_D + I_D^2 \cdot 10^6)$$

$$I_D = 600I_D^2 - 1.44I_D + 864\mu$$

$$0 = I_D^2 + \frac{-2.44}{600} I_D + \frac{864\mu}{600}$$

$$0 = I_D^2 + (-4.067m)I_D + 1.44\mu$$

$$I_D = \frac{4.067 \text{ m} \pm \sqrt{(4.067 \text{ m})^2 - 4(1.44 \mu)\cdot 1}}{2}$$

$$= \frac{4.067 \text{ m} \pm \sqrt{\cancel{6.757 \text{ m}^2} - 5.76 \mu}}{2}$$

$$= \frac{4.067 \text{ m} \pm 3.28 \text{ m}}{2}$$

$$V_D = 9 - 10 \text{ k} \cdot 393 \mu = 5.07 \text{ V}$$

$$V_G = 2 \text{ V}$$

$$V_S = 1 \text{ k} \cdot I_D = 393 \text{ mV}$$

$$I_D = 393 \mu$$

$$g_m = \text{kp} \cdot \frac{W}{L} (V_{GS} - V_{TH})$$


$$= 120 \mu \cdot \frac{10}{1} (2 - 0.8)$$

$$g_m = 968 \mu \text{ S/V}$$

CMOSedu.com



$$g_m = 9684 \text{ A/V}$$

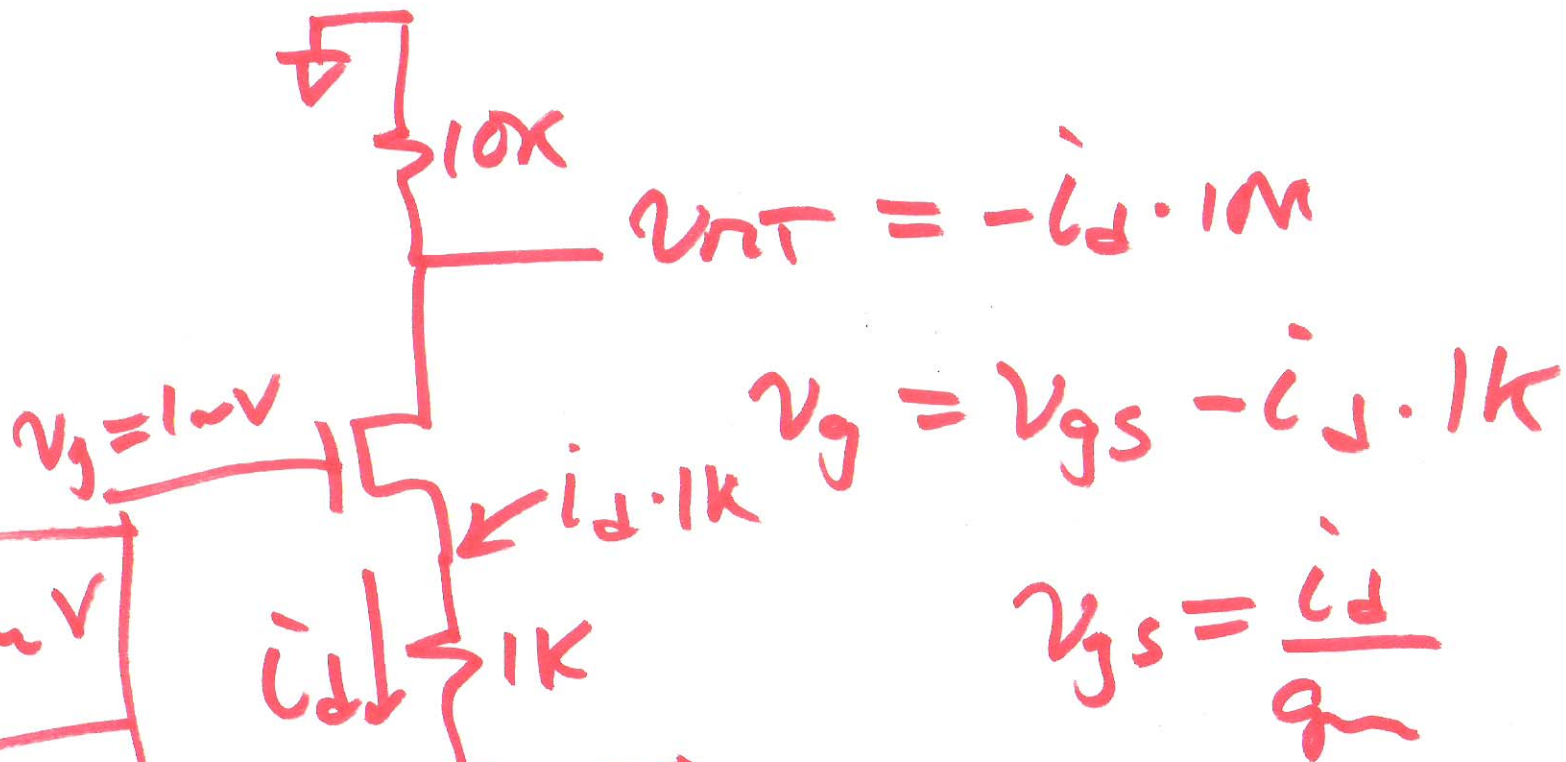

$$v_g = 1 \text{ mV}$$

$$i_d \cdot 1 \text{ k}$$

$$v_s = i_d \cdot 1 \text{ k} \approx 500 \mu \text{ V}$$

$$v_D = -i_D \cdot 10 \text{ k} \approx -5 \text{ mV}$$


$$1 \text{ mV} = i_D \left( \frac{1}{9684} + 1 \text{ k} \right)$$

$$i_D \approx 500 \text{ nA}$$

$$\approx 2 \text{ k}$$

4)

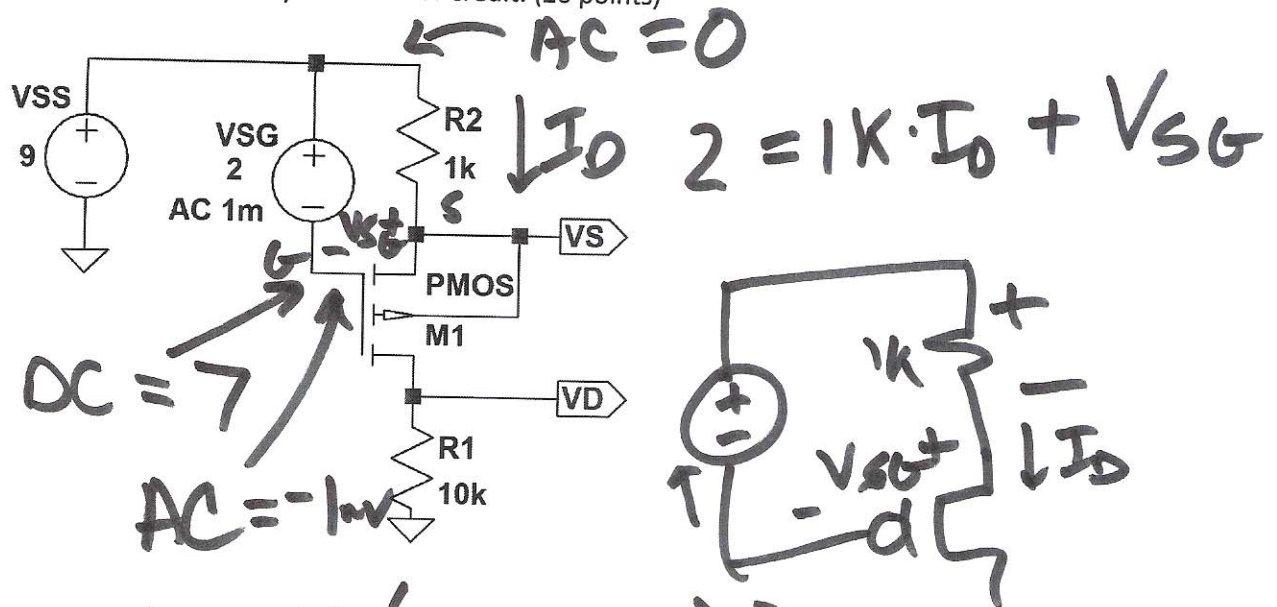3. Calculate the AC and DC voltages on the gate, drain, and source of the PMOS transistor in the following circuit. Show your work for credit. (20 points)



$$I_D = \frac{40\mu}{2} \cdot \frac{10}{1} (V_{SG} - .9)^2$$

$$2 = 1k \cdot 200\mu (V_{SG}^2 - 1.8V_{SG} + .81)$$

$$2 = 0.2V_{SG}^2 - .36V_{SG} + .162 + V_{SG}$$

$$0 = 0.2V_{SG}^2 + ~~1.64~~ .64V_{SG} - 1.838$$

$$0 = V_{SG}^2 + 3.2V_{SG} - 9.19$$

$$V_{SG} = \frac{-3.2 \pm \sqrt{~~3.16~~ 10.24 + 36.76}}{2}$$

5)

$$V_{SG} = \frac{-3.2 \pm 6.85}{2} = 1.83V$$

$$V_S = -i_D \cdot 1K = 270\mu V$$

$$\frac{2 - 1.83}{1K} = I_D = 170\mu A$$

$$g_m = 40\mu \frac{10}{\sqrt{2I_D}} (1.83 - 0.9)V$$

$$g_m = 400\mu \cdot 0.93$$


$$g_m = 372\mu A/V$$

$$V_G = 7$$

$$V_D = I_D \cdot 10K = 1.7V$$

$$V_S = 9 - 1K \cdot I_D = 8.83V$$

$$I_D = 170\mu A$$

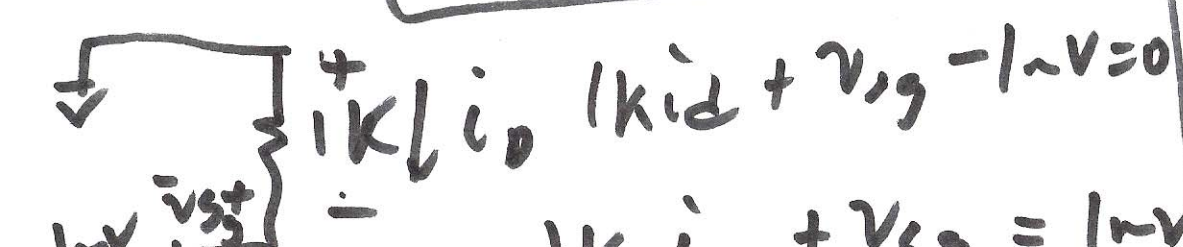

$$1K \cdot i_D + V_{SG} = 1\mu V$$

$$V_S = -270\mu V$$

$$V_G = -1\mu V$$


$$V_D = 2.71mV$$

$$i_D = \frac{1\mu V}{1K + \frac{1}{372\mu}} = 271\mu A$$

$$V_D = 271\mu A \cdot 1K = 271\mu V = 2.71\mu V$$



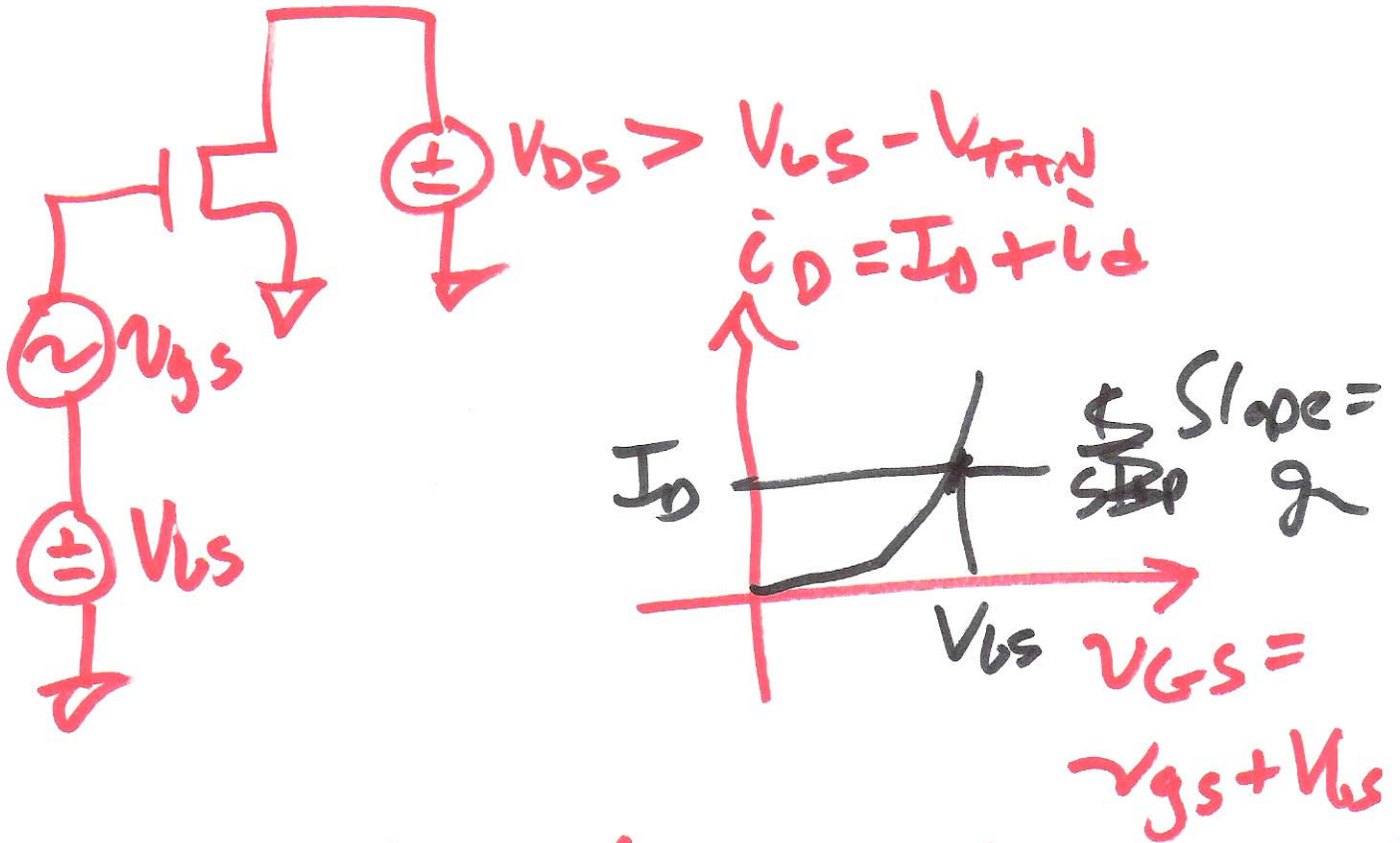4. Show, using both figures and equations, how to derive the small-signal transconductance of an NMOS transistor. (20 points)




$$g_m = \frac{\delta(I_D + i_d)}{\delta v_{GS}} = \frac{\delta \left( \frac{K_P}{2} \cdot \frac{W}{L} (v_{gs} + v_{ds} - V_{THN})^2 \right)}{\delta v_{GS}}$$

$I_D = \text{CONST}$   
 $v_{ds} = \text{CONST}$

$v_{ds} \gg v_{gs}$   
 $g_m = K_P \cdot \frac{W}{L} (v_{ds} + v_{gs} - V_{THN})$   
 $g_m = K_P \cdot \frac{W}{L} (v_{ds} - V_{THN})$



7)

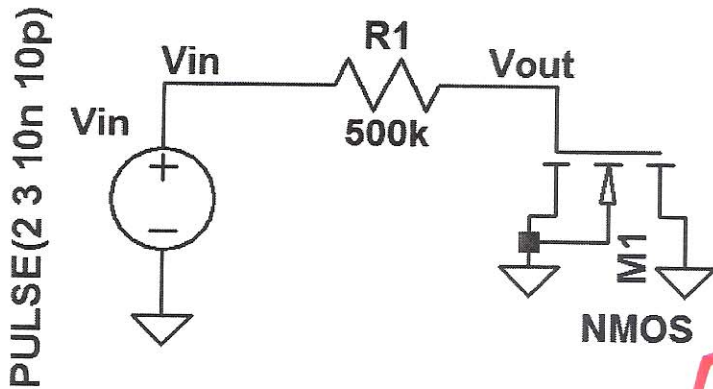5. Sketch  $V_{in}$  and  $V_{out}$  versus time on the same plot for the following circuit. Note that  $V_{in}$  is a pulse transitioning at 10 ns from 2 to 3 V in 10 ps. (20 points)



$$C_{ox} = 1.75 \text{ fF} \cdot 10 \cdot 1$$

$$C_{ox} = 17.5 \text{ fF}$$

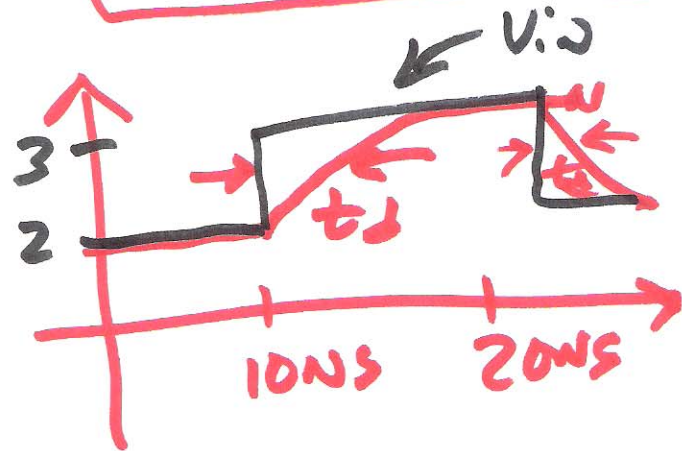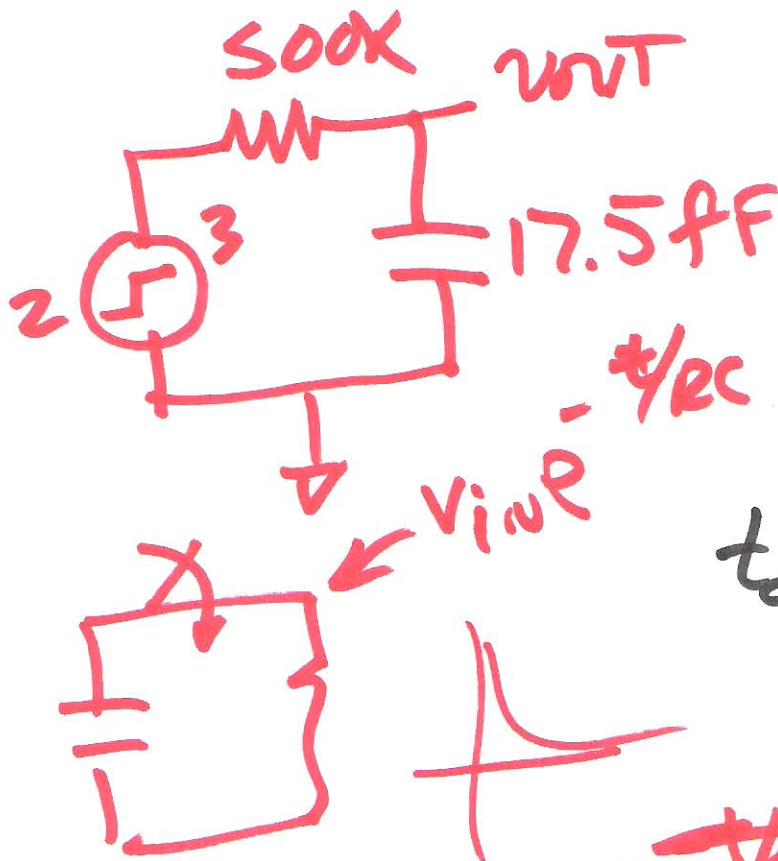

$$t_d = 0.7RC$$



$$= 0.7 \cdot 500k \cdot 17.5f$$


$$t_d = 6.125 \text{ ns}$$

$$V_{out} = 2 + 1 \cdot \left( 1 - e^{-t/RC} \right)$$

8)



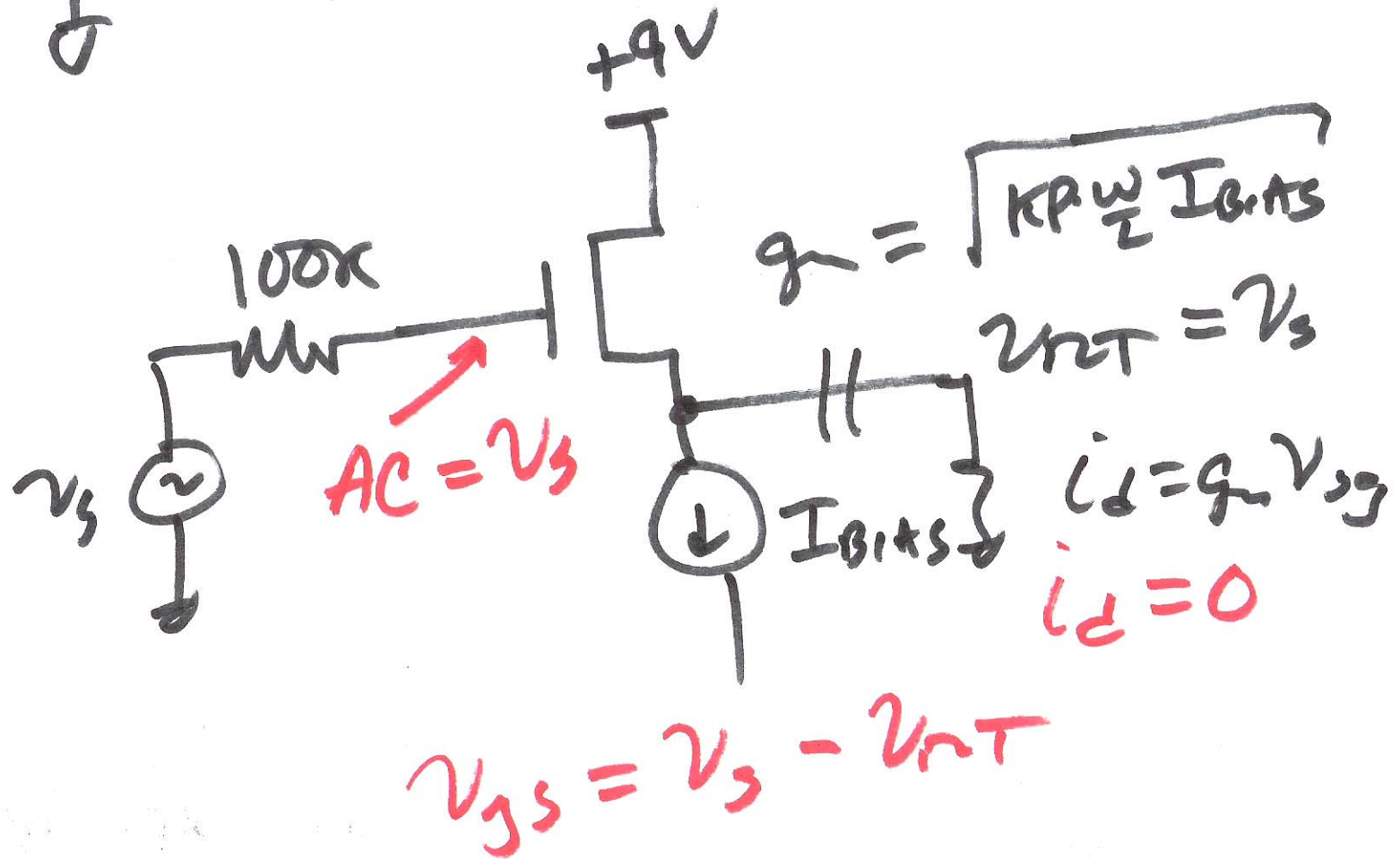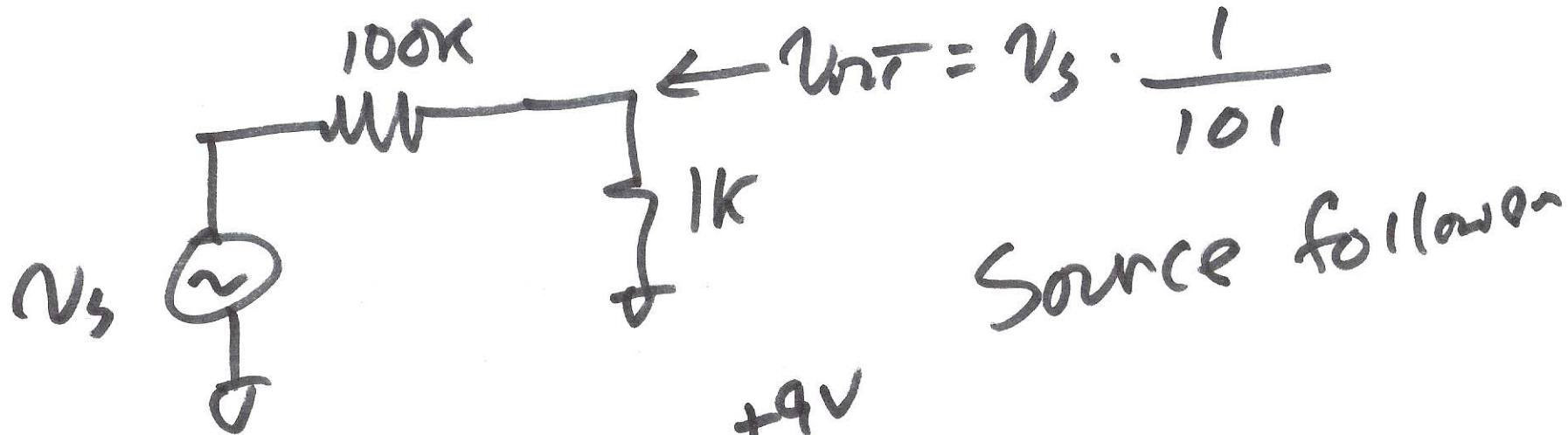

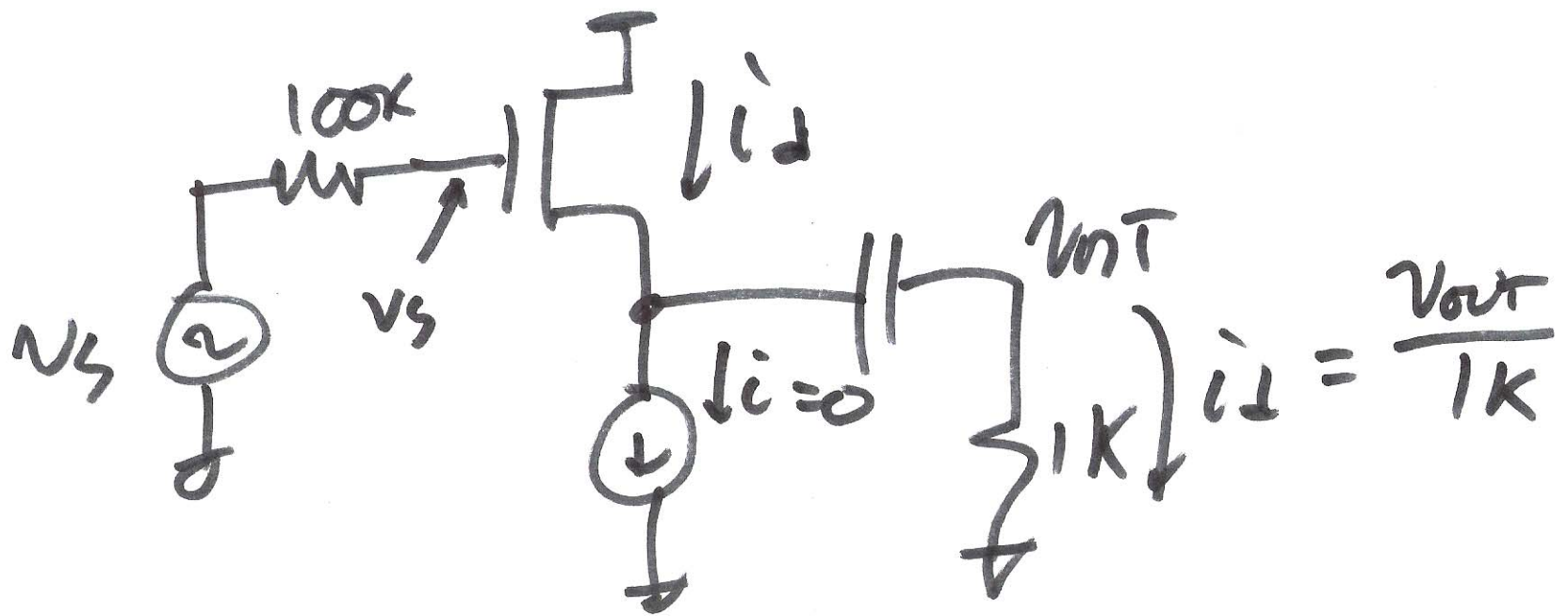

$$g_m = 1 \mu A/V \quad i_d = \frac{2mV}{1k} = g_m (v_s - 2mV)$$

$$\frac{2mV}{v_s} = \frac{1 \mu A/V}{\frac{1 \mu A}{V} + \frac{1 \mu A}{V}} = \frac{1}{2} v_{out} \left( \frac{1}{1k} + g_m \right) = g_m v_{gs}$$

$$\frac{v_{out}}{v_s} = \frac{g_m}{1k + g_m}$$