

EE 320

Engineering




Electronics I


1/22/14

Spring

2014

Lecture 1

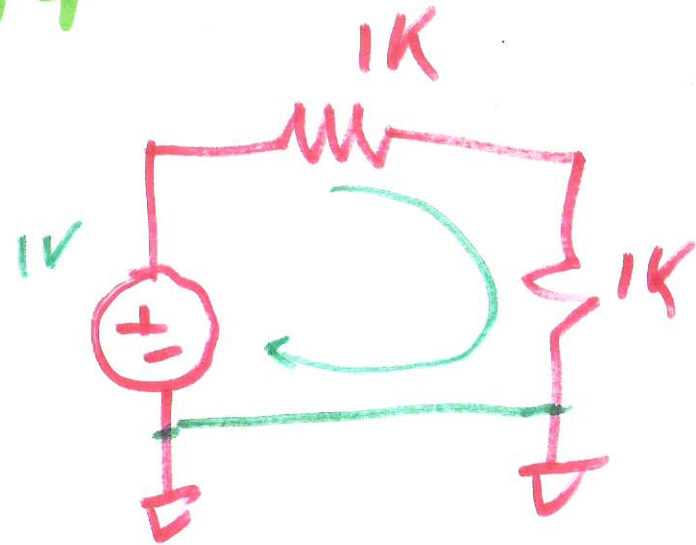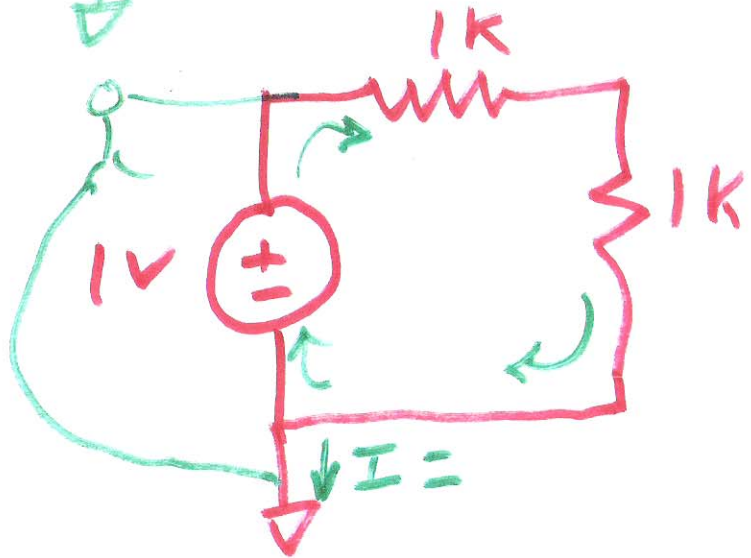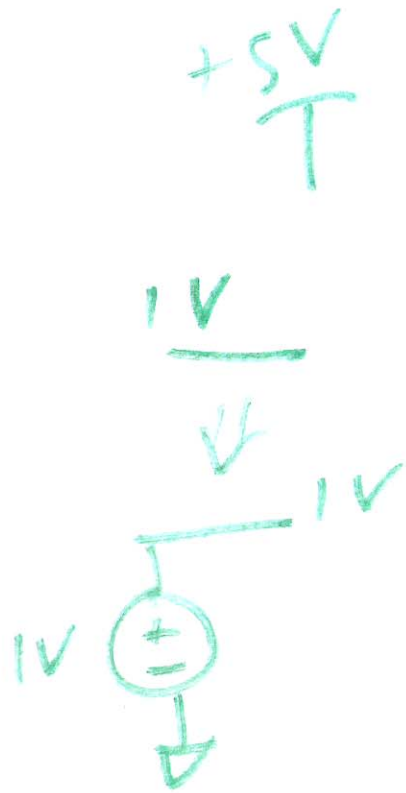

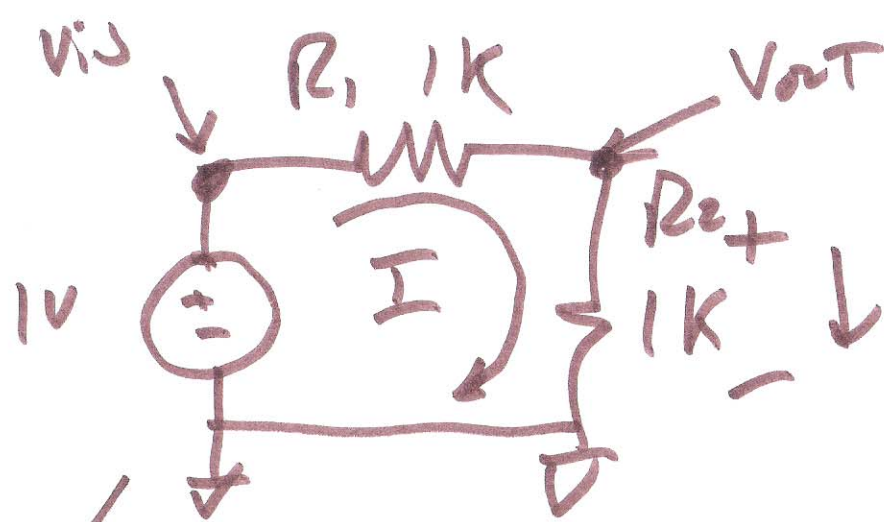

$$I = \frac{V}{R} = \frac{1V}{2k}$$

$$I = \frac{1 \cdot 10^0}{2 \cdot 10^3}$$

$$= \frac{1}{2} \cdot 10^{-3}$$

$$= \frac{1}{2} \text{ mA}$$

$$= 500 \mu\text{A}$$


$$V_{in} = 1V$$


$$V_{out} = 1k \cdot \frac{1}{2} \text{ mA}$$

$$= \frac{1}{2} V$$

$$V_{in} - V_{out} = 1 - \frac{1}{2} = \frac{1}{2}$$
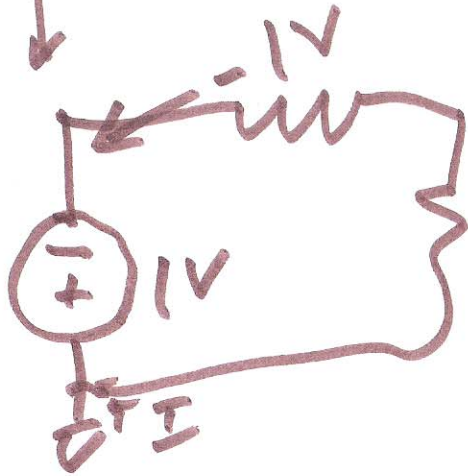
$$V_{out} = \frac{V_{in}}{R_1 + R_2} \cdot R_2 = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$



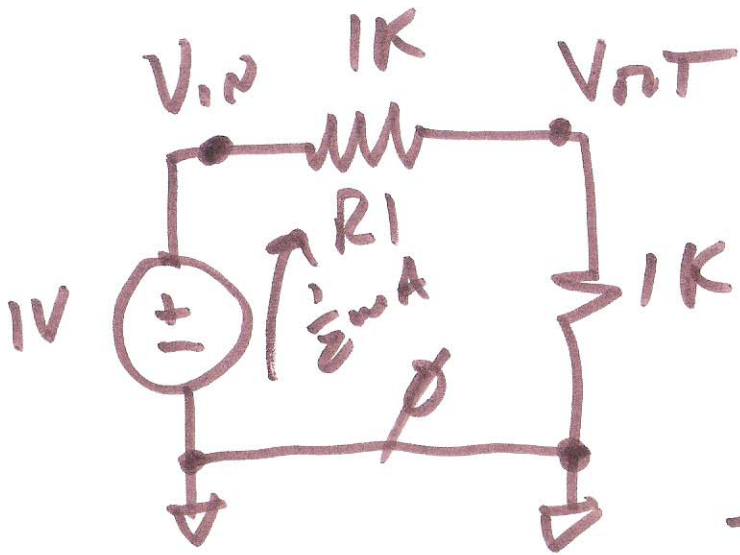

Prob. 1a H.w. #1


Vin	Vin	0	DC	1
R1	Vin	Vout	1K	
R2	Vout	0	1K	

$$\frac{1}{10^3} = 10^{-3}$$


$$\frac{1}{200} = \frac{1}{\frac{1}{5} \cdot 10^3} = 5ms$$

.OP

Prob 1c

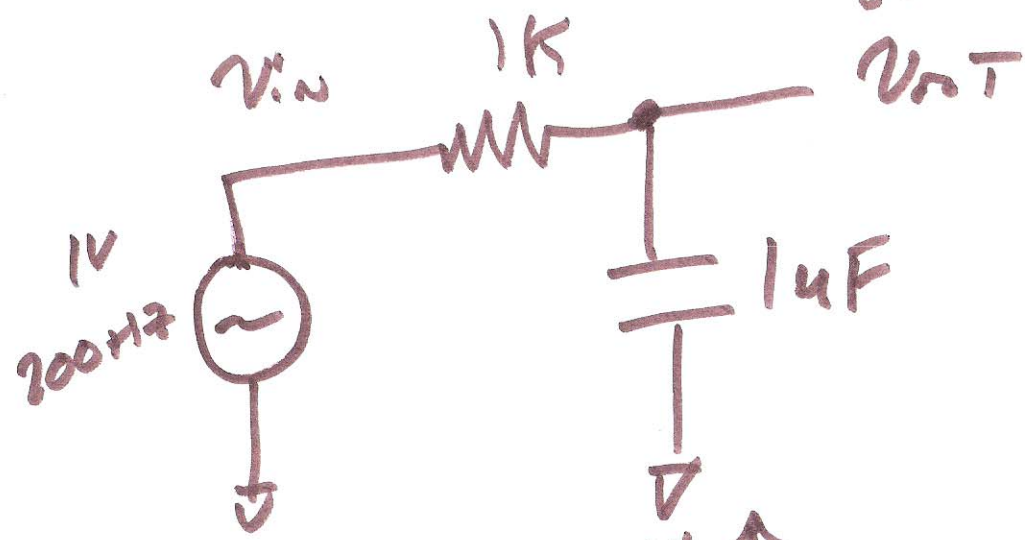


RA	Vin	Vout	1K
CA	Vout	0	1u
Vin	Vin	0	2

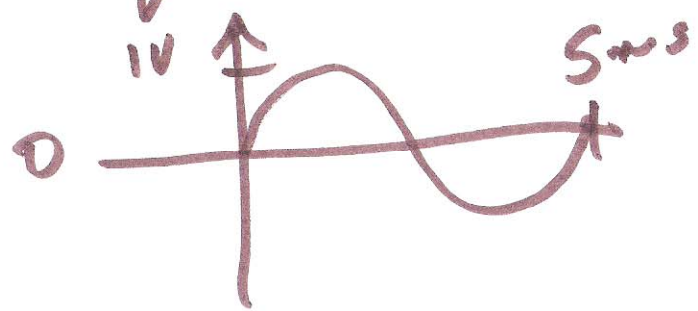

SIN 0 1V 200
 .tran 2000
 offset
 ↑ peak ↑ freq.
 CMOSedu.com

3)

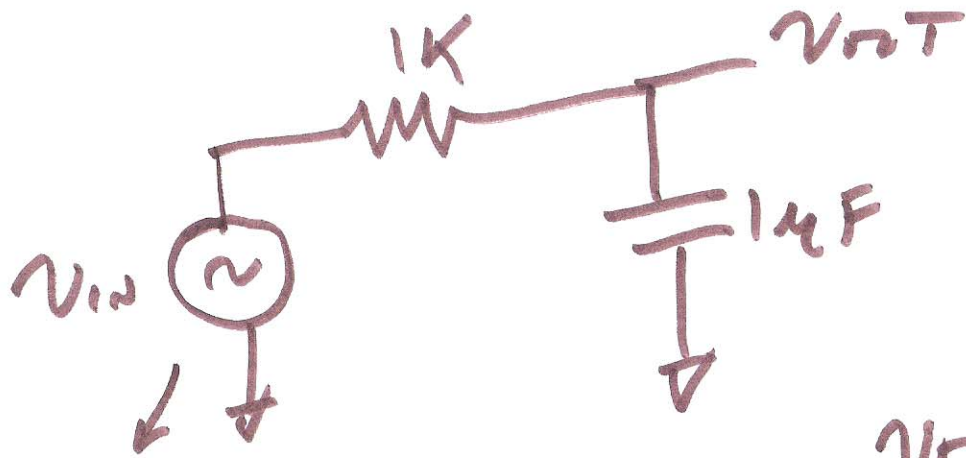

$$V_p = 1V, \angle$$

$$f = 200$$

$$\frac{3.14 \cdot 1}{1.256}$$

$$\frac{1.2}{1.6}$$

$$|a + ib| = \sqrt{a^2 + b^2}$$

$$1.256$$

$$\frac{v_{out}}{v_{in}} =$$

$$\tan^{-1} \frac{b}{a}$$

$$v_{out} = \frac{1}{1 + j1.26}$$

$$v_{out} = \frac{v_{in} \cdot \frac{1}{j \cdot 2\pi f \cdot 10^{-6}}}{1k + \frac{1}{j \cdot 2\pi f \cdot 10^{-6}}}$$

$$1 + j2\pi f \cdot 10^{-3}$$

$$1 + j \cdot 2\pi \cdot 200 \cdot 10^{-6}$$

$$1 + j0.4\pi$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1^2 + (1.26)^2}} = .62$$

$$\angle \frac{V_{out}}{V_{in}} = -\tan^{-1} 1.26 = -.9 \cdot \frac{360}{2\pi} = -51.56$$

$$\theta = \frac{\Delta t}{T} \cdot 360 = f \cdot \Delta t \cdot 360$$

$$51.56 = \frac{\Delta t}{5\text{ms}} \cdot 360$$

$$\frac{1}{7} \cdot 5\text{ms} = \Delta t \approx 700\mu\text{s}$$

5)