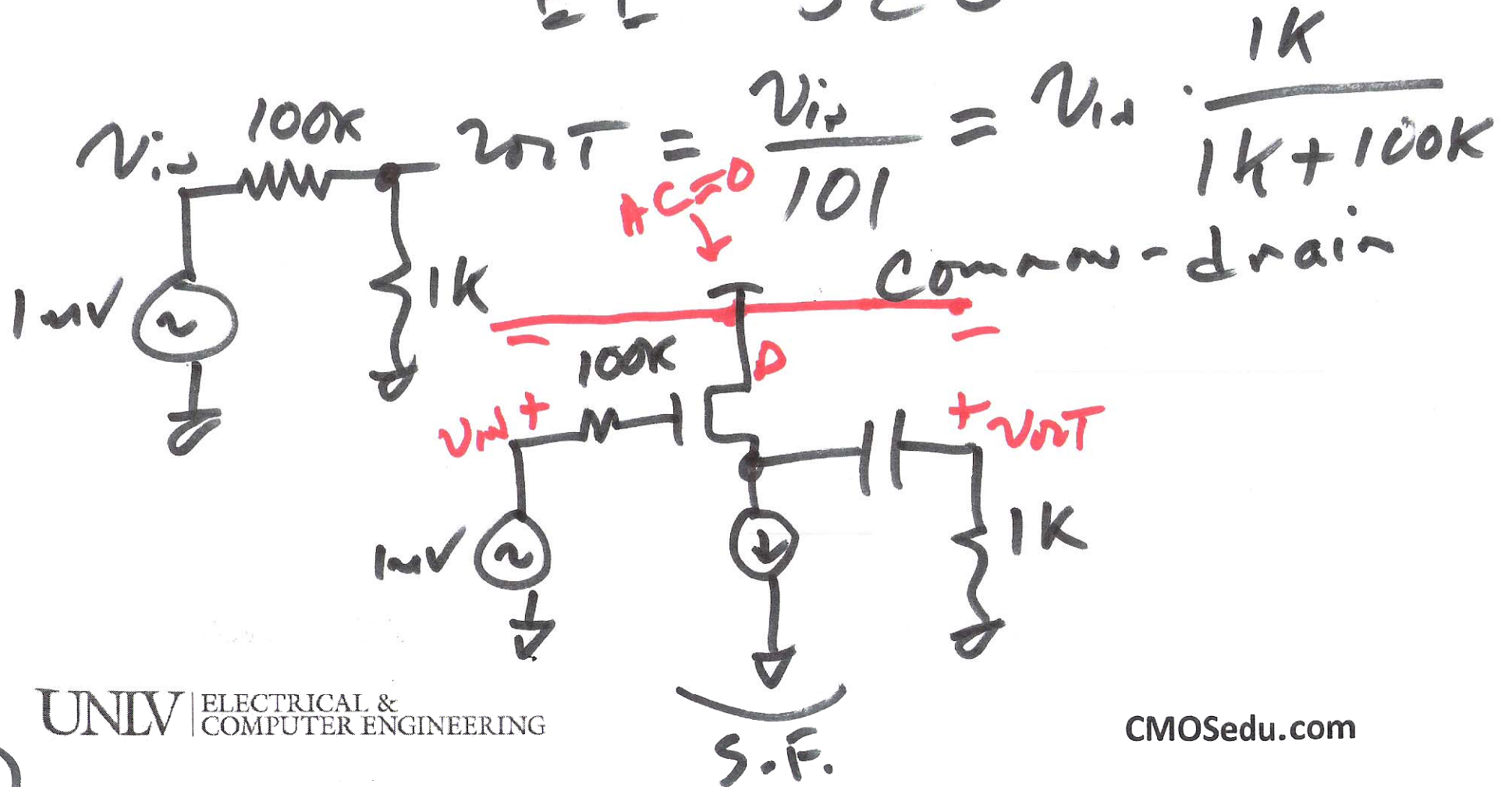



Lecture 20

April 16, 2014

EE 320


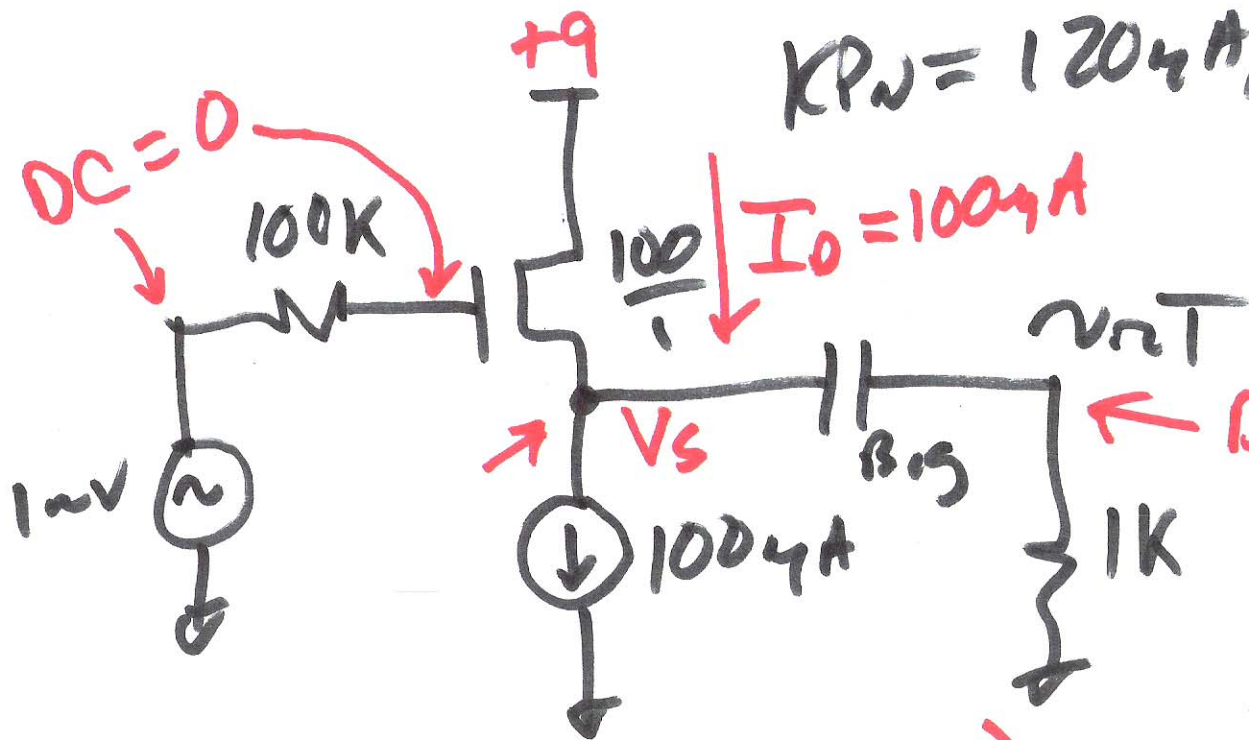
$$K_{PN} = 120 \mu\text{A}/\text{V}^2 \quad V_{TH} = 800\text{mV}$$



$$V_{GS} = \sqrt{\frac{2I_D}{K_{PN} \frac{W}{L}}} + V_{TH}$$

$$I_D = \frac{K_{PN} W}{2 L} (V_{GS} - V_{TH})^2$$

$$g_m = \frac{120 \mu\text{A}}{\text{V}^2} \cdot \frac{100}{1} (.92 - .8)$$

$$100 \mu\text{A} = \frac{120 \mu\text{A}}{\text{V}^2} \cdot \frac{100}{1} (0 - V_S - .8)^2$$


$$= 120 \mu \cdot 12$$

$$g_m = 1.44 \frac{\text{mA}}{\text{V}}$$


$$V_{GS} = 0 - V_S = \frac{.92}{\sqrt{\frac{200}{120 \cdot 100} + .8}}$$

$$V_S = -.92$$

2)

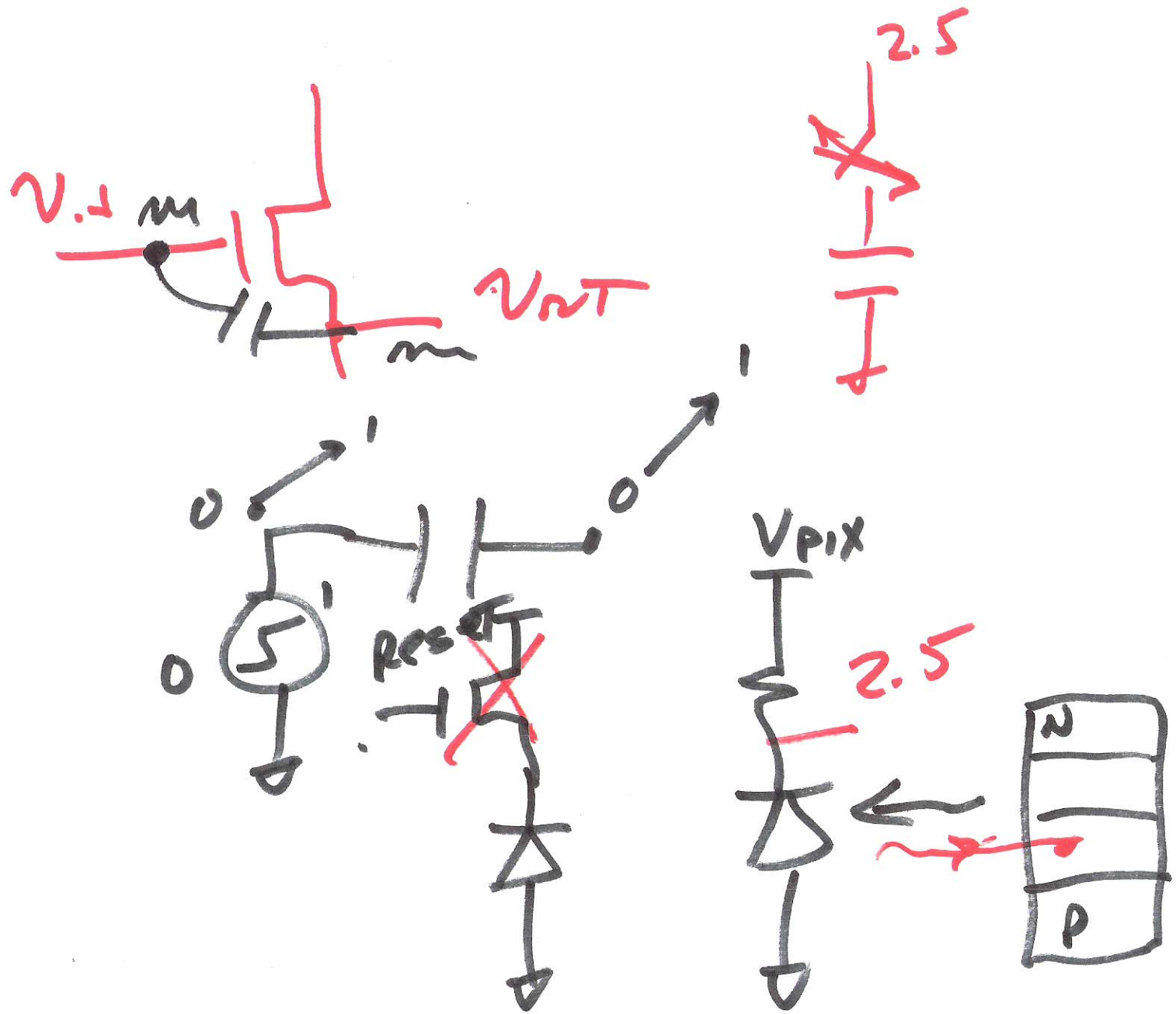

4)

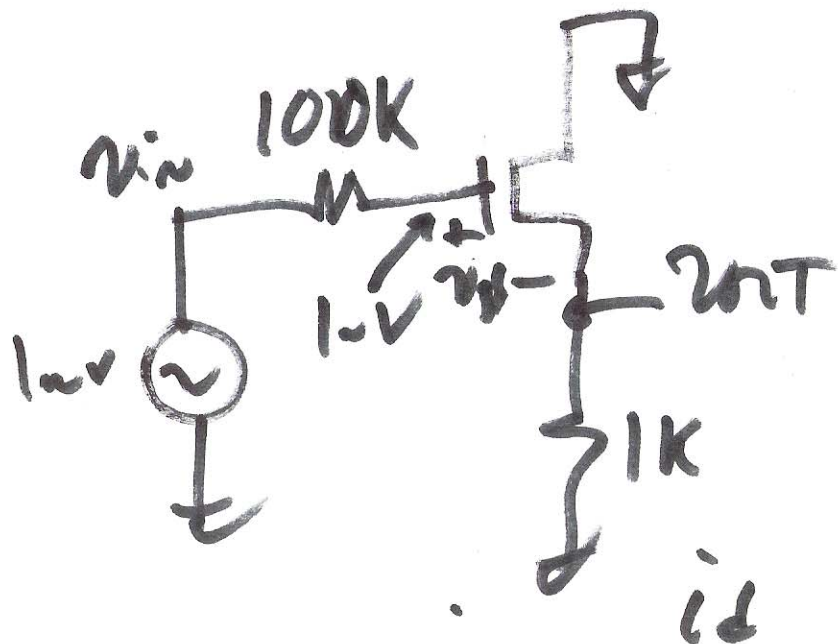

$$1mV = V_{gs} + i_d \cdot 1k$$

$$V_{gs} = \frac{i_d}{g_m}$$

$$1mV = i_d \left(\frac{1}{g_m} + 1k \right)$$

$$V_{out} = 1k \cdot \cancel{1.44} \cdot .594$$

$$= \cancel{1.44} \mu V$$

$$= \underline{\underline{0.59 \mu V}}$$

$$\underline{\underline{0.01 \mu V}}$$


$$g_m = 1.44 \mu A$$



$$i_d = \frac{1mV}{1694}$$

$$= \cancel{1.44} \mu A$$

$$\cdot .594$$

3)

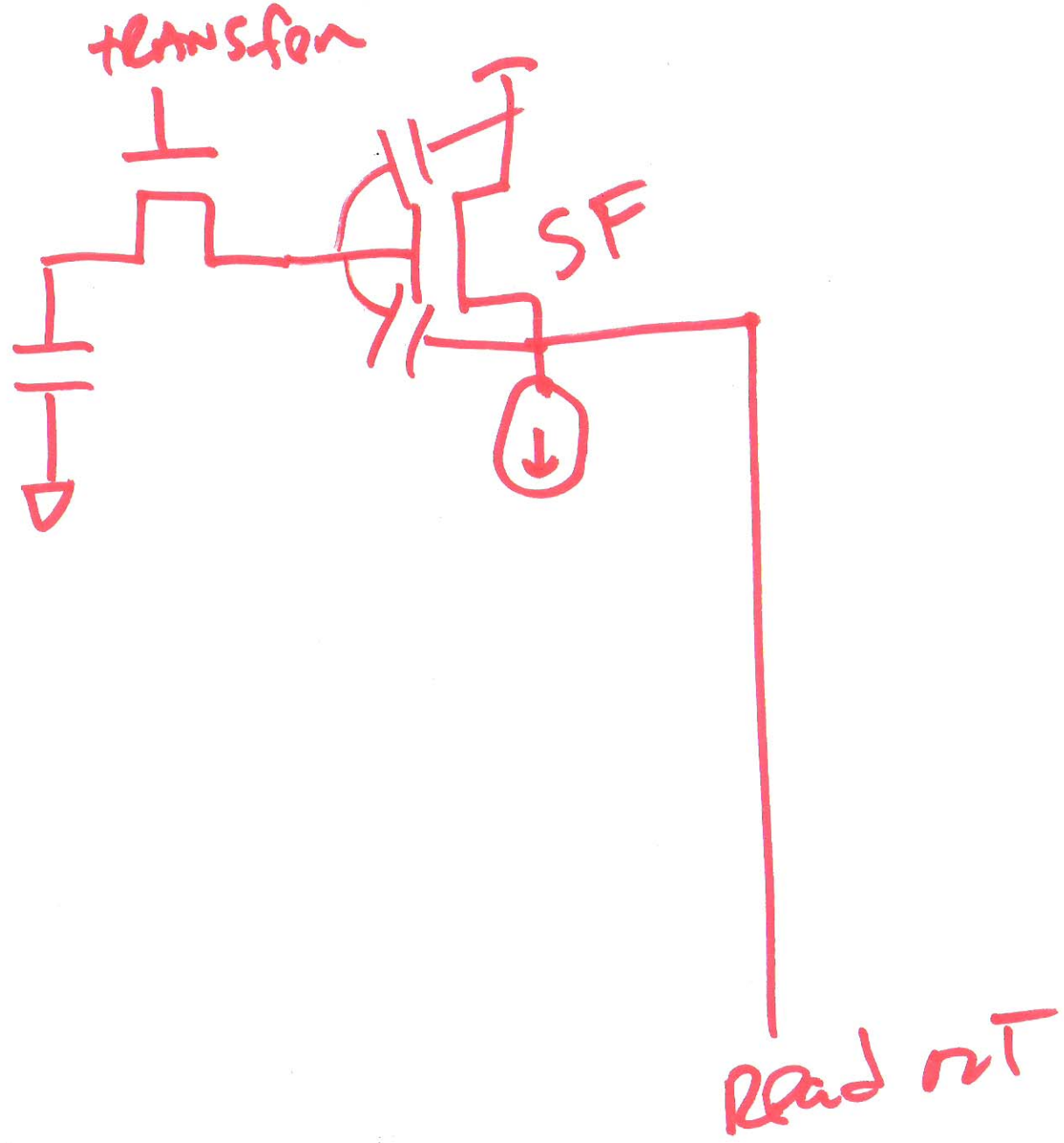


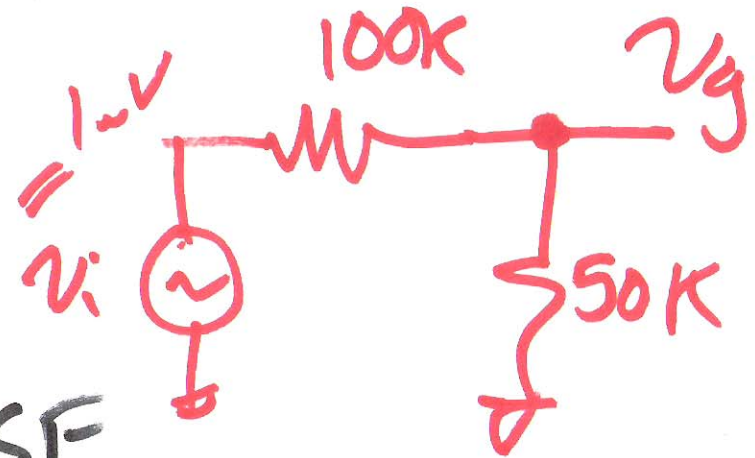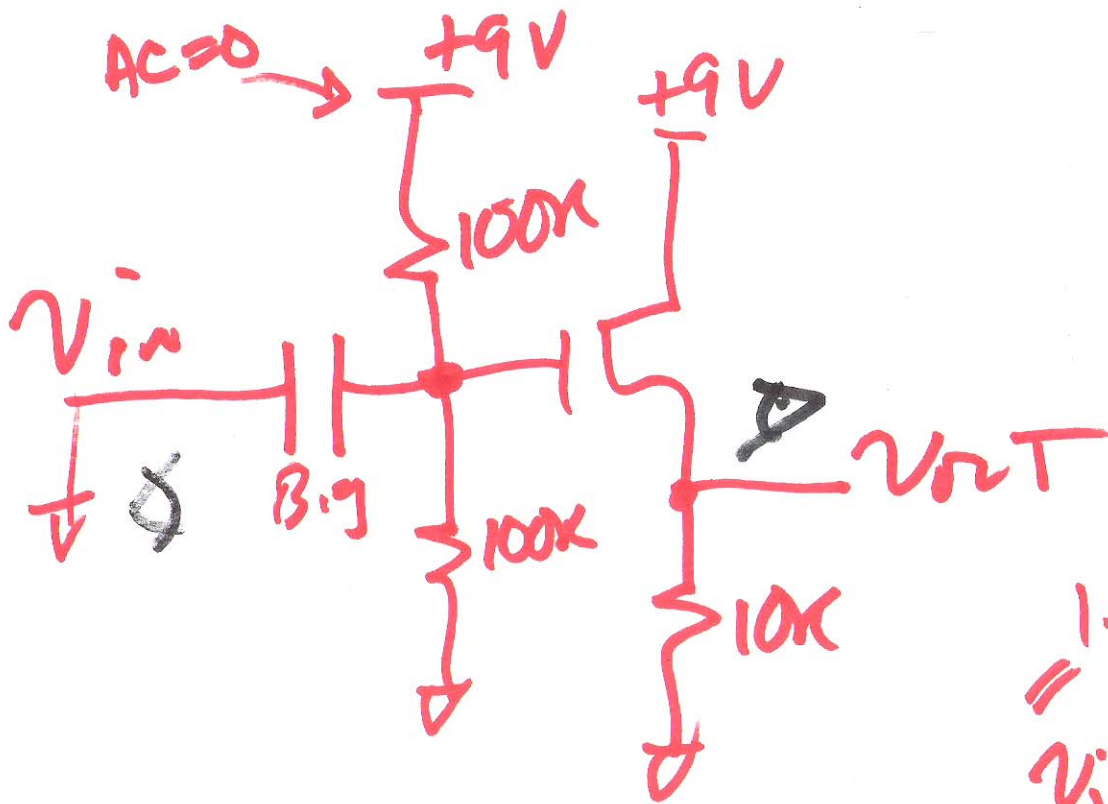

$R_{in} = ?$ of this SF

$$V_g = V_i \frac{.50k}{100k + 50k}$$

6)

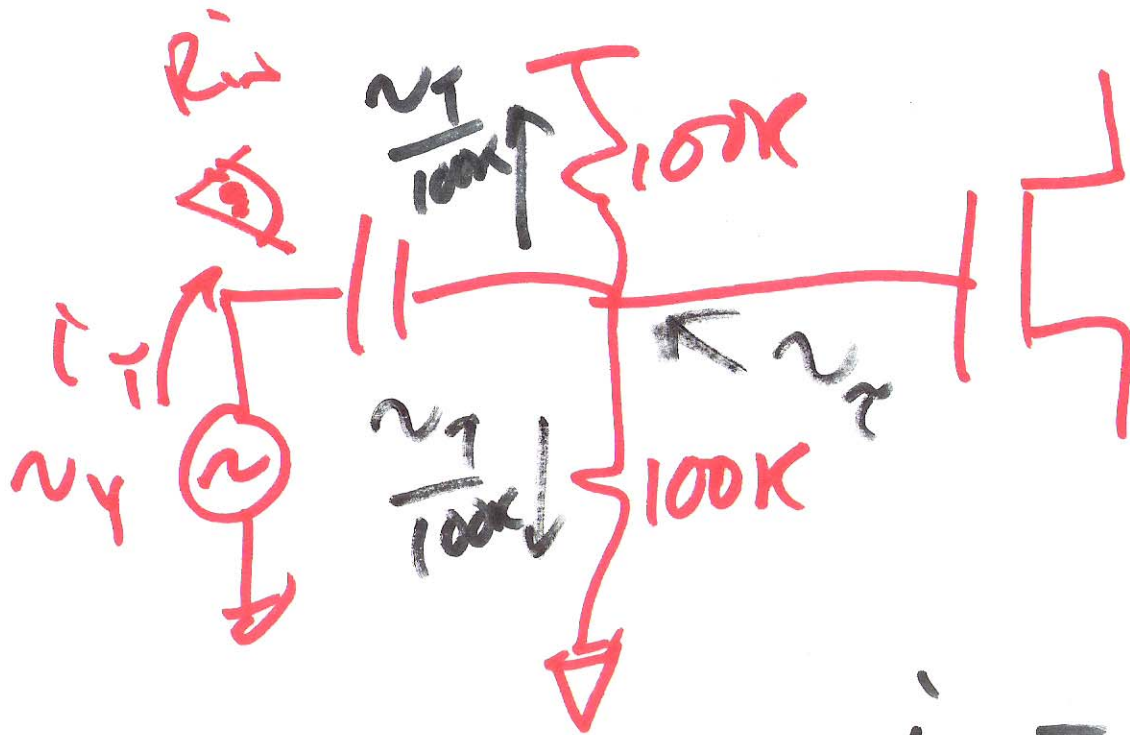


$$R_{in} = \frac{v_T}{i_T}$$

$$i_T = \frac{v_T}{100k} + \frac{v_T}{100k}$$

$$R_{in} = \frac{v_T}{i_T} = \frac{1}{\frac{1}{100k} + \frac{1}{100k}}$$

$$= 100k \parallel 100k$$

$$= 50k$$

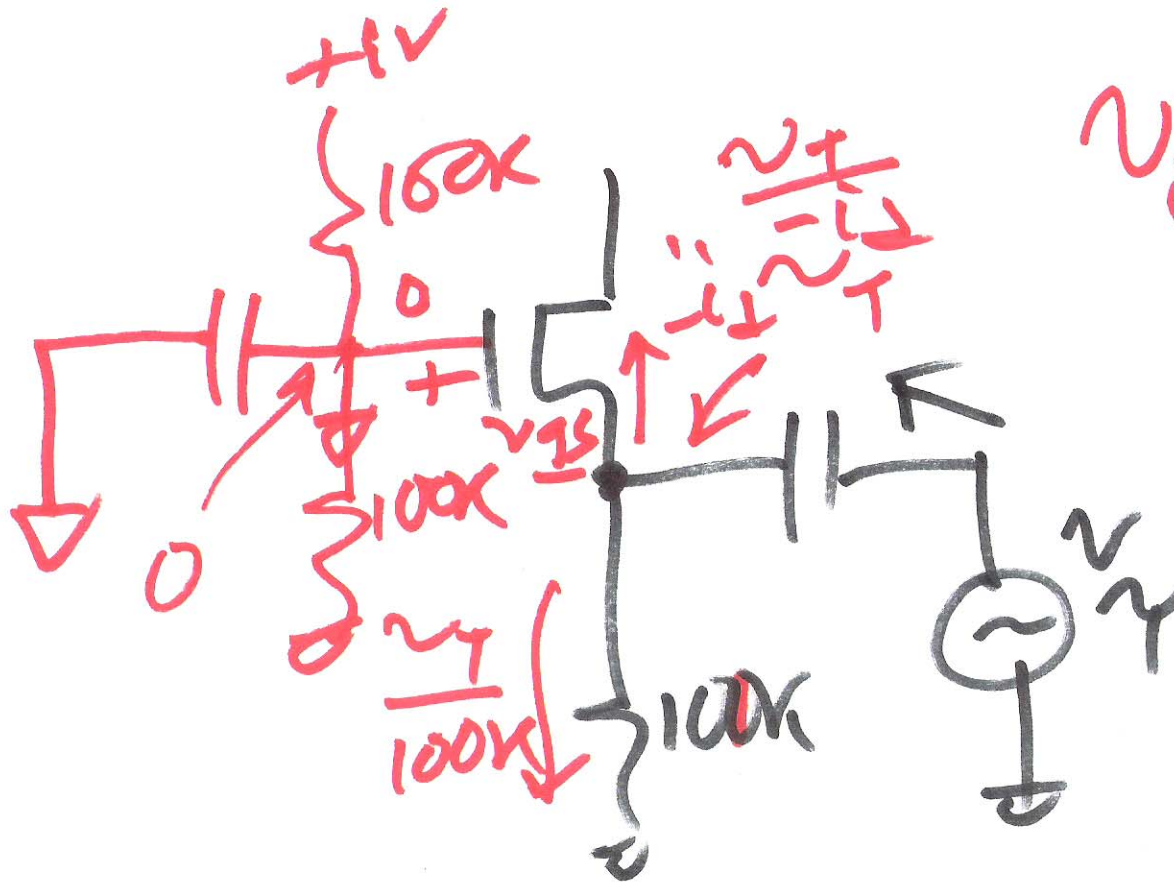


$$v_{gs} = 0 - v_T$$

$$v_{gs} = -v_T$$

$$v_{gs} = \frac{i_d}{g_m}$$

$$-v_T = \frac{i_d}{g_m}$$

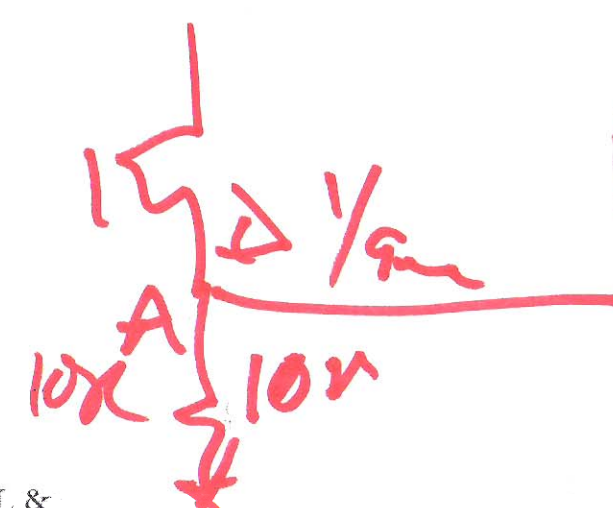


$$R_{out} = 100k \parallel \frac{1}{g_m}$$

$$100k \parallel \frac{1}{0.00288}$$

$$\approx \frac{1}{g_m}$$

$$= 340\Omega$$

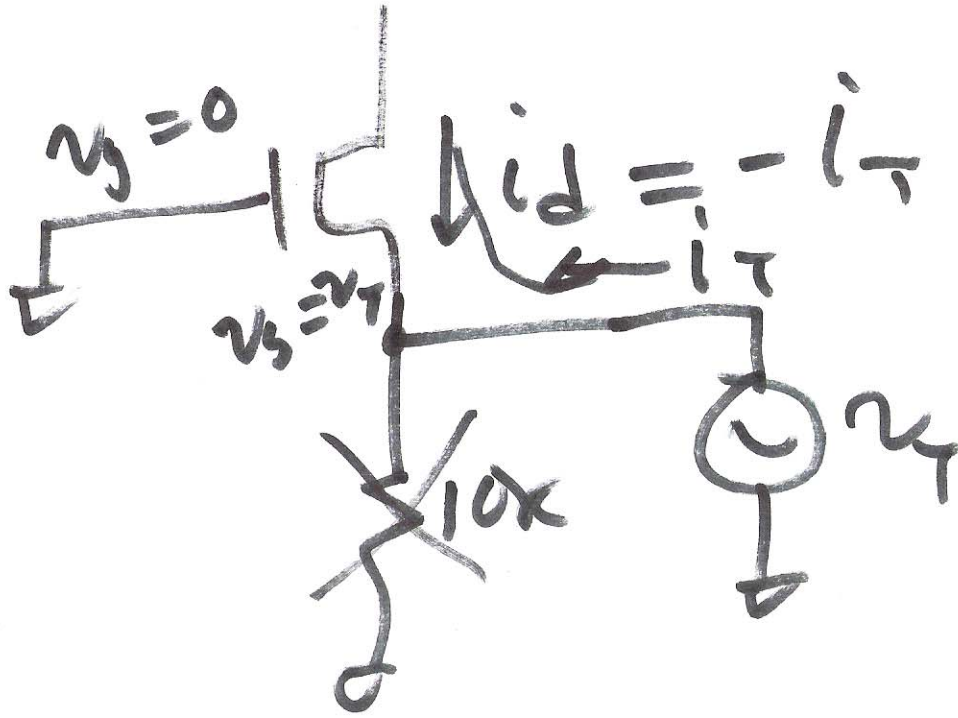

$$V_{gs} = -V_{ds}$$

Resistor source


$$= \frac{V_{ds}}{i_D}$$

$$= \frac{-V_{gs}}{-i_D}$$

$$= \frac{1}{g_m}$$

$$R_{out} = 10k \parallel \frac{1}{g_m}$$

a)

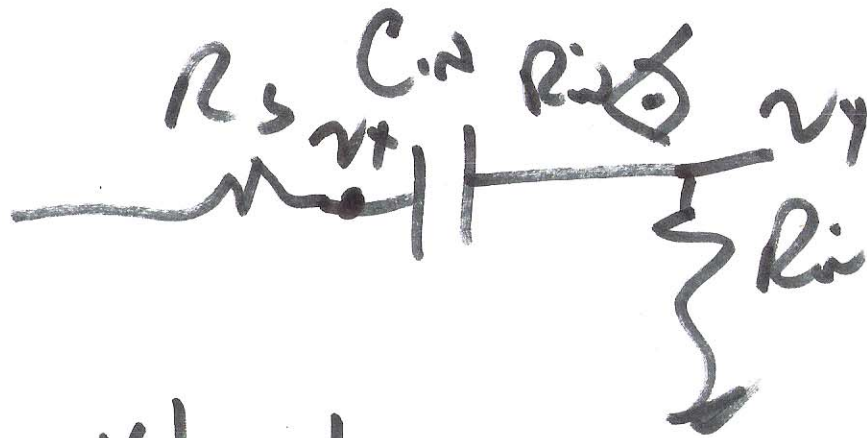


$$\left| \frac{v_y}{v_x} \right| = 1$$



$$f = \frac{1}{2\pi C_{in} (R_s + R_{in})} \text{ 3dB}$$

10)

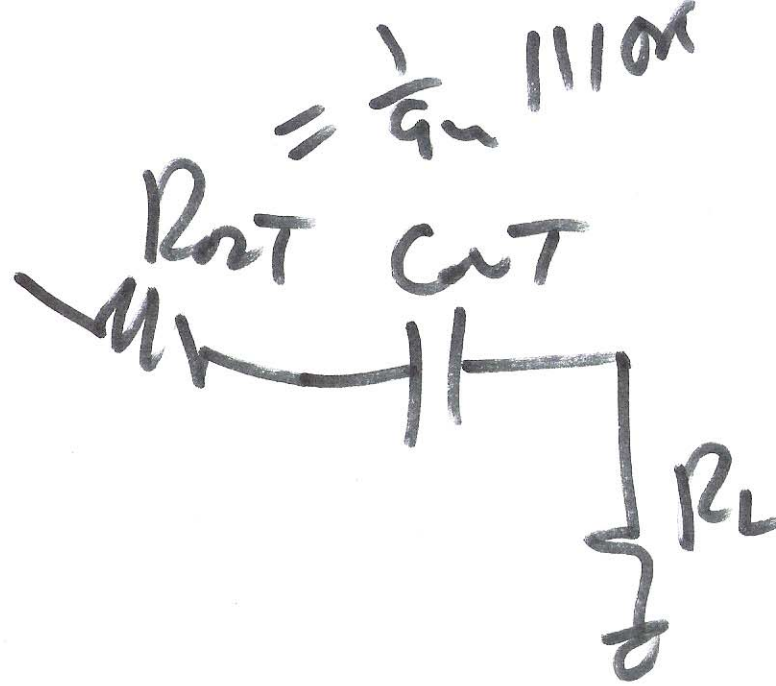

$$f_{3dB} = \frac{1}{2\pi C_{out} (R_{out} + R_L)}$$