
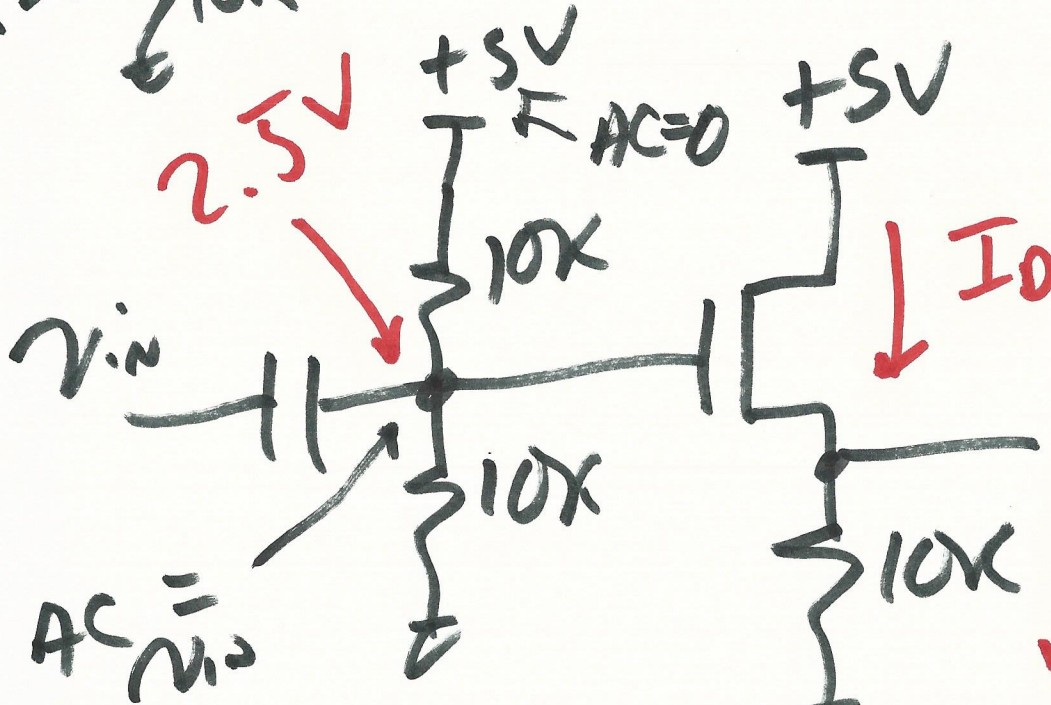


Lecture 23

April 23, 2014

EE 340²

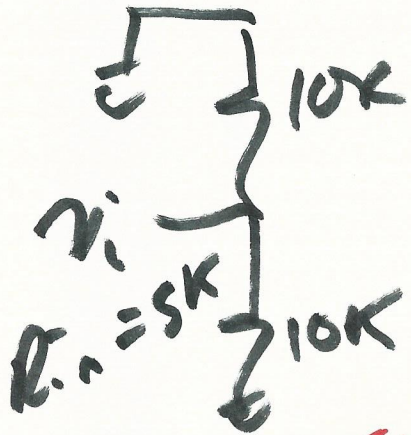

$$I_D = \frac{1204}{2} \cdot \frac{100}{1} (2.5 - I_D \cdot 10k - 0.8)^2$$

$$v_{inT} = V_S = I_D \cdot 10k$$


$$I_D = 1544 \mu A$$

$$V_S = 1.544 V$$

$$g_m = \sqrt{2 \cdot 1204 \cdot \frac{100}{1} \cdot 1544}$$

$$g_m = 1.922 \text{ mA/V}$$

1)

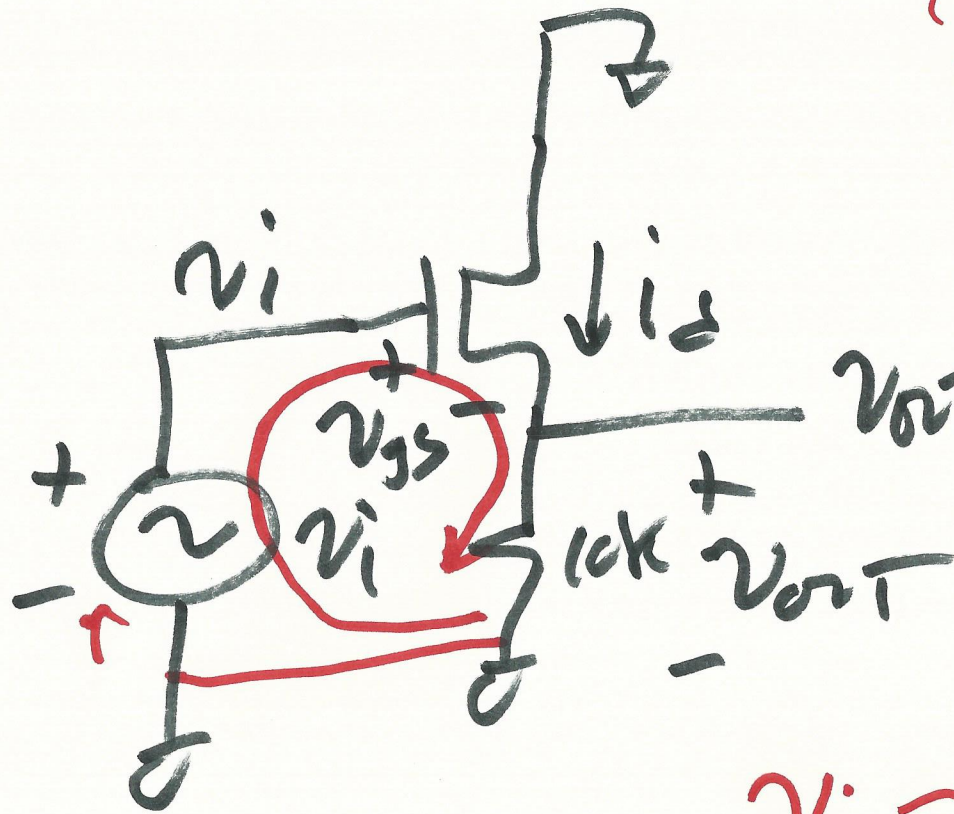

$$\frac{v_{out}}{v_i} = \frac{10k}{10k + \frac{1}{1.922mA}} \rightarrow \infty$$


$$v_{out} = i_d \cdot 10k \approx 0.985$$

$$v_i - v_{gs} - v_{out} = 0$$

$$v_i = i_d \left(10k + \frac{1}{g_m} \right)$$

$$\frac{v_{out}}{v_i} = \frac{i_d \cdot 10k}{i_d \cdot \left(10k + \frac{1}{g_m} \right)}$$

2)

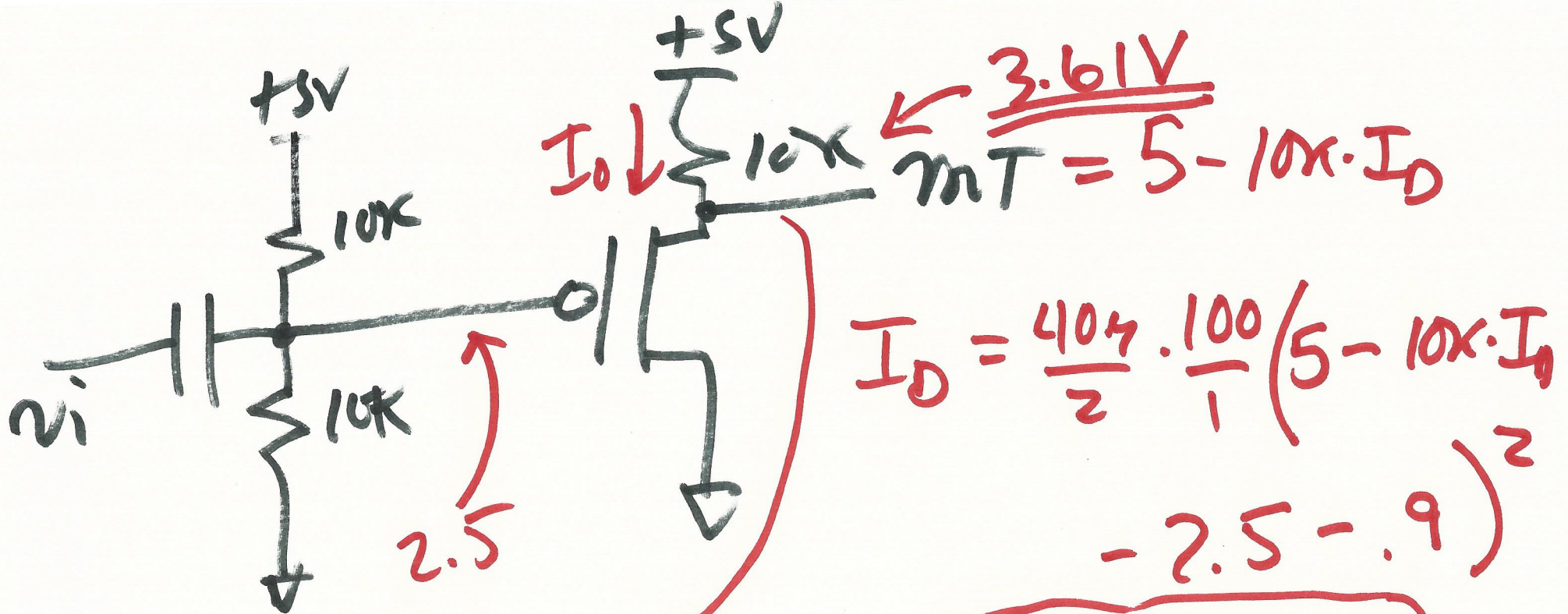

$$I_D = 1394A$$

$$1804A$$


$$g_m = \sqrt{2 \cdot 40\mu \cdot \frac{100}{1} \cdot 1394} \cdot 5 - 10k \cdot 1394$$

$$g_m = 1.036mA/V = 3.61V$$

$$\frac{1}{g_m} \approx 1k \quad 5 - 10k \cdot 1804 = 3.2V$$

$$V_S - V_D = 3.2 - 2.5 = .7 < .9$$

3)

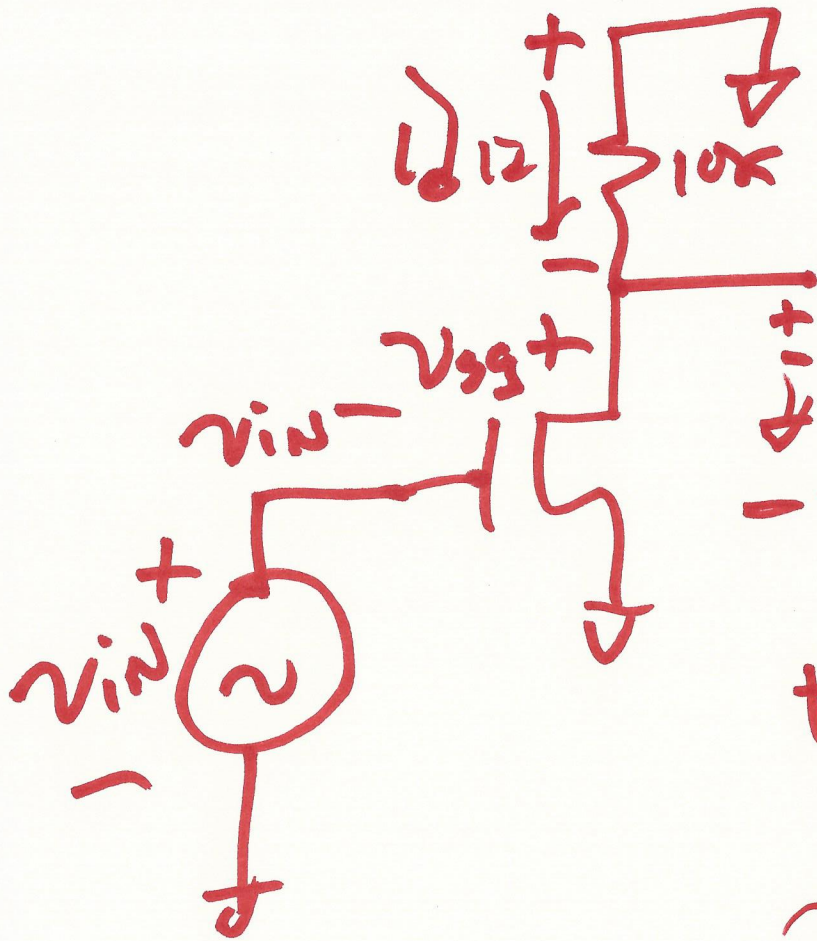

$$i_d \cdot 10k$$

$$v_{out} = -i_d \cdot 10k$$

$$-v_{out} + v_{gs} + v_{in} = 0$$

$$+i_d \cdot 10k + \frac{i_d}{g_m} + v_{in} = 0$$

$$v_{in} = -i_d \left(10k + \frac{1}{g_m} \right)$$


$$\frac{v_{out}}{v_{in}} = \frac{-i_d \cdot 10k}{-i_d \cdot \left(10k + \frac{1}{g_m} \right)}$$

$$= \frac{10k}{11k} = .91$$

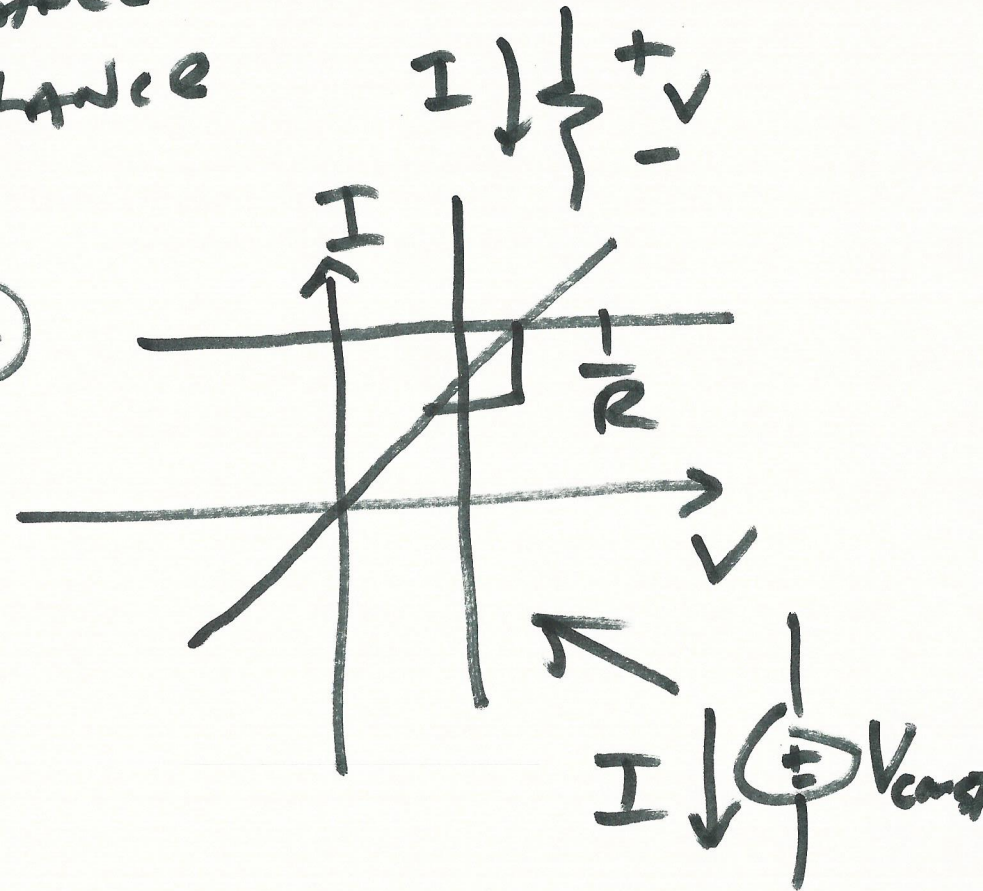4)

S.F.

High input Resistance
Low output Resistance
No voltage gain
good current gain \downarrow




C. S.

High DC input resistance

High input C

High voltage gain

High current gain

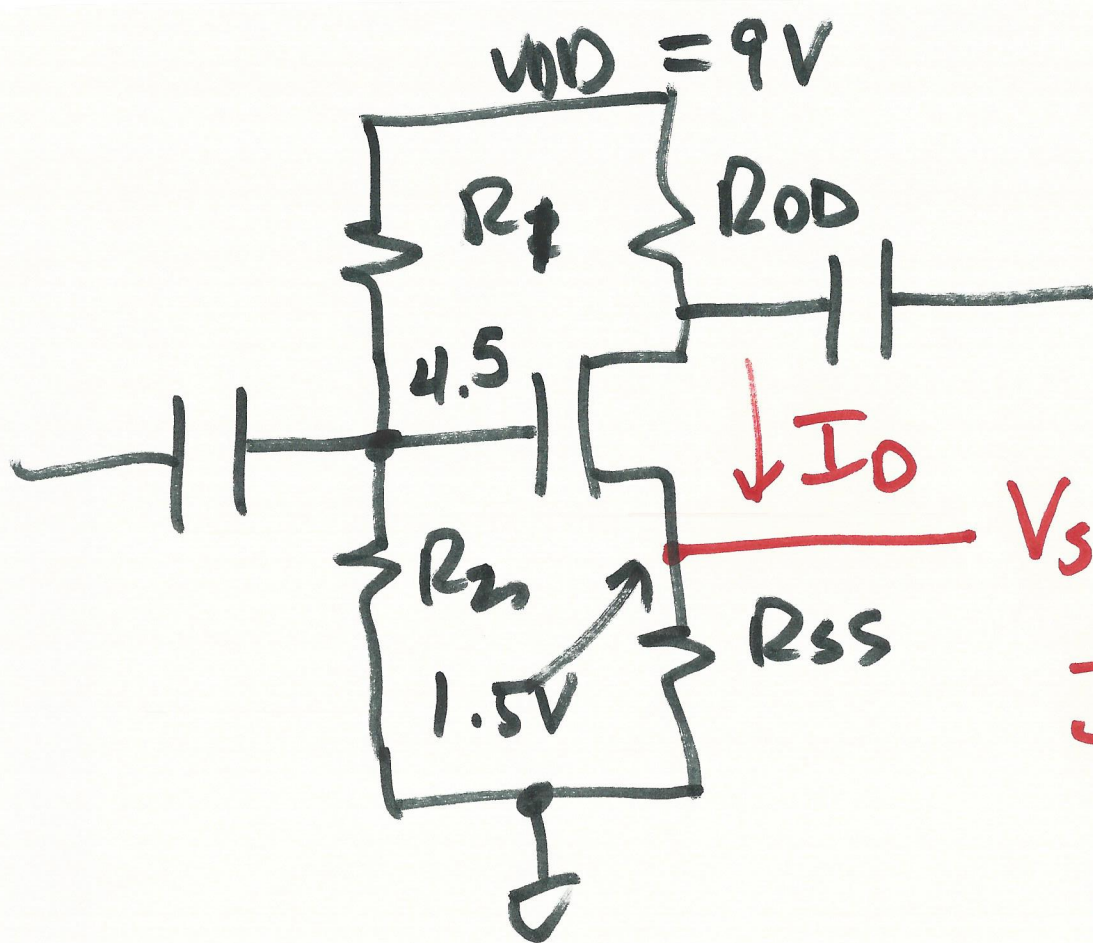

$$V_s = I_O \cdot R_{ss}$$

$$I_O = \frac{V_s}{R_{ss}}$$


$$100\mu A = I_O$$

$$1.5 = V_s$$

$$R_{ss} = \frac{1.5}{100\mu A} = \underline{\underline{15K}}$$

$$I_O = \frac{V_s}{15K}$$



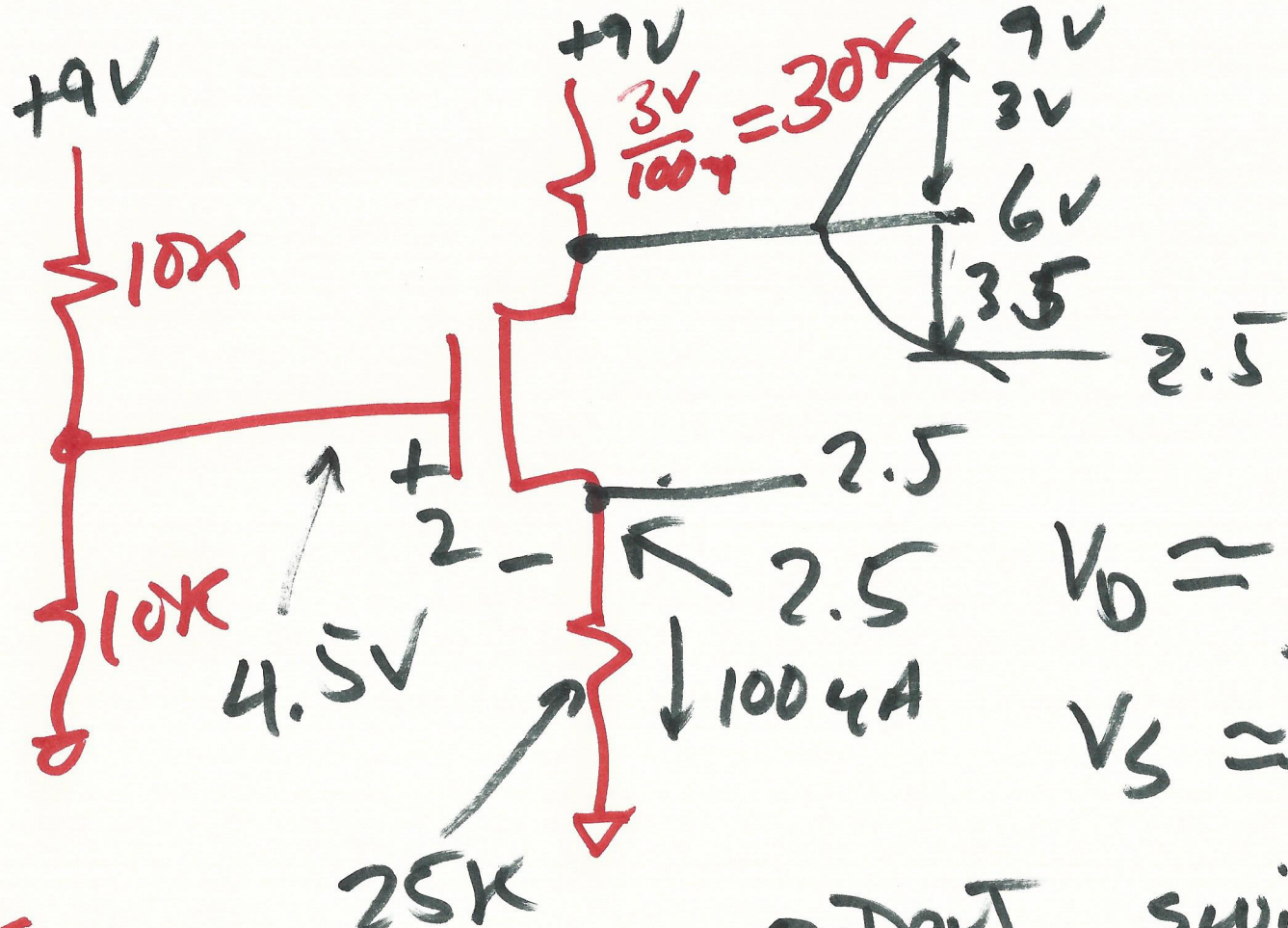


$$V_D \approx \frac{2}{3} V_{DD}$$

$$V_S \approx \frac{1}{3} V_{DD}$$

output swing

$$V_{DD} - \frac{1}{3} V_{DD}$$
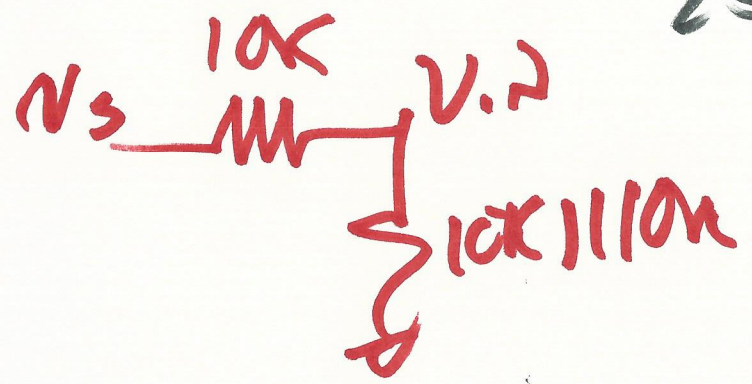
$$\text{Swing} \approx \frac{2}{3} V_{DD}$$




8)

$$g_m = \frac{I_{DQ}}{V}$$


$$\frac{1}{g_m} \approx 200 \Omega$$



$$v_{OUT} = -i_d R_{OD}$$

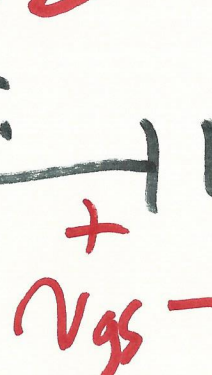

$$v_i = v_{GS} + i_d \cdot R_{SS}$$

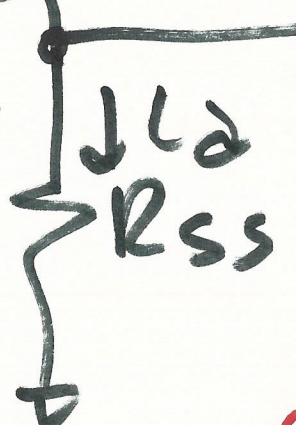

$$i_d R_{SS2} = i_d \left(\frac{1}{g_m} + R_{SS} \right)$$

$$\frac{-R_{OD}}{\frac{1}{g_m} + R_{SS} \parallel R_{SS2}}$$

$$\frac{-R_{OD}}{\frac{1}{g_m} + R_{SS2}}$$

$$\approx \frac{-R_{OD}}{\frac{1}{g_m} + R_{SS2}}$$

$$R_{SS2} \ll R_{SS}$$

$$\frac{v_{OUT}}{v_i} =$$

$$\frac{-R_{OD}}{\frac{1}{g_m} + R_{SS}}$$

$$= -g_m R_{OD}$$

Know this!

a)