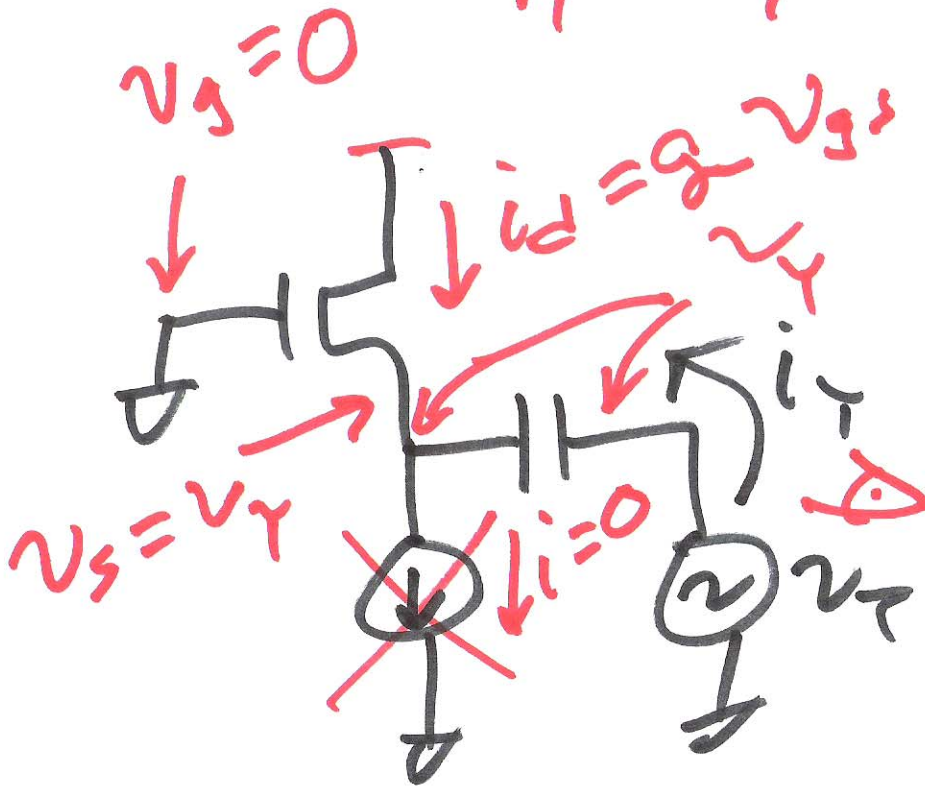


EE 320

Lecture 24

4/28/14

Spring 2014



$$V_{gs} = V_g - V_s$$

$$= -V_T$$

$$i_D = -i_T$$

$$R_{out} = \frac{V_T}{i_T}$$

$$-i_T = g_m (-V_T)$$

$$i_D = g_m V_{gs}$$


$$R_{out} = \frac{1}{g_m}$$

CMOSedu.com

11)


Open book and closed notes.

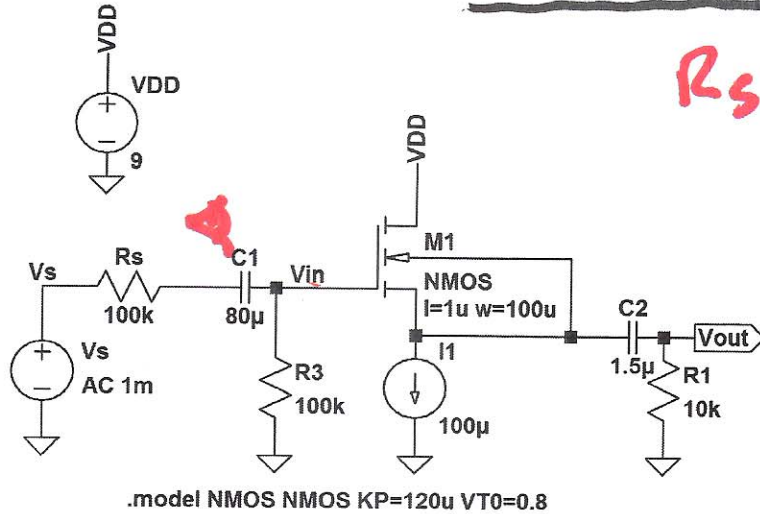1. For the following SF amplifier what is: a) the amplifier's input resistance? b) output resistance? c) gain,  $V_{out}/V_{in}$ , and d) gain,  $V_{out}/V_s$ . Show your work for credit.




$R_s = 100k$

$R_L = 10k$

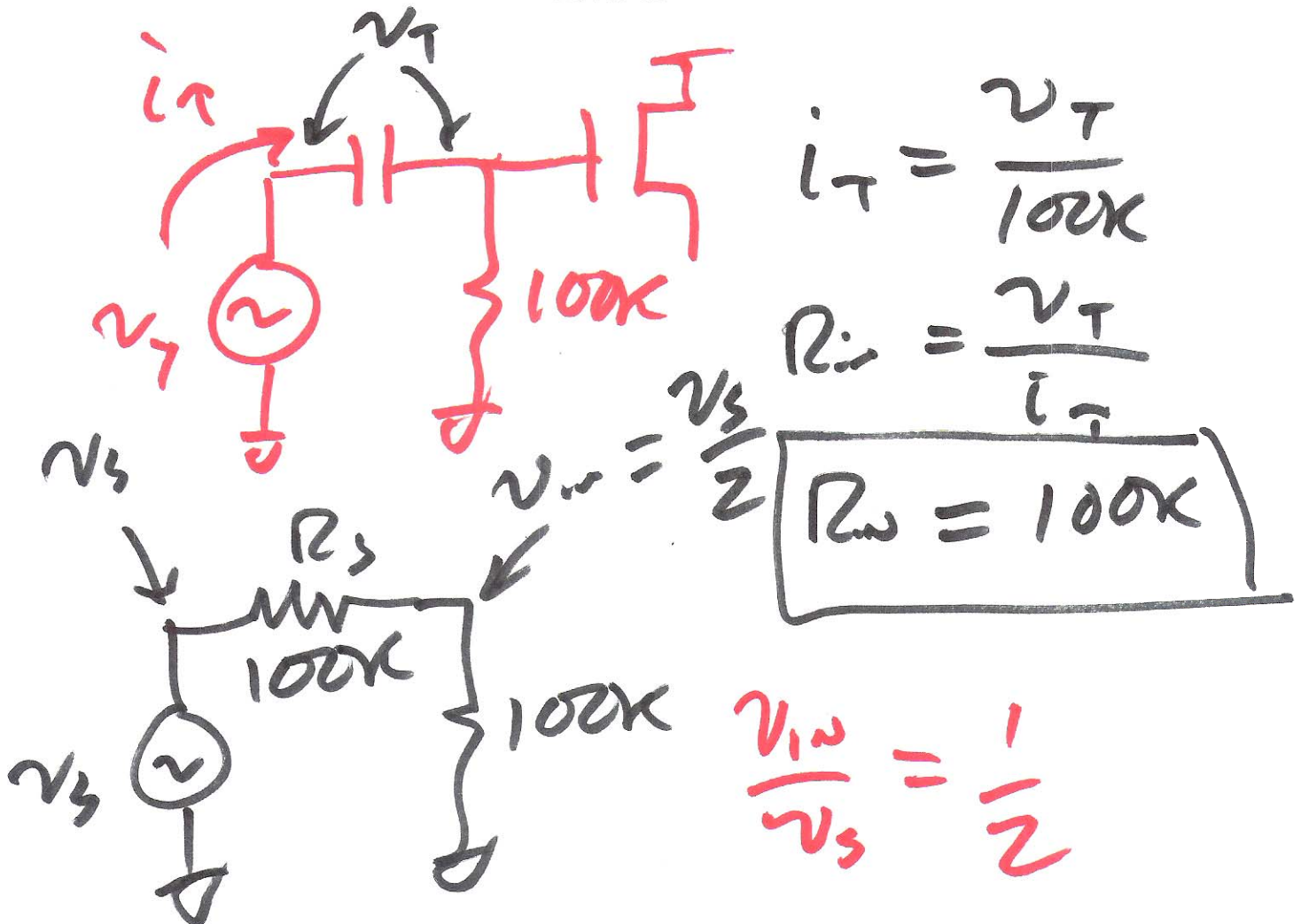

2)

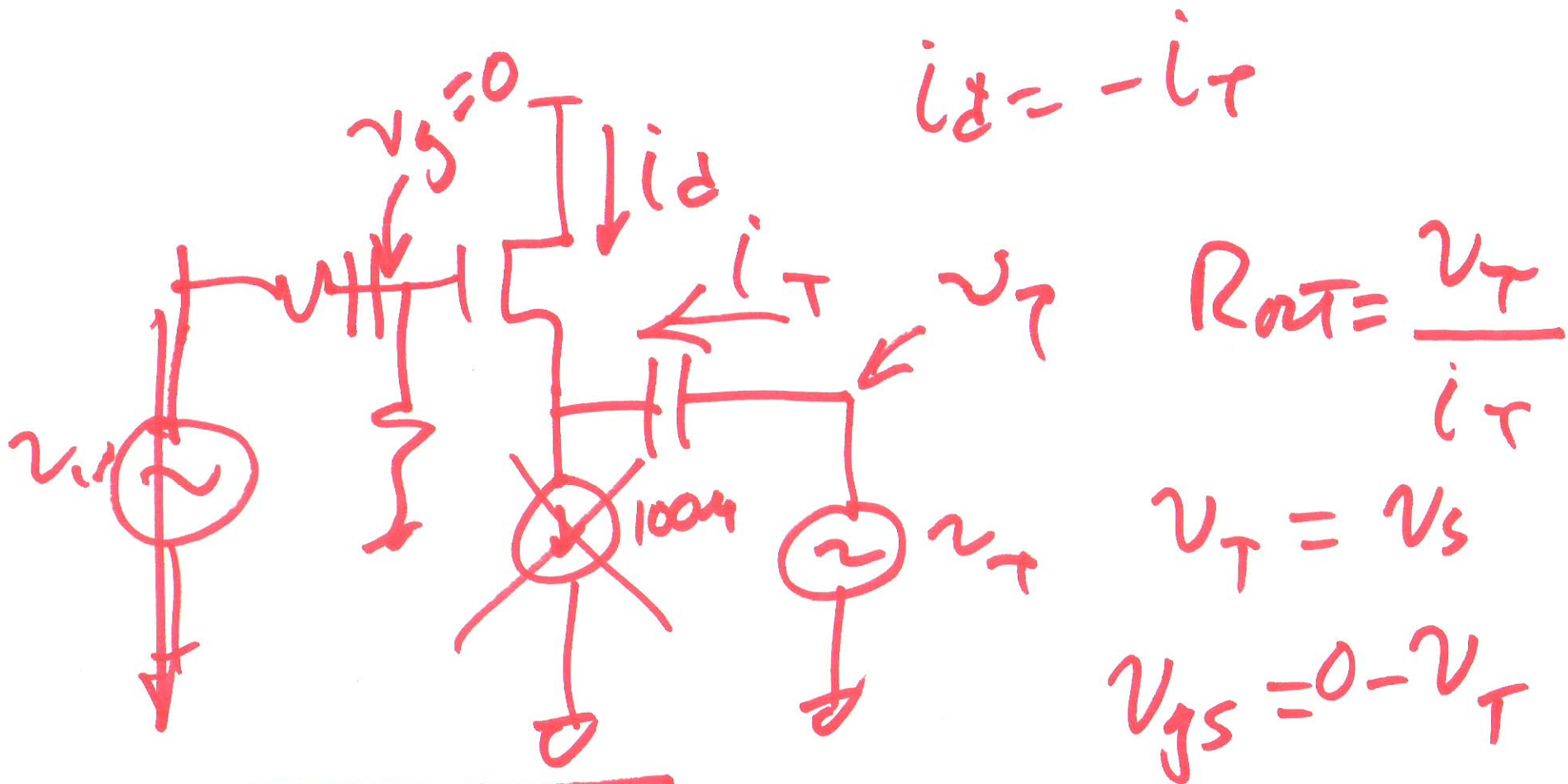

$$g_m = \sqrt{2 \mu_n \frac{W}{L} \cdot 100 \mu A}$$

$$= \sqrt{2 \cdot 200 \mu A \cdot \frac{100}{1} \cdot 100 \mu A}$$

$$R_{out} = \frac{v_T}{i_T} = \frac{-v_T}{-i_d} = \frac{1}{g_m}$$


$$R_{out} = 645$$

$$g_m = 1.55 \mu A$$

CMOSedu.com

3)

$$\frac{v_{in}}{v_s} = \frac{1}{2}$$

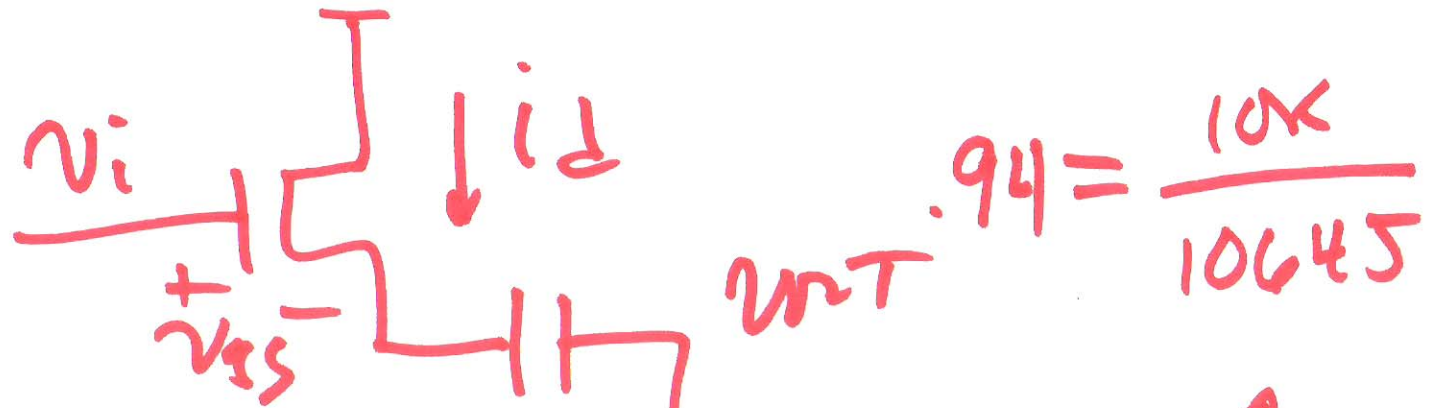

$$v_{out} = i_d \cdot 10K$$

$$v_i = v_{gs} + v_{out}$$


$$= i_d \left( \frac{1}{g_m} + 10K \right)$$

$$0.94 = \frac{v_{out}}{v_i} = \frac{10K}{\frac{1}{g_m} + 10K}$$

$$0.47 = \frac{v_{out}}{v_s} = \frac{1}{2} \frac{10K}{\frac{1}{g_m} + 10K}$$

4)



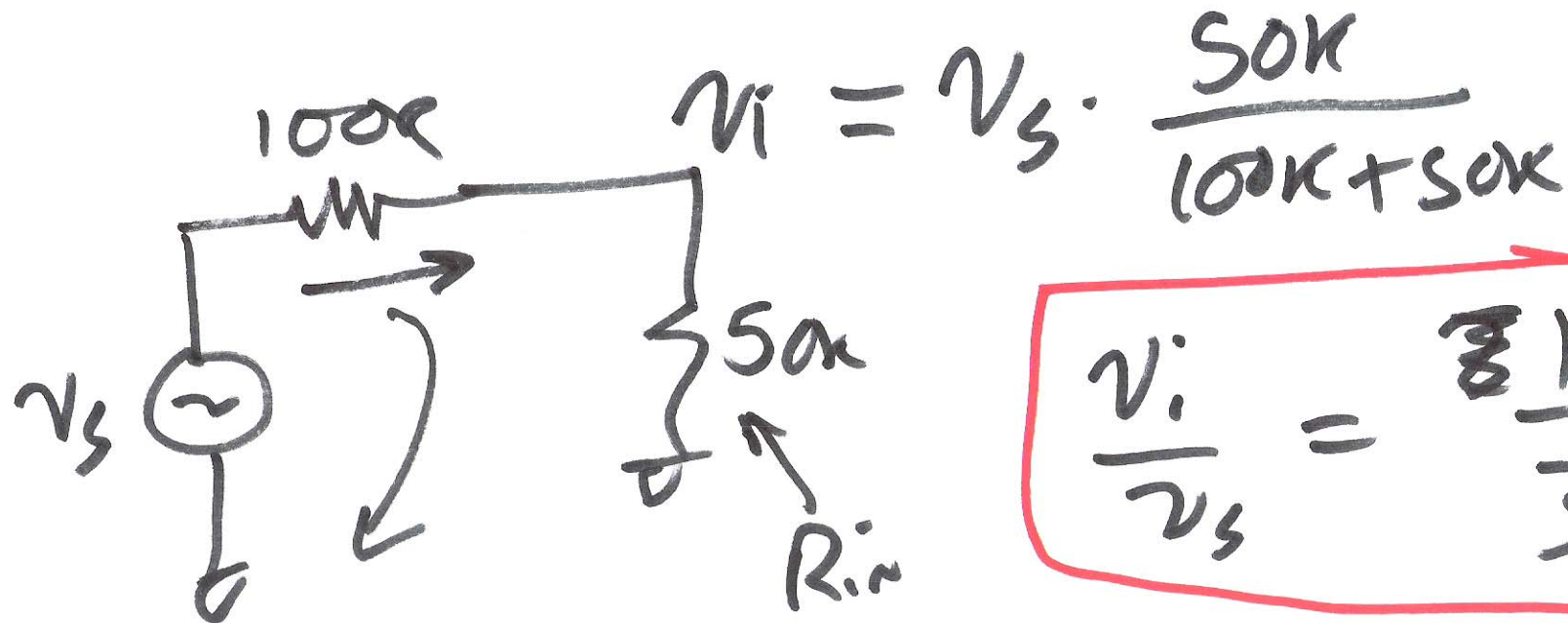

$$v_i = v_s \cdot \frac{50k}{100k + 50k}$$


$$\frac{v_i}{v_s} = \frac{1}{3}$$

$$\frac{v_s - v_i}{100k} = \frac{\frac{2}{3}v_s}{100k}$$


$$\frac{v_o}{v_s} = \frac{v_i}{v_s} \cdot \frac{v_o}{v_i} = \frac{1}{3} \cdot .88 = .293$$

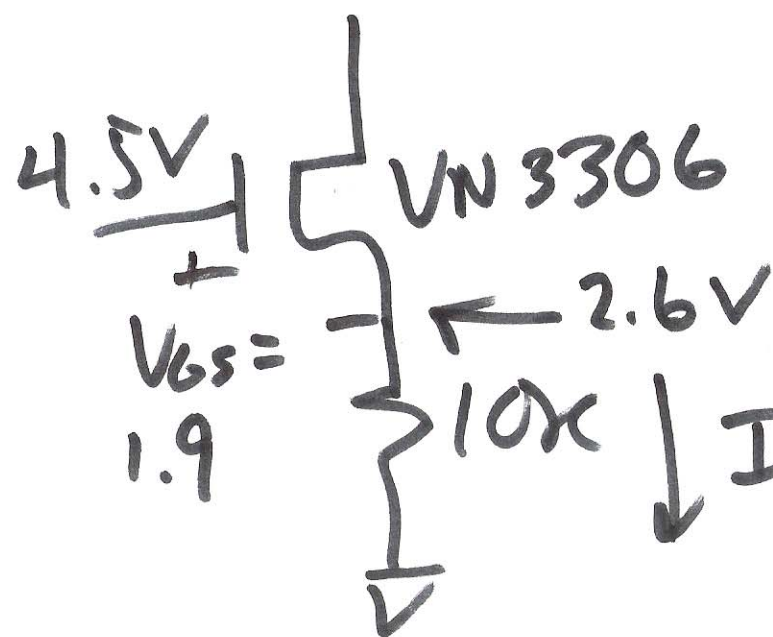5)

$$g_m = \frac{8 \mu A}{V} = 8 \text{ mS} = 8 \mu S$$




$$I_D = \frac{2.6}{10k} = 260 \mu A$$

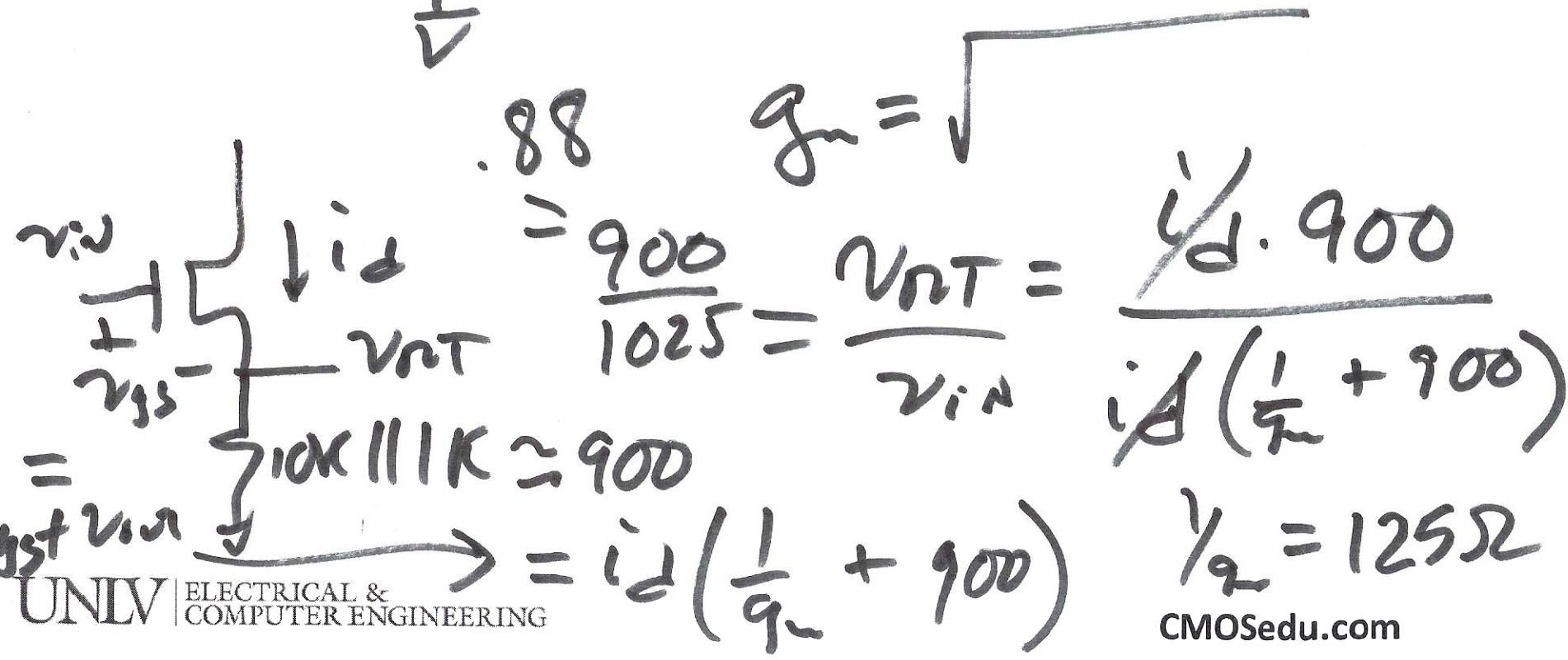

$$g_m = \sqrt{\frac{i_D \cdot 900}{v_{in}}} = \frac{1}{2} = 125 \Omega$$

6)

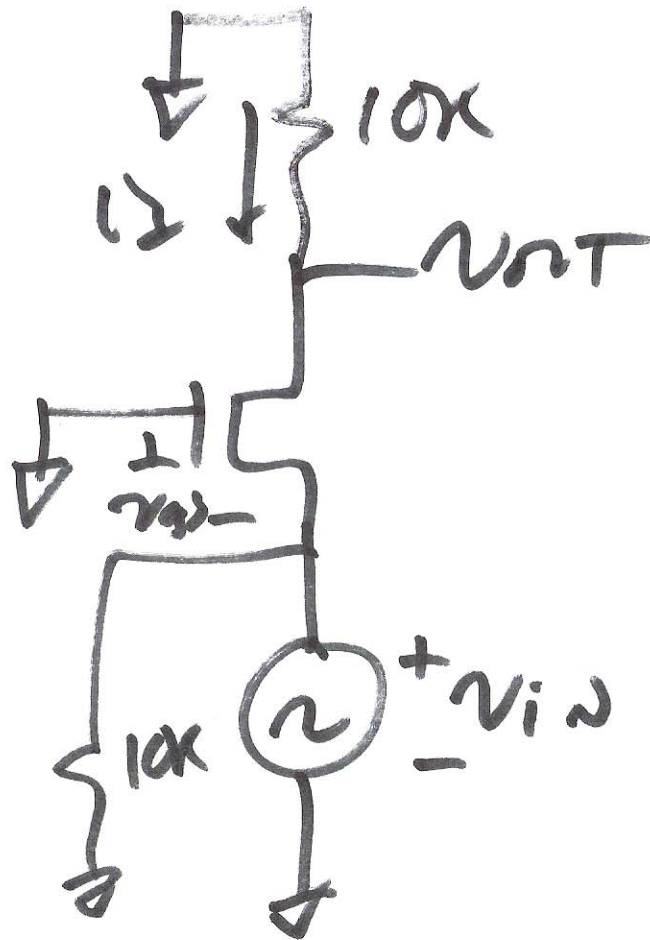

$$v_{gs} = -v_{in}$$

$$i_d = g_m v_{gs}$$


$$= -g_m v_{in}$$

$$v_{out} = i_d \cdot 10k$$

$$\frac{v_{out}}{v_{in}} = +g_m \cdot 10k$$

$$= 8mA \cdot 10k$$



$$= 80 \frac{V}{V}$$

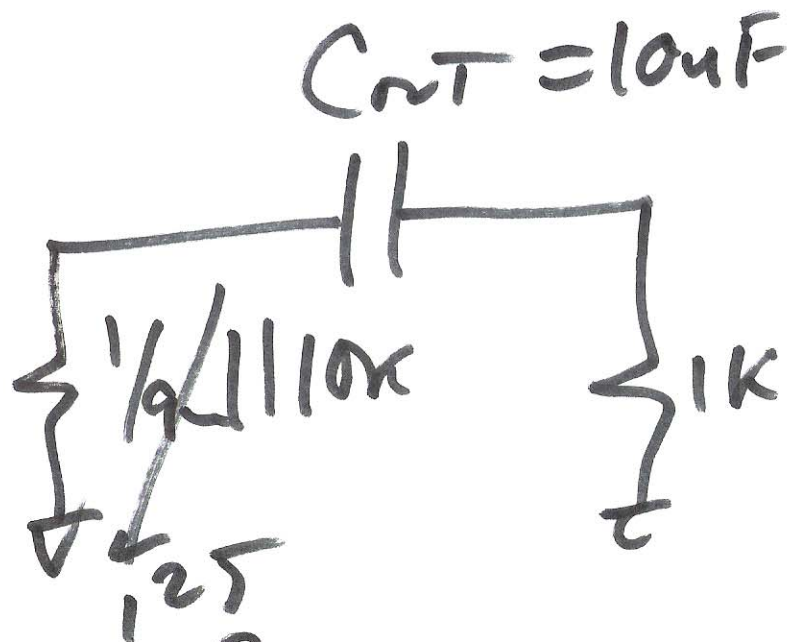


$$f_{3dB} = \frac{1}{2\pi \cdot 10\mu F \cdot (1/2.5)}$$
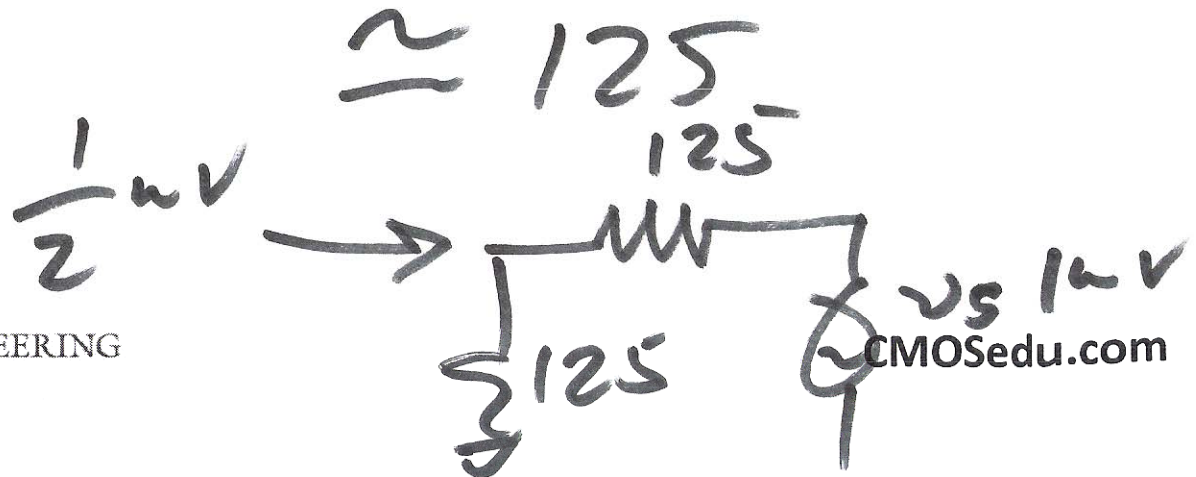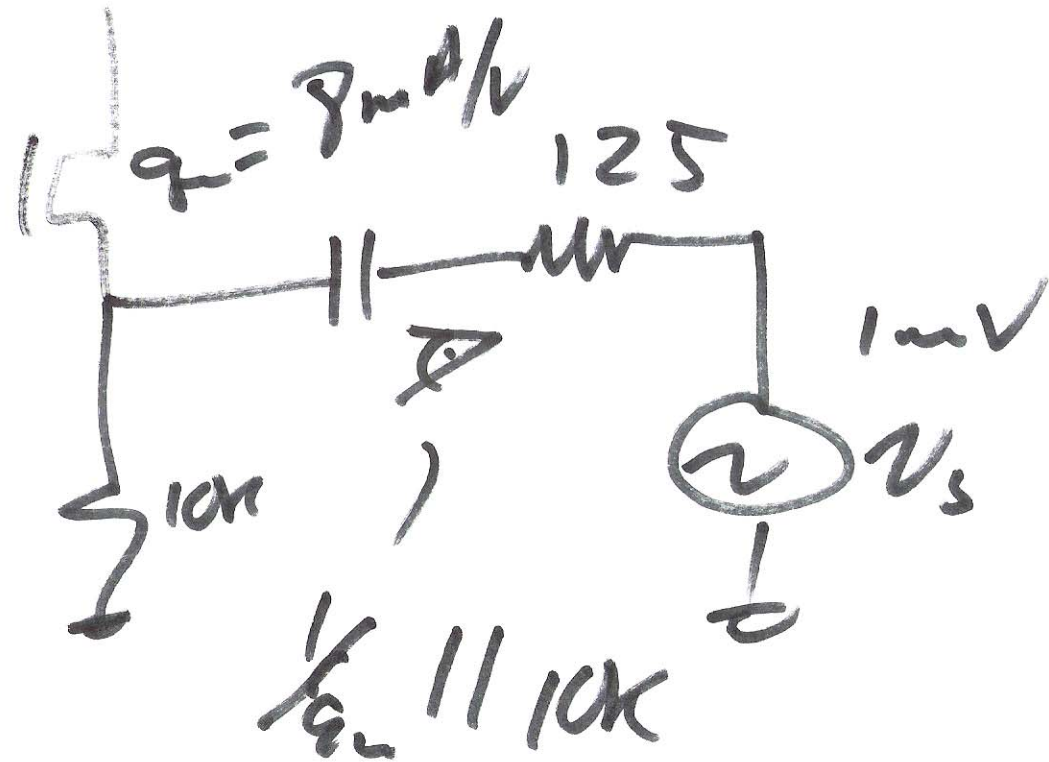
$$14 \text{ Hz} \Rightarrow 70 \text{ms}_T$$





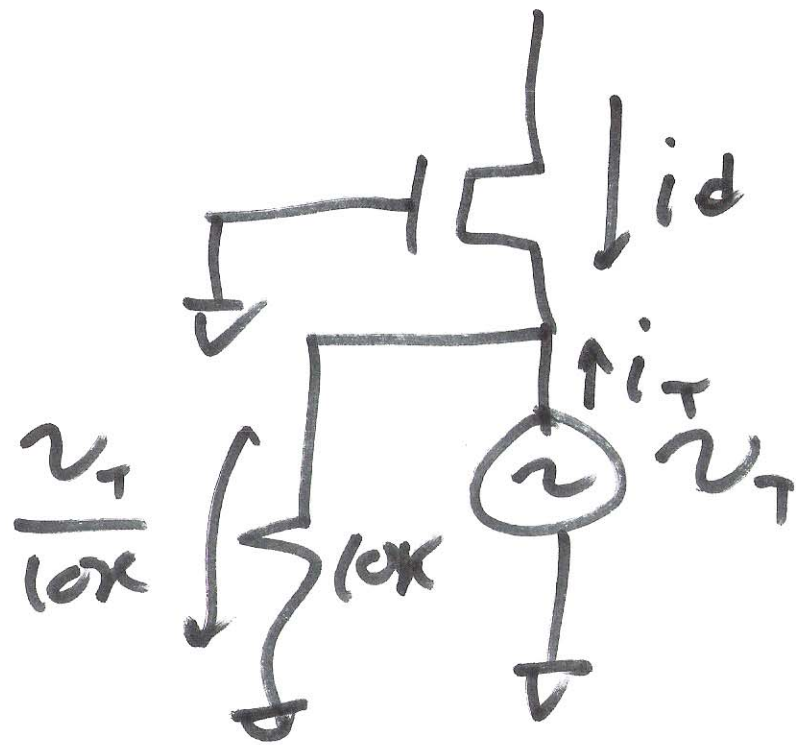

$$R_{in} = \frac{v_T}{10k} + \frac{v_T}{-i_d}$$

$$v_{gs} = -v_T$$

$$R_{in} = \frac{v_T}{10k} +$$

$$10k \parallel \frac{v_T}{i_T} = 10k \parallel \frac{1}{g_m}$$

~~$$\frac{v_{gs}}{-i_T} = \frac{1}{g_m}$$~~

10)